
EE1101: Circuits and Network Analysis

Lecture 25: Sinusoidal Response of First-Order Circuits

September 23, 2025

Topics :

1. Sinusoidal Response using complex exponentials
 2. Role of Phasors and Impedances
-

Sinusoidal Response using Complex Exponentials

The DE that describes a first-order CKT excited by a sinusoidal source is

$$\frac{dx}{dt} + P(t)x(t) = q(t) \quad \text{where } q(t) = A \cos(\omega t + \phi) \rightarrow (1)$$

In addition $P(t) = P$

Complex exponential Route:- \hat{x} to a complex exponent $e^{j(\omega t + \phi)}$

x is $\text{Re}\{\hat{x}\} \leftarrow$

DE with complex exponential input

$$\frac{d\hat{x}}{dt} + P\hat{x}(t) = A e^{j(\omega t + \phi)} \rightarrow (2)$$

$$\text{Integrating factor} = e^{\int P dt} = e^{Pt} \quad (\because P(t) = P) \rightarrow (3)$$

Mul (2) with IF & upon simplification

$$\frac{d}{dt} (e^{Pt} \hat{x}(t)) = A e^{Pt} e^{j(\omega t + \phi)} = A e^{(P+j\omega)t} e^{j\phi} \rightarrow (4)$$

Integrating on both sides of (4)

$$e^{Pt} \hat{x}(t) = \frac{A e^{j\phi}}{(P+j\omega)} e^{(P+j\omega)t} + C \rightarrow (5)$$

Sinusoidal Response using Complex Exponentials

$$\hat{x}(t) = \frac{A e^{j\phi}}{(P+j\omega)} e^{j\omega t} + \underbrace{C e^{-Pt}}_{\textcircled{II}}$$

Term $\textcircled{II} \rightarrow 0$ as $t \rightarrow \infty$ if $P > 0$ (true for ckt's)

Term \textcircled{I} : as $t \rightarrow \infty$: sinusoidal in nature

for first order ckt's: sinusoidal excitation

\Downarrow
Sinusoidal response in steady state.

Steady state response:

$$\hat{x}_{ss}(t) = \frac{\overbrace{A e^{j\phi}}}{P+j\omega} e^{j\omega t} = \underbrace{\frac{\sqrt{2} \vec{A}}{\vec{Z}}}_{\text{phasor form}} e^{j\omega t} \quad \text{where } \vec{Z} = P+j\omega$$

$$\begin{aligned} \text{Steady state response } x \text{ in } \left\{ \begin{array}{l} \text{Phasor form} \end{array} \right. & \vec{x}_{ss} = \frac{\sqrt{2} \vec{A}}{\vec{Z}} \quad (\text{in phasor form}) \\ & = \frac{A e^{j\phi}}{Z e^{j\theta}} = \frac{A}{Z} e^{j(\phi-\theta)} \end{aligned}$$

$$\text{Steady state response in } \left\{ \begin{array}{l} \text{time-domain} \end{array} \right. \left\{ \begin{array}{l} x_{ss}(t) = \frac{A}{Z} \cos(\omega t + \phi - \theta) \end{array} \right.$$

$$\text{where } Z = \sqrt{P^2 + \omega^2} \text{ and } \theta = \tan^{-1}(\omega/P)$$

Sinusoidal Response using Complex Exponentials

$$\begin{aligned}
 \hat{x}(t) &= \frac{A e^{j\phi}}{(p+j\omega)} e^{j\omega t} + c e^{-pt} \\
 &= \frac{(p-j\omega)}{p^2+\omega^2} A [\cos(\omega t + \phi) + j \sin(\omega t + \phi)] + c e^{-pt} \\
 &= \frac{A}{p^2+\omega^2} \left\{ [p \cos(\omega t + \phi) + \omega \sin(\omega t + \phi)] + j [p \sin(\omega t + \phi) - \omega \cos(\omega t + \phi)] \right\} + c e^{-pt} \\
 &= \frac{A}{\sqrt{p^2+\omega^2}} [\cos(\omega t + \phi - \theta) + j \sin(\omega t + \phi - \theta)] + \underbrace{c e^{-pt}}_{\in \mathbb{R}} \quad \text{where } \theta = \tan^{-1}(\omega/p)
 \end{aligned}$$


$$\text{Real} \{ \hat{x}(t) \} = x(t) = \underbrace{\frac{A}{\sqrt{p^2+\omega^2}} \cos(\omega t + \phi - \theta)}_{\text{Steady state resp}} + \underbrace{c e^{-pt}}_{\text{Transient response}}$$

Example

Example 1:-

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V_m}{L} \cos(\omega t + \phi) \quad \text{where } V_m = \sqrt{2} V \quad \text{V L } \phi$$

(for $t > 0$)

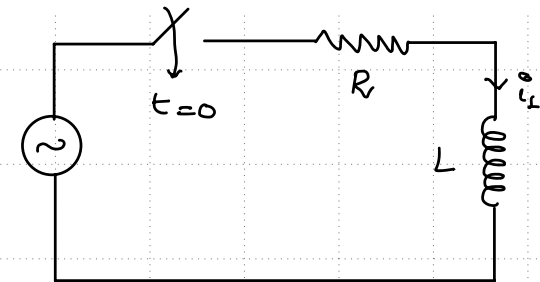

$$P = R/L$$

$$i(t) = \left(\frac{V_m}{L} \right) \frac{1}{\sqrt{R^2/L^2 + \omega^2}} \cos(\omega t + \phi - \theta) + c e^{-R/L t} \quad \text{where } \theta = \tan^{-1}(\omega / (R/L)) = \tan^{-1}(\omega L / R)$$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta) + c e^{-R/L t} \leftarrow$$

given $i_L(0) = 0 \Rightarrow c = -\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta)$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left[\cos(\omega t + \phi - \theta) - \cos(\phi - \theta) e^{-R/L t} \right]$$

Steady state sol in phasor form:

$$\vec{I} = \frac{V_m}{\sqrt{2} \sqrt{R^2 + \omega^2 L^2}} e^{j(\phi - \theta)} = \frac{V e^{j\phi}}{\sqrt{2} \sqrt{R^2 + \omega^2 L^2}} e^{-j\theta} = \frac{V e^{j\phi}}{\sqrt{R^2 + \omega^2 L^2} e^{j\theta}} = \frac{\vec{V}}{\vec{Z}}$$


Example use of Phasors for Computing S.S. response.

① replace sources by phasor representation


② Replace R, L & C by Impedances.

③ Apply Node/mesh analysis \Rightarrow Circuit resp in phasor form

\Downarrow
Convert it to time domain.

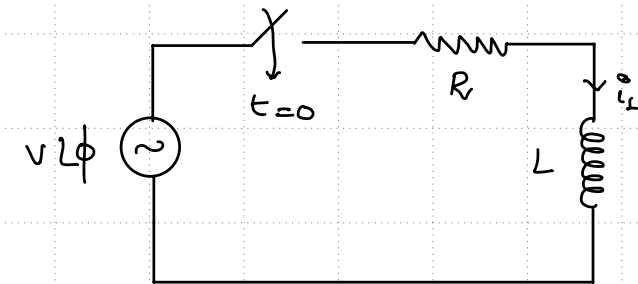


\Downarrow

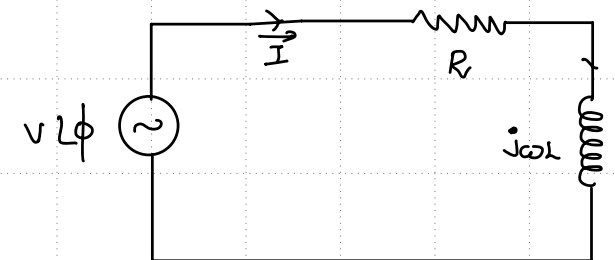

by KVL: $(R + j\omega L) \vec{I} = \vec{V}$

$$\Rightarrow \vec{I} = \frac{\vec{V}}{(R + j\omega L)}$$

Series:

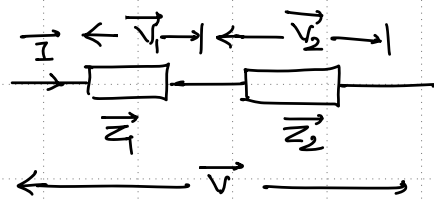

$$\vec{V} = \vec{I} \vec{Z}_1 + \vec{I} \vec{Z}_2$$

$$= \vec{I} (\vec{Z}_1 + \vec{Z}_2) \Rightarrow \frac{\vec{V}}{\vec{I}} = \vec{Z}_1 + \vec{Z}_2$$

Parallel: $\vec{I} = \vec{I}_1 + \vec{I}_2$

$$= \frac{\vec{V}}{\vec{Z}_1} + \frac{\vec{V}}{\vec{Z}_2}$$

$$\frac{\vec{V}}{\vec{I}} = \frac{\vec{Z}_1 \vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2}$$

