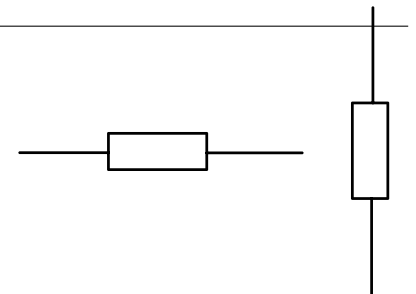

EE1101: Circuits and Network Analysis

Lecture 04: DC Circuit Analysis

August 4, 2025

Topics :


1. Resistance
2. KCL and KVL



($R \rightarrow \infty$) ($R \rightarrow 0$)

Resistance - Open Circuit and Short Circuit

from a CKT point of view: Two terminal element whose V & i \leftarrow Current through it
 \hookrightarrow Voltage across the element

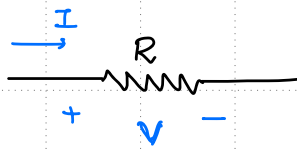CKT representation:  $V \propto i \rightarrow$ The Const of Prop is Resistance (R)
 \downarrow
 geometry & the material prop

for a Conductor: $R = \frac{\rho l}{A}$ where


ρ = Resistivity

l = length of the Cond.

A = area of cross section

governing Eqn for a Resistor $V = IR$ or $V = iR$ (under passive sign convention)

V - i characteristic :-

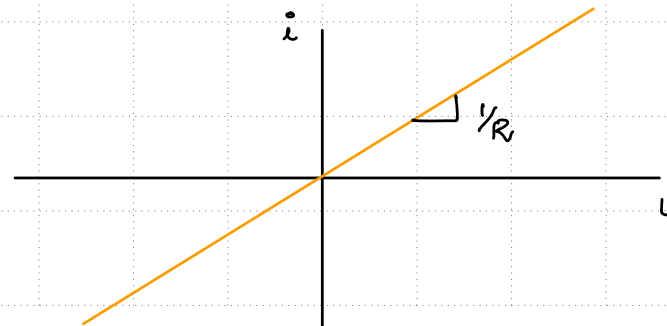

operating points are in

Quad I or Quad III

$$P = VI > 0$$


$$P = VI > 0$$

under passive sign convention } \downarrow Sink / Load

Elements in Series and Parallel

Series Connection:-

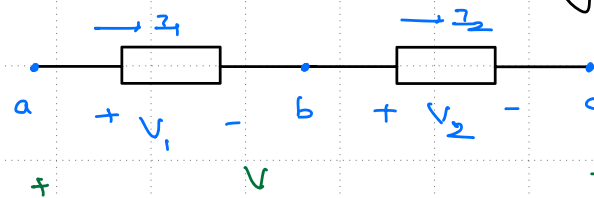
Two elements that are connected in an end-to-end manner & have the same current flow through them.



only under chosen convention

$$I_1 = I_2$$

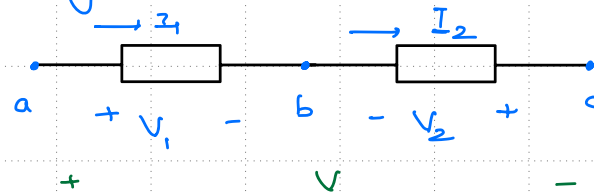what will be the voltage across the combination? $V = ? = V_1 + V_2$.




$$\Rightarrow V = V_1 - V_2$$

$$\begin{aligned} V &= -\int_c^a \vec{E} \cdot d\vec{l} = -\underbrace{\int_c^b \vec{E} \cdot d\vec{l}}_{= -V_2} - \underbrace{\int_b^a \vec{E} \cdot d\vec{l}}_{= V_1} \\ &= -V_2 + V_1 \\ &= V_1 - V_2 \end{aligned}$$

Parallel Connection:

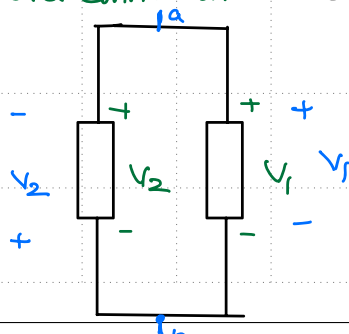Two elements connected b/w the same nodes.



same potential across the elements (account for sign convention)

for ref in green: $V_1 = V_2$

for ref in blue: $V_1 = -V_2$

Guidelines for Circuit Analysis

→ given a N/w built using Circuit elements

goal: To be able to compute the desired voltages/currents

① Node Naming: use lower case alphabets
(for this course)

We need to identify a ref node
↓
mark as '0'

Assumption: $V_0 = 0$ (reference node)

When def potential = $-\int_0^P \vec{E} \cdot d\vec{l}$
 $\infty \leftarrow$ ref node (0)

Node Potential $V_{P0} = -\int_0^P \vec{E} \cdot d\vec{l} \rightarrow$ Simply put it as V_P instead of V_{P0}


Potential diff b/w nodes = $V_{ab} = V_a - V_b$ (a & b need not be connected directly)

② Clearly mark the polarity & reference.

Source (V, I) → Active sign convention.

③ Clearly mark the mesh/loops.

Sink (R) → Passive sign convention.

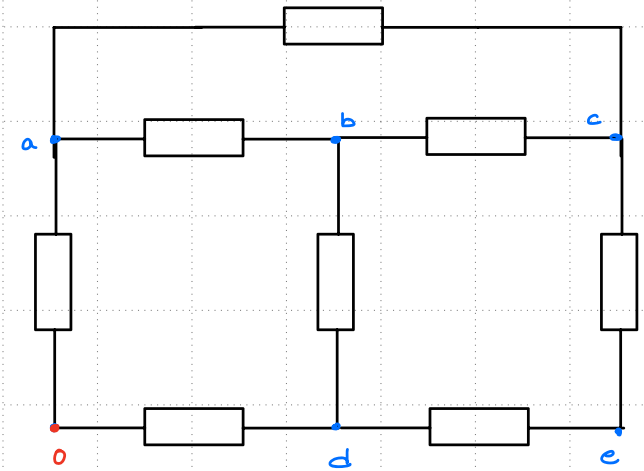

Krichhoff's Voltage Law (KVL)


Application of Maxwell's 2nd Equation

(for DC ckt)
(static fields)

$$\oint \vec{E} \cdot d\vec{l} = 0$$

closed path

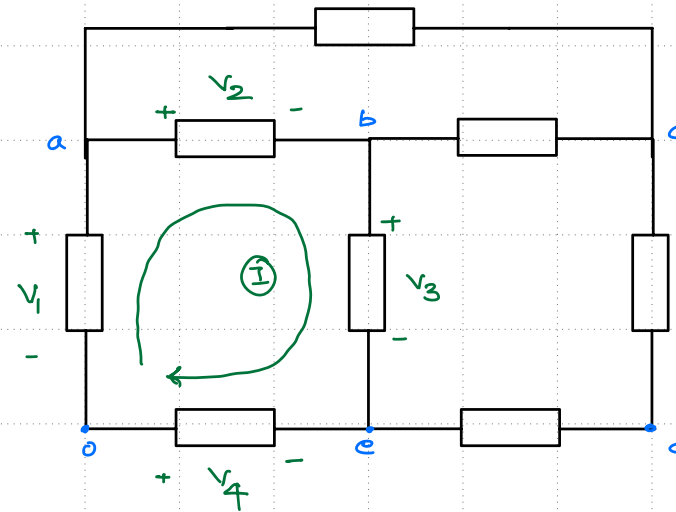referred to as a loop/mesh
in ckt analysis.



for loop \textcircled{I} : by 2nd eqn $\oint \vec{E} \cdot d\vec{l} = 0$

$$\int_a^b \vec{E} \cdot d\vec{l} + \int_b^e \vec{E} \cdot d\vec{l} + \int_e^f \vec{E} \cdot d\vec{l} + \int_f^a \vec{E} \cdot d\vec{l} = 0$$

$$V_{ab} + V_{be} + V_{ef} + V_{fa} = 0 \Rightarrow \sum V = 0$$

algebraic sum of voltages in
a closed loop is 0.

When polarity is specified:
for loop \textcircled{I} $\rightarrow \int_a^b \vec{E} \cdot d\vec{l} + \int_b^e \vec{E} \cdot d\vec{l} + \int_e^f \vec{E} \cdot d\vec{l} + \int_f^a \vec{E} \cdot d\vec{l} = 0$

$$-V_1 + V_2 + V_3 - V_4 = 0$$


Kirchhoff's Current Law (KCL)

↓
Application of Maxwell's 4th Eqn.
↓
 $\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t}$ (for DC ckts)

from Vec. Calculus $\nabla \cdot (\nabla \times \vec{H}) = 0 \Rightarrow \nabla \cdot \vec{J} = 0$

$$\Rightarrow \oint \vec{J} \cdot d\vec{S} = 0 \rightarrow \textcircled{1}$$

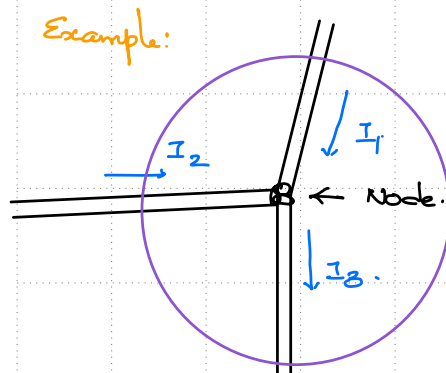flux of \vec{J} (or alg. sum of currents) = 0



mark reference for currents

by def $I_1 = \int \vec{J}_1 \cdot d\vec{S}_1$, $I_2 = \int \vec{J}_2 \cdot d\vec{S}_2$

and $I_3 = \int \vec{J}_3 \cdot d\vec{S}_3$

Application of ① to specific example for a spherical surface.

$$\int \vec{J} \cdot d\vec{S} = 0$$

outward normal

3 Contributions namely $-I_1$, $-I_2$ and I_3
bec of the ref for current & choice of $d\vec{S}$

$$\int \vec{J} \cdot d\vec{S} = -I_1 - I_2 + I_3 = 0$$

alg. sum of currents leaving a node = 0

or alternately Sum of currents entering = Sum of currents leaving a node.