

---

# EE1101: Circuits and Network Analysis

## Lecture 24: First-Order Circuits

September 22, 2025

---

### Topics :

1. Quantifying Transient Response
  2. Examples of First-order Circuits
-

## Examples of First-order Circuits

by KCL,  $I_s = i_r + i_c$

$$I_s = \frac{v_c}{R} + C \frac{dv_c}{dt}$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{I_s}{C} \rightarrow \textcircled{1}$$

Integrating factor  $= e^{\int \frac{1}{RC} dt} = e^{t/RC}$

mul  $\textcircled{1}$  on both sides with IF  $\Rightarrow$

$$\frac{d}{dt} (e^{t/RC} v_c(t)) = \frac{I_s}{C} e^{t/RC}$$


Integrate on both sides.

$$e^{t/RC} v_c = \frac{I_s}{C} \times RC e^{t/RC} + C$$

$$v_c = RI_s + C e^{-t/RC}$$

C:  $v_c(0) = 0 \Rightarrow C = -RI_s$  &  $v_c(t) = RI_s (1 - e^{-t/RC})$

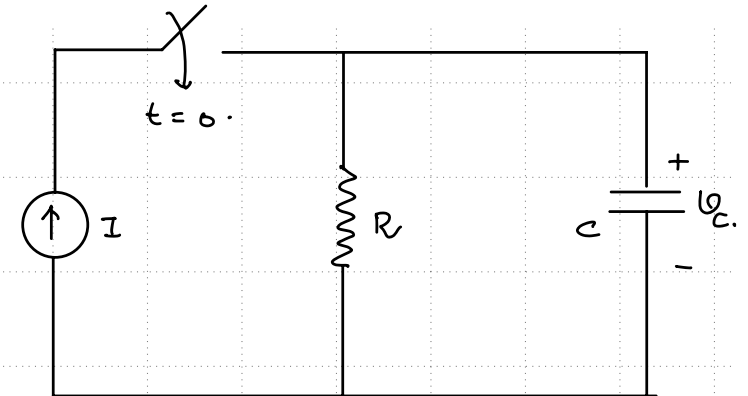as  $t \rightarrow \infty$   $v_c = RI_s$  (steady state response)  $\leftarrow$



Transient Response:

$$v_c(t) - \underbrace{v_c(\infty)}_{\text{steady state value}} = -RI_s \underbrace{e^{-t/RC}}_{\text{determines the variation of transient response}}$$

## Quantifying Transient Response

for first order circuits: Nature of transient response is exponentially decaying

for Series RL ckt

$$\tau = L/R$$


for parallel RC ckt

$$\tau = RC$$

one way to Quantify the transient response is to indicate the rate of decay.  
 $\downarrow$   
 time constant  $:(\tau)$   
 $e^{-t/\tau}$

for higher order ckt's (ckt's having L, C & multiple energy storage elem)

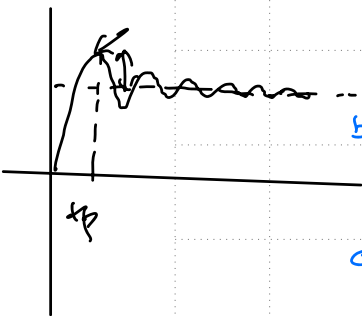a) rise time ( $t_r$ ): time taken from 2% of the final value to 98% of final value  
 (5% - 95%) (or) (10 - 90%)



b) settling time ( $t_s$ ): time to reach 98% (or) 95% of the final value. ( $\pm 2\%$  of final value)

c) Peak overshoot ( $M_p$ ): Peak value as a fraction of final value (%)

d) time to peak ( $t_p$ ): time to reach Peak value

## Examples of First-order Circuits

for  $0 < t < t_0$ : RL Ckt driven by  $V_S u(t)$

$$i(t) = \frac{V_S}{R_1} (1 - e^{-t/\tau})$$

$$\text{where } \tau = L/R_1$$


at  $t_0$  when switch transition happens

$$i_L(t_0^-) = i_L(t_0^+)$$

$t_0$ : large enough for the Ckt to operate in  
steady-state

$\Rightarrow t_0$  is large enough for  $i_L(t_0) = \text{Steady State Current}$

$V_L(t_0) = \text{Steady State Voltage}$

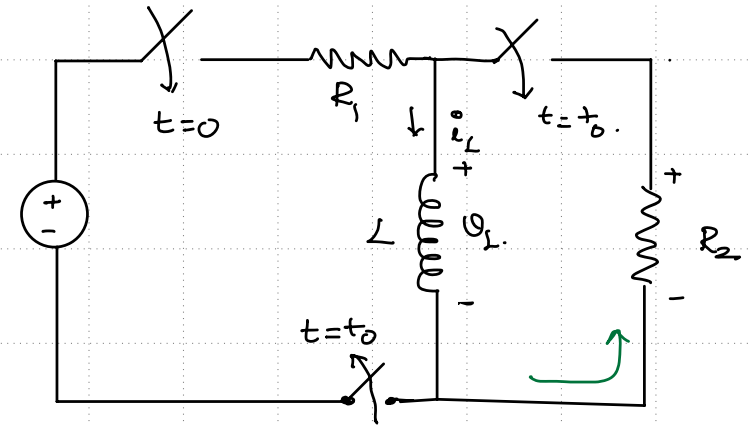

for  $t > t_0$ :

$$V_{R_2} = V_L$$

$$L \frac{di_L}{dt} = V_{R_2} = -i_L R_2$$

$$\frac{di_L}{dt} + \frac{R_2}{L} i_L = 0 \rightarrow (3)$$

$$\text{IF} = e^{t/\tau_2} \quad \text{where } \tau_2 = L/R_2$$

mul (3) by IF on both sides

$$\frac{d}{dt} (e^{t/\tau_2} i_L) = 0$$

$$i_L = c e^{-t/\tau_2}$$

$$\text{at } t_0: i_L(t_0) = c e^{-t_0/\tau_2}$$

$$c = i_L(t_0) e^{t_0/\tau_2}$$

$$\Rightarrow i_L(t) = i_L(t_0) e^{-(t-t_0)/\tau_2}$$

## Examples of First-order Circuits (Response to $e^{-2t}$ )

by KVL (for  $t > 0$ ):

$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L} e^{-2t} \rightarrow \textcircled{1}$$

Integrating factor =  $e^{R/L t}$


upon mul  $\textcircled{1}$  by IF & rearranging

$$\frac{d}{dt} (e^{R/L t} i(t)) = \frac{1}{L} e^{(R/L - 2)t}$$

$$i(t) = \frac{e^{-R/L t}}{L} \cdot \frac{1}{(R/L - 2)} e^{R/L t} e^{-2t} + C e^{-R/L t}$$

$$i(t) = \frac{1}{(R - 2L)} e^{-2t} + C e^{-R/L t}$$

C: based on Init Cond.

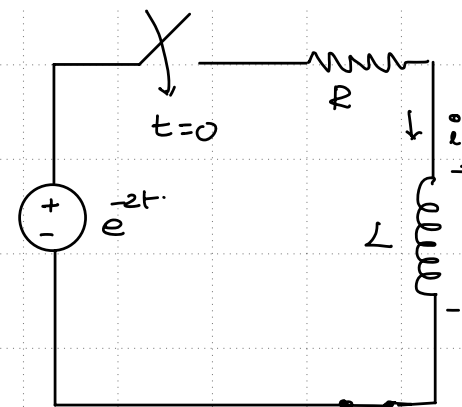

## Zero-input and Zero-state Response

