

.

---

# EE1101: Circuits and Network Analysis

## Lecture 12: Circuits with Three Terminal Elements

August 25, 2025


---

### Topics :

1. Three Terminal Circuit Elements
  2. Bipolar Junction Transistor (BJT)
-

## Three Terminal Circuit Elements

Representation:-

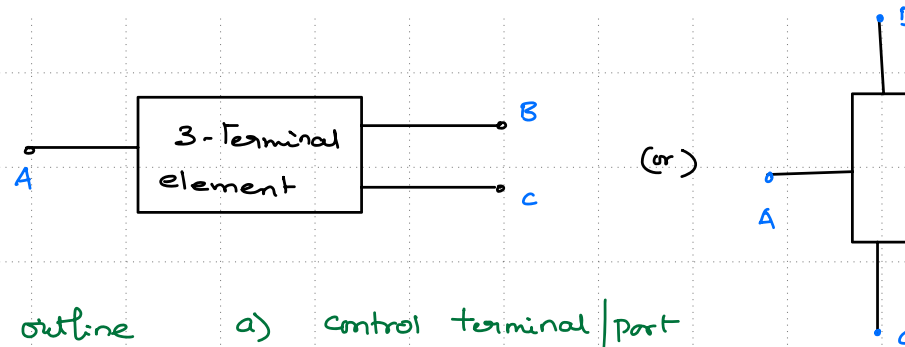

clearly outline

- a) control terminal/port
- b) main ckt/port.

Typically two modes


- a) Switch (ON & OFF state)
- b) Amplifier

conditions that define the operating mode must be known.

- when operating as a switch:
  - ON  $\rightarrow$  Very small resistance (ideally SC)
  - OFF  $\rightarrow$  Very large " (ideally OC)
- when operating as an Amplifier  $\rightarrow$  Model using dependent sources.

Not every 3-terminal element exhibit both the modes.
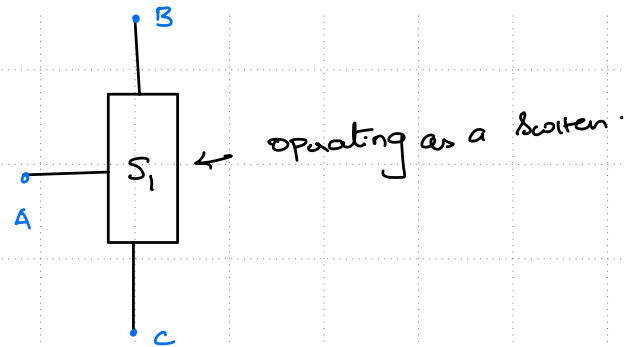
## Example: Three Terminal Circuit Elements



Def of 3-terminal element

a) A-C : Control part


b) B-C : main CKT

c)  $V_{AC} \leq 0$  : OFF state (B-C is  $\infty$ )

d)  $V_{AC} \geq 5V$  : ON state (B-C is SC)

e)  $0 < V_{AC} < 5$  : Amplifier

from prev. lec:

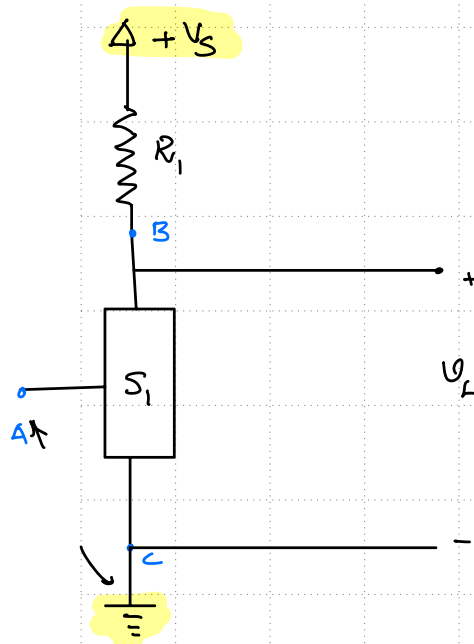


① if  $V_{AC} = 0V$  :  $S_1$  is acting as a switch in OFF state  
(Open CKT of B & C)

$$V_L = V_S$$


② if  $V_{AC} > 5V$  :  $S_1$  is acting as a switch in ON state  
(Short CKT of B & C)

$$V_L = 0$$


Eq. Circuit is

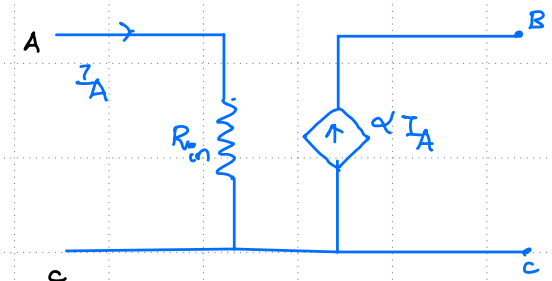

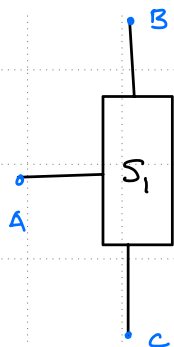
## Example: Three Terminal Circuit Elements



from prev. lec:

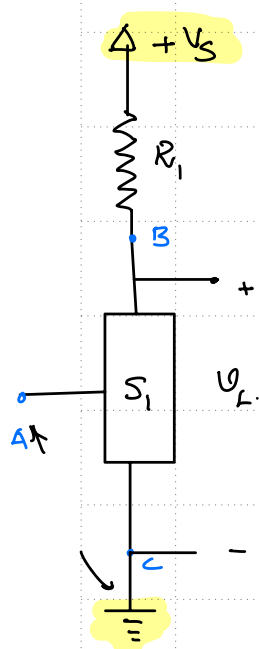

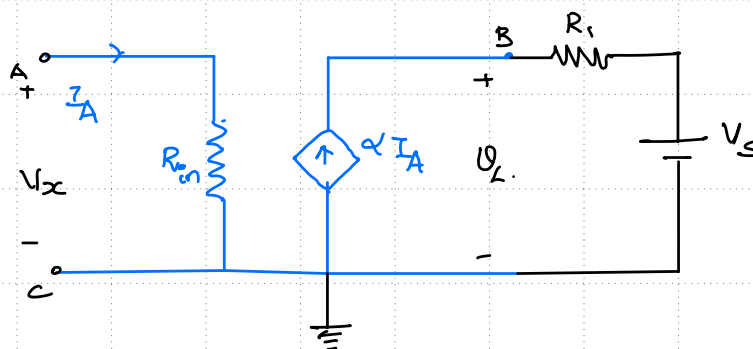③ if  $0 < V_{AC} < 5$  (operating as an amp)  
(or)  
 $V_x$



derive  $V_L$  in terms of  $V_x$

def of 3-terminal element

a) A-C : Control part


b) B-C : main CKT

c)  $V_{AC} \leq 0$  : OFF state (B-C is  $\infty$ )


d)  $V_{AC} \geq 5V$  : ON state (B-C is SC)

e)  $0 < V_{AC} < 5$  : Amplifier

Eq. circuit is

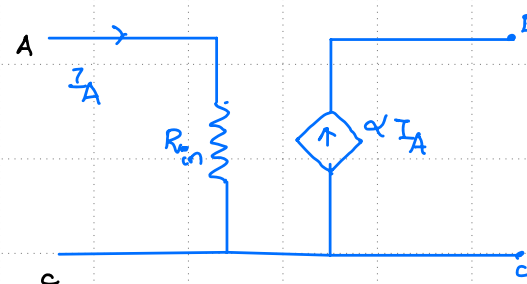
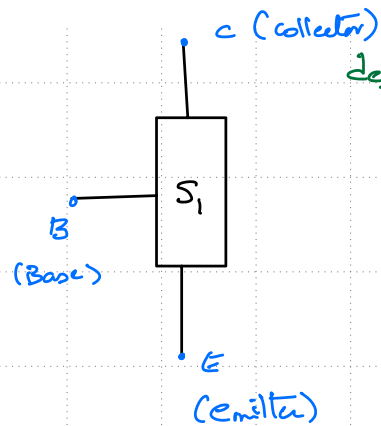
## Example: Three Terminal Circuit Elements (leading to def of BJT from a ckt point of view)



def of 3-terminal element

a) B-E : Control part



b) C-E : main ckt

c)  $V_{BE} \leq 0$  : OFF state (CE is OC)


e)  $0 \leq V_{BE} < V_{ON}$  Amplifier

d)  $V_{BE} > V_{ON}$  : ON state (CE is SC)

Eq. Circuit is

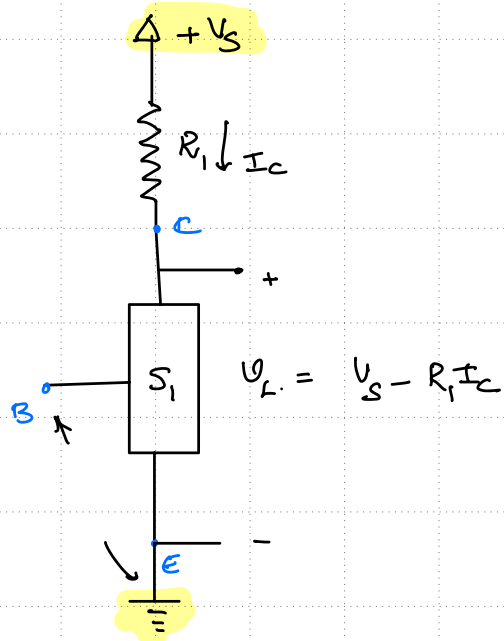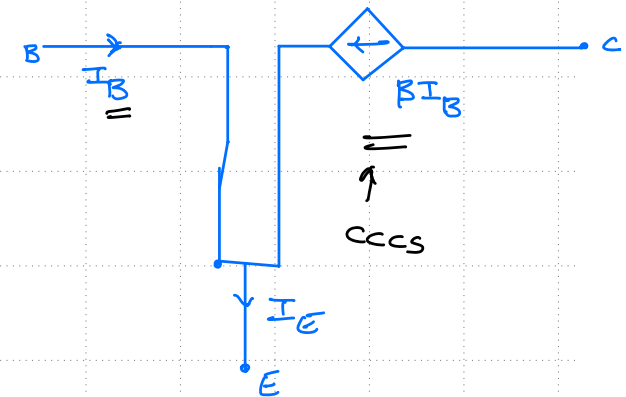
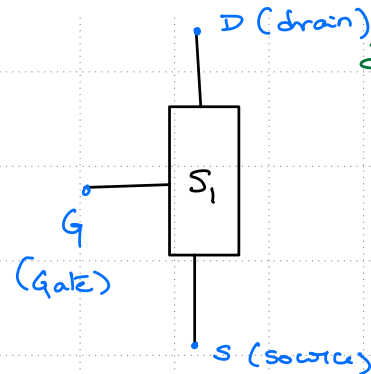
## Example: Three Terminal Circuit Elements (leading to def of MOSFET from a ckt point of view)



def of 3-terminal element

a)  $G-S$ : Control part



b)  $D-S$ : main ckt

c)  $V_{GS} \leq 0$ : OFF state ( $D-S$ )

d)  $V_{GS} \geq V_{ON}$ : ON state ( $D-S$  is SC)

e)  $0 \leq V_{GS} < V_{on}$  Amplifier &

Eq. Circuit is

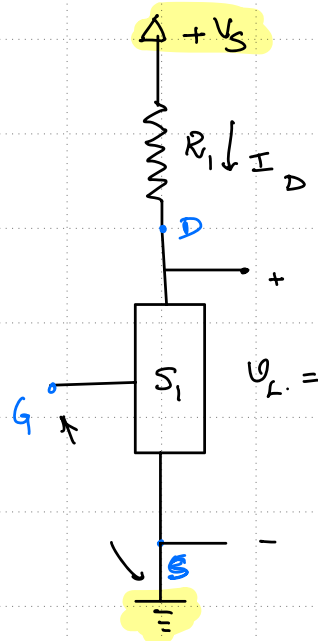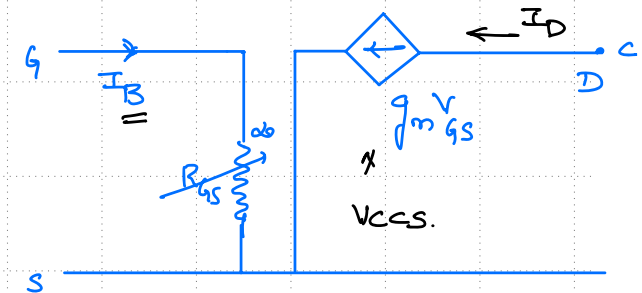

$$\text{as } V_{GS} > 0 \Rightarrow I_D > 0$$

$\downarrow$

$$V_L = V_S - R_L I_D \rightarrow \downarrow \text{ when } V_{GS} \text{ increases}$$

$\downarrow$  beyond a threshold  
 $V_L \approx 0 \rightarrow \text{SC} \rightarrow \text{ON state \& acts as a switch.}$