
EE1101: Circuits and Network Analysis

Lecture^{Eq 21} 20: Inductance


September 15, 2025 | Sep 16, 2025

Topics :

1. Response of inductors for Sinusoidal Signals
 2. Power and Energy Associated with Inductors
-

Inductors - Sinusoidal Response

Recall : Inductor \rightarrow 2 terminal ckt elem that satisfies $e_L(t) = \frac{d\lambda}{dt}$

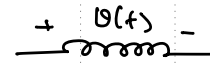
ckt symbol \rightarrow 
 $\rightarrow i_L$

passive sign convention is
used to ref v/i .

where $\lambda = L i$
 \downarrow
 inductance
 (determined by
 the geometry &
 mat. prop)

Typically L is assumed constant $\Rightarrow v_L(t) = L \frac{di}{dt}$

Example:

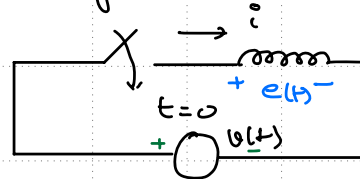

\rightarrow Time Varying Current \Rightarrow time varying mag field

$$e = v_L = L \frac{di}{dt} \Leftarrow \frac{d\lambda}{dt} \neq 0 \Leftarrow \text{with an inductor} \leftarrow \begin{array}{l} \text{2 loops of interest} \\ \downarrow \end{array}$$

$$\text{KVL} \Leftarrow \frac{d\lambda}{dt} \neq 0 \left\{ \begin{array}{l} \text{loop formed by} \\ \text{the ckt} \end{array} \right. \leftarrow$$


$$v_L(t) = e_L(t) = L \frac{di}{dt}$$

Example: $v_L(t)$ is applied to an inductor & goal is to compute $i_L(t)$. $\Rightarrow i_L(t) = \frac{1}{L} \int v_L(t) dt$

when $v_L(t) = \delta(t) \Rightarrow i_L(t) = \frac{1}{L} u(t)$

when $v_L(t) = u(t) \Rightarrow i_L(t) = \frac{1}{L} \int u(t) dt \Rightarrow \frac{1}{L} 't' \quad (\text{ramp signal}) \quad (for t \geq 0)$

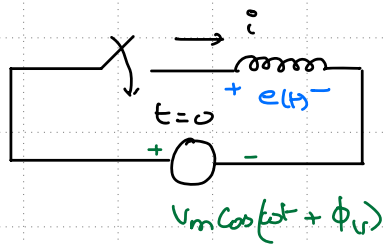Inductors - Impedance and Frequency Response



flux linkage associated with an inductor cannot change instantaneously

↓ results in an impulse voltage (x)

Current through an inductor cannot change instantaneously.

Example: $v(t) = V_m \cos \omega t$; $\frac{di}{dt} = \frac{1}{L} V_m \cos \omega t u(t)$; $i(0) = 0$.

$$\Rightarrow di = \frac{V_m}{L} \cos \omega t u(t) dt$$

$$\int_{i(0)}^{i(t)} di = \int_0^t \frac{V_m}{L} \cos \omega t dt$$

$$\Rightarrow i = \frac{V_m}{\omega L} \sin \omega t$$

Example: $v(t) = V_m \cos(\omega t + \phi_v)$; $\frac{di}{dt} = \frac{1}{L} V_m \cos(\omega t + \phi_v) u(t)$; $i(0) = 0$

$$di = \frac{V_m}{L} \cos(\omega t + \phi_v) u(t) dt$$

$$i(t) = \frac{V_m}{\omega L} [\sin(\omega t + \phi_v) - \sin \phi_v]$$

Inductors - Impedance and Frequency Response

Example: $e(t) = V_m \cos(\omega t + \phi_V)$ (During sinusoidal steady state)

$$i(t) = \frac{1}{L} \int e(t) dt = \frac{V_m}{\omega L} \sin(\omega t + \phi_V)$$

$$= \frac{V_m}{\omega L} \cos(\omega t + \phi_V - \pi/2)$$

In sinusoidal steady state use phasors to relate voltage & current associated with an inductor)

$$\vec{V}_L = \frac{V_m}{\sqrt{2}} \angle \phi_V$$

$$\vec{I}_L = \frac{V_m}{\sqrt{2} \omega L} e^{j(\phi_V - \pi/2)} = \frac{V_m}{\sqrt{2} \omega L} \angle \phi_i \text{ where } \phi_i = \phi_V - \pi/2.$$

Phase of current $(\phi_i) = \phi_V - \pi/2 \Rightarrow$ Current lags voltage by $\pi/2$

$$\vec{I}_L = \frac{1}{\omega L} \vec{V} e^{-j\pi/2} = \frac{1}{j\omega L} \vec{V}$$

def: only in sinusoidal steady state Impedance of an elem $= \frac{\vec{V}}{\vec{I}} \propto f(\omega)$
(Z)

for an inductor $= j\omega L.$


Inductors - Impedance and Frequency Response

$$\vec{Z} = j\omega L \propto f(\omega)$$

and $\vec{Z} \uparrow$ as $\omega \uparrow$

} magnitude of impedance ($\propto \omega$)

Phase ($\pi/2$)

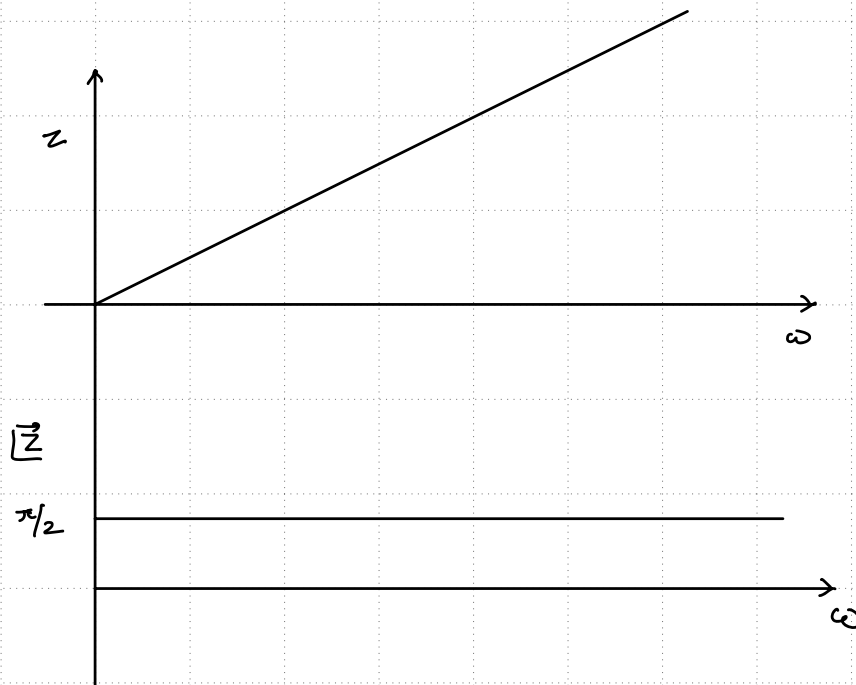


Complex Power Associated with Inductors

In steady state $\vec{V} = V \angle \phi_V$ and $\vec{I} = I \angle \phi_i = \frac{V}{Z} \angle \phi_V - \pi/2 = \frac{\vec{V}}{\underline{Z}}$

Complex power $\vec{S} = \vec{V} \vec{I}^* = (V \angle \phi_V) \left(\frac{\vec{V}}{\underline{Z}} \right)^* = \frac{V \angle \phi_V \cdot V \angle -\phi_V}{\underline{Z}^*}$
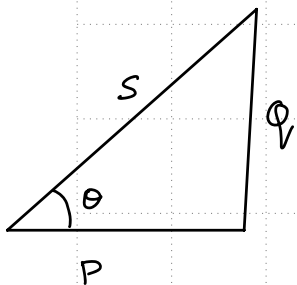
$$= j \frac{V^2}{Z} = j \left(\frac{V^2}{\omega L} \right) = P + jQ$$



$$\Rightarrow P = 0$$

$$Q = \frac{V^2}{\omega L} (>0)$$

Power factor = $\cos \theta = P/S = 0 \Rightarrow \theta = \pi/2$
(Lagging) or (Lag)

instantaneous Reactive power = $Q \sin 2\omega t = \frac{V^2}{\omega L} \sin 2\omega t$

instantaneous power = $\frac{V^2}{\omega L} \sin 2\omega t$

Energy associated with Inductors

$$\text{Energy} = \int \sin dt$$

Inductor \rightarrow Steady State $\&$ t_{ref} : $e(0) = 0$.

$$E(t) = \int_0^t \frac{V^2}{\omega L} \sin 2\omega t \, dt$$

$$E(t) = \frac{V^2}{2\omega^2 L} - \cos 2\omega t \Big|_0^t = \frac{V^2}{2\omega^2 L} (1 - \cos 2\omega t)$$

$$= \frac{V^2}{\omega^2 L} \sin^2 \omega t$$

$$= \left(\frac{V}{\omega L} \right)^2 L \sin^2 \omega t$$

$$= \underbrace{L I_m^2}_{\text{Energy}} \sin^2 \omega t$$

$$= L \frac{I_m^2}{2} \sin^2 \omega t$$

$$= \frac{1}{2} L \underbrace{I_m^2 \sin^2 \omega t}_{e(t)}$$

$$= \frac{1}{2} L e^2$$