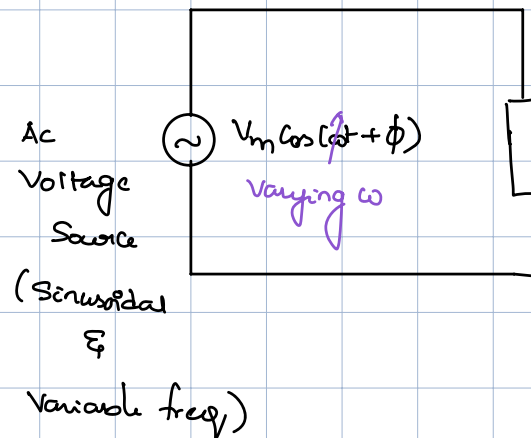


## Resonance in AC circuits:-



$$\vec{Z}_{eq} = R + jX$$

↓                  ↓  
Resistance    Reactance  $\propto$  freq.  
but  $L, C \rightarrow$  fixed.

(Sinusoidal Steady State)

Lec-38

Question: When is the mag. of current drawn from the source is Max

RMS value of  $I$

value of  $\omega$  for which  $I$  is Max  
 $|\vec{I}|$

$$\vec{I} = \frac{\vec{V}}{\vec{Z}_{eq}} \Rightarrow |\vec{I}| = \frac{|\vec{V}|}{|\vec{Z}_{eq}|}$$

for  $|\vec{I}|$  to maximum,  $|\vec{Z}_{eq}|$  must be minimum.

↓

minimum possible value:  $\vec{Z}_{eq} = R$

$$\Rightarrow X = 0$$

if such a possibility exists, ckt is under resonance

& freq at which  $X = 0$  occurs

is called the resonant freq.

when applied to


first-order ckt:

Resonance (??) { Series RL ( $X = 0$  when  $\omega = 0$ )  
RC ( $X = 0$  when  $\omega = \infty$ )

↓

Some additional condition rather than  $X = 0$ .

## Series RLC :-

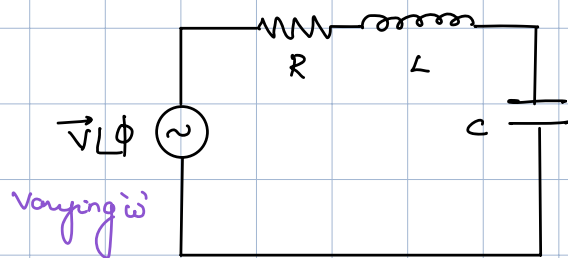

At  $f_{\text{res}} \omega = \frac{1}{\sqrt{LC}}$

$$\vec{Z}_{\text{eq}} = R$$

$$\vec{I} = \frac{\vec{V}}{\vec{R}} \Rightarrow |\vec{I}| = \frac{V}{R}$$

observation ①:  $\vec{V}$  and  $\vec{I}$  are in phase.

observation ②:  $\vec{S} = \vec{V} \vec{I}^*$

Source.  $= \vec{V} \frac{\vec{V}^*}{R} = \frac{|\vec{V}|^2}{R}$

$$= |\vec{I}|^2 R$$

Net power from source  
= active

observation ③:  $v(t) = R I_m \cos(\omega_0 t + \phi)$

$$i(t) = I_m \cos(\omega_0 t + \phi)$$

$$e_L(t) = \frac{1}{2} L \dot{i}^2(t) = \frac{1}{2} L I_m^2 \cos^2(\omega_0 t + \phi)$$

$$e_C(t) = \frac{1}{2} C \dot{v}_C^2(t) =$$

$$\vec{Z}_{\text{eq}} = R + j(\underbrace{\omega L - \frac{1}{\omega C}}_{X})$$

$\omega$  for which  $X=0$  results in Max. mag of  $|\vec{I}|$

$$\omega_0: \omega L - \frac{1}{\omega C} = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \leftarrow \text{resonant freq}$$

Question: for a Series RLC  $\omega_0 = \frac{1}{\sqrt{LC}}$  is the cond for  $X=0$

(commonly ref to as resonant freq)

While for a Series RL Ckt  $\omega=0$  is the cond for  $X=0$

(Not considered as resonance)

What completes the def of resonance?

$$v_L(t) = \frac{1}{C} \int i dt = \frac{I_m}{\omega_0 C} \sin(\omega_0 t + \phi)$$

$$e_C(t) = \frac{1}{2} C v_C^2(t) = \frac{1}{2} \frac{I_m^2}{\omega_0^2 C} \sin^2(\omega_0 t + \phi)$$

$$e_S(t) = e_x(t) + e_C(t) = \frac{1}{2} L I_m^2 \cos^2(\omega_0 t + \phi) + \frac{1}{2} \frac{I_m^2}{\omega_0^2 C} \sin^2(\omega_0 t + \phi)$$

energy stored in the ckt

$$\omega_0^2 C = \frac{1}{L} \cdot C = \frac{1}{L}$$

$$e_S(t) = \frac{1}{2} L I_m^2$$

(energy exchange b/w reactive elem in the ckt)

→ for a first order RL

ckt  $e_S(t)$  is not constant when  $x=0$ .

observation ④: Voltage across L+C (x): when  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\vec{V}_L = (j\omega_0 L) \vec{I} = j\omega_0 L \frac{\vec{V}}{R} = j\sqrt{\frac{L}{C}} \frac{\vec{V}}{R}$$

$$\vec{V}_C = \frac{1}{j\omega_0 C} \vec{I} = \frac{-j}{\omega_0 C} \frac{\vec{V}}{R} = -j\sqrt{\frac{L}{C}} \frac{\vec{V}}{R}$$

$\vec{V}_L$  &  $\vec{V}_C$  are out of phase (same mag)

$$\vec{V}_L + \vec{V}_C = 0$$

Voltage across individual LC is not zero.

which is not the case with a first order

RL ckt.

observation ⑤:

$$e_d(t) = \int s(t) dt = \int R I_m \cos(\omega_0 t + \phi) I_m \cos(\omega_0 t + \phi) dt$$

$$e_R(t) = I_m^2 R$$

energy per cycle

$$E_d(t) = \int_0^T e_d(t) = \left( \frac{1}{2} I_m^2 R \right) T$$

Observation ⑥: energy from source =  $E_d(t)$  + energy stored in Ckt per cycle  
Per cycle

↓  
Is this true??

(True provided  
initially the Ckt is  
at rest)