

.

EE1101: Circuits and Network Analysis

Lecture 26: Sinusoidal Response of First-Order Circuits

October 6, 2025

Topics :

1. Sinusoidal Response using complex exponentials
2. Role of Phasors and Impedances

Sinusoidal Response of First-Order Circuits : Recap from Lecture 25

$$\frac{dx}{dt} + Px(t) = A \cos(\omega t + \phi) \rightarrow (1)$$

use Complex exponentials : $\frac{d\hat{x}}{dt} + P\hat{x}(t) = Ae^{j(\omega t + \phi)} \rightarrow (2)$

sol of (1) $x(t) = \text{Re}\{\hat{x}(t)\}$

$$= \frac{A}{\sqrt{P^2 + \omega^2}} \cos(\omega t + \phi - \theta) + Ce^{-Pt}$$

where $\theta = \tan^{-1}(\omega/P)$

if $P > 0$: then as $t \rightarrow \infty$, $x(t) = x_{ss}(t) = \frac{A}{\sqrt{P^2 + \omega^2}} \cos(\omega t + \phi - \theta)$

for computing SS response \rightarrow phasor approach.

$$\vec{F} = \frac{A}{\sqrt{2}} \angle \phi$$


$$\vec{x}_{ss} = \frac{\vec{F}}{P + j\omega} \angle C$$

Steady-State Response-Phasors and Impedances (Equivalent Impedances and Divider Circuits)

governing DE: $\frac{di}{dt} + \frac{R}{L} i = \frac{V_m}{L} \cos(\omega t + \phi)$


Complete
response

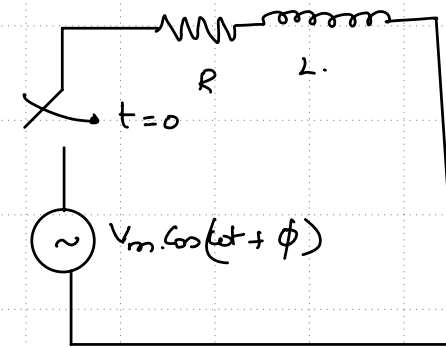$\rightarrow i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta) + C e^{-Rt/L}$
 where $\theta = \tan^{-1}(\omega L/R)$



Steady-state response \rightarrow Phasor domain approach.

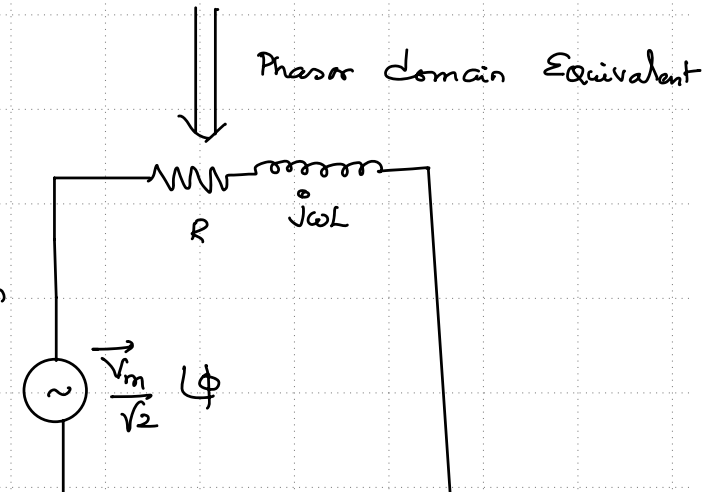- Replace source w/tn phasor representation
- " ckt elem w/tn impedances (written w/tn final pos)
- apply ckt laws / Mesh or node analysis



Ckt elem	Impedance
R	$\rightarrow R$
L	$\rightarrow j\omega L$
C	$\rightarrow 1/j\omega C$

Series Connection $\vec{Z}_{eq} = \sum_i \vec{Z}_i \rightarrow$ Voltage divider


Parallel Connection $\frac{1}{\vec{Z}_{eq}} = \sum_i \frac{1}{\vec{Z}_i} \rightarrow$ Current divider

Example - RC Circuit

Governing DE :- $v(t) = R i(t) + v_c(t)$

$$v(t) = R C \frac{dv_c}{dt} + v_c(t)$$
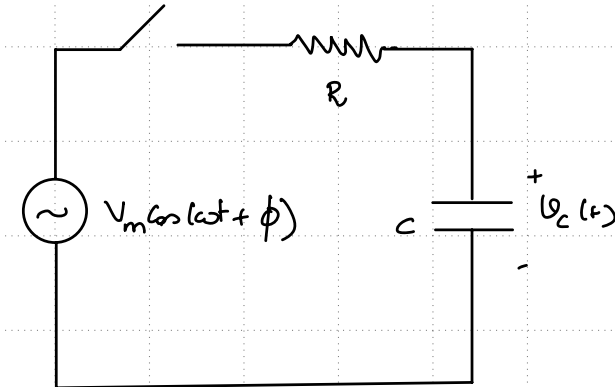
$$\Rightarrow \frac{dv_c}{dt} + \underbrace{\frac{1}{RC}}_{P(t)} v_c(t) = \underbrace{\frac{1}{RC} V_m \cos(\omega t + \phi)}_{A.}$$




$$\text{Complete response} = \frac{A}{\sqrt{P^2 + \omega^2}} \cos(\omega t + \phi - \theta) + c e^{-Pt}$$

$$= \frac{V_m}{RC \sqrt{\left(\frac{1}{RC}\right)^2 + \omega^2}} \cos(\omega t + \phi - \theta) + c e^{-t/RC} \quad \text{where } \theta = \tan^{-1}(\omega RC)$$

Steady State response (using Phasors)

$$\vec{V}_c = \frac{\vec{Z}_c}{\vec{Z}_R + \vec{Z}_c} \vec{V}_s = B e^{j\phi_B}$$
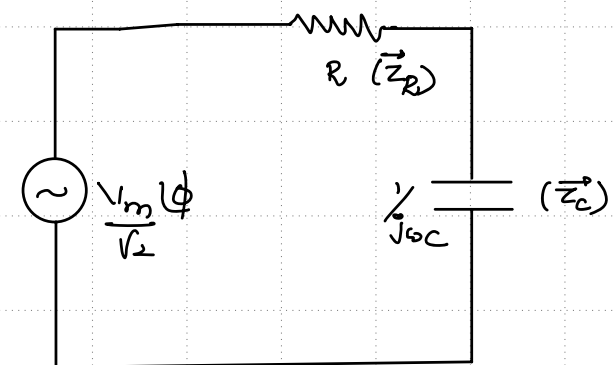
$$v_{c,ss}(t) = \sqrt{2} B \cos(\omega t + \phi_B)$$



Introduction to Response of Second-Order Circuits (2 energy storage elements)

Std form:- $\frac{d^2x}{dt^2} + 2\xi\omega_n \frac{dx}{dt} + \omega_n^2 x(t) = f(t) \leftarrow \textcircled{1}$

$\xi \rightarrow$ damping factor

$\omega_n \rightarrow$ natural freq
(or)

$$\frac{d^2x}{dt^2} + \underbrace{\frac{\omega_n}{Q}} \frac{dx}{dt} + \omega_n^2 x(t) = f(t)$$

\hookrightarrow Quality factor = $\frac{1}{2\xi}$


2 initial cond: $x(t_0)$ & $\left. \frac{dx}{dt} \right|_{t_0}$

Sol:-

$$x(t) = x_c(t) + x_p(t) \rightarrow \text{Particular Sol}$$

\downarrow
Complementary Sol
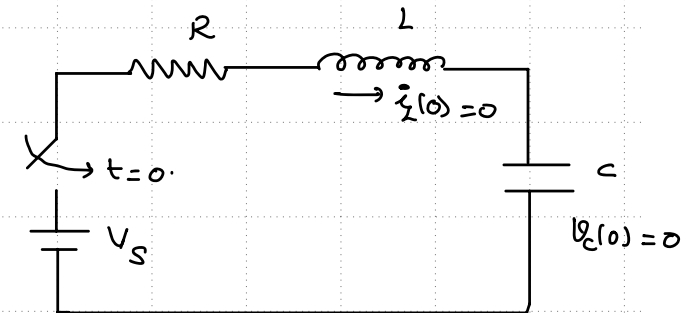
$$x_c(t) = \left\{ x : \frac{d^2x}{dt^2} + 2\xi\omega_n \frac{dx}{dt} + \omega_n^2 x(t) = 0 \right\}$$




by KVL: $V_S = Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int i dt$ (for $t > 0$)

diff wrt 't' $0 = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i(t)$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i(t) = 0$$

$$i(0) = 0$$

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{V_S(0)}{L} \quad (\because v_C(0) = 0)$$

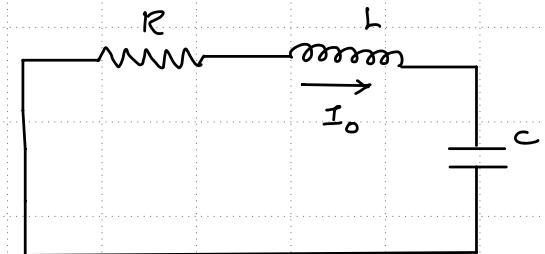

by KVL

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i(t) = 0$$

$$i(0) = I_0 \quad \text{and} \quad \left. \frac{di}{dt} \right|_{t=0} = -R I_0 / L$$