

.

EE1101: Circuits and Network Analysis

Lecture 34: Two-Port Networks

October 27, 2025

Topics :

1. Introduction to Two-Port Networks
2. Admittance and Impedance Parameters

Introduction to Two-Port Networks


Analysis of single-port networks

a) Port properties (OCV, SCC, Eq. impedance)

b) Thevenin & Norton Equivalent
(OCV + Eq. imp) (SCC || Eq. imp)

Deriving the Equivalent

Computing the Parameters of the Eq. ckt.

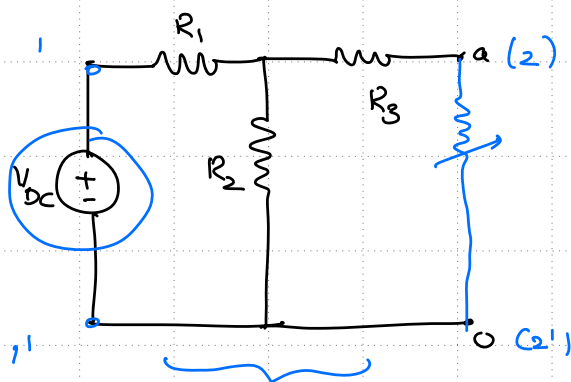


$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{DC}$$

$$R_{Th} = (R_1 || R_2) + R_3$$

When computing parameters,
the commonly employed route does not
involve Substitution / Superposition
Theorem.

Two-port Network :-

Use Case:

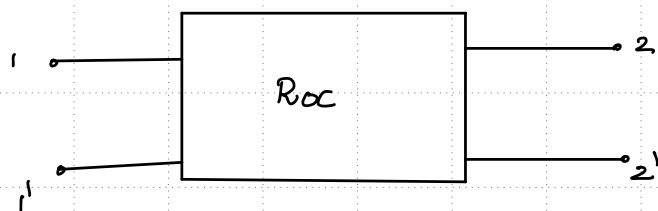

a) Useful when the goal is to compute response
associated with elements connected across two ports


Goal: Come with a mathematical rep of the Roc

so that Computing the resp associated with the two ports is
efficient

Can determine as
along as ckt is linear

Useful: if Roc: does not contain indep sources.

Introduction to Two-Port Networks

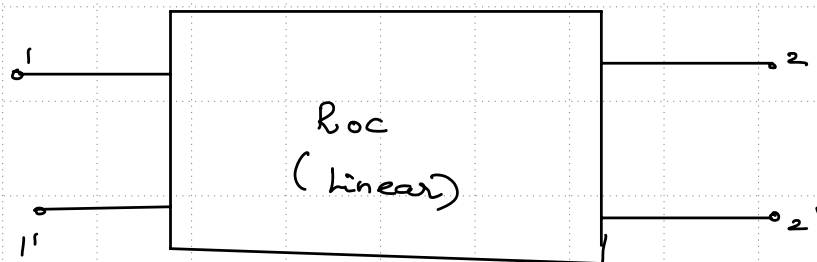

⇒ Come up with a simpler
mathematical rep

↓
can be achieved in

multiple ways

↓
each way has a
unique use case.

- 4 Possibilities
- ①-①' → V_1 , ②-②' → V_2
 - ①-①' → I_1 , ②-②' → I_2
 - ①-①' → I_1 , ②-②' → V_2
 - ①-①' → V_1 , ②-②' → I_2


① Connect a Vol Source &
Compute the Current
associated with it

② Connect a Curr Source & Compute the
Voltage associated with it.

Transmission & Inverse Transmission. ← ③ other ways.

Admittance Parameters (deriving the model)

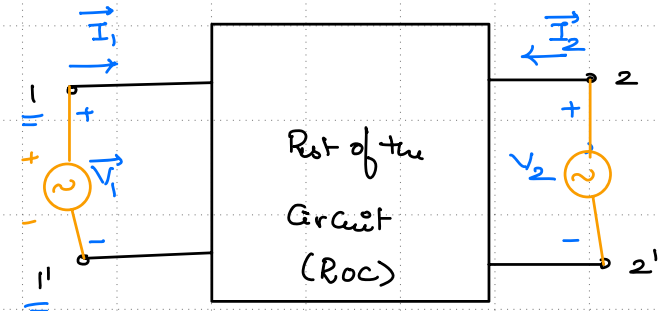→ involves using independent
Vol. Sources at both ports
& trying to express the
associated currents



$$\vec{I}_1 = \vec{I}_{1a} + \vec{I}_{1b}$$

$$\vec{I}_2 = \vec{I}_{2a} + \vec{I}_{2b}$$


Sub-ckt (a): Source at Port 2-2' is Null. (Short Circuit of Port 2-2')
($\vec{V}_2 = 0$)

$$\vec{I}_{1a} = \left(\frac{1}{\vec{Z}_{11}} \right) \vec{V}_1$$

$\vec{Z}_{11} \rightarrow \vec{Z}_{11} \rightarrow$ Eq. imp of Port
1-1' with 2-2'

$\vec{Y}_{11} \rightarrow$ admittance.

Short Circuited = 1'

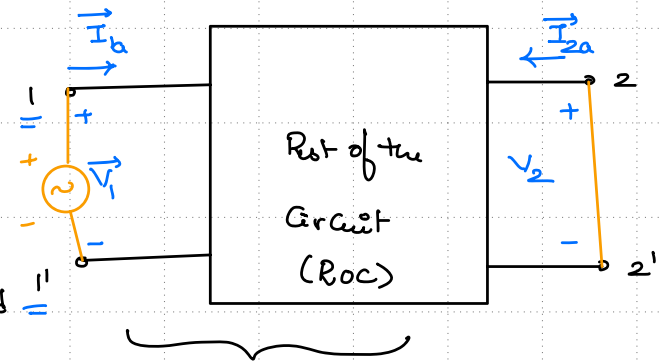

$$\vec{I}_{2a} = -\vec{I}_{sc} \text{ of Port } 2-2'$$


$$= \vec{Y}_{21} \vec{V}_1$$

$\vec{Y}_{21} \rightarrow$ admittance

Admittance Parameters (Short Circuit Parameters)

Sub-ckt (b): Source at Port 1-1' is Null. (Short Circuit of Port 1-1')
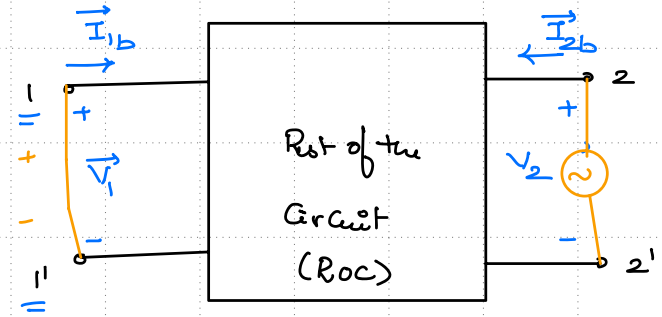
$$\begin{aligned}\vec{I}_{1b} &= -(\text{SC Current of Port 1-1'}) \\ &= \vec{y}_{12} \vec{V}_2\end{aligned}$$



$$\vec{I}_{2b} = \frac{1}{\vec{Z}_{22}} \vec{V}_2 = \vec{y}_{22} \vec{V}_2$$

$\vec{Z}_{22} \rightarrow$ Eq. imp of Port 2-2' when 1-1' is short circuited
 \vec{y}_{22}

Overall model:

$$\vec{I}_1 = \vec{I}_{1a} + \vec{I}_{1b} = \vec{y}_{11} \vec{V}_1 + \vec{y}_{12} \vec{V}_2 \quad - (\text{SCC associated w/tn 1-1'})$$

$$\vec{I}_2 = \vec{I}_{2a} + \vec{I}_{2b} = \vec{y}_{21} \vec{V}_1 + \vec{y}_{22} \vec{V}_2$$

$- (\text{SCC associated w/tn 2-2'})$

$$\begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} \vec{y}_{11} & \vec{y}_{12} \\ \vec{y}_{21} & \vec{y}_{22} \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}$$

$\vec{y}_{11} \rightarrow$ Eq. admittance w/tn 2-2' Shorted
 $\vec{y}_{22} \rightarrow$ Eq. admittance w/tn 1-1' Shorted

Methodology to derive the mathematical model of a 2-part n/w.

Step 1: Connect a Source at each port

(if \vec{V} source is connected, Derive an expression for Current)

(if \vec{I} " " " , Derive " " " Voltage)

↓
function of port Prop.
(or)

response of 2 sub ccts

Step 2: Compute the desired responses as a sum of resp. obtained from 2 sub ccts

sub ckt (a) & (b)

Step 3: Put them together & build matrix rep of the 2-part n/w.

for admittance parameters

$$\begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} \vec{Y}_{11} & \vec{Y}_{12} \\ \vec{Y}_{21} & \vec{Y}_{22} \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}$$

Computing

$$\vec{Y}_{11} = \frac{\vec{I}_1}{\vec{V}_1} \bigg|_{\vec{V}_2=0} \quad \vec{Y}_{21} = \frac{\vec{I}_2}{\vec{V}_1} \bigg|_{\vec{V}_2=0}$$

$$\vec{Y}_{12} = \frac{\vec{I}_1}{\vec{V}_2} \bigg|_{\vec{V}_1=0} \quad \vec{Y}_{22} = \frac{\vec{I}_2}{\vec{V}_2} \bigg|_{\vec{V}_1=0}$$