

FIGURE 6.17 Coupling to floating victim

$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \Delta V_{\text{aggressor}}$$

 


FIGURE 6.18 Coupling to driven victim

$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \frac{1}{1 + k} \Delta V_{\text{aggressor}}$$



 
 



FIGURE 6.28 Wire shielding topologies

 

(a)




 


(b)

 

(c)

FIGURE 6.29 Crosstalk control schemes

  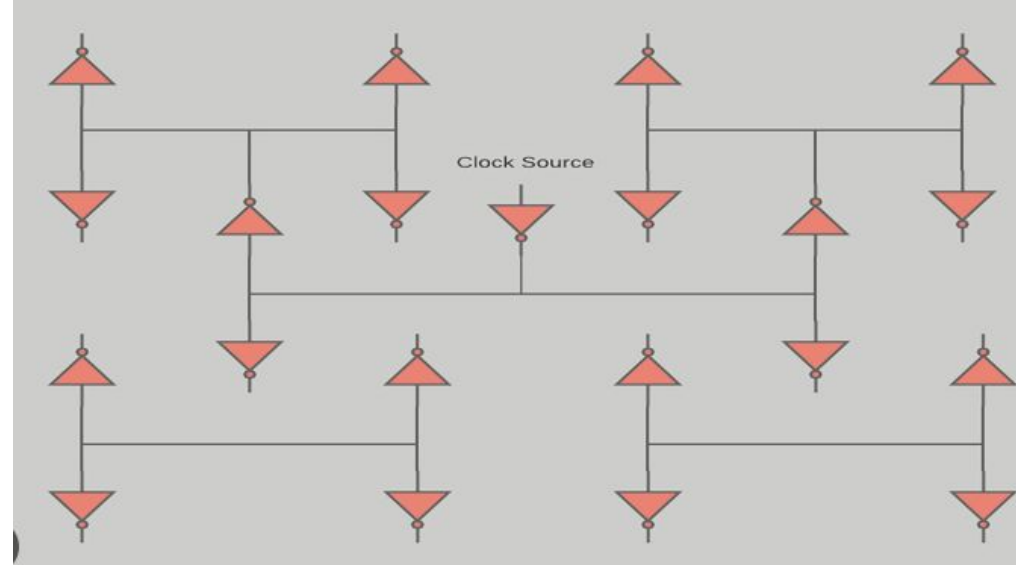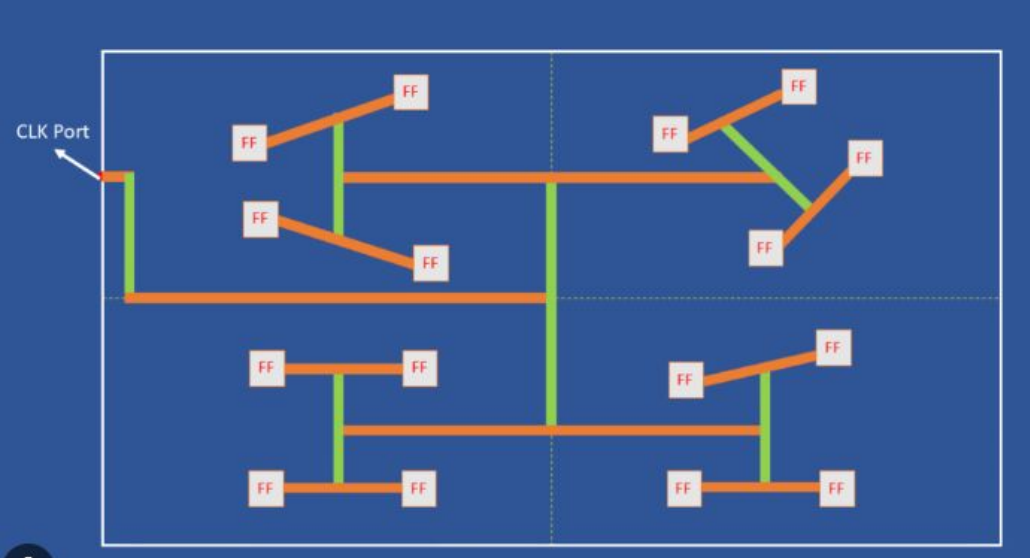

 


FIGURE 6.6

Two conductors with equal resistance

TABLE 6.2 Bulk resistivity of pure metals at 22 °C

Metal	Resistivity ($\mu\Omega \cdot \text{cm}$)
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Molybdenum (Mo)	5.3
Titanium (Ti)	43.0

Compute the sheet resistance of a 0.22 μm thick Cu wire in a 65 nm process. Find the total resistance if the wire is 0.125 μm wide and 1 mm long. Ignore the barrier layer and dishing.

SOLUTION: The sheet resistance is

$$R_{\square} = \frac{2.2 \times 10^{-8} \Omega \cdot \text{m}}{0.22 \times 10^{-6} \text{ m}} = 0.10 \Omega/\square \quad (6.4)$$

The total resistance is

$$R = (0.10 \Omega/\square) \frac{1000 \mu\text{m}}{0.125 \mu\text{m}} = 800 \Omega \quad (6.5)$$

 


FIGURE 6.11 Multilayer capacitance model

 


FIGURE 6.14 Equivalent circuit for example

 


FIGURE 6.16 Capacitances to adjacent neighbor and to ground

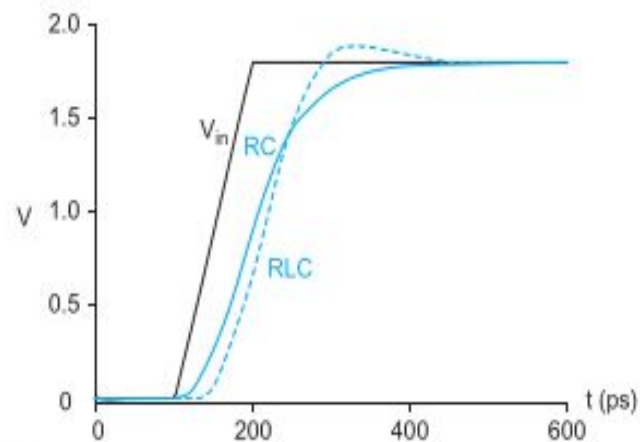
 
 


FIGURE 6.21 Wide clock line modeled with and without inductance

 
 


FIGURE 6.22 Wide clock line interdigitated with power and ground lines to reduce inductance

 


FIGURE 6.23 Inductive and capacitive crosstalk in a bus

 
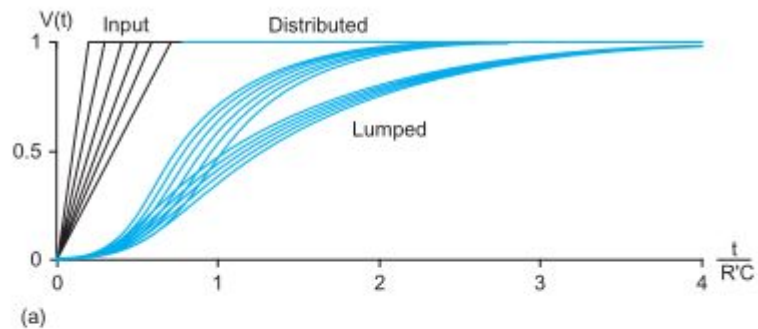


FIGURE 6.25 Effect of rise time on lumped and distributed RC circuit delays

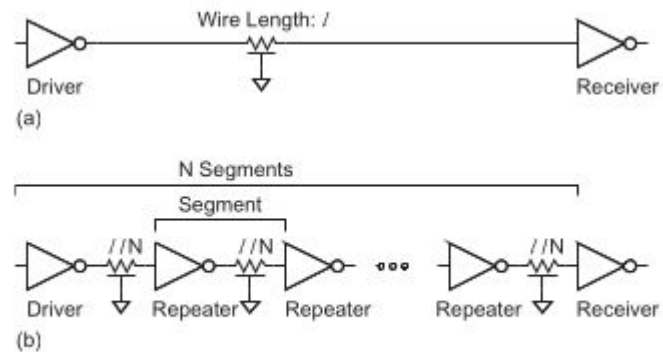


FIGURE 6.26 Wire with and without repeaters

 


FIGURE 6.31

Regenerator




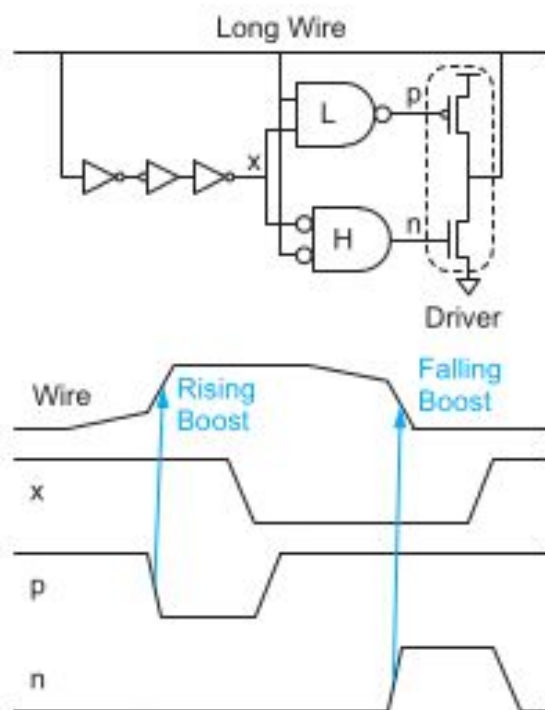
 



FIGURE 6.32 Regenerator

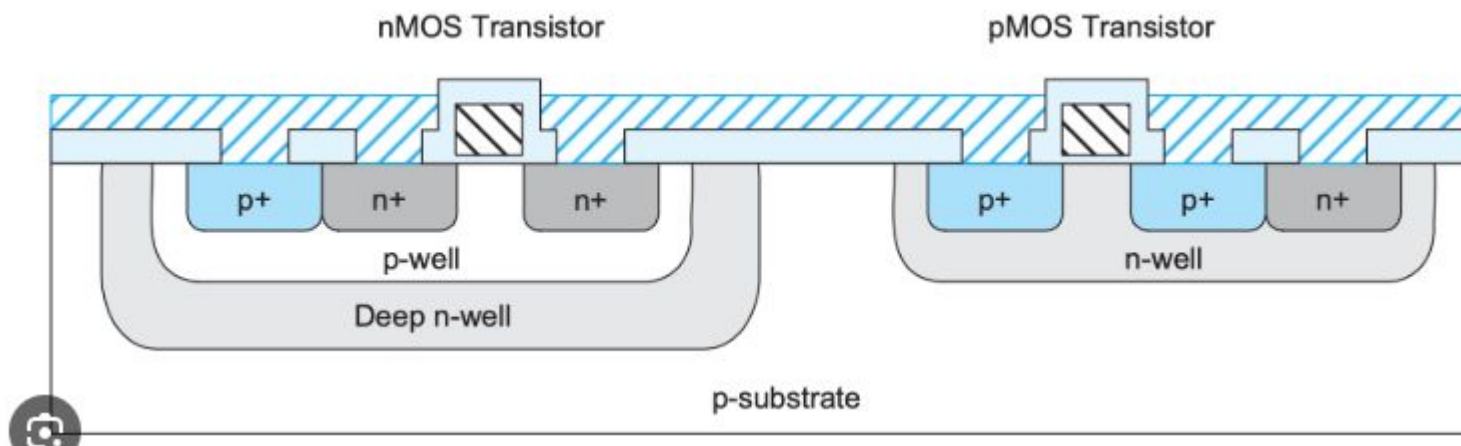

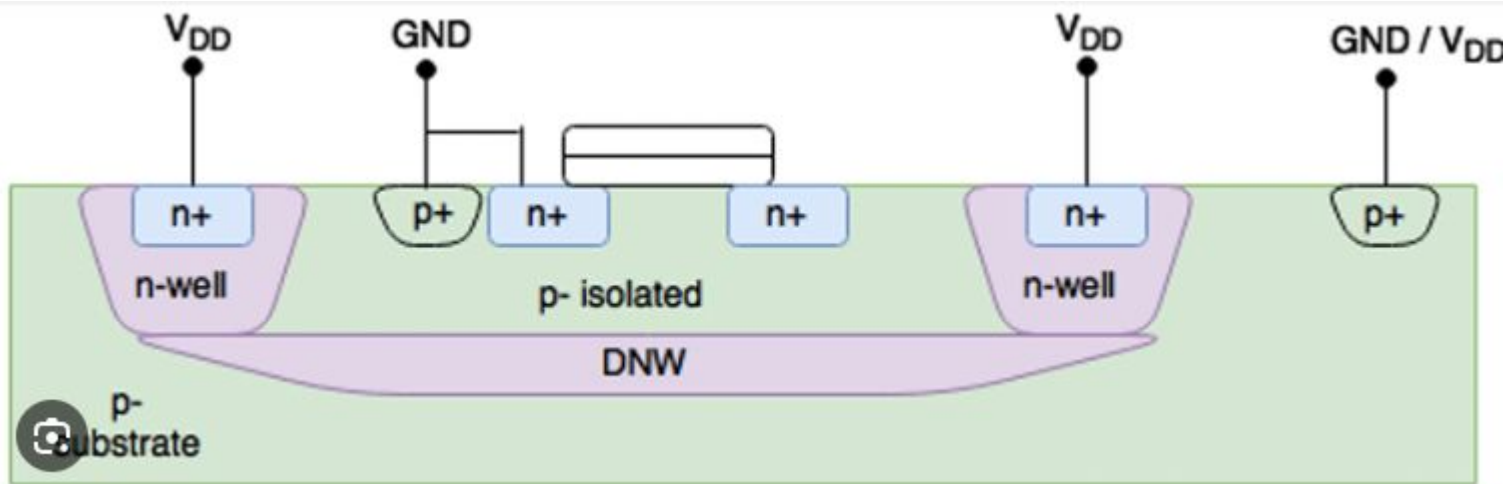


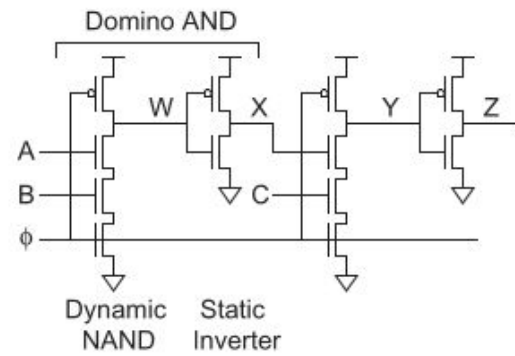

(a)

 


(b)

 


(c)


FIGURE 9.28 Domino gates

 

(a)

 

(b)

 

(c)

FIGURE 9.30 Dual-rail domino gates

TABLE 9.2 Dual-rail domino signal encoding

<i>sig_h</i>	<i>sig_l</i>	Meaning
0	0	Precharged
0	1	'0'
1	0	'1'
1	1	Invalid

 


FIGURE 9.31 Dual-rail domino gate with completion detection

Multiple-Output Domino Logic (MODL)

$$c_1 = g_1 + p_1 c_0$$

$$c_2 = g_2 + p_2 (g_1 + p_1 c_0)$$

$$c_3 = g_3 + p_3 (g_2 + p_2 (g_1 + p_1 c_0))$$

$$c_4 = g_4 + p_4 (g_3 + p_3 (g_2 + p_2 (g_1 + p_1 c_0)))$$

$$g_i = a_i b_i$$

$$p_i = a_i \oplus b_i$$


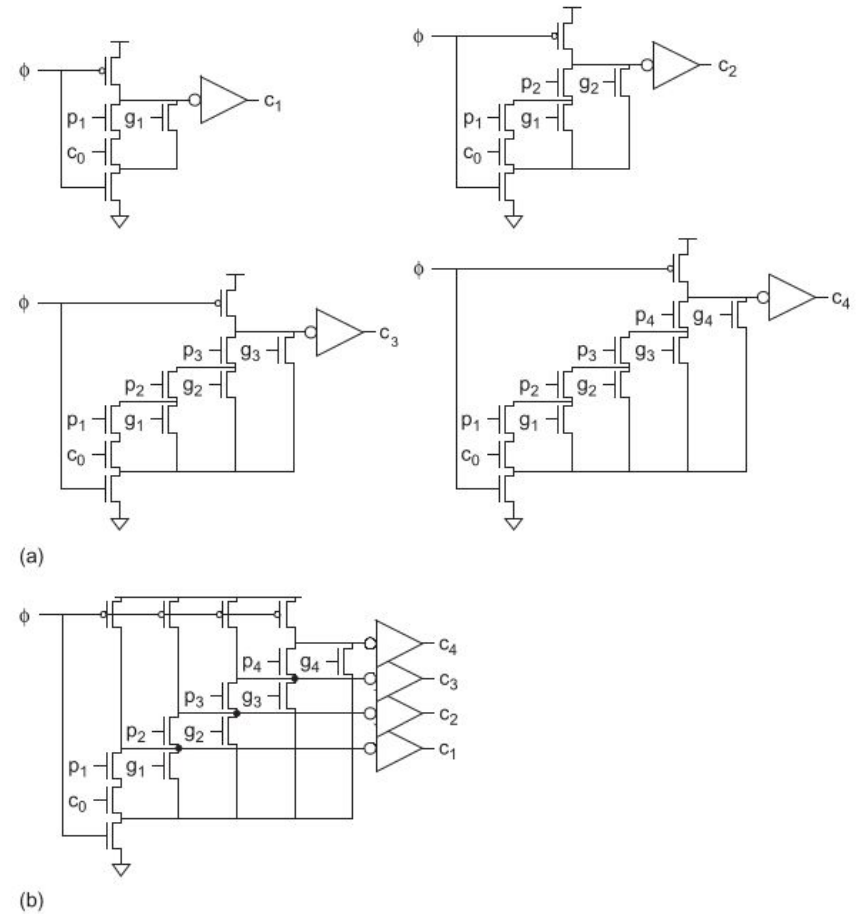



FIGURE 9.44 Conventional and MODL carry chains

Circuit Pitfalls

 - ❖ Threshold drops
- ❖ Ratio failures
- ❖ Leakage
- ❖ Charge sharing
- ❖ Power supply noise
- ❖ Coupling
- ❖ Minority carrier injection
- ❖ Back-gate coupling
- ❖ Diffusion input noise sensitivity
- ❖ Race conditions
- ❖ Delay matching
- ❖ Metastability
- ❖ Hot spots
- ❖ Soft errors
- ❖ Process sensitivity



(a)

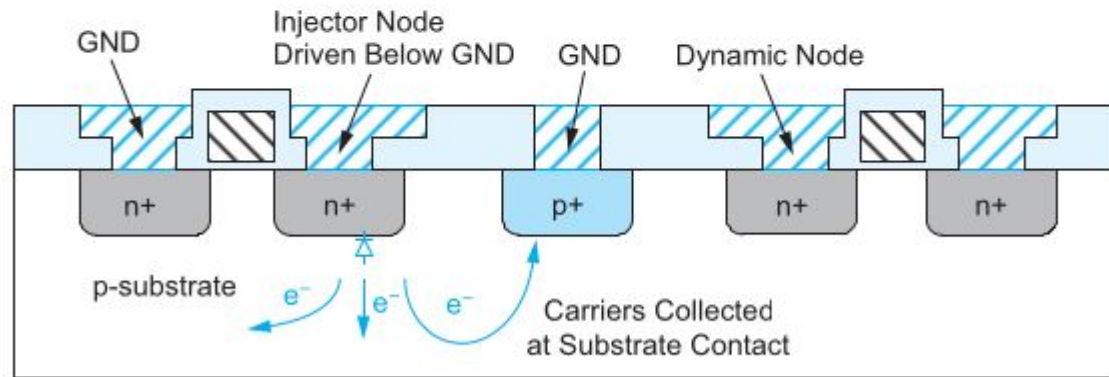

(b)

FIGURE 9.58 Minority carrier injection and collection

 


FIGURE 9.56 Charge sharing on dynamic gate driving pass transistor

 
 


FIGURE 9.57 Power supply IR drops


 


FIGURE 9.59 Back-gate coupling

 

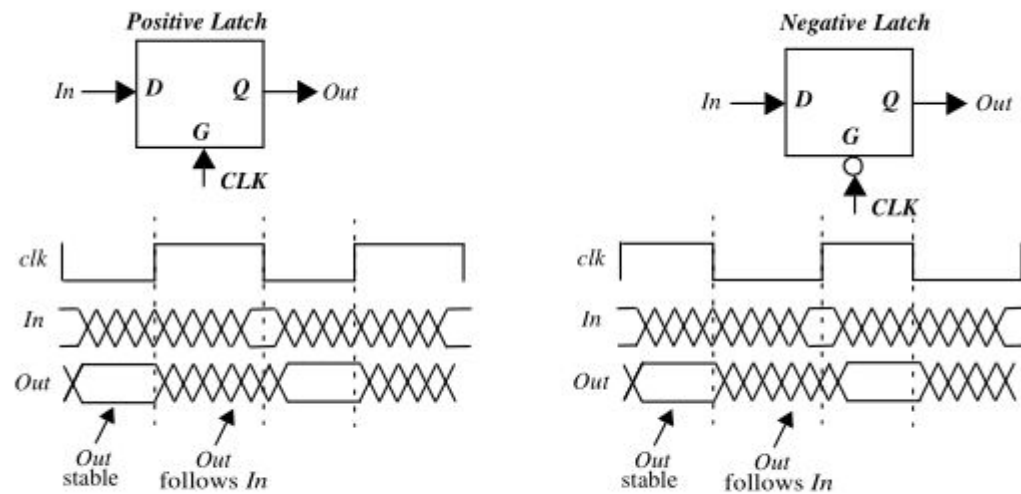


Figure 7.3 Timing of positive and negative latches.

 


Figure 7.4 Two cascaded inverters (a) and their VTCs (b).


 
 


Figure 7.12 Positive latch built using transmission gates.

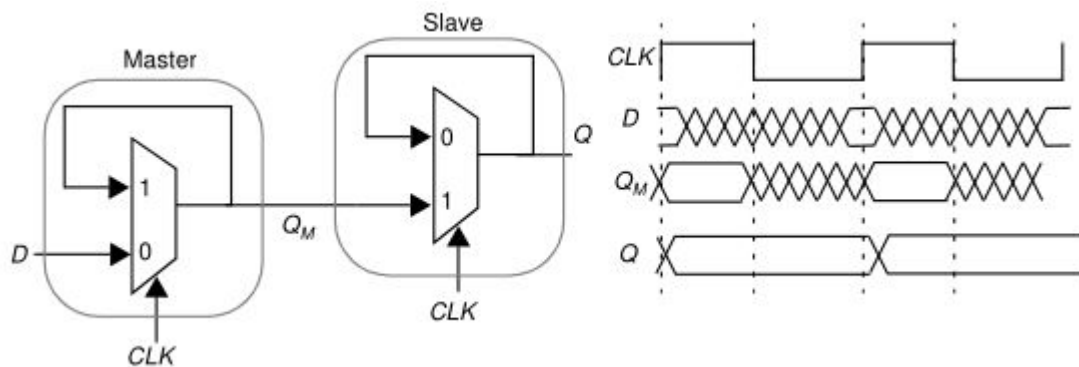


 
 


Figure 7.20 Master-slave register based on NMOS-only pass transistors.

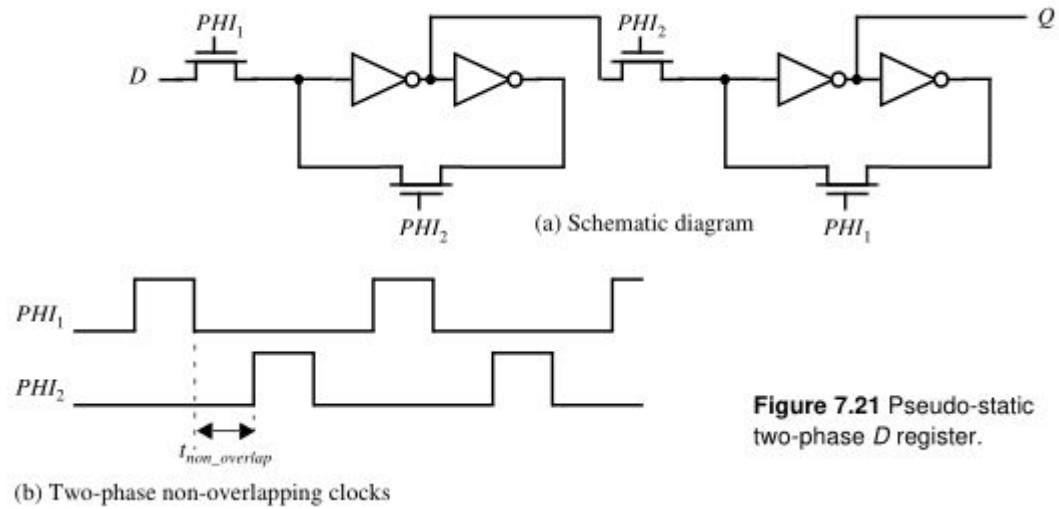

 


Figure 7.24 Dynamic *edge-triggered* register.

$$t_{overlap0-0} < t_{T1} + t_{I1} + t_{T2}$$


 
 


Figure 7.25 Impact of non-overlapping clocks.

Similarly, the constraint for the 1-1 overlap is given as:

$$t_{hold} > t_{overlap1-1}$$

register (Cuzak175), and operates in two phases.

 

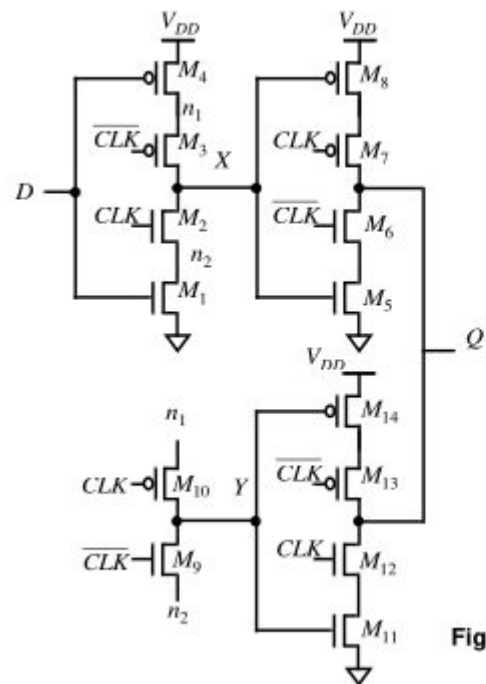


Figure 7.29 C²MOS based dual-edge triggered register.

 
 


Figure 7.30

 


Figure 7.31

 


Figure 7.32 Simplified TSPC latch (also called split-output).

 


Figure 7.33 Positive edge-triggered register TSPC.

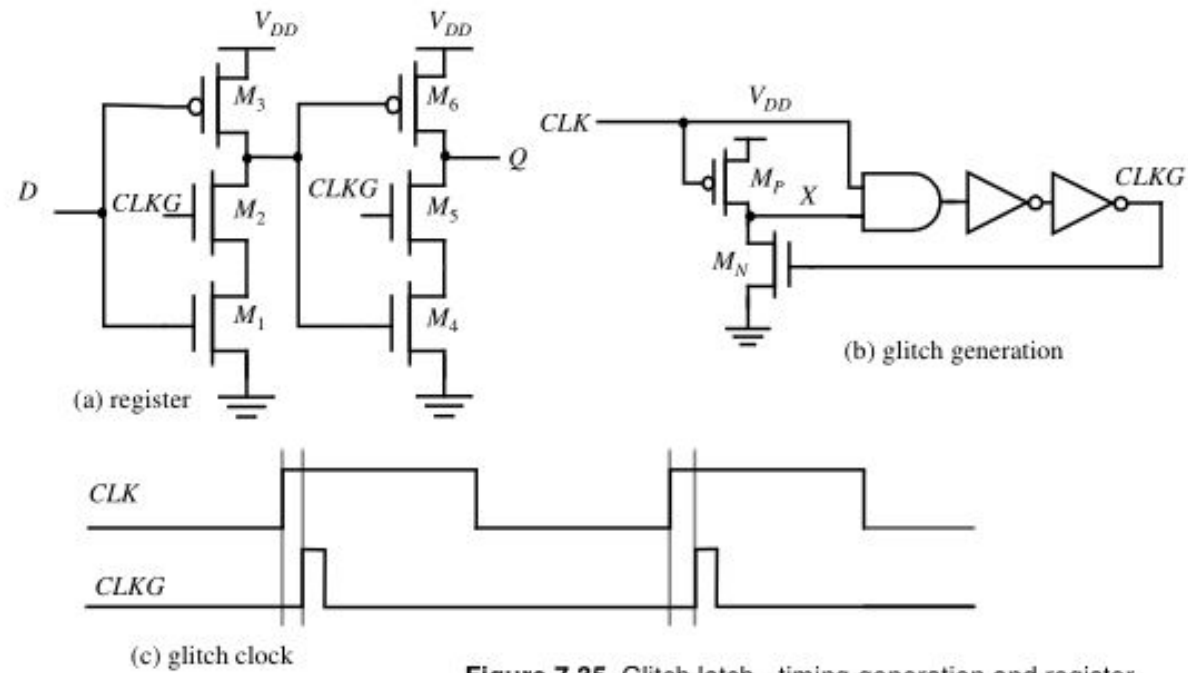


Figure 7.35 Glitch latch - timing generation and register.

