

---

# EE1101: Circuits and Network Analysis

## Lecture 37: Two Port Networks

---

### Topics :

1. Transmission Parameters
  2. Series and Cascade Connection of Two-port networks
-

## Transmission parameters


Model

$$\begin{bmatrix} \vec{V}_S \\ \vec{I}_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \vec{V}_R \\ \vec{I}_R \end{bmatrix}$$

Complex valued

$$\left. \begin{aligned} A &= \left. \frac{\vec{V}_S}{\vec{I}_R} \right|_{\vec{I}_R=0} \\ C &= \left. \frac{\vec{I}_S}{\vec{V}_R} \right|_{\vec{I}_R=0} \end{aligned} \right\} \text{open of Port } R-R'$$

$$\left. \begin{aligned} B &= \left. \frac{\vec{V}_S}{\vec{I}_R} \right|_{\vec{V}_R=0} \\ D &= \left. \frac{\vec{I}_S}{\vec{I}_R} \right|_{\vec{V}_R=0} \end{aligned} \right\} \text{Short circuit of Port } R-R'$$

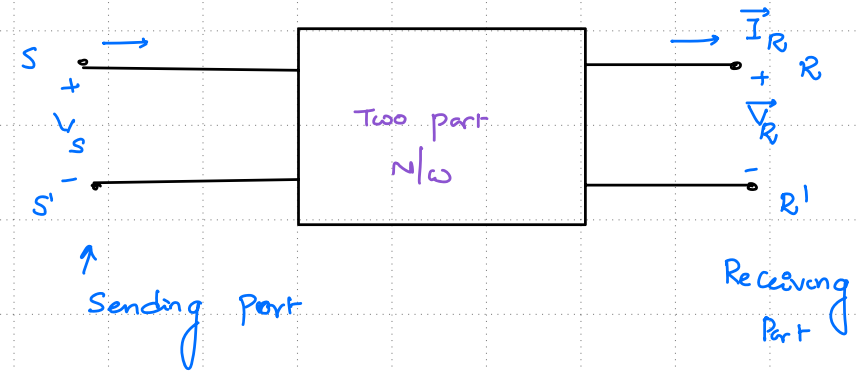

2 diff :-


- Ports are ref as Sending & Receiving Port
- Sending Port & Receiving Port adopt different sign convention.

Computing Parameters (A, B, C, D)


open circuit of Port R-R' (A, C)

Short circuit of Port R-R' (B, D)

## Transmission parameters - Example

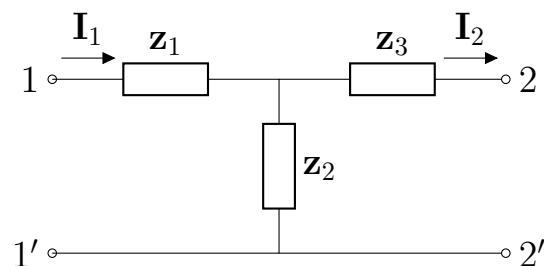
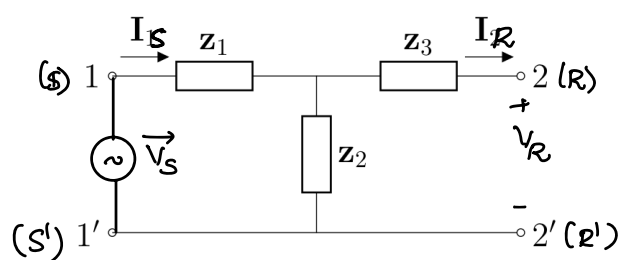
$$\begin{bmatrix} \vec{V}_S \\ \vec{I}_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \vec{V}_R \\ \vec{I}_R \end{bmatrix}$$




$$A = \left. \frac{\vec{V}_S}{\vec{V}_R} \right|_{\vec{I}_R = 0}$$

$$\vec{V}_R = \frac{\vec{z}_2}{\vec{z}_1 + \vec{z}_2} \vec{V}_S \Rightarrow A = \frac{\vec{z}_2 + \vec{z}_1}{\vec{z}_1}$$

$$C = \left. \frac{\vec{I}_S}{\vec{V}_R} \right|_{\vec{I}_R = 0}$$
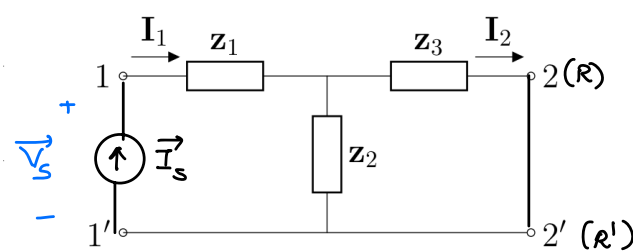
$$\vec{I}_S = \frac{\vec{V}_S}{\vec{z}_1 + \vec{z}_2} \Rightarrow C = \frac{A}{\vec{z}_1 + \vec{z}_2} = \frac{1}{\vec{z}_2}$$



$$D = \left. \frac{\vec{I}_S}{\vec{I}_R} \right|_{\vec{V}_R = 0}$$

$$\vec{I}_R = \frac{\vec{z}_2}{\vec{z}_1 + \vec{z}_2} \vec{I}_S \Rightarrow D = \frac{\vec{z}_3 + \vec{z}_2}{\vec{z}_2}$$


$$B = \left. \frac{\vec{V}_S}{\vec{I}_R} \right|_{\vec{V}_R = 0}$$

$$\vec{V}_S = \vec{V}_{z_1} + \vec{V}_{(\vec{z}_2 \parallel \vec{z}_3)} \quad \vec{z}_{eq} = \vec{z}_1 + (\vec{z}_2 \parallel \vec{z}_3)$$

$$\vec{V}_S = \vec{I}_S \vec{z}_{eq}$$

$$\vec{V}_S = D \vec{I}_R \vec{z}_{eq}$$
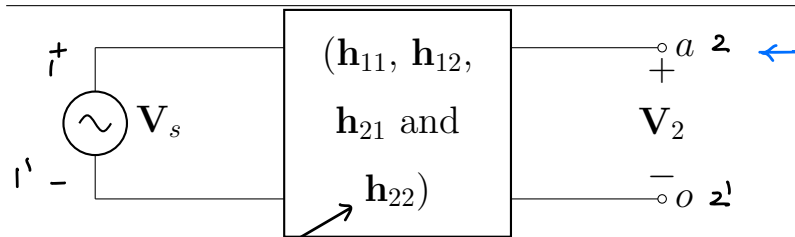
## Computing Thevenin Equivalent of a Port




given: a) a 2-port rep of the N/w & h-parameters

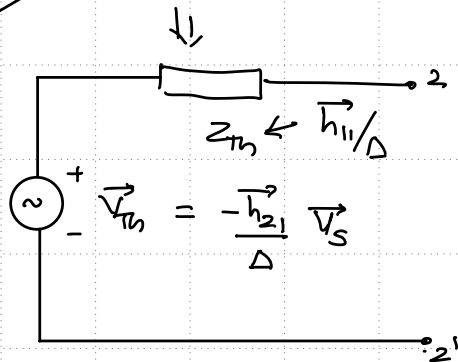b) Port 1-1' has a fixed source connected to it.

Compute: Thevenin EQ. as seen from 2-2'

When  
Roc has  
no independent  
source.



$$\vec{Z}_{th} = \left. \frac{\vec{V}_2}{\vec{I}_2} \right|_{\vec{V}_s = 0 \text{ (or) } \vec{V}_1 = 0}$$

$$\text{from (a): } 0 = h_{11}\vec{I}_1 + h_{12}\vec{V}_2 \rightarrow (3)$$

$$\text{from (b): } \vec{I}_2 = h_{21}\vec{I}_1 + h_{22}\vec{V}_2 \rightarrow (4)$$

Compute  $\vec{I}_1$  from (3) & plug in (4)

$$\frac{\vec{V}_2}{\vec{I}_2} = \frac{h_{11}}{\Delta}$$

$$\begin{bmatrix} \vec{V}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{V}_2 \end{bmatrix} \quad \vec{V}_1 = h_{11}\vec{I}_1 + h_{12}\vec{V}_2 \rightarrow (a)$$

$$\vec{I}_2 = h_{21}\vec{I}_1 + h_{22}\vec{V}_2 \rightarrow (b)$$

$\vec{V}_{th}$  = open ckt vol of 2-2' ( $\vec{I}_2 = 0$ ) & given

$$\because \vec{I}_2 = 0 \Rightarrow \vec{V}_2 = -\frac{h_{21}}{h_{22}}\vec{I}_1 \rightarrow (1) \quad \vec{V}_1 = \vec{V}_s \text{ (from (b))}$$


$$\text{from (a): } \vec{I}_1 = \frac{\vec{V}_s - h_{12}\vec{V}_2}{h_{11}} \rightarrow (2)$$

$$\text{Plug in (2) in (1)} \Rightarrow \vec{V}_2 = \frac{-h_{21}}{h_{22}} \left( \frac{\vec{V}_s - h_{12}\vec{V}_2}{h_{11}} \right)$$

$$\Rightarrow \vec{V}_2 = -\frac{h_{21}}{\Delta}\vec{V}_s$$

$\vec{V}_{th} \rightarrow \Delta \leftarrow \det \text{ of } h\text{-param matrix.}$

## Series Connection of Two Port Networks

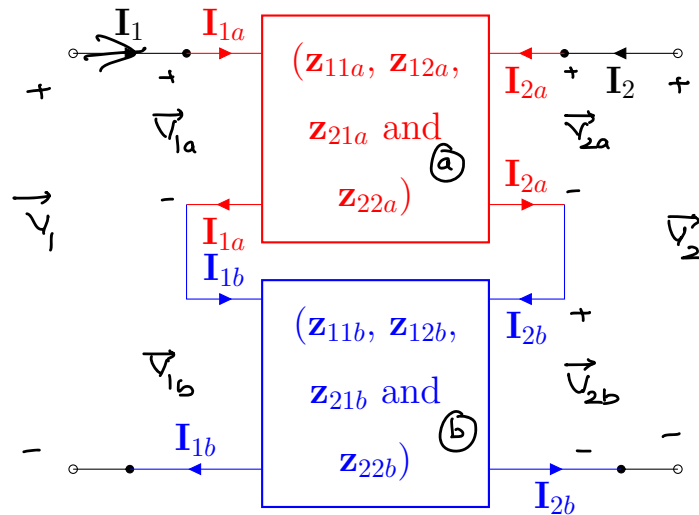

for 2-port N/a (a)

$$\begin{bmatrix} \vec{V}_{1a} \\ \vec{V}_{2a} \end{bmatrix} = \begin{bmatrix} \vec{z}_{11a} & \vec{z}_{12a} \\ \vec{z}_{21a} & \vec{z}_{22a} \end{bmatrix} \begin{bmatrix} \vec{I}_{1a} \\ \vec{I}_{2a} \end{bmatrix}$$

for 2-port N/b (b)

$$\begin{bmatrix} \vec{V}_{1b} \\ \vec{V}_{2b} \end{bmatrix} = \begin{bmatrix} \vec{z}_{11b} & \vec{z}_{12b} \\ \vec{z}_{21b} & \vec{z}_{22b} \end{bmatrix} \begin{bmatrix} \vec{I}_{1b} \\ \vec{I}_{2b} \end{bmatrix}$$


(a) & (b) are connected in series.

$$\Rightarrow \begin{cases} \vec{V}_1 = \vec{V}_{1a} + \vec{V}_{1b} \\ \vec{V}_2 = \vec{V}_{2a} + \vec{V}_{2b} \end{cases} \quad \begin{cases} \vec{I}_{1a} = \vec{I}_{1b} = \vec{I}_1 \\ \vec{I}_{2a} = \vec{I}_{2b} = \vec{I}_2 \end{cases}$$

$$\begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} \vec{z}_{11a} + \vec{z}_{11b} & \vec{z}_{12a} + \vec{z}_{12b} \\ \vec{z}_{21a} + \vec{z}_{21b} & \vec{z}_{22a} + \vec{z}_{22b} \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix}$$

Sum of imp. param matrices

## Cascade Connection of Two Port Networks

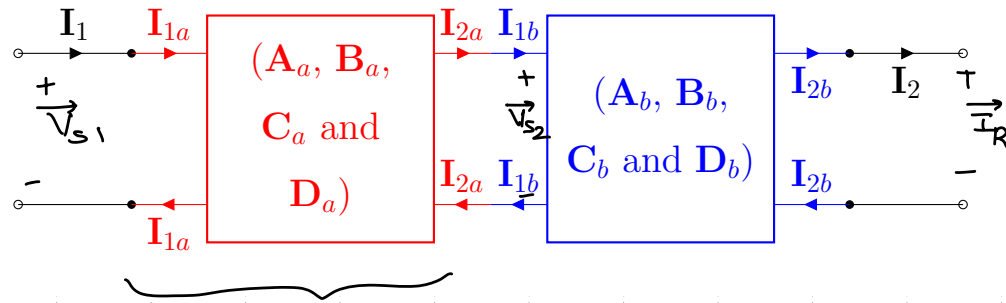

for 2-port  $N|a$  (a)

$$\begin{bmatrix} \vec{V}_{s_a} \\ \vec{I}_{s_a} \end{bmatrix} = \underbrace{\begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix}}_{T_a} \begin{bmatrix} \vec{V}_{R_a} \\ \vec{I}_{R_a} \end{bmatrix}$$

for  $N|b$  (b)

$$\begin{bmatrix} \vec{V}_{s_b} \\ \vec{I}_{s_b} \end{bmatrix} = \underbrace{\begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}}_{T_b} \begin{bmatrix} \vec{V}_{R_b} \\ \vec{I}_{R_b} \end{bmatrix}$$

$$\begin{bmatrix} \vec{V}_{R_a} \\ \vec{I}_{R_a} \end{bmatrix} = \begin{bmatrix} \vec{V}_{s_b} \\ \vec{I}_{s_b} \end{bmatrix}$$

$$\begin{bmatrix} \vec{V}_{s_a} \\ \vec{I}_{s_a} \end{bmatrix} = [T_a][T_b] \begin{bmatrix} \vec{V}_{R_b} \\ \vec{I}_{R_b} \end{bmatrix}$$