
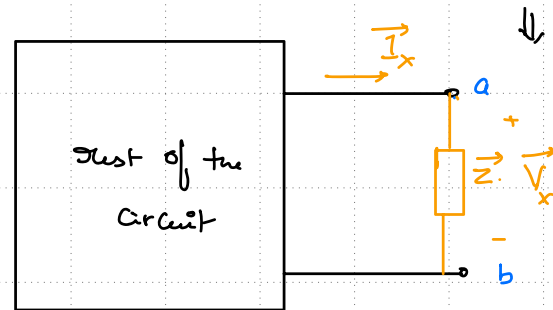


Thevenin's Theorem

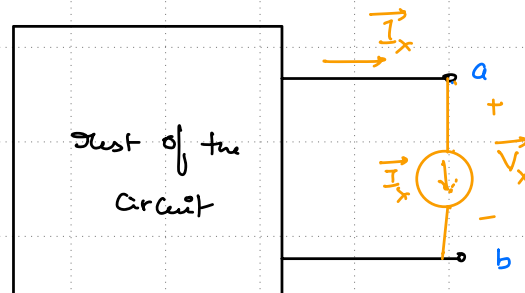given: A circuit where it's sufficient to find the response associated with a particular elem (or) pair of terminals (single or a combination of elem can be connected across it)



goal is to find response associated with a-b (V_x, I_x)



Step 1: Make use of substitution theorem


Replace Z with a Current source I_x
 I_x is unknown

If V_x can be computed, $I_x = \frac{V_x}{Z}$

Step 2: Use superposition theorem

V_x = Sum of Voltages obtained from solving 2 cts.

Thevenin's Theorem

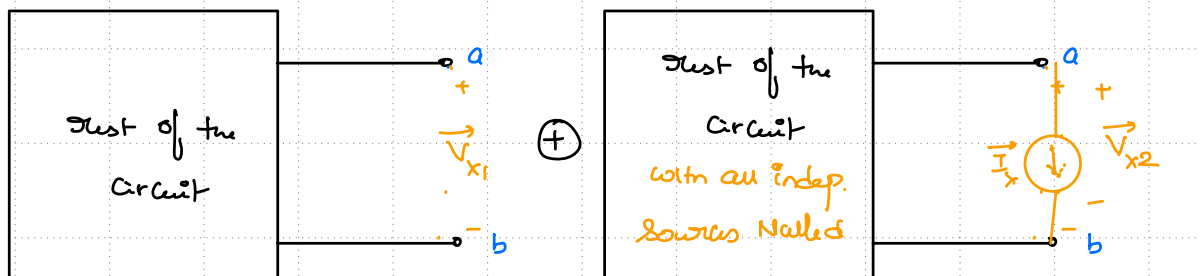

Sub Ckt ①

↓
All sources is the n/wexcept \vec{I}_x

(\vec{V}_{x1} = open ckt voltage of part a-b)

↓

\vec{V}_{Th} → Thevenin Voltage


Sub Ckt ②

$\vec{V}_{x2} = -\vec{Z}_{eq} \cdot \vec{I}_x$

↓

Equivalent imp of the part

\vec{Z}_{Th} → Thevenin impedance.

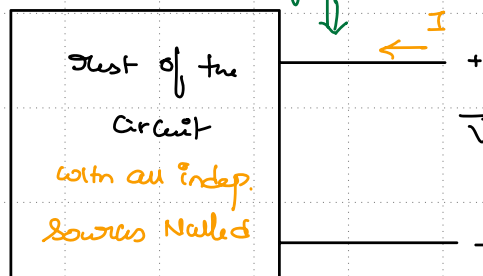Ref for Computing \vec{Z}_{Th} :-

$$\vec{Z}_{eq} = \frac{\vec{V}}{\vec{I}}$$

Step 2: Use superposition theorem

$$\vec{V}_x = \vec{V}_{x1} + \vec{V}_{x2}$$

$$\vec{V}_x = \vec{V}_{Th} - \vec{Z}_{Th} \vec{I}_x \rightarrow \textcircled{2}$$

Step 3: Simplification

$$\vec{V}_x = \vec{I}_x \vec{Z} \rightarrow \textcircled{3}$$


Sub ③ in ②

$$\vec{I}_x \vec{Z} = \vec{V}_{Th} + \vec{Z}_{Th} \vec{I}_x$$

$$\text{or } \vec{I}_x = \frac{\vec{V}_{Th}}{\vec{Z} + \vec{Z}_{Th}} \rightarrow \textcircled{1}$$


$$\text{and } \vec{V}_x = \frac{\vec{V}_{Th}}{\vec{Z} + \vec{Z}_{Th}} \times \vec{Z} \rightarrow \textcircled{II}$$

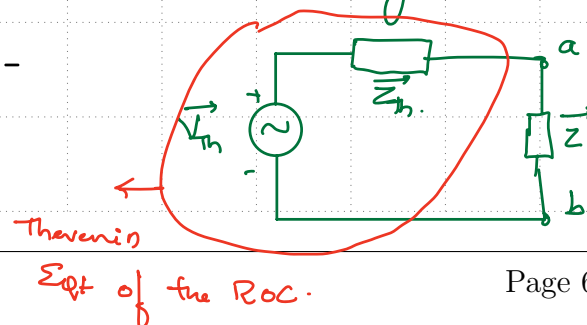Eq ① & ② can be combined into following Eq. ckt




Norton's Thevenin's Theorem

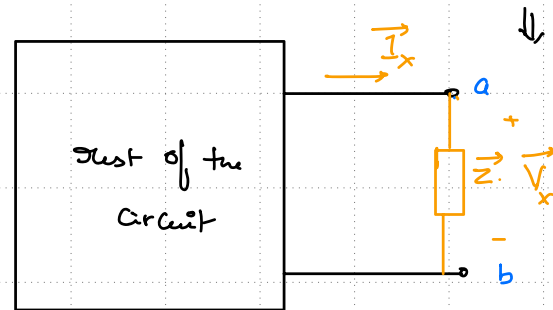given: A circuit where it's sufficient to find the response associated with a particular elem (or) pair of terminals (single or a combination of elem can be connected across it)



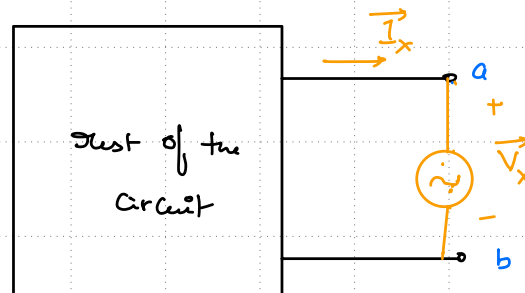goal is to find response associated with a-b (\vec{V}_x, \vec{I}_x)



Step 1: Make use of substitution theorem

Replace \vec{Z} with a voltage source \vec{V}_x
 unknown
 If \vec{I}_x can be Comp, $\vec{V}_x = \vec{Z}\vec{I}_x$

Step 2: Use superposition theorem

\vec{I}_x = Sum of currents obtained from solving 2 ccts.

Thevenin's Theorem

