

.

---

# EE1101: Circuits and Network Analysis

## Lecture 13: BJT and MOSFET Circuits

August 26, 2025


---

### Topics :

1. Bipolar Junction Transistor (BJT)
  2. Metal Oxide Semiconductor Field Effect Transistor (MOSFET)
-

## BJT from a Circuit Perspective

Circuit symbol:

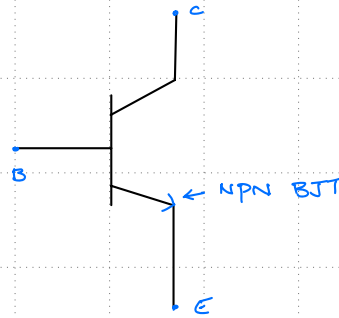

Control Part: B-E

Main CKT: C-E

OFF State:  $V_{BE} < 0.7V$  (typically) (range is 0.5-2V)

cut-off mode.

ON State:  $V_{CE} < V_{CE,sat}$  (typically 0.2V) &  $V_{BE} > 0.7V$  (typically)


(saturation mode)

Amplifier:  $V_{BE} > 0.7V$  &  $V_{CE} > V_{CE,sat} \Rightarrow$

(Active mode)

$$I_C = \beta I_B \quad \leftarrow \text{Current gain}$$


$$I_E = (1 + \beta) I_B$$

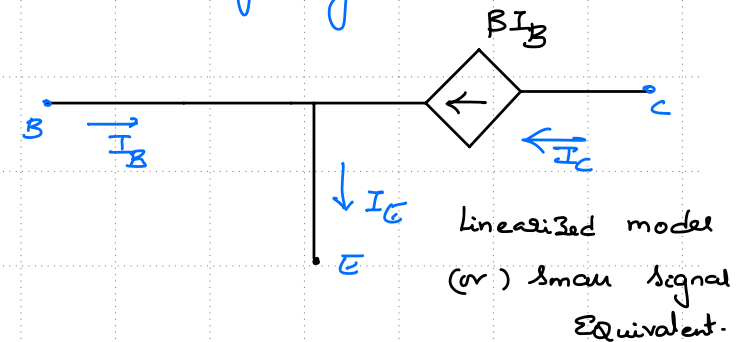

To operate as a switch: avoid Amplifier mode

- Pick  $V_{BE}$  high enough
- if max  $V_{BE}$  is fixed, adjust the CKT design.

## Example

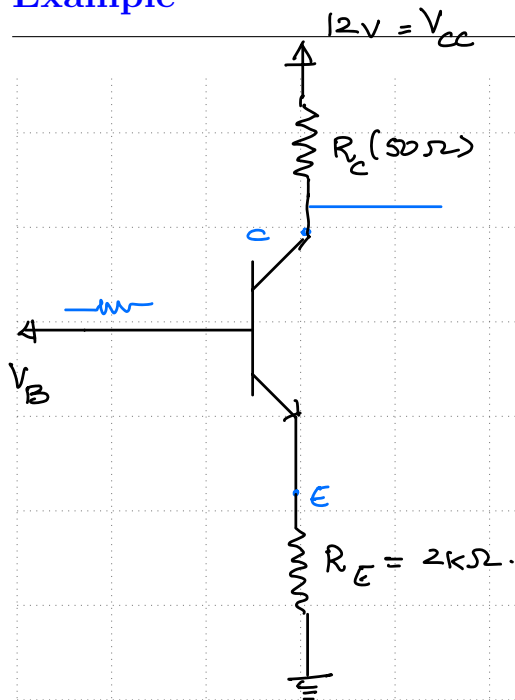

$\beta = 99$  : Compute  $V_B$  such that BJT operates in ON state

Beac the Snp is OFF — Amp — ON

↓  
use the Eq ckt & find  $V_B$  when

$$V_{CE} \approx 0.2V : V_{B,ON}$$

↓  
any  $V_B$  above  $V_{B,ON}$  will drive the ckt into ON state.

$$\textcircled{1} V_C = V_{CC} - I_C R_C$$


$$= V_{CC} - \beta I_B R_C$$

$\textcircled{2}$  How to Compute  $I_B$ ?


by KVL in loop 1:  $I_B (1 + \beta) R_E = V_B$

$$\Rightarrow I_B = \frac{V_B}{R_E (1 + \beta)}$$

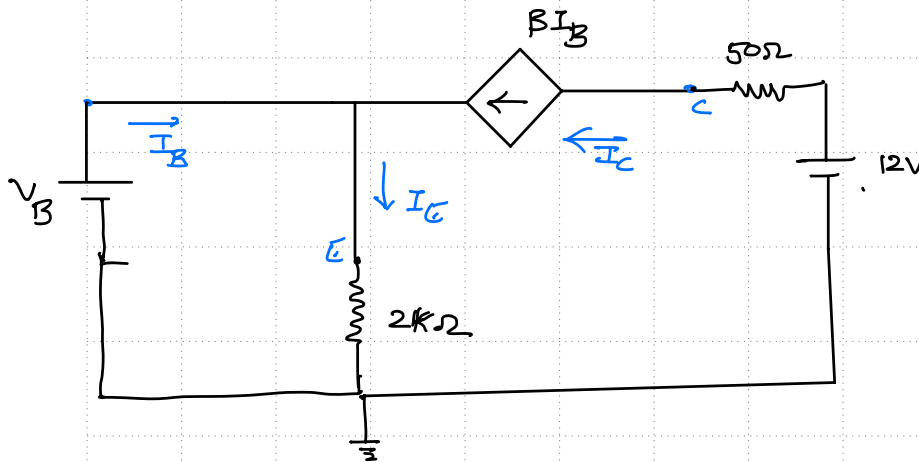for given values:  $I_B = \frac{V_B}{2} \times 10^{-5}$



## Example

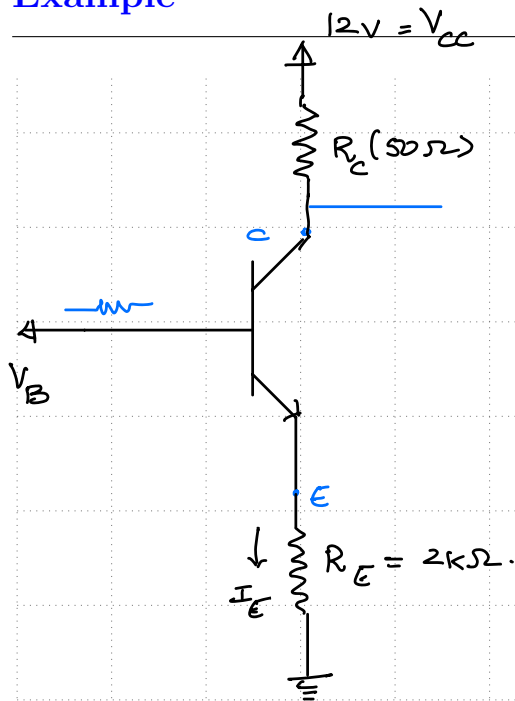

To drive the Ckt to on state:

$$V_{CE} < 0.2V$$

$$V_C - V_E < 0.2V$$

$$V_C - V_B < 0.2V$$

$$\left[ V_{CC} - \frac{\beta V_B}{(1+\beta) R_E} R_C \right] - V_B = 0.2V \rightarrow \text{Solve to get } V_B.$$

$$V_{B,ON} = V_B$$


$$V_{B,ON} \approx 11.5$$

$$V_{B,ON} > 11.5V.$$


if  $R_C$  is changed to  $2k\Omega$

$$V_{B,ON} = 5.92V.$$

$$V_B > 5.92V$$

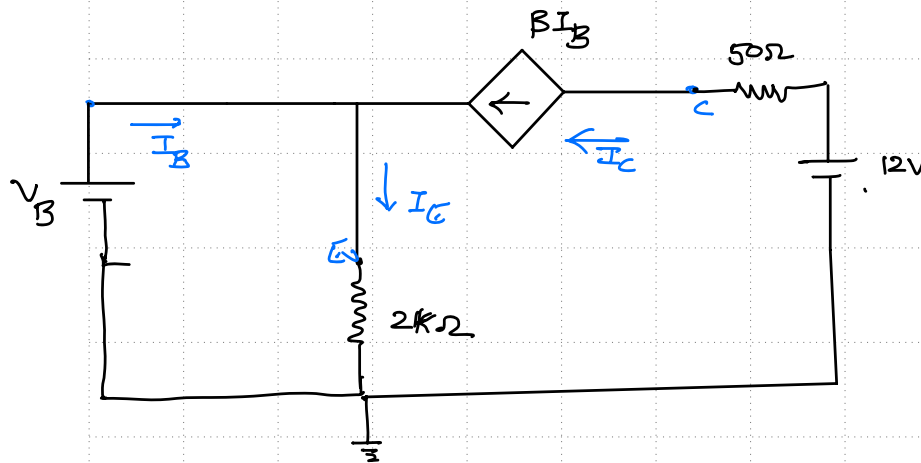

## MOSFET from a Circuit Perspective

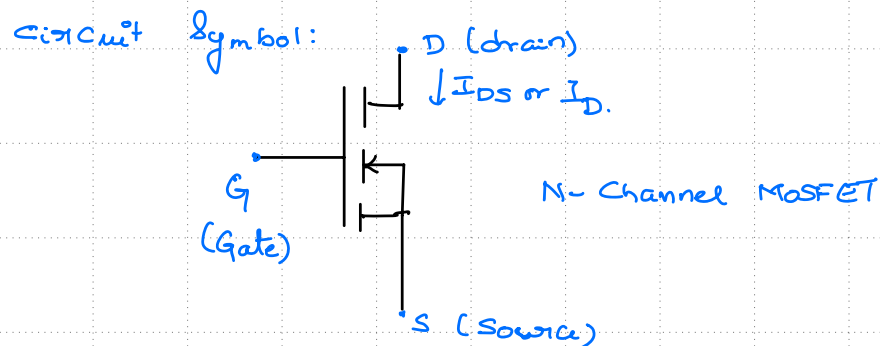

Control Part: G-S

Main CKT: D-S

OFF State:  $V_{GS} < V_t$

ON State:  $V_{GS} > V_t$  and  $V_{DS} < V_{GS} - V_t$

Amplifier:  $V_{GS} > V_t$  and  $V_{DS} > V_{GS} - V_t$

typical range of  $V_t$  is 0.6V to 2.5V.

