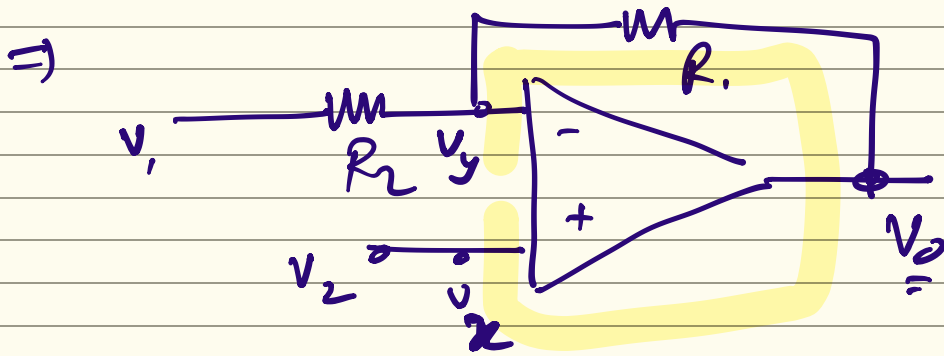



Analog Elms

FEB-03




$$V_0 = -\frac{R_1}{R_2} V_{in}$$
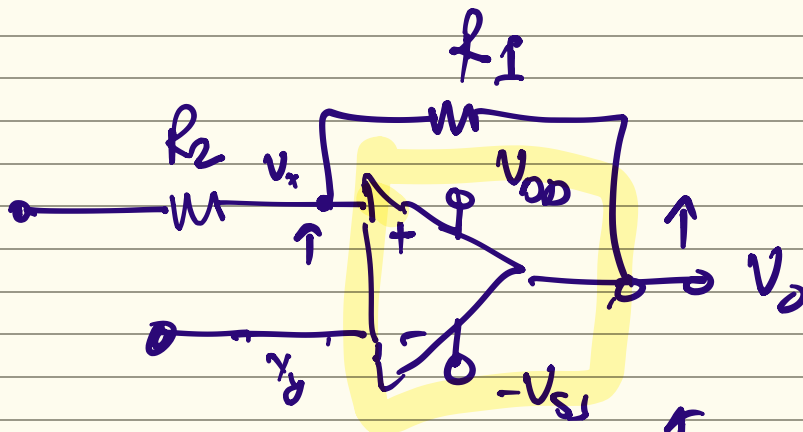
$$V_0 = \left(1 + \frac{R_1}{R_2}\right) V_{in}$$



$$A (V_x - V_y) = V_0$$

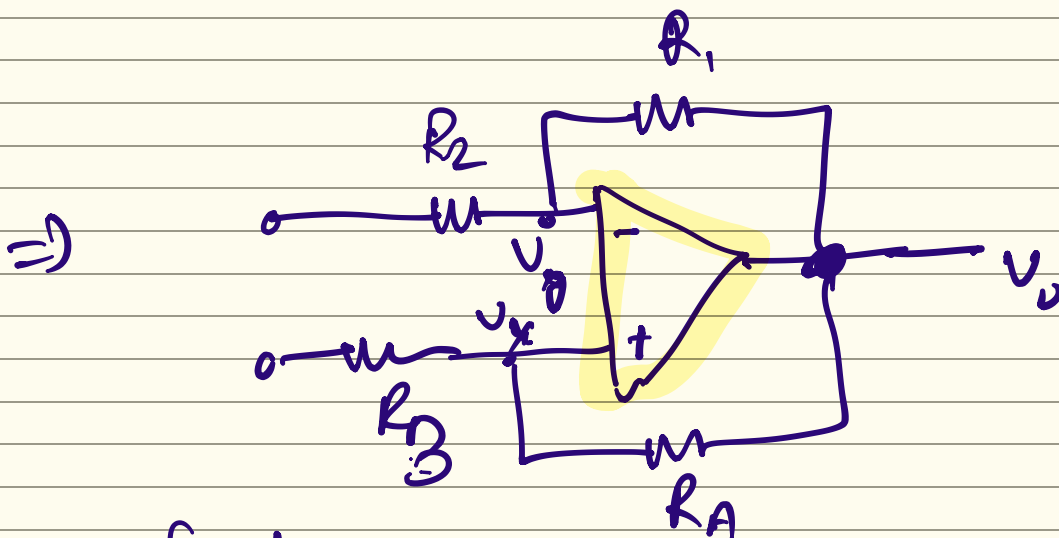

the feedback $\beta_+ =$


$$\frac{R_3}{R_3 + R_A}$$

$<$

$$\frac{R_2}{R_2 + 1}$$

For
-ve
feedback

#

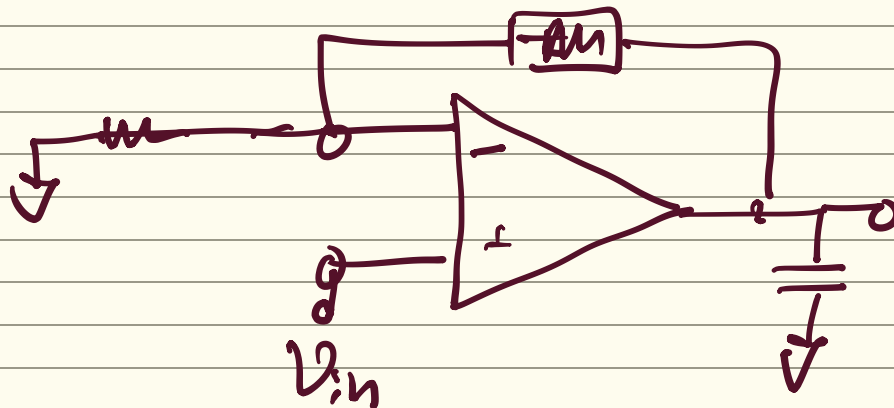


$$\frac{A}{1 + \frac{s}{a}}$$


$$a = B \cdot \omega_{op}$$

$$\frac{\frac{A}{1 + AB}}{1 + \frac{s}{a(1 + AB)}}$$

$$a(AB + 1) = BW_{CL}$$

(-ve) feed back

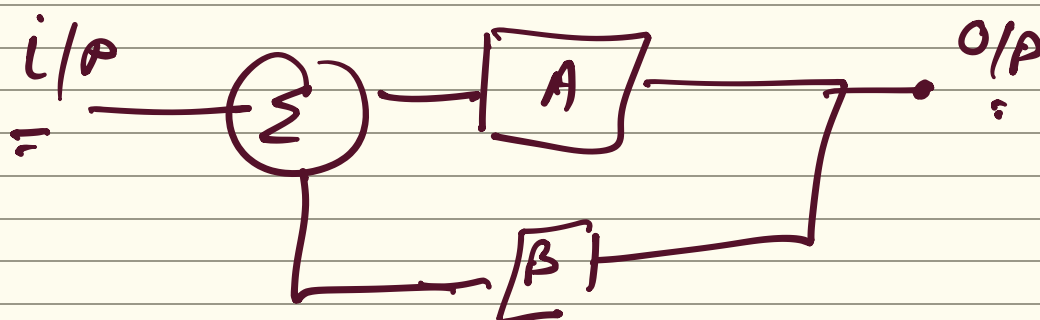

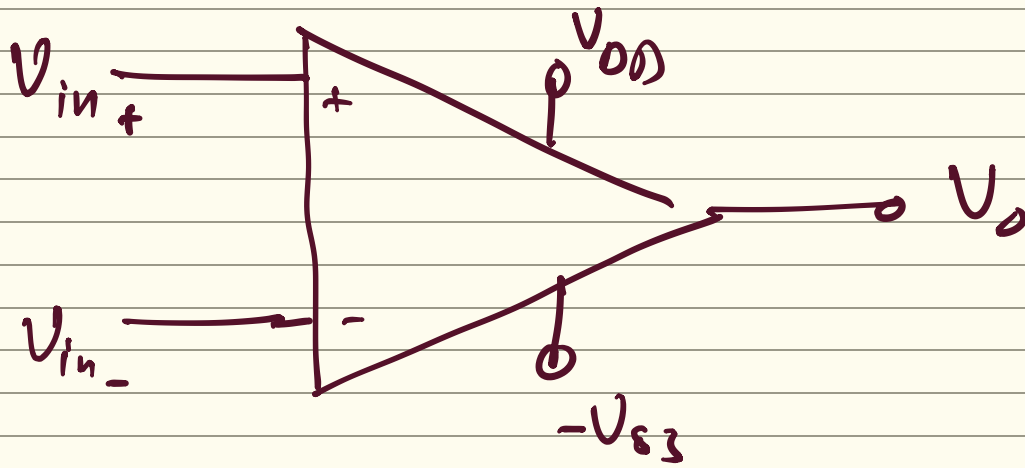




$$A (V_{in+} - V_{in-}) = V_o$$

$$\Rightarrow \text{when } V_{in+} = V_{in-}$$


then ?

$$V_o = ? = 0 \quad \neq$$

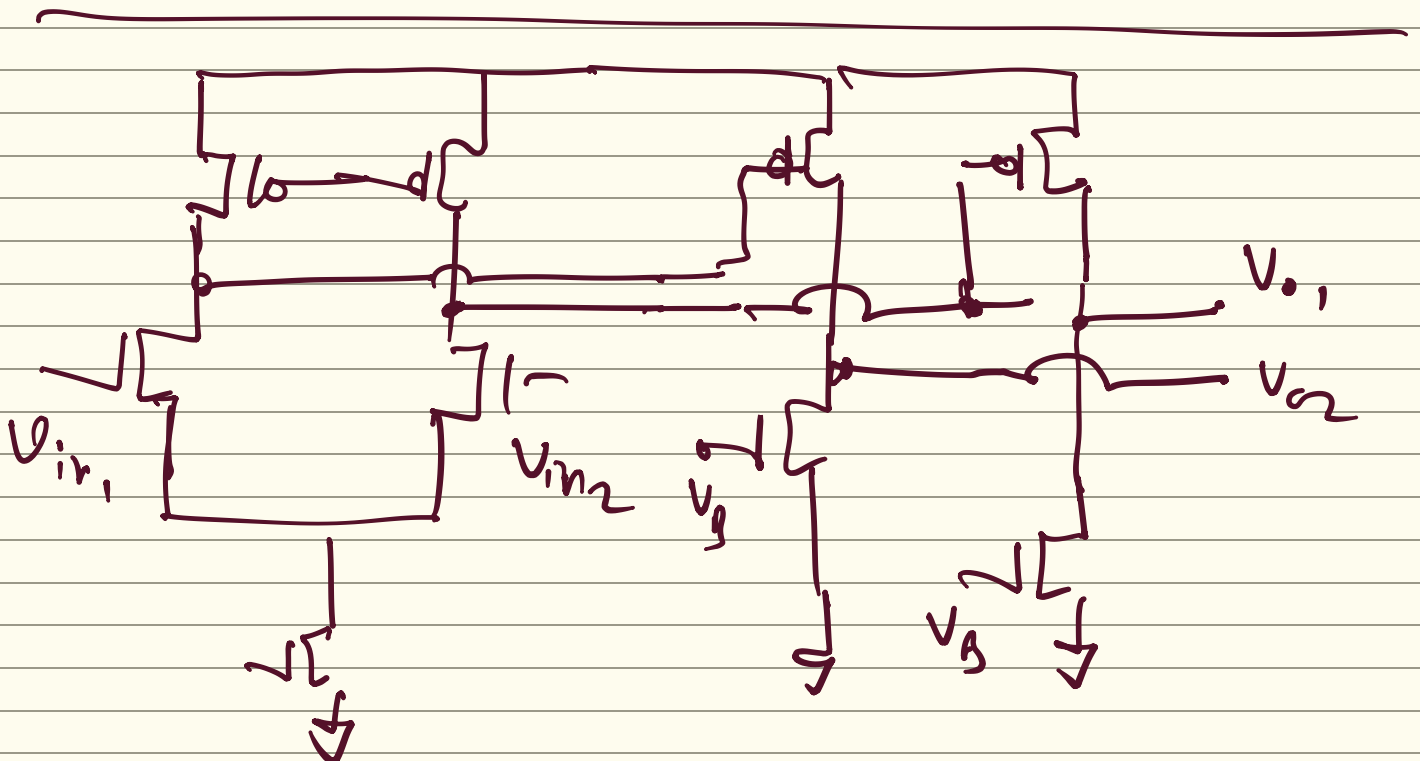

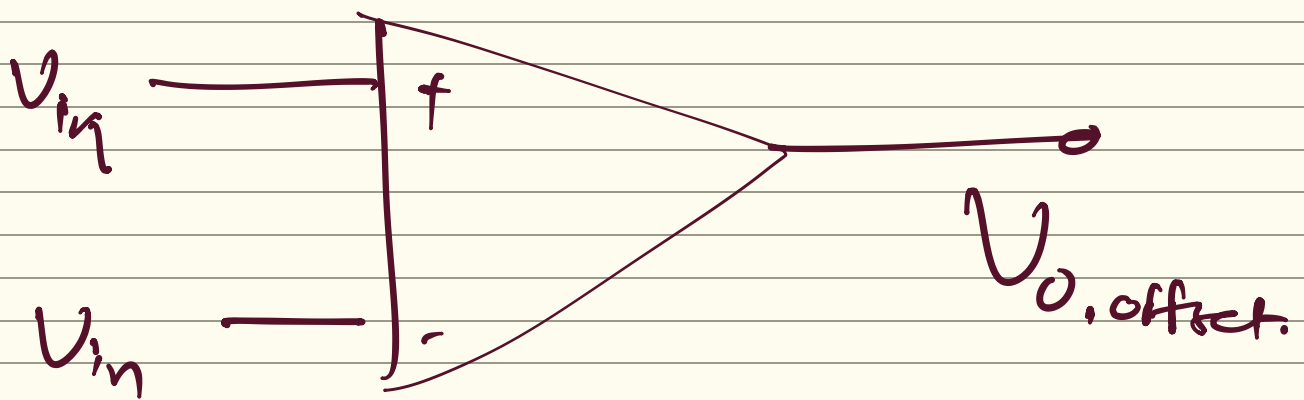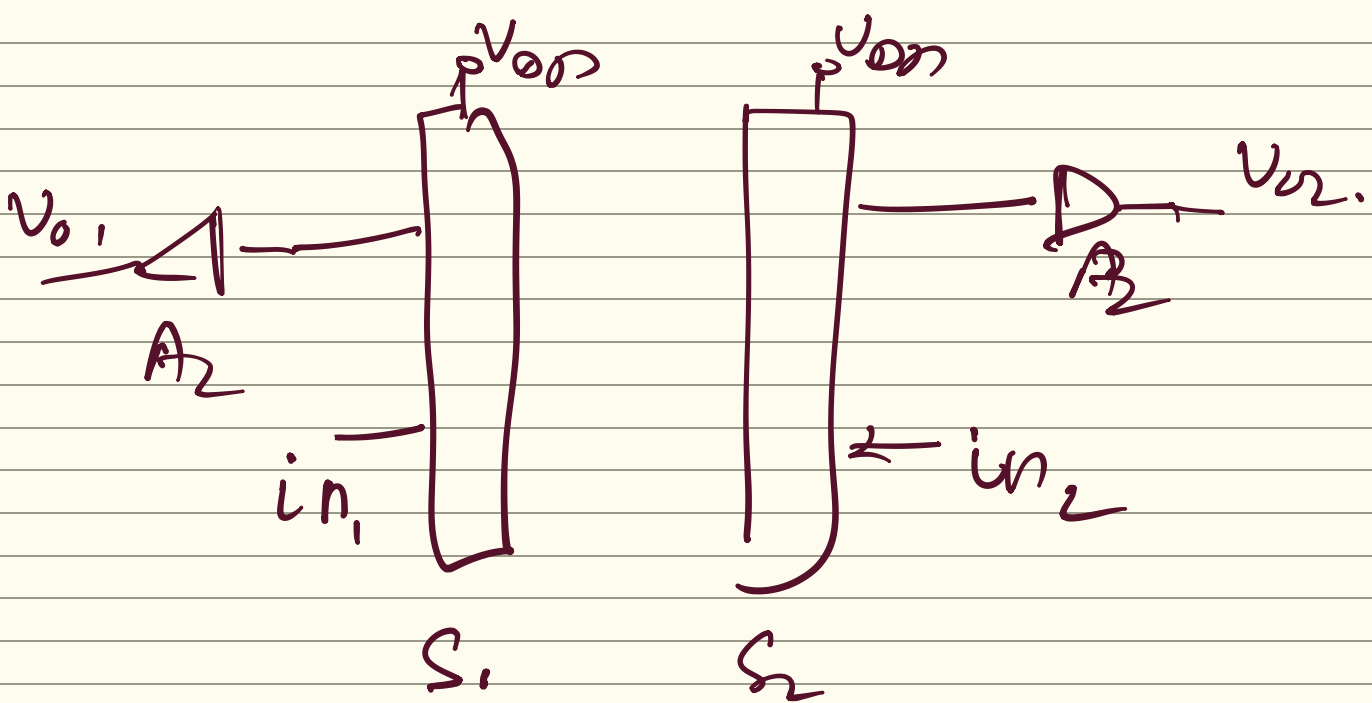


$$A(V_{in} - V_{in}) \neq 0$$

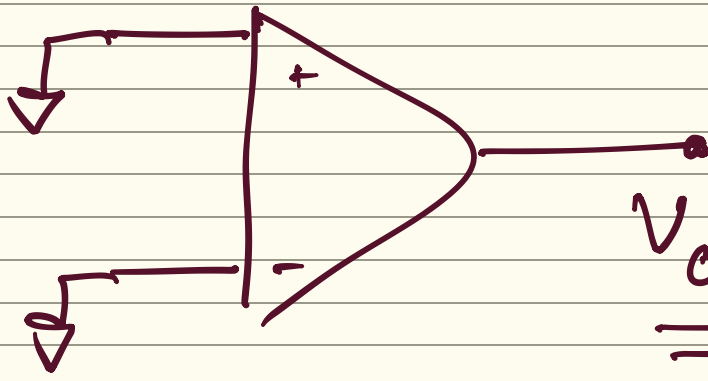


$V_{O, off}$ = Due to
Mismatch /



Other reasons

$$V_{off}/A = V_{i, off}$$

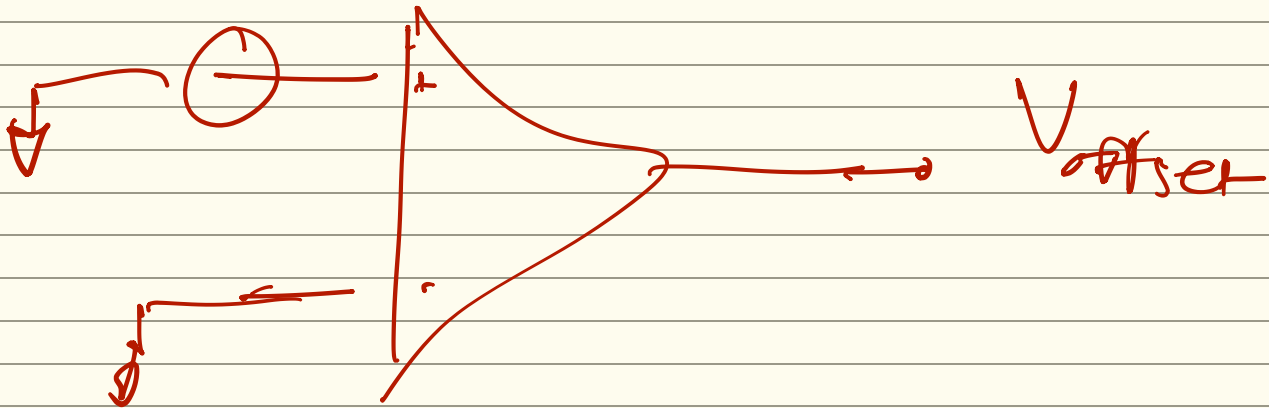


Correction:

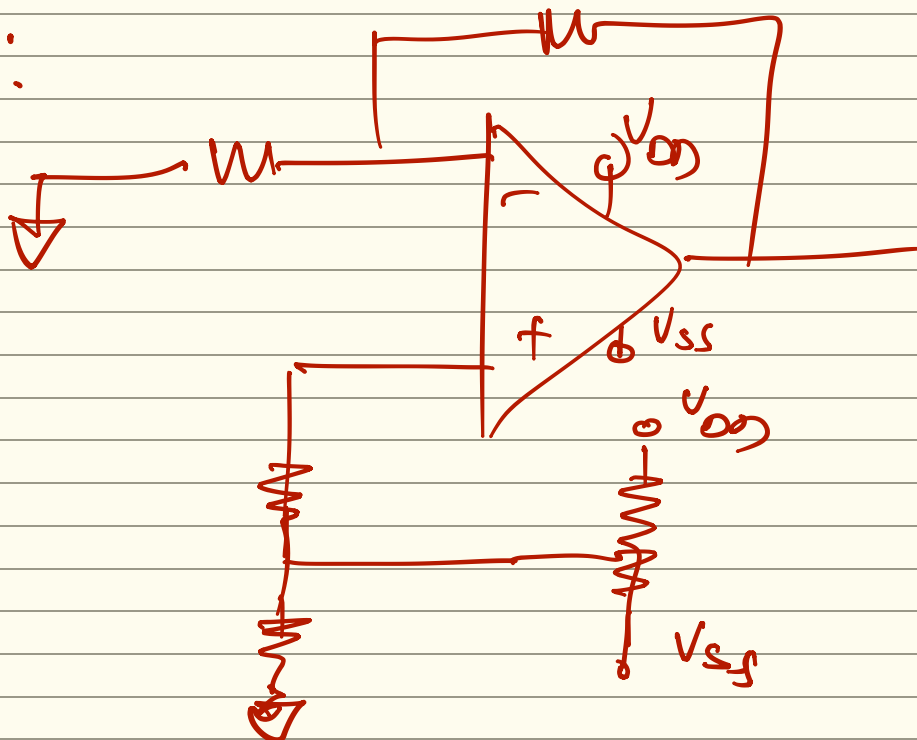

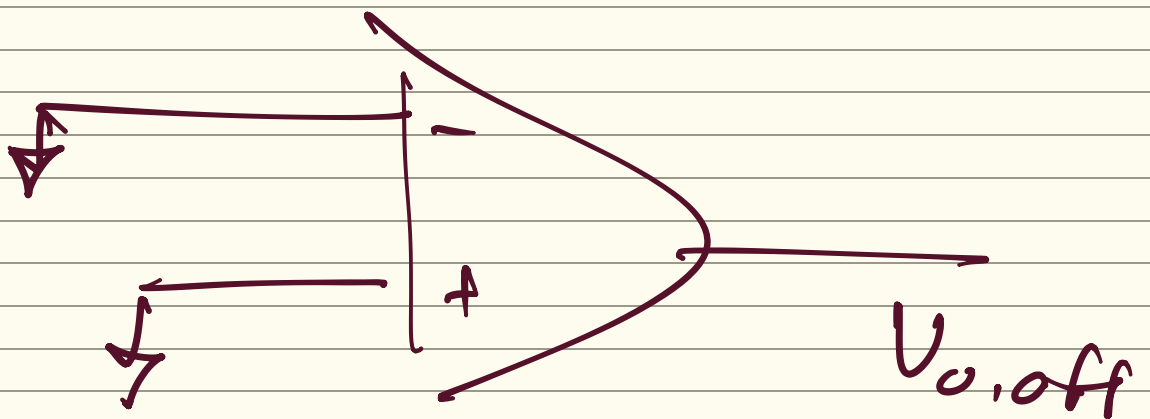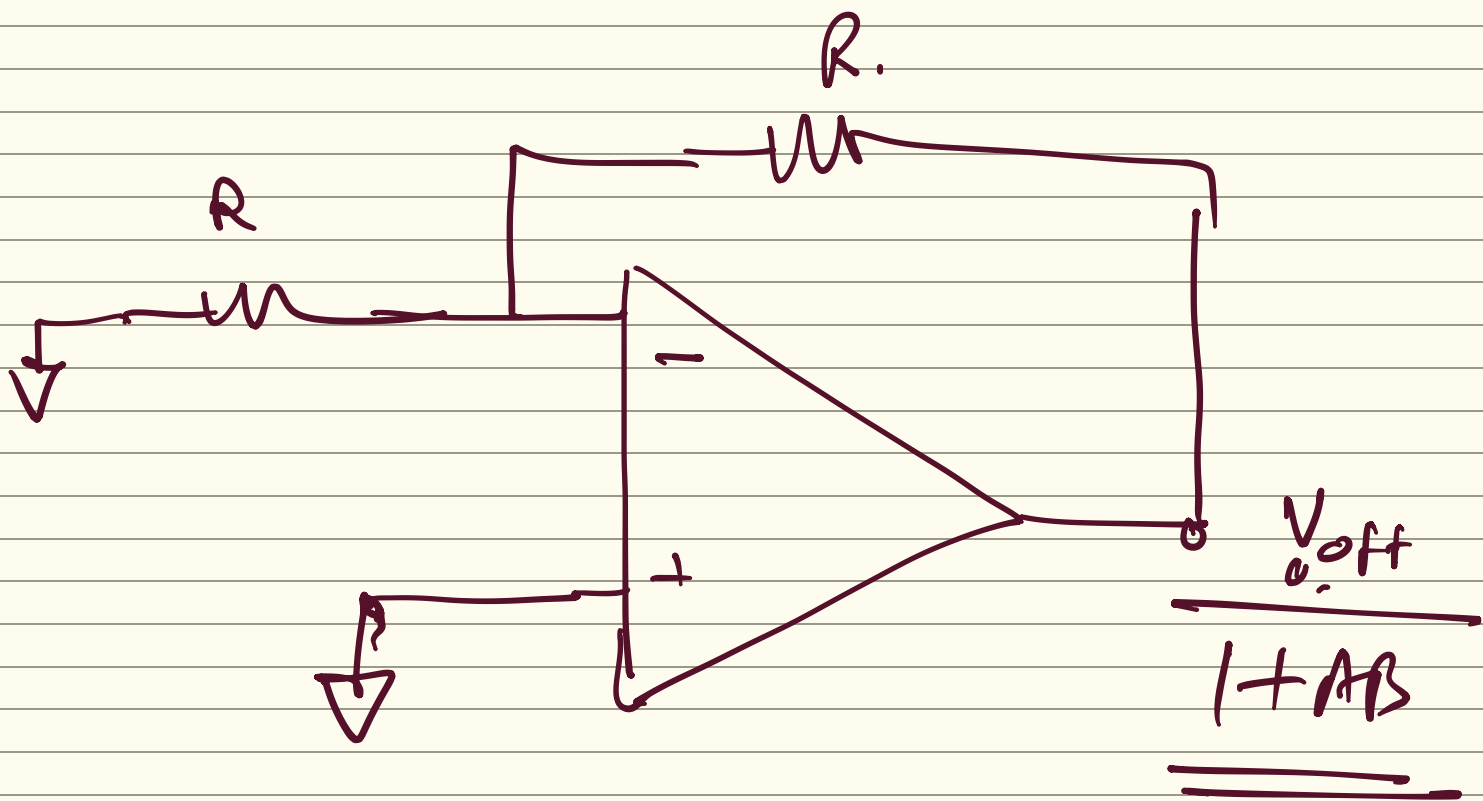

$$V_{o,off,fb} = \frac{V_{o,off,ol}}{1+AB}$$

or

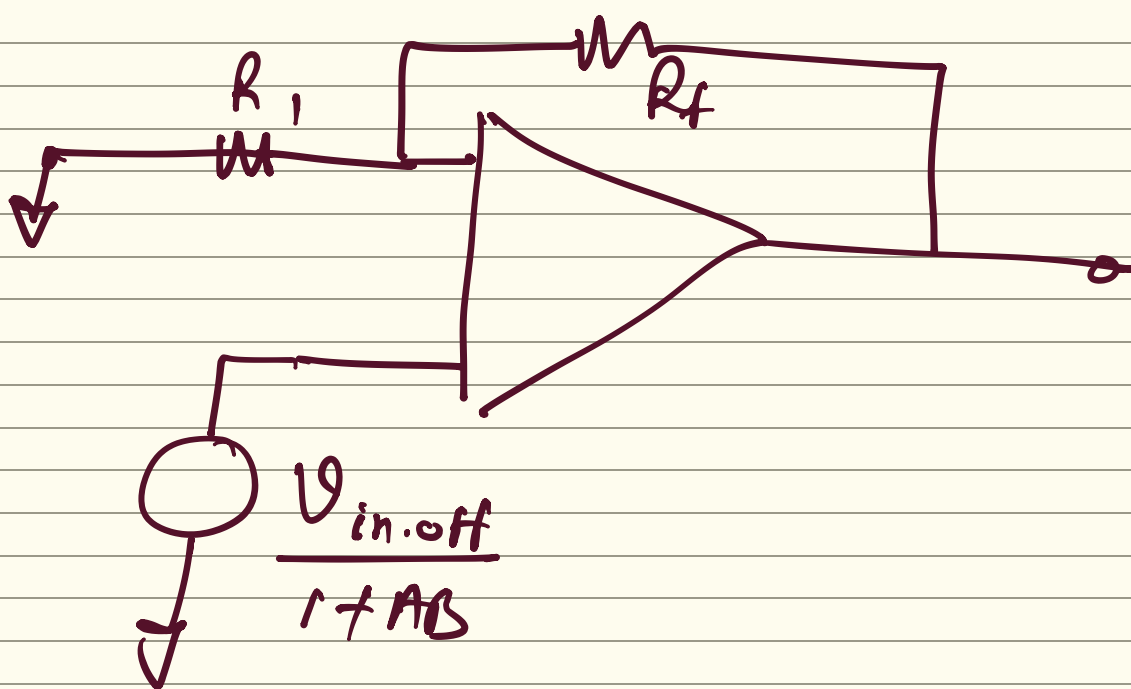

input referred noise

$$\Rightarrow \frac{O/p \text{ Noise}}{A_{OL}}$$

$$i_{IP} \gg N_{iP \text{ referred}}$$

High gain \rightarrow



Better stability
(-ve feed
back)



Linearity
-ve f/b



low i/p
referred
Noise



Better B.W
(-ve f/b)



low i/p
offset

#

Analog Exp

6 Feb

Ckts "opamp Bascel"

integrator ✓



Differentiator ✓

Precision amplifiers ✓

Wave form generators ✓


#


Integrator

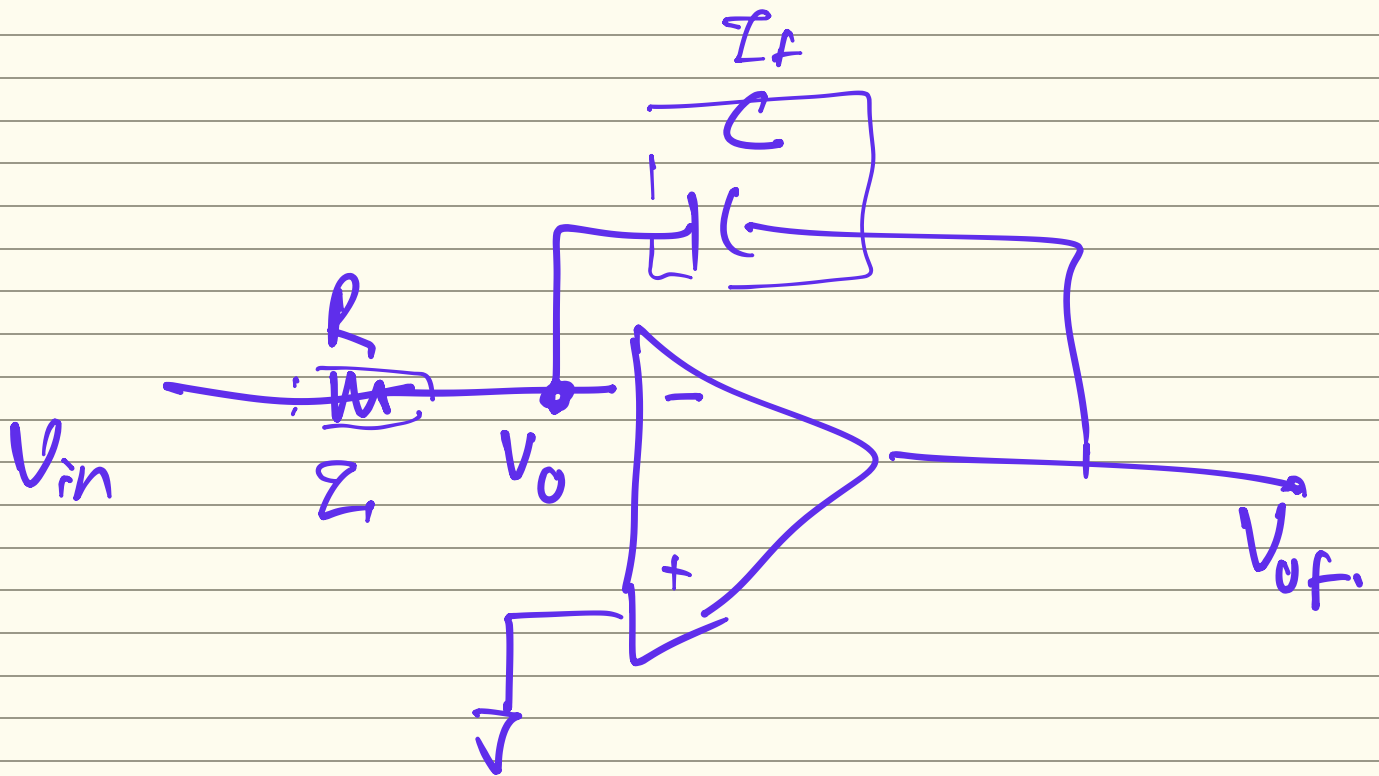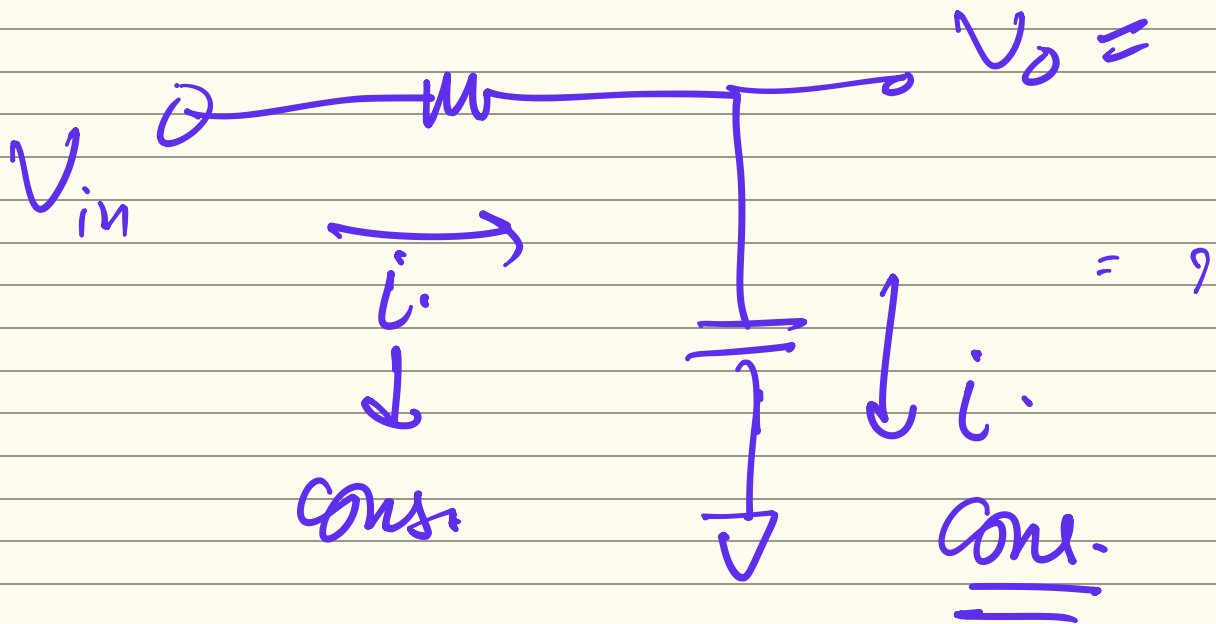


$$V_{of} = - \frac{1}{sC \cdot R} V_{in} = - \frac{R_f}{R} V_{in}(t)$$
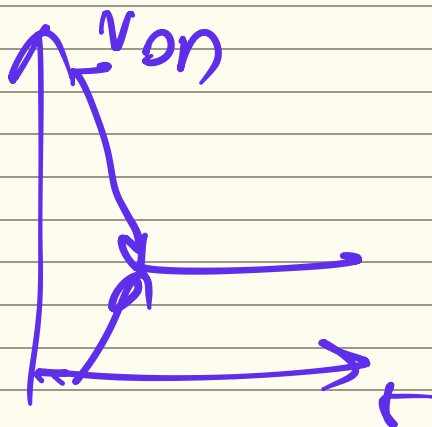
$$\frac{V_o(s)}{V_{in}(s)} = \frac{1}{sCR}$$




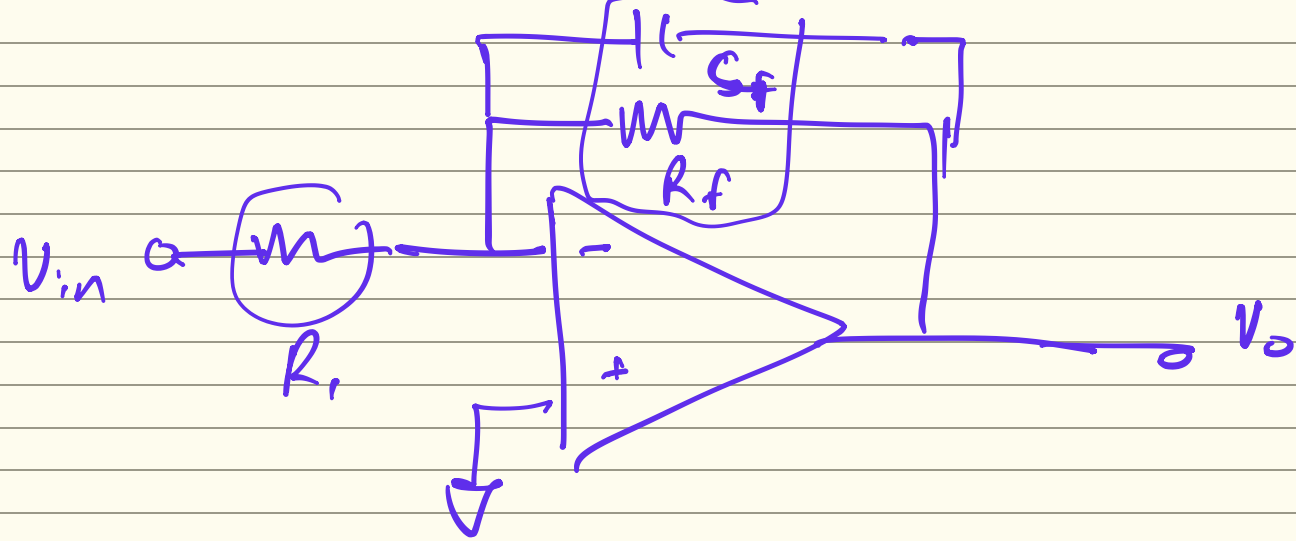

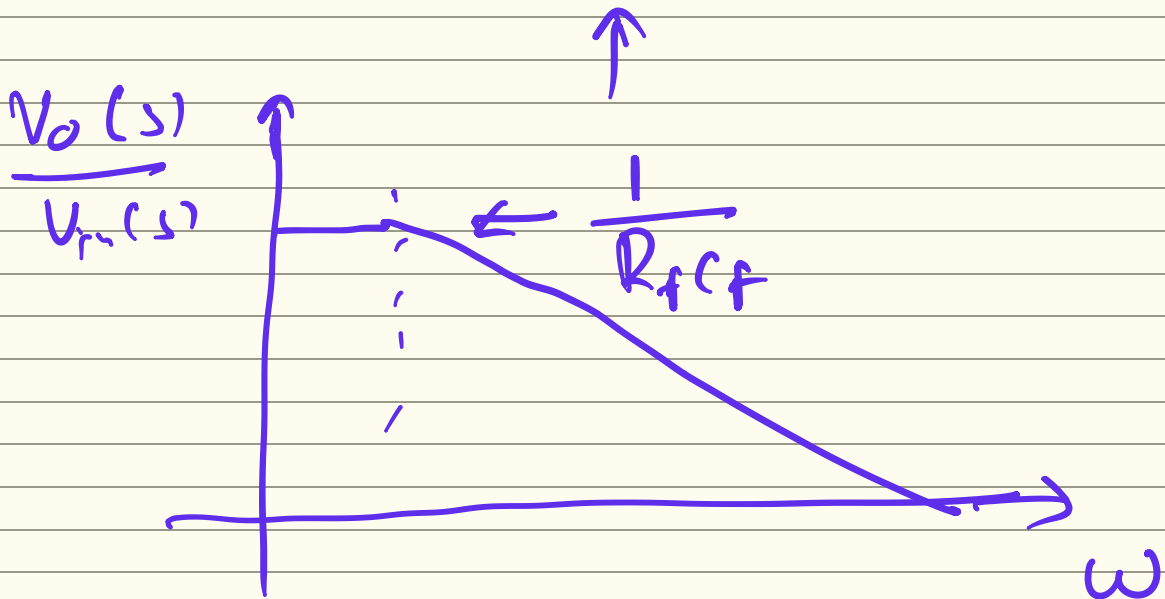
$$\frac{V_o(s)}{V_{in}(s)} = \frac{1}{(R_f C_f s + 1) \cdot R_i}$$





$$A \left(1 + \frac{s}{q} \right)$$

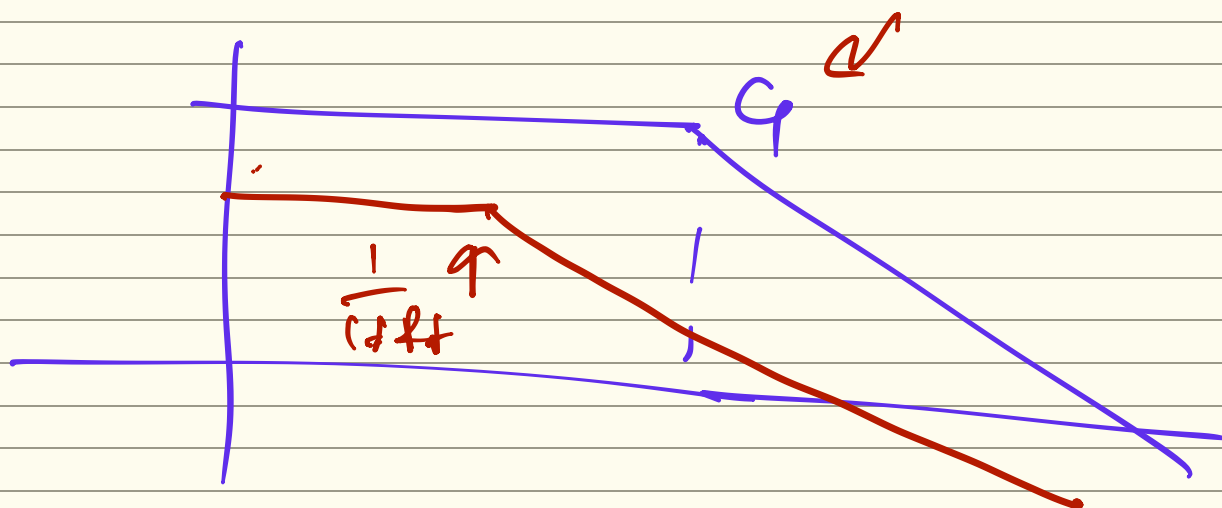

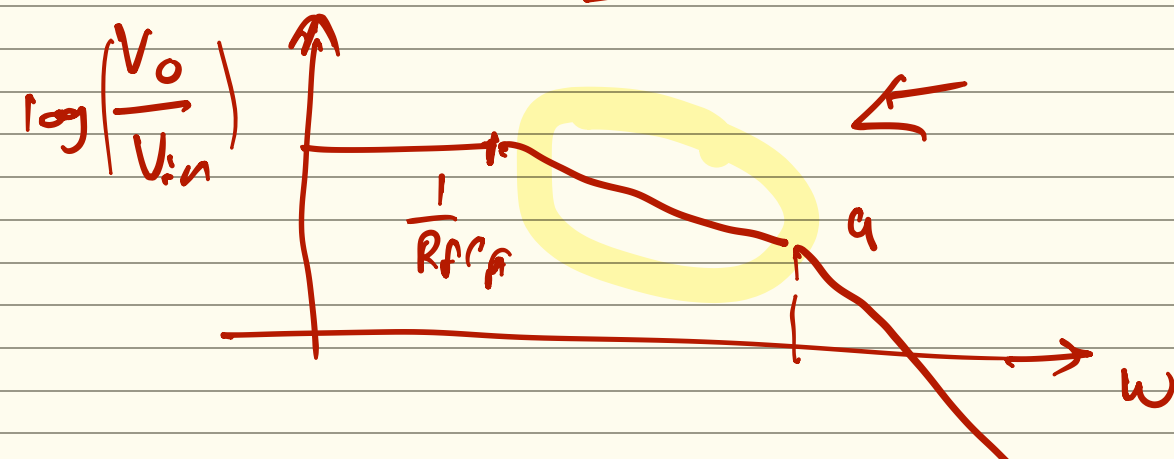
$$\frac{V_o}{V_{in}} = \frac{1}{\underbrace{(R_F C_F s + 1)}_{\text{int.}} \underbrace{R_i \left(1 + \frac{s}{q} \right)}_{\text{B.W. } \underline{\underline{v_{pump}}}}}$$




Differentiator

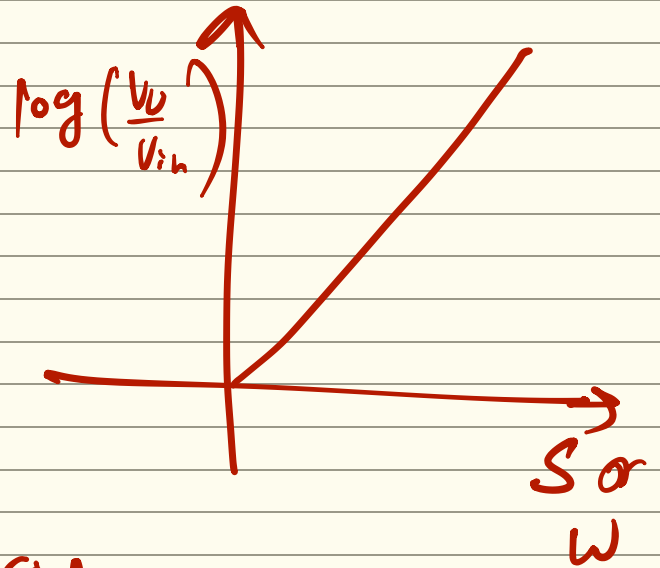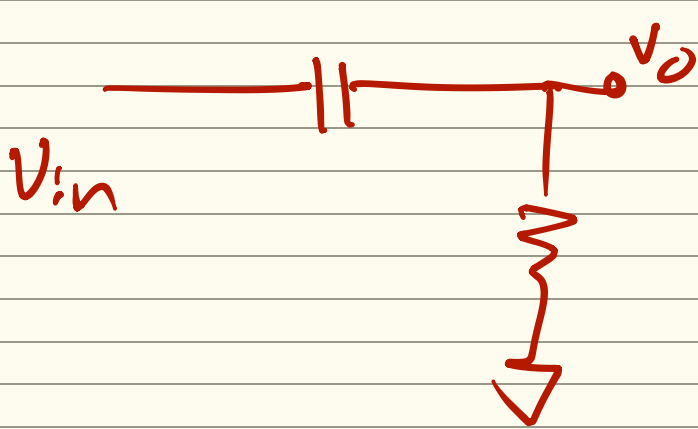




$$V_o(s) = A s \cdot V_{in}(s)$$

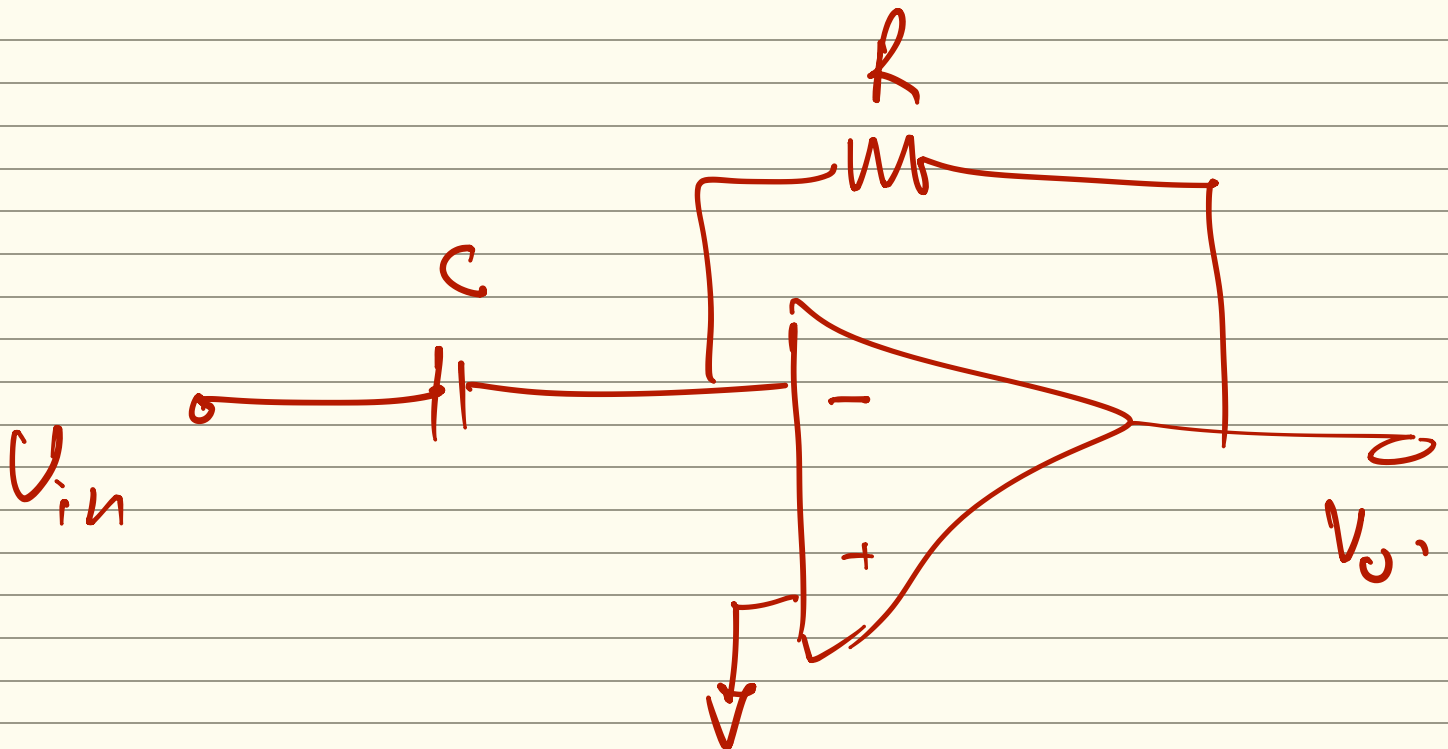


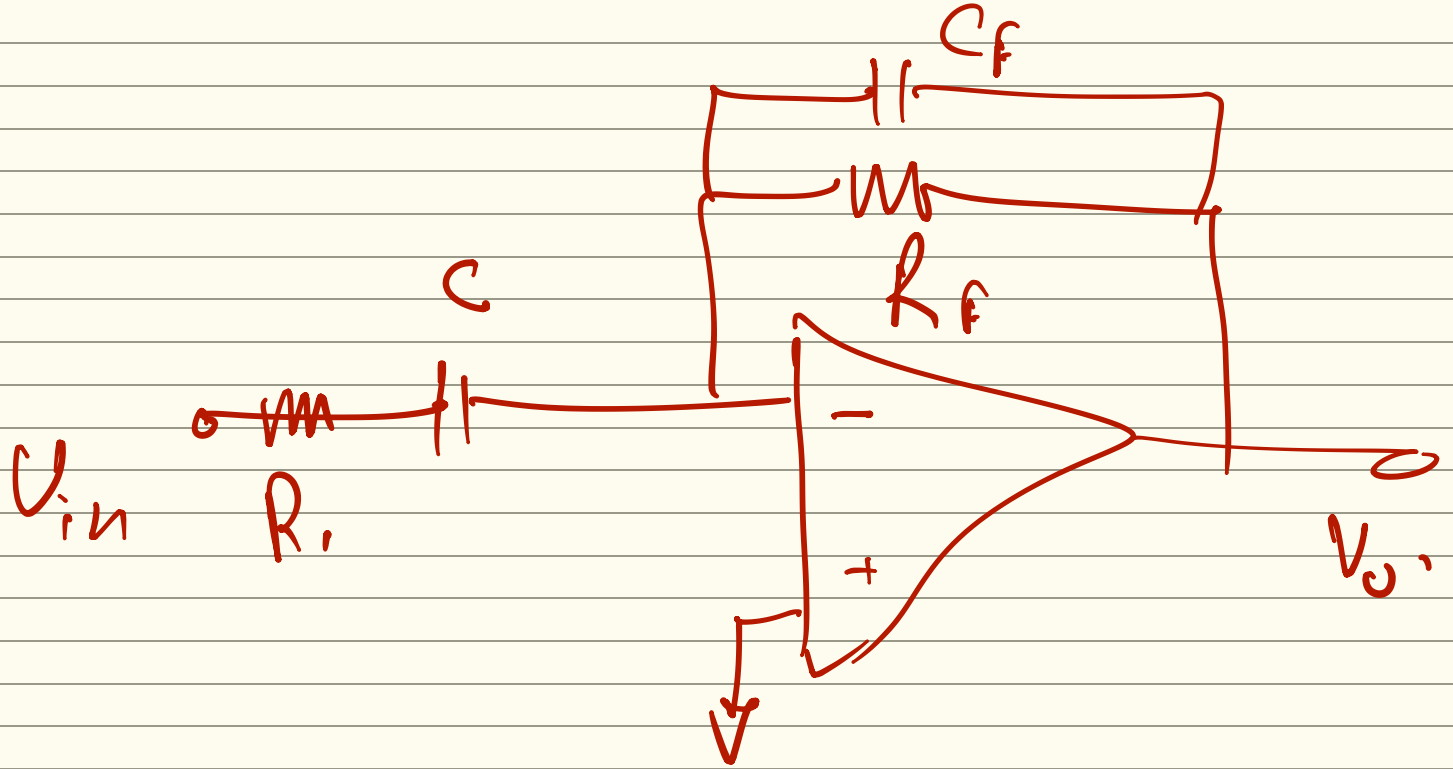
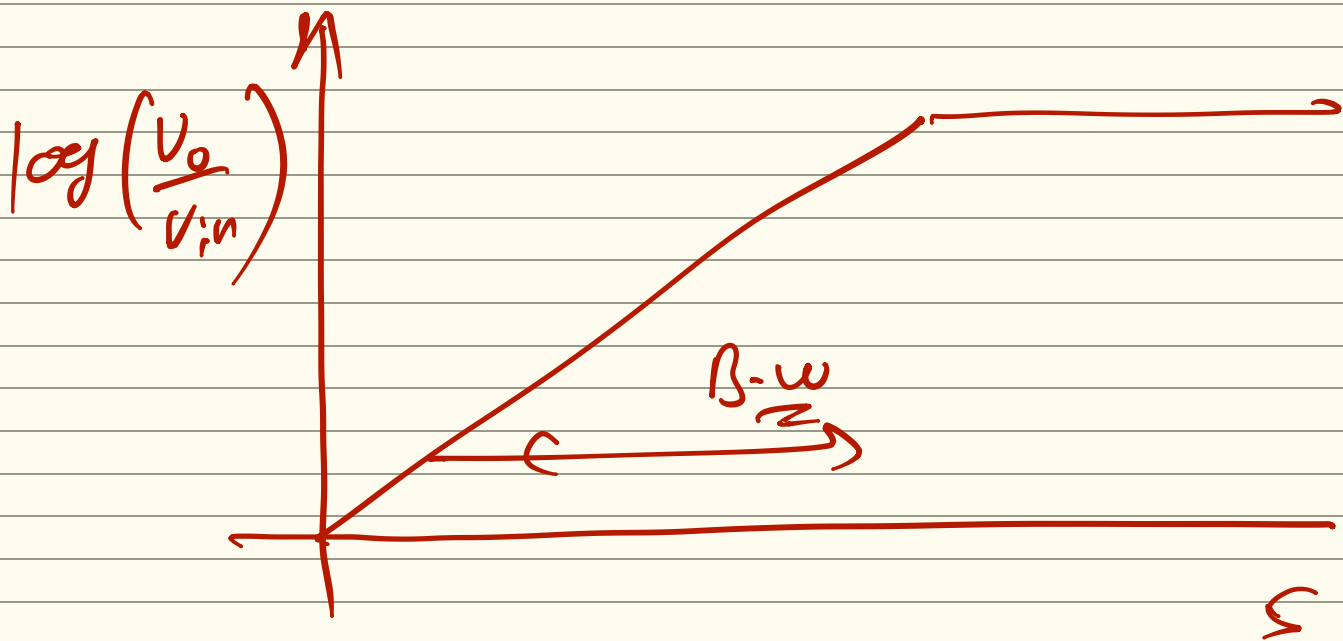
$$V_o(s) = \frac{s C_i V_{in}(s)}{1 + C_f R_f s}$$




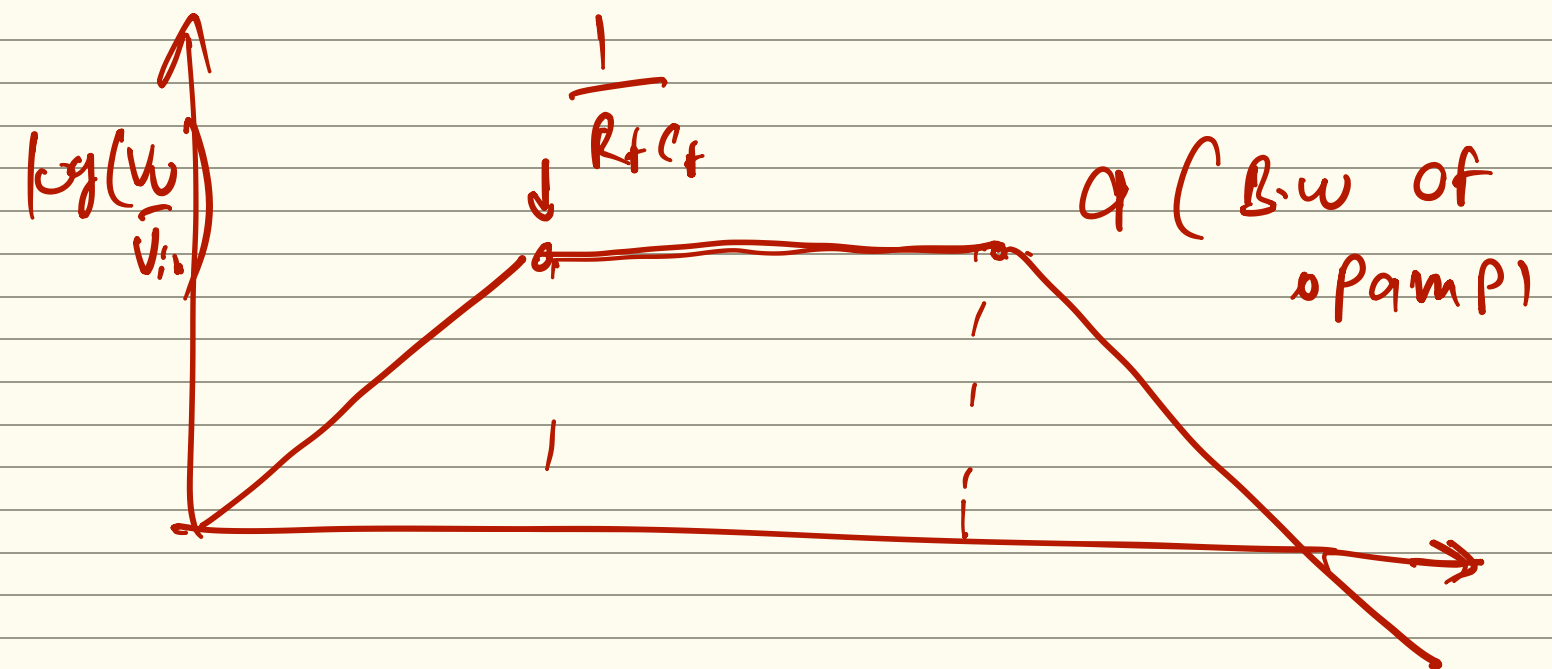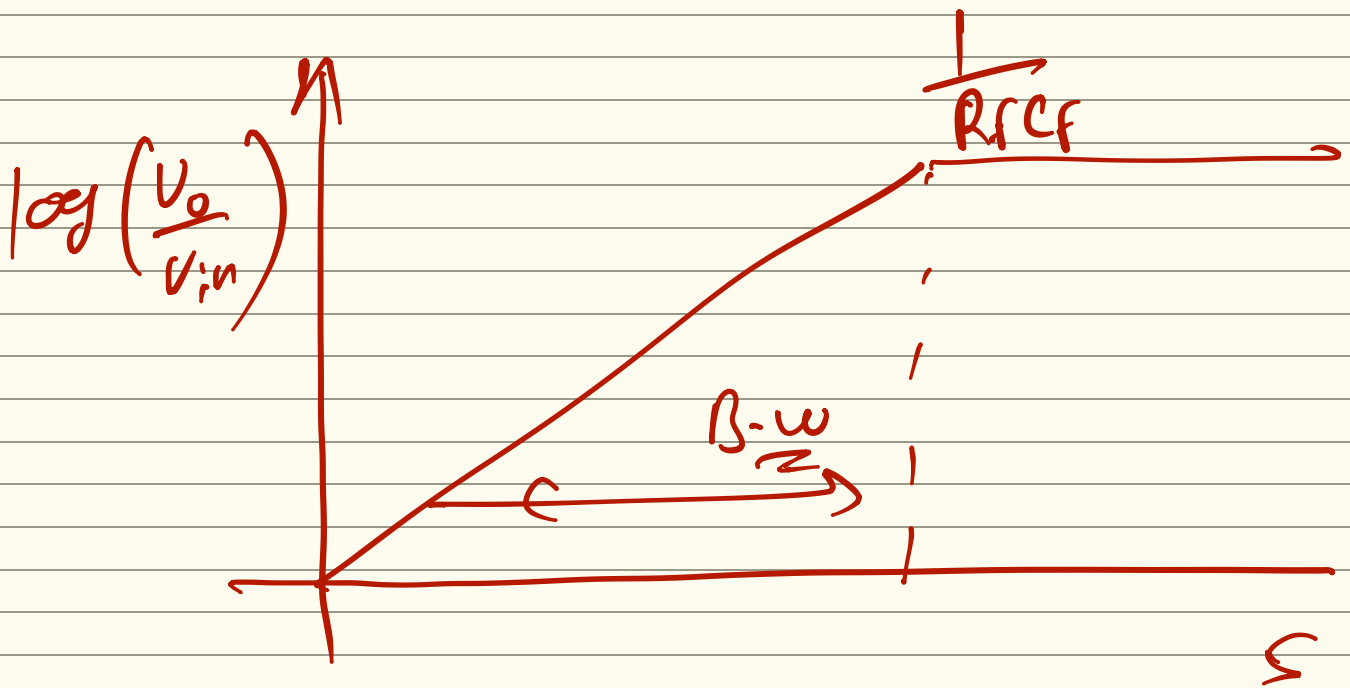

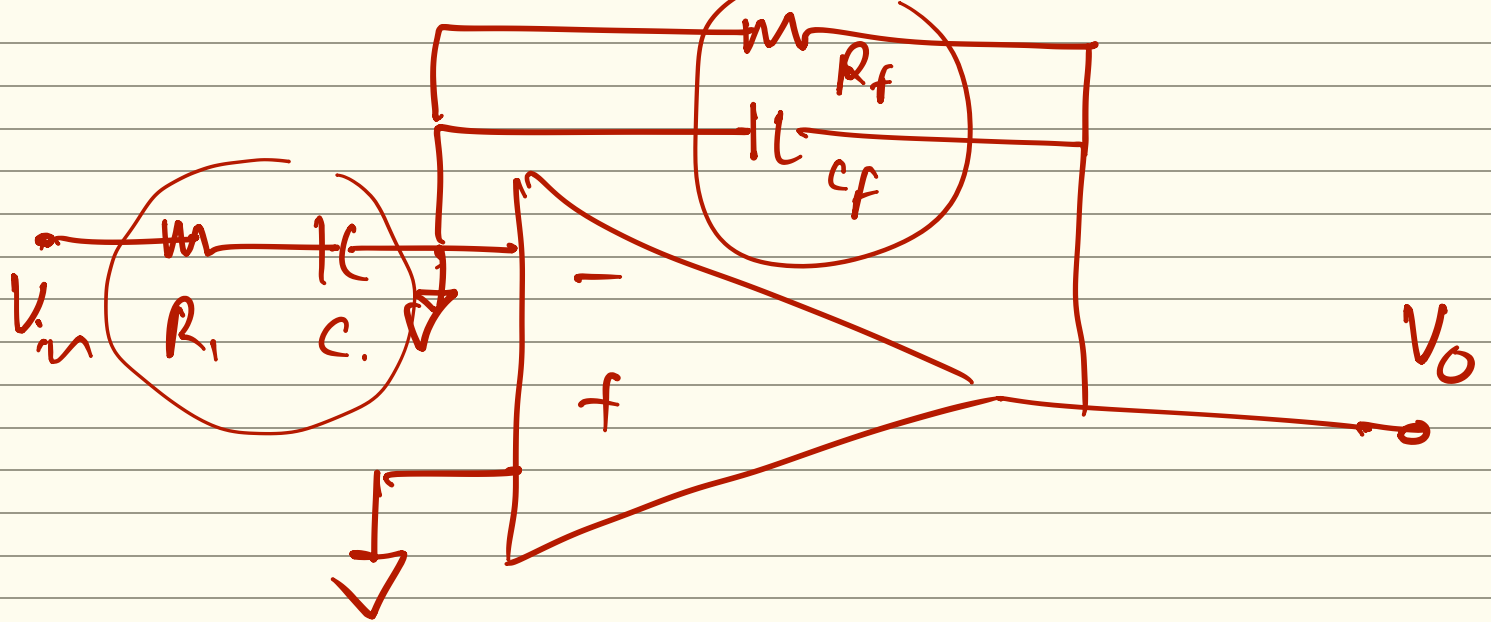


SCR.
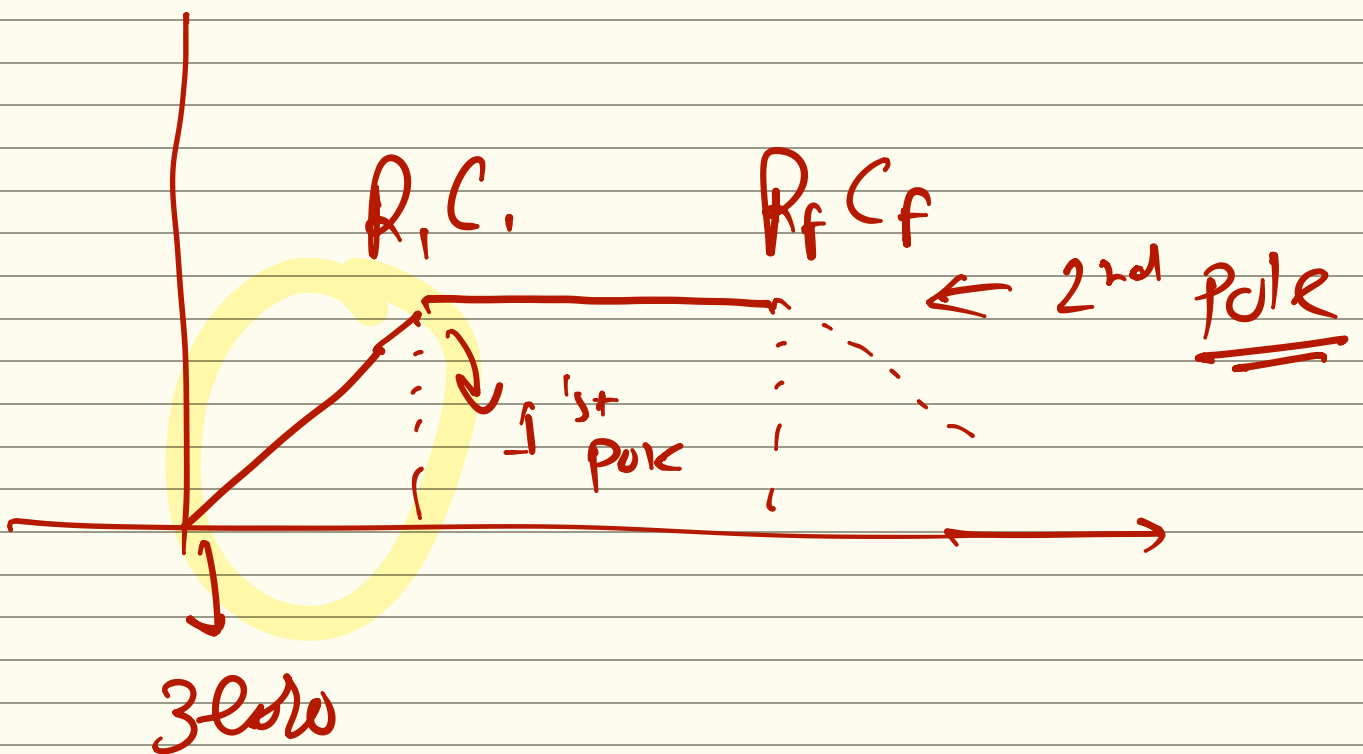
$$A(s) \Rightarrow \frac{1}{(1 + R_1 C_1 s)(1 + R_f C_f s)}$$




#

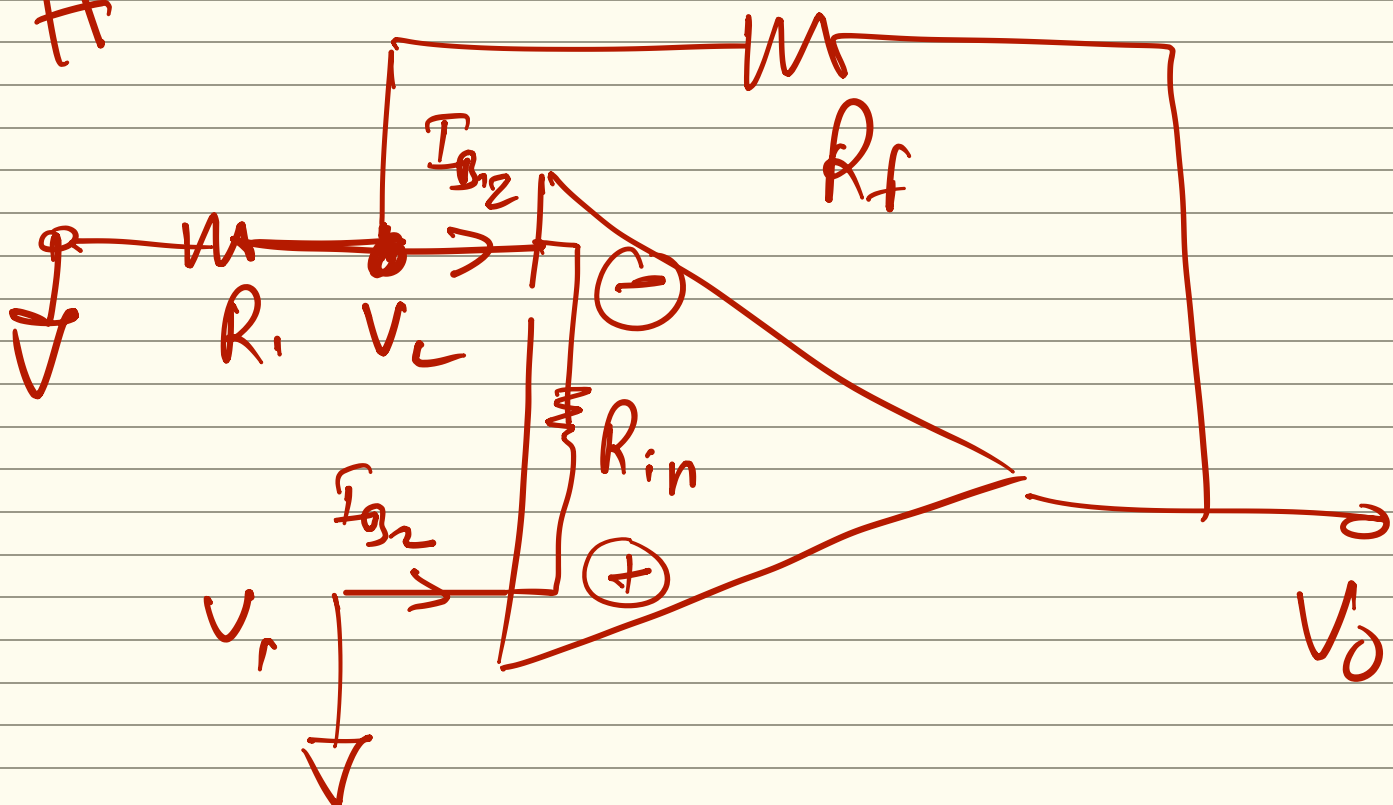

$$I_{B1} = I_{B2} = I_B$$

Bias current of op-amp

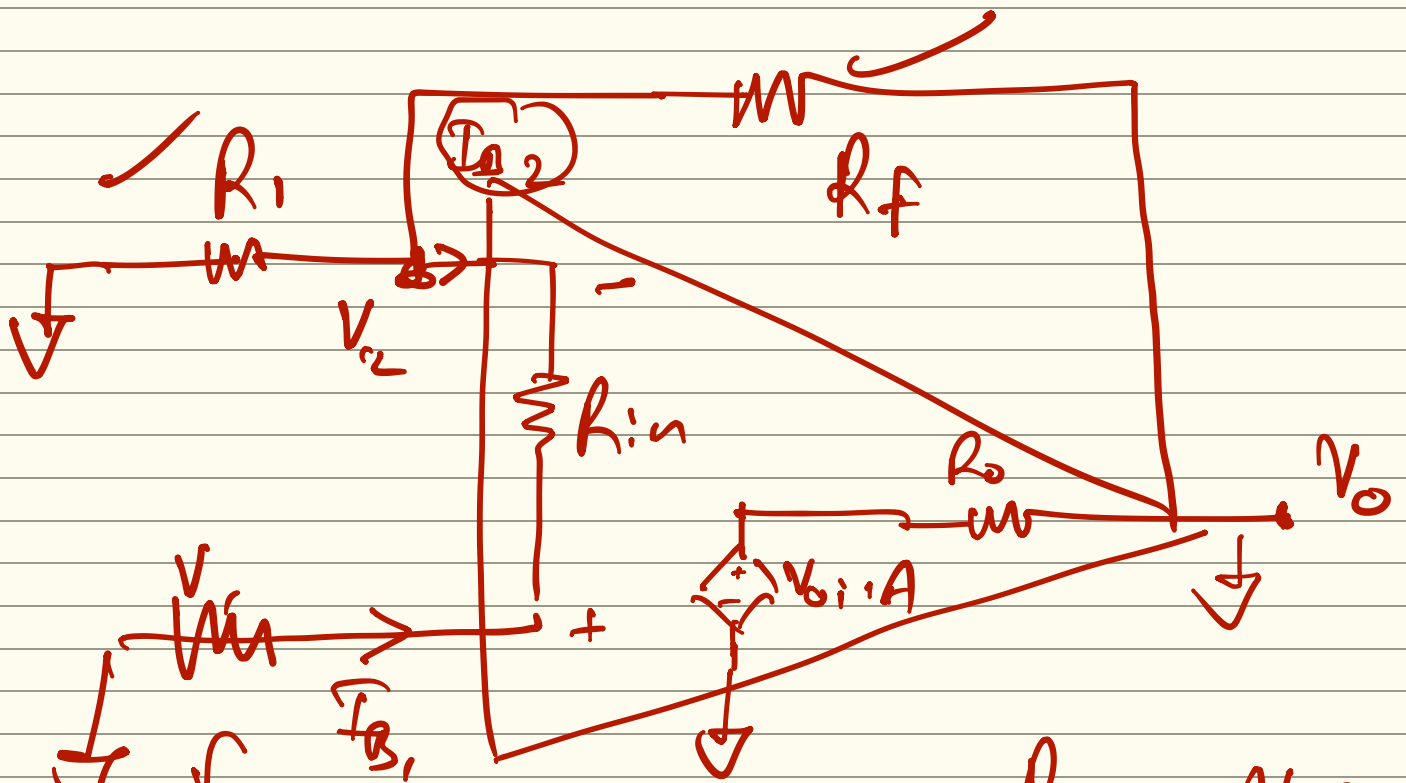

$$R_f \parallel R_i$$

$$I_{B2}$$

$$R_o = \text{very low}$$

$$V_{io} = \text{very low}$$

$$V_2 = f(I_{B2})$$

$$= (R_f \parallel R_i) \cdot I_{B1}$$