

Instructions:

1. Use LT Spice and/or MATLAB for the simulations.

1. Consider a RC circuit (R and C in series) with $RC = 10\mu s$ given with an input of square waveform with 50% duty cycle (0 to 1 Volts) with T_{ON} (time interval for level high) varies from 1ns to 1 μs . Plot the output waveform across capacitor for different T_{ON} (simulate for $T_{ON} = 1ns, 10ns, 100ns, \text{ and } 1\mu s$).
2. Consider A PMOS device (ideal) with following specifications: N_d varies from 10^{14} to 10^{20} atoms/cm³, $N_i = 10^{10}$ atom/cm³, Oxide thickness: 10nm, Temperature: 300K, $\epsilon_0 = 8.85 \times 10^{-14}$ F/cm, $\epsilon_{si} = 12\epsilon_0$, $\epsilon_{sio2} = 4\epsilon_0$, Applied voltage at Gate terminal = -2V,
 - (a). Plot graphs for voltage drop across oxide layer and semiconductor to calculate the threshold voltage.
 - (b). Draw the profile of electric field inside Si-bulk and SiO₂.
 - (c). Draw the graph between Gate voltage and drop across semiconductor. Show the shift of the curve with the variation of Gate oxide thickness from 1nm to 10 nm?
 - (d). Repeat all for NMOS device with Gate voltage = 2 volts and consider N_a instead of N_d .
3. For the Fig. 1, find the value of R_2 and C_2 to get the circuit response (output) free from delay or any transient behavior. $R_1 = 100 \text{ k}\Omega$ and $C_1 = 10\mu F$.

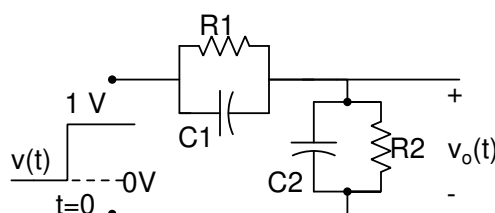


Figure 1:

4. Find out the threshold voltage for a MOS Device using following method:
 1. Keep Width/Length = 1.
 2. Body and source terminal shorted.
 3. Keep $V_{DS} = 0.1V$ fixed and vary the value of V_{GS} till I_{DS} is not reaching to 100 nA .
 4. Now keep $V_{DS} = 1V$ fixed and vary the value of V_{GS} till I_{DS} is not reaching to 100 nA
 5. The obtained value of V_{GS} can be considered as the threshold voltage of the device in each case of V_{DS} .
5.
 - i Generate a square waveform (approximate) using sinusoidal waveforms with different frequencies. (start from 5 kHz)
 - ii Pass this square waveform with an amplifier with a gain $A(\omega)$ and the following frequency response
 - (upto 10 kHz $A(\omega) = 5$)
 - (From 10 kHz to 50 kHz $A(\omega) = 3$)
 - (Above 50 kHz to 200 kHz $A(\omega) = 2$)
 - (Above 200 kHz to 1 MHz $A(\omega) = 1$)
 - (Above 1 MHz to 1.1 MHz $A(\omega) = 20$)
 - (Above 1.1 MHz to 2 MHz $A(\omega) = 2$)
 - (Above 2 MHz $A(\omega) = 0$)
 - iii Pass the square waveform generated in (1) with an ideal low-pass filter with cut-off frequency = 9 kHz. Get the output waveform.