

.

---

# EE1101: Circuits and Network Analysis

## Lecture 33: Network Theorems

October 24, 2025


---

### Topics :

1. Maximum Power Transfer Theorem
  2. Examples
-

## Maximum Power Transfer Theorem - Scenario 1

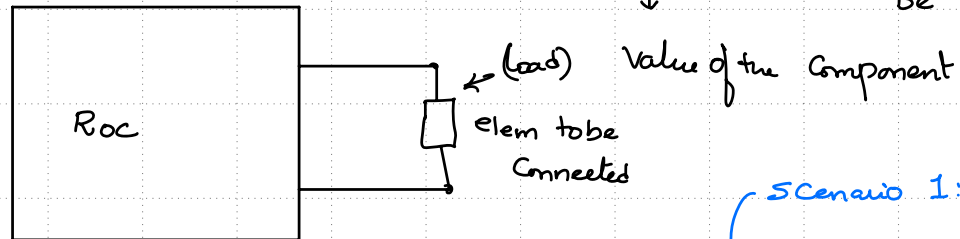**Problem Statement :** to connect a network element such that maximum active power can be extracted from the network



Set up an optimization Problem

Scenarios 1 & 2:  $\max_{R_L} P_L$

Scenario 3:  $\max_{R_L, X_L} P_L$

**Scenario 1:**  $Roc \rightarrow$  dependent + Independent sources + Resistive elements

elem to connect  $\} \rightarrow R =$  (for what value of  $R$ , max. power is extracted from the  $Roc$ )


**Scenario 2:**  $Roc \rightarrow$  dependent + Independent sources +  $(R, L, C)$

**Scenario 3:**  $Roc \rightarrow$  dependent + Independent sources +  $(R, L, C)$

elem to connect  $\} \rightarrow R + jX$  (for what value of  $R$  and  $X$ , max. power is extracted from the  $Roc$ )

elem to connect  $\} \rightarrow R =$  (for what value of  $R$ , max. power is extracted from the  $Roc$ )
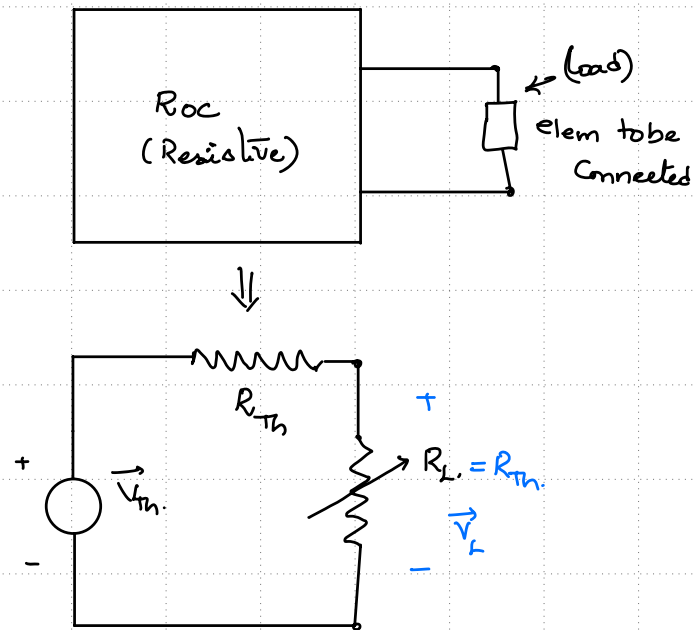
## Maximum Power Transfer Theorem - Scenario 1



$$\max_{R_L} P_L$$

$$P_L \text{ (for a time varying source): } \vec{S}_{\text{load}} = \vec{V}_L \vec{I}_L^*$$

↓  
Sinusoidal signal

$$\text{for a resistor: } \vec{I}_L = \frac{\vec{V}_L}{R} \text{ (or) } \vec{V}_L = \vec{I}_L R$$

$$\vec{S}_{\text{load}} = \frac{|\vec{V}_L|^2}{R} = \frac{V_L^2}{R} \text{ or } \underset{\substack{\uparrow \\ \text{RMS value}}}{I_L^2} R$$


$$\text{mathematical Problem: } \max_{R_L} |\vec{I}_L|^2 R_L = \left( \frac{|\vec{V}_{th}|}{R_{th} + R_L} \right)^2 R_L$$

$$\left. \begin{array}{l} \text{optimum value.} \\ \text{(Max)} \rightarrow \text{check for 2nd} \\ \text{order cond} \end{array} \right\} R_L: \frac{dP_L}{dR_L} = 0 \Rightarrow R_L = R_{th}$$

(go back & verify)

$$\left. \begin{array}{l} \text{Voltage across the load} \\ \text{under max. power transfer} \end{array} \right\} = \frac{\vec{V}_{th}}{2}$$
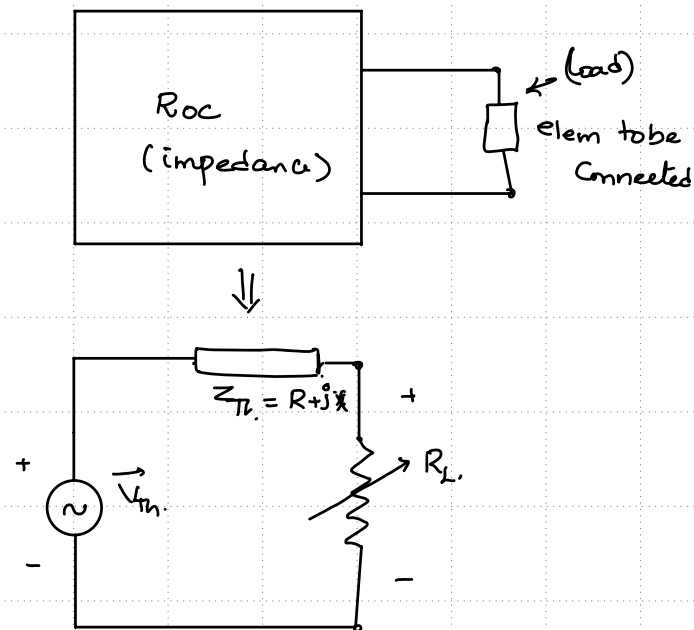
## Maximum Power Transfer Theorem - Scenario 2



$$\max_{R_L} P_L$$

$$\max_{R_L} |\vec{I}_L|^2 R_L$$

for this scenario  $\vec{I}_L = \frac{\vec{V}_{th}}{R_{th} + jX_{th} + R_L}$

$$|\vec{I}_L|^2 = \frac{|\vec{V}_{th}|^2}{(R_{th} + R_L)^2 + X_{th}^2}$$



mathematically  $\max_{R_L} \frac{|\vec{V}_{th}|^2}{(R_{th} + R_L)^2 + X_{th}^2} \cdot R_L$

optimum value of  $R_L$  :  $\left. \frac{dP_L}{dR_L} \right| = 0$

Value of  $R_L = \sqrt{R_{th}^2 + X_{th}^2} = |\vec{Z}_{th}| \leftarrow \text{Verify}$

Voltage under max. power T/F } = ??
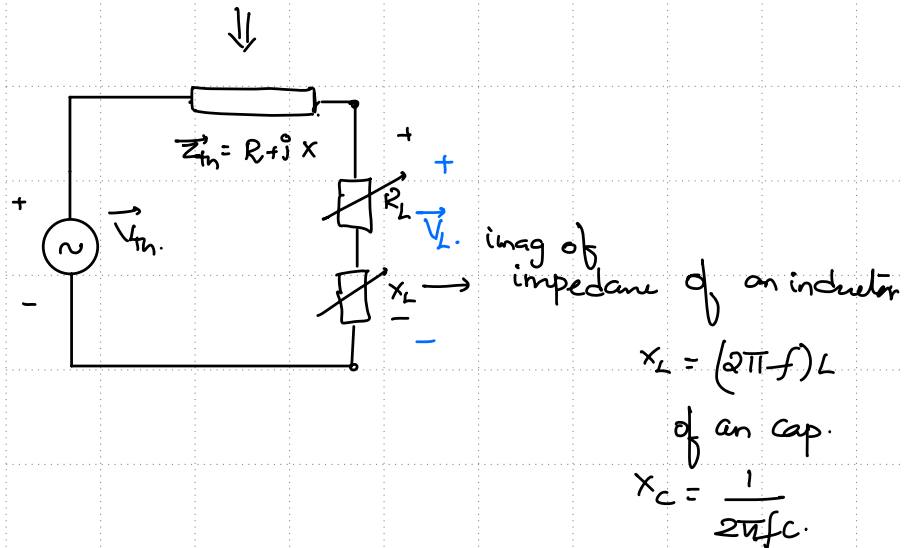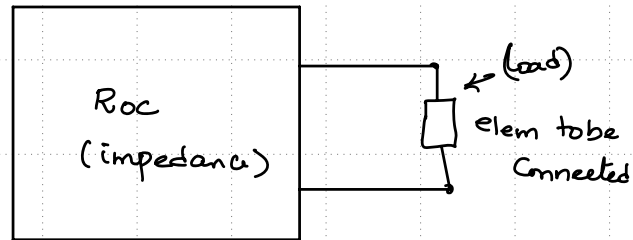
## Maximum Power Transfer Theorem - Scenario 3



$$\max_{(R_L, X_L)} P_L$$

$$\max_{(R_L, X_L)} |\vec{I}_L|^2 R_L$$

for this scenario  $\vec{I}_L = \frac{\vec{V}_{th}}{R_{th} + jX_{th} + (R_L + jX_L)}$

$$|\vec{I}_L|^2 = \frac{|\vec{V}_{th}|^2}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

Mathematically  $\max_{R_L, X_L} |\vec{I}_L|^2 R_L$

$$\max_{R_L, X_L} \frac{|\vec{V}_{th}|^2}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} R_L$$


optimum value of  $R_L: \frac{dP_L}{dR_L} = 0$  and  $X_L: \frac{dP_L}{dX_L} = 0$

value of  $R_L: R_{th}$  and  $X_L = -X_{th}$

Voltage Under maximum Power T/F: ??

## Maximum Power Transfer Theorem - Scenario 3

---

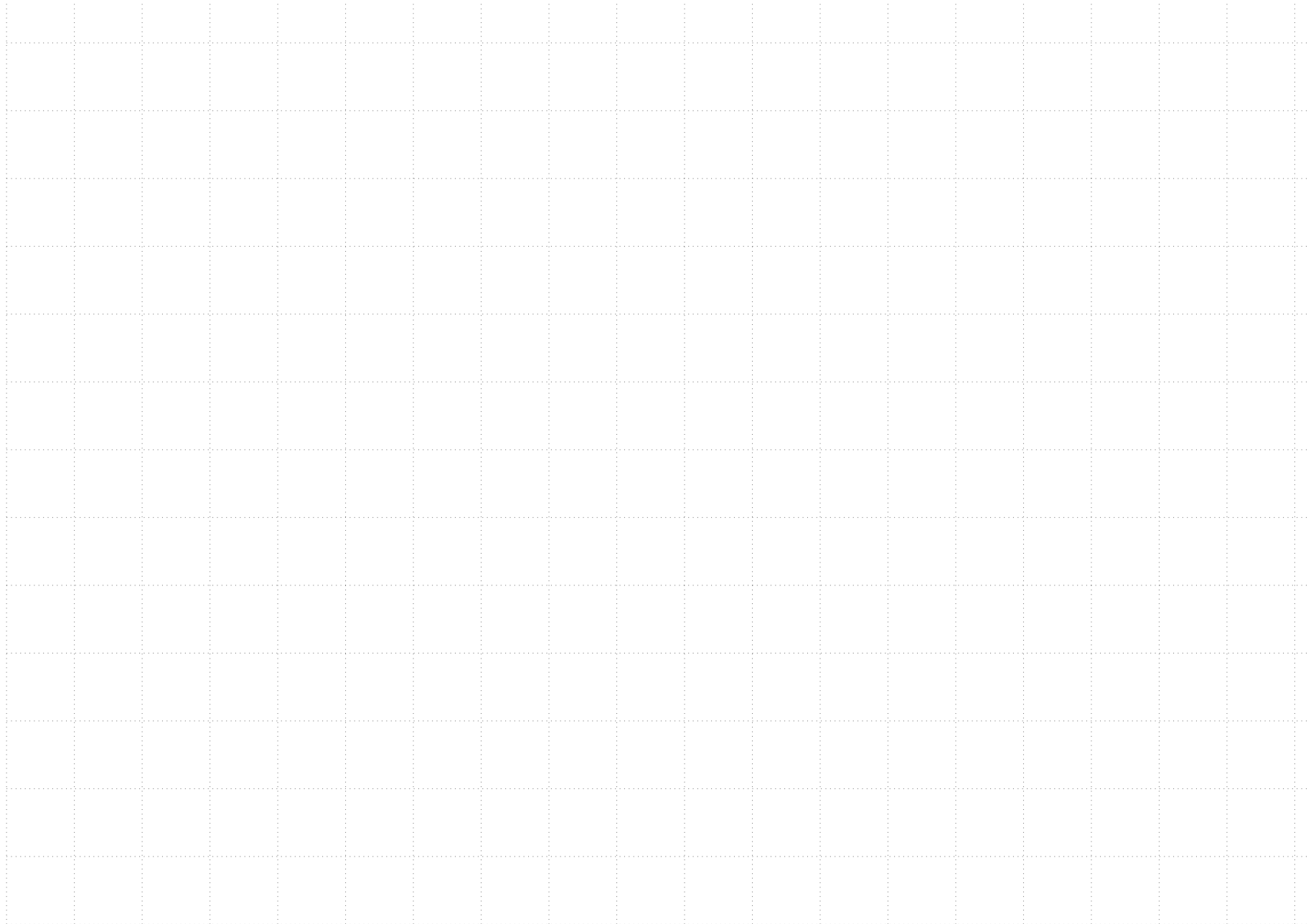

## Example

---

