

---

# EE1101: Circuits and Network Analysis

## Lecture 19: KVL and Inductance

September 12, 2025


---

### Topics :

1. Kirchhoff's Voltage Law (KVL) for AC Circuits
  2. Inductance
-

# KVL for AC Circuits (Not a Practical Scenario; but Chosen to demonstrate the validity of KVL)

Example:-

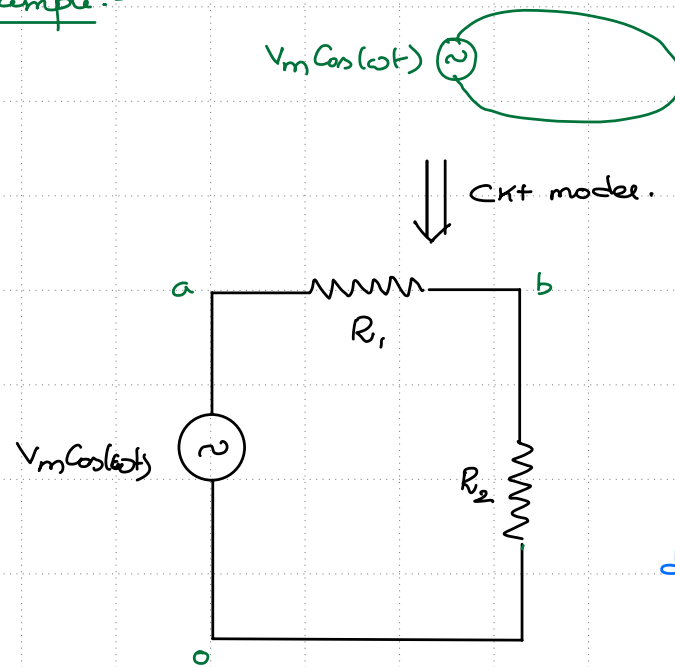

$V_m \cos(\omega t)$   $\Rightarrow$  Wire can be modelled as a resistance.

$\Downarrow$   
Resistance  
 $\Downarrow$

Assume that mag of  $\leftarrow$  def the magnitude of  
Current is not constant in the  
Wire.  
Very large (x)


def:  $V_{ab} = - \int_b^a \vec{E} \cdot d\vec{l}$  ( $\because$  path independence of potential is  
not established, def potential  
where path is along the ckt elem)

Apply Maxwell's 2<sup>nd</sup> Eqn:  $\oint \vec{E} \cdot d\vec{l} = - \frac{d\lambda}{dt}$  (Lenz's Law)

$$\int_o^a \vec{E} \cdot d\vec{l} + \int_a^b \vec{E} \cdot d\vec{l} + \int_b^o \vec{E} \cdot d\vec{l} = - \frac{d\lambda}{dt}$$

$$- V_{ao} - V_{ba} - V_{ob} = - \frac{d\lambda}{dt} \Rightarrow V_{ao} + V_{ba} + V_{ob} = \frac{d\lambda}{dt}$$

## KVL for AC Circuits

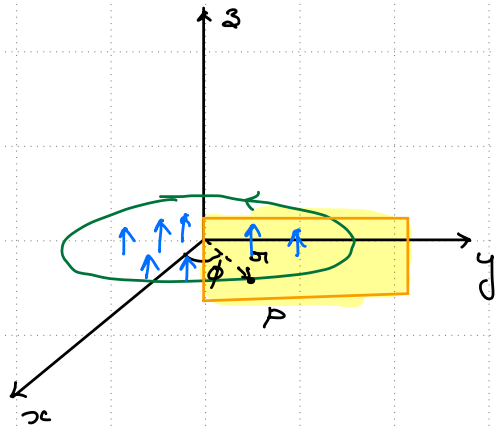

Current  $\rightarrow \hat{\phi}$

mag. field intensity  $\vec{H} = \text{along } \hat{z}$

magnetic field:  $\oint \vec{H} \cdot d\vec{l} = I_{enc}$

$$\oint H_z d\vec{z} = I_{enc} = N i \quad \leftarrow \text{no. of turns}$$

$$|H| \propto N i$$

Circuit domain (in simple terms)

$\mu_r N^2 I (\pi r^2) \omega$  is not

significant  $\Rightarrow \frac{d\lambda}{dt} \approx 0$

$\Downarrow$

$$KVL \Rightarrow \oint \vec{E} \cdot d\vec{l} = 0 \Rightarrow \sum V = 0$$

$$KVL \text{ for Circuit domain} = \sum_{i \in \text{loop}} V_i = 0 \quad \left( \text{both for DC \& AC} \right)$$

$\vec{B}$  (mag flux density):  $\vec{B} = \mu \vec{H} \Rightarrow |\vec{B}| \propto \mu_0 \mu_r N I \cos \omega t$

$$\text{flux } \phi = \int \vec{B} \cdot d\vec{S} \propto \mu_r N I \cos \omega t (\pi r^2)$$

$$\text{flux linkage } \lambda = N \phi \propto \mu_r (N^2) I \cos \omega t (\pi r^2)$$

$$\frac{d\lambda}{dt} \propto \underbrace{\mu_r N^2 I (\pi r^2)}_{\text{dominant}} \omega$$

while building inductor

on the other hand, for long transmission lines,  $(\pi r)$  is significant even though freq is low.


effective radius is very small for circuits

on the other hand, for antennas & waveguides, freq of operation is high


freq of operation  $\left( \frac{d\lambda}{dt} \right)$  at low freq is not significant

so  $\frac{d\lambda}{dt}$  is significant

## Inductance Ckt elem:

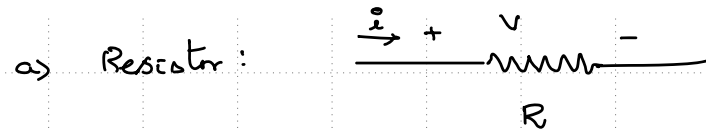

$$V = iR$$

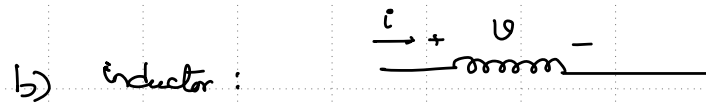

$$V = \frac{d\lambda}{dt} = L \frac{di}{dt} \quad (\lambda = Li)$$

↓

mag core where  $\mu_r \gg 1$   
 $\epsilon$   
 No. of turns are relatively high

↓  
 dep on geometry &

Prop of magnetic core.