

---

# EE1101: Circuits and Network Analysis

## Lecture 35: Two-Port Networks

October 28, 2025

---

### Topics :

1. Admittance and Impedance Parameters
2. Hybrid and Inverse Hybrid Parameters


3 important aspects:

① Deriving the model

② Computing the parameters of  
the model

③ Use case.  $\rightarrow$  when RoC is linear & has  
no varying independent sources.
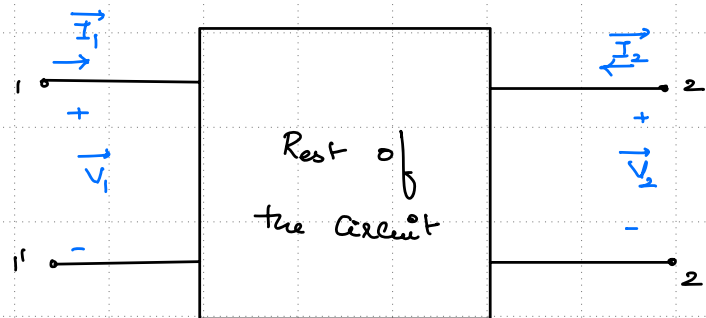
# Admittance Parameters (Deriving the model $\rightarrow$ by connecting a voltage source at both ports)



goal: to derive expression for currents  $\vec{I}_1$  and  $\vec{I}_2$

Sub Ckt-a:- Null the source at port 2-2' ( $\vec{I}_b, \vec{I}_{2a}$ ) (Short circuit of port 2-2')

Sub Ckt-b:- Null the source at port 1-1' ( $\vec{I}_b, \vec{I}_{2b}$ ) (Short ckt of port 1-1')

$$\vec{I}_1 = \vec{I}_{1a} + \vec{I}_b \text{ and } \vec{I}_2 = \vec{I}_{2a} + \vec{I}_b$$

for sub ckt-a:-

$$\vec{I}_{1a} = \frac{\vec{V}_1}{\vec{Z}_{eq,1}} \quad \vec{Z}_{eq,1} \rightarrow \text{Equivalent imp of the ROC w/tn port 2-2' shorted}$$

$$\vec{I}_{2a} = - (\text{SCC associated w/tn port 2-2'})$$


$$\vec{I}_{1a} = \vec{y}_{11} \vec{V}_1 \text{ and } \vec{I}_{2a} = \vec{y}_{21} \vec{V}_1$$

$\vec{y}$  Trans Conductance


for sub ckt-b:

$$\vec{I}_{2b} = \frac{\vec{V}_2}{\vec{Z}_{eq,2}}, \quad \vec{Z}_{eq,2} \rightarrow \text{Eq. imp of the ROC w/tn port 1-1' shorted}$$
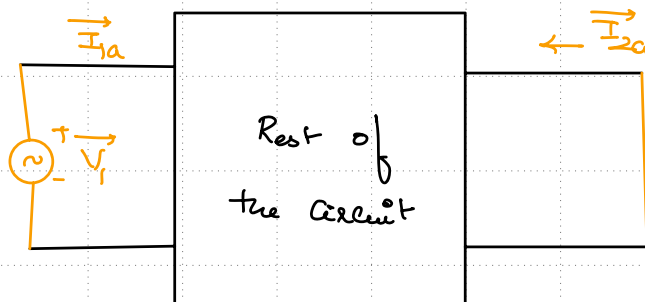
$$\vec{I}_{1b} = - (\text{SCC associated w/tn port 1-1'})$$




Sub Ckt-a.

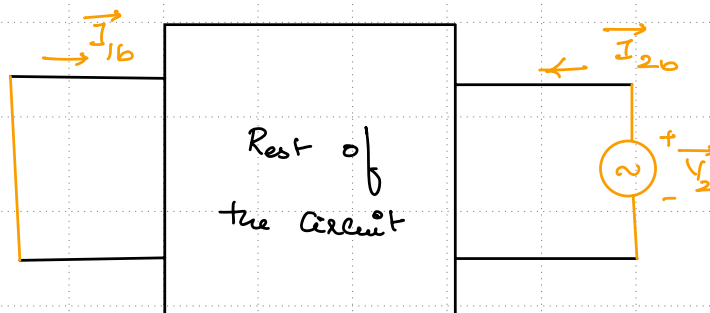

Sub Ckt-b.

$$\vec{I}_{2b} = \vec{y}_{22} \vec{V}_2 \text{ and } \vec{I}_{1b} = \vec{y}_{12} \vec{V}_2$$

## Admittance Parameters

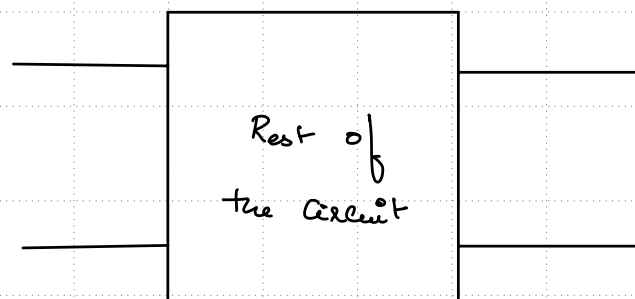

final mathematical model

$$\begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} \vec{Y}_{11} & \vec{Y}_{12} \\ \vec{Y}_{21} & \vec{Y}_{22} \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} \rightarrow \text{Admittance parameter model of a 2-Port N/w.}$$

Approach for computing the parameters:


$$\vec{Y}_{11} = \left. \frac{\vec{I}_1}{\vec{V}_1} \right|_{\vec{V}_2=0} \quad (\text{Short circuit of Port 2-2'})$$

$$\vec{Y}_{21} = \left. \frac{\vec{I}_2}{\vec{V}_1} \right|_{\vec{V}_2=0} \quad (\text{Short circuit of Port 2-2'})$$

$$\vec{Y}_{22} = \left. \frac{\vec{I}_2}{\vec{V}_2} \right|_{\vec{V}_1=0} \quad (\text{Short circuit of Port 1-1'})$$

$$\vec{Y}_{12} = \left. \frac{\vec{I}_1}{\vec{V}_2} \right|_{\vec{V}_1=0} \quad (\text{Short circuit of Port 1-1'})$$
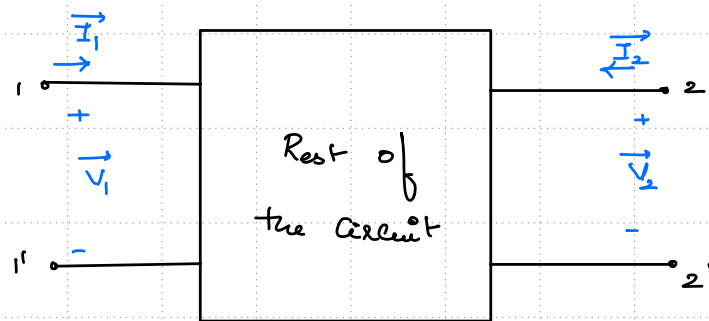
# Impedance Parameters (Deriving the model $\rightarrow$ by connecting a current source at both ports)




goal: to derive expression for voltages  $\vec{V}_1$  and  $\vec{V}_2$

Sub-circuit a: Null the source at 2-2'  
(open circuit of port 2-2')

$$\vec{V}_{1a} \text{ and } \vec{V}_{2a}$$

Sub-circuit b: Null the source at 1-1'  
(open circuit of port 1-1')
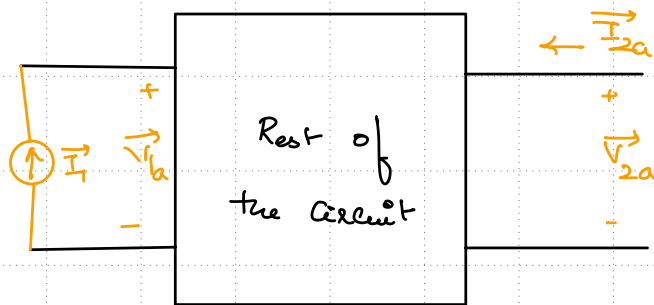
$$\vec{V}_{1b} \text{ and } \vec{V}_{2b}$$




Sub circuit-a.

Sub-circuit a: (open circuit Port 2-2')

$$\begin{aligned} \vec{V}_{1a} &= \vec{I}_1 \vec{Z}_{eq,1'} \\ &= \vec{I}_1 \vec{Z}_{11} \end{aligned}$$

EQ. imp of Port 1-1'  
with 2-2' open.
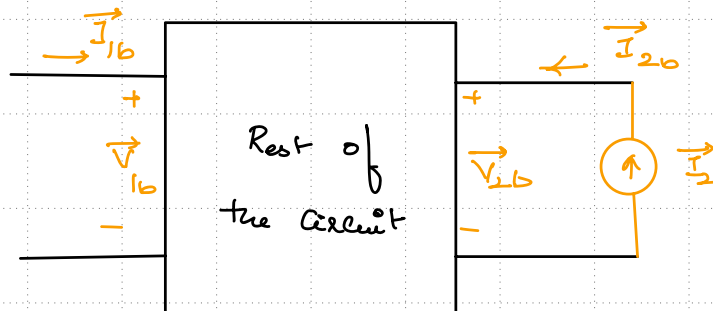
$$\begin{aligned} \vec{V}_{2a} &= \text{open ckt vol of Port 2-2'} \\ &= \vec{Z}_{21} \vec{I}_1 \end{aligned}$$



Sub circuit-b.


Sub-circuit b: (open circuit of Port 1-1')

$$\begin{aligned} \vec{V}_{2b} &= \vec{I}_2 \vec{Z}_{eq,2} \\ &= \vec{I}_2 \vec{Z}_{22} \end{aligned}$$

EQ. imp of Port 2-2'  
with 1-1' open

$$\begin{aligned} \vec{V}_{1b} &= \text{open ckt vol of Port 1-1'} \\ &= \vec{Z}_{12} \vec{I}_2 \end{aligned}$$

## Impedance Parameters

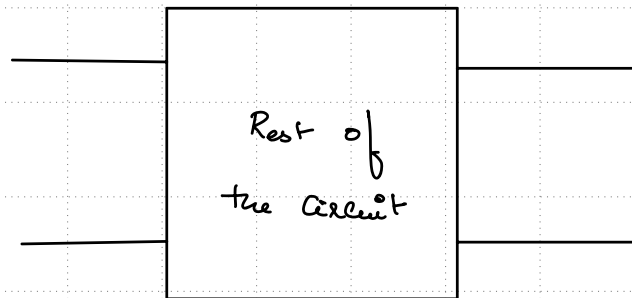

final mathematical model

$$\begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} \vec{Z}_{11} & \vec{Z}_{12} \\ \vec{Z}_{21} & \vec{Z}_{22} \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} \leftarrow \text{impedance parameter model of a 2 port N/w}$$

Approach for Computing Parameters:

$$[\vec{Y}_{\text{param}}] = [\vec{Z}_{\text{param}}]^{-1}$$

$$\vec{Y}_{11} = \frac{\vec{Z}_{22}}{\Delta} \quad \text{where } \Delta = \det[\vec{Z}_{\text{param}}]$$

$$\vec{Y}_{22} = \frac{\vec{Z}_{11}}{\Delta}$$

open circuit  
Parameters.

$$\vec{Z}_{11} = \left. \frac{\vec{V}_1}{\vec{I}_1} \right|_{\vec{I}_2=0}$$

(open circuit of port 2-2')

$$\vec{Z}_{21} = \left. \frac{\vec{V}_2}{\vec{I}_1} \right|_{\vec{I}_2=0}$$

(open circuit of port 2-2')

$$\vec{Z}_{22} = \left. \frac{\vec{V}_2}{\vec{I}_2} \right|_{\vec{I}_1=0}$$

(open circuit of port 1-1')


$$\vec{Z}_{12} = \left. \frac{\vec{V}_1}{\vec{I}_2} \right|_{\vec{I}_1=0}$$

(open circuit of port 1-1')
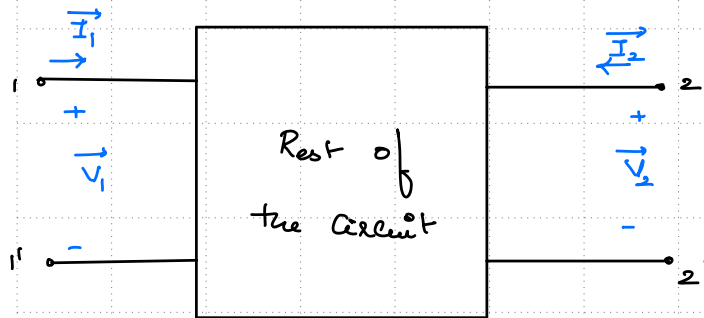
# Hybrid Parameters *(Deriving the model → by Connecting*

1-1' → Current source.  
2-2' → Voltage source.

Goal: to derive expression  $\vec{V}_1$  and  $\vec{I}_2$




Sub Ckt a: Null at 2-2' (Short circuit of 2-2')

Sub Ckt b: Null at 1-1' (open circuit of 1-1')

Sub Ckt a: (Null the source at 2-2')  
(Short circuit of 2-2')

$$\begin{aligned}\vec{V}_{1a} &= \vec{Z}_{eq1} \vec{I}_1 \\ &\quad \text{EQ. imp of part 1-1' w/tn 2-2' shorted} \\ &= \vec{h}_{11} \vec{I}_1 \quad (= 1/\vec{y}_{11})\end{aligned}$$
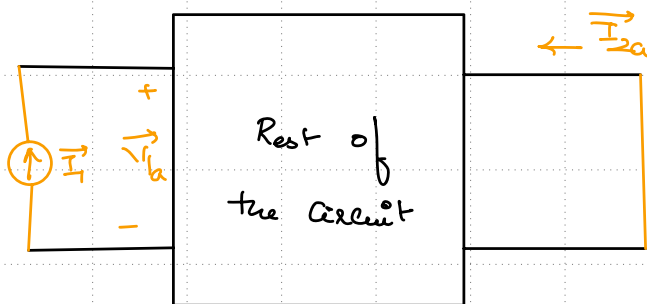
$$\begin{aligned}\vec{I}_{2a} &= -(\text{SCC of 2-2'}) \leftarrow \text{in terms of } y\text{-para} \\ &= \vec{h}_{21} \vec{I}_1 \quad \vec{y}_{21} \vec{V}_1\end{aligned}$$




Sub Ckt-a.

Sub Ckt b: (Null the source at 1-1')  
(open ckt of 1-1')


$$\begin{aligned}\vec{V}_{1b} &= \text{open ckt Vol of part 1-1'} \leftarrow \text{in terms of } z\text{-param} \\ &= \vec{h}_{12} \vec{V}_2 \quad \vec{z}_{12} \vec{I}_2\end{aligned}$$
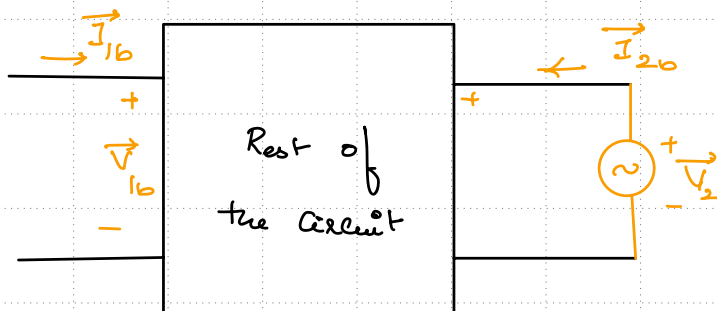
$$\vec{I}_{2b} = \frac{\vec{V}_2}{\vec{Z}_{eq2}} = \vec{h}_{22} \vec{V}_2 \quad (\vec{h}_{22} = 1/\vec{Z}_{22})$$



Sub Ckt-b.

## Hybrid Parameters

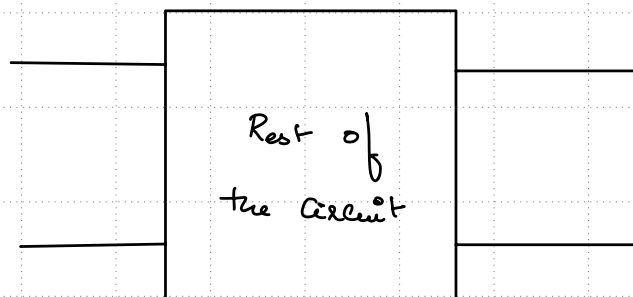

final mathematical model:

$$\begin{bmatrix} \vec{V}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} \vec{h}_{11} & \vec{h}_{12} \\ \vec{h}_{21} & \vec{h}_{22} \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{V}_2 \end{bmatrix} \leftarrow \text{hybrid parameter model of a 2-port n/w.}$$

Computing the parameters

$$\vec{h}_{11} = \frac{1}{\vec{y}_{11}}$$

$$\vec{h}_{22} = \frac{1}{\vec{z}_{22}}$$

$$\vec{h}_{21} \vec{I}_1 = \vec{y}_{21} \vec{V}_1$$

$$\text{and } \vec{h}_{12} \vec{V}_2 = \vec{z}_{12} \vec{I}_2$$

$$\vec{h}_{11} = \left. \frac{\vec{V}_1}{\vec{I}_1} \right|_{\vec{V}_2=0} \quad (2-2' \text{ shorted})$$

$$\vec{h}_{21} = \left. \frac{\vec{I}_2}{\vec{I}_1} \right|_{\vec{V}_2=0} \quad (2-2' \text{ shorted})$$


$$\vec{h}_{12} = \left. \frac{\vec{V}_1}{\vec{V}_2} \right|_{\vec{I}_1=0} \quad (1-1' \text{ open})$$

$$\vec{h}_{22} = \left. \frac{\vec{I}_2}{\vec{V}_2} \right|_{\vec{I}_1=0} \quad (1-1' \text{ open})$$
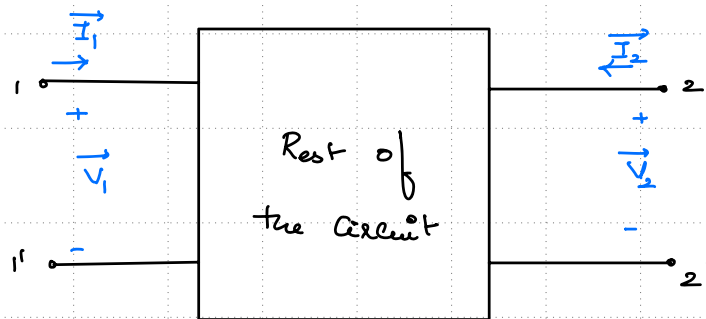
# Inverse Hybrid Parameters (Deriving the model $\rightarrow$ by Connecting

$1-1' \rightarrow$  Voltage Source.  
 $2-2' \rightarrow$  Current Source.

goal: to derive expression  $\vec{I}_1$  and  $\vec{V}_2$



Sub CKT-a: Null the Source at 2-2' (Open the Port)


$$\vec{I}_{1a} = \frac{1}{\vec{Z}_{eq,1}} \vec{V}_1$$

Eq. imp of 1-1' with 2-2' open

$$\vec{g}_{11} = \frac{1}{\vec{Z}_{11}}$$

$$\vec{V}_{2a} = (\text{open ckt vol of } 2-2') = \text{intems of } \vec{Z}\text{-params}$$

$$= \vec{g}_{21} \vec{V}_1$$

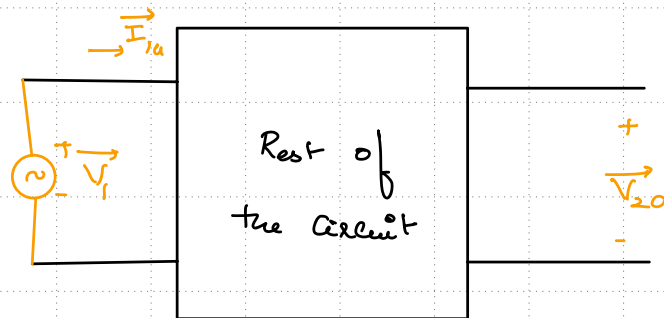


Sub CKT-a.

Sub CKT-b: Null the Source at 1-1' (Shorting Port)

$$\vec{I}_{1b} = -(\text{SCC associated with } 1-1') = \text{intems of } \vec{y}\text{-params}$$

$$= \vec{g}_{12} \vec{I}_2$$

$$= \vec{y}_{12} \vec{V}_2$$

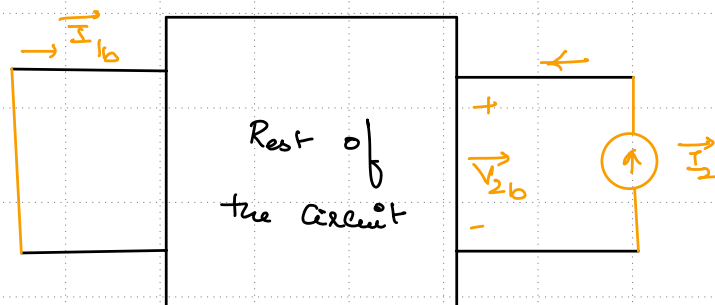

Sub CKT-b.


$$\vec{V}_{2b} = \vec{Z}_{eq,2} \vec{I}_2$$

Eq. imp of 2-2' with 1-1' Shorted

$$\vec{g}_{22} = \frac{1}{\vec{Z}_{22}}$$



## Inverse Hybrid Parameters

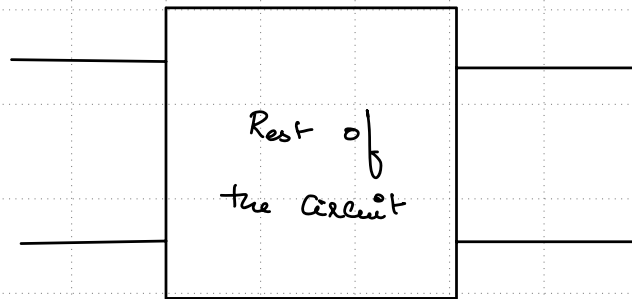

final model

$$\begin{bmatrix} \vec{I}_1 \\ \vec{V}_1 \end{bmatrix} = \begin{bmatrix} \vec{g}_{11} & \vec{g}_{12} \\ \vec{g}_{21} & \vec{g}_{22} \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{I}_2 \end{bmatrix} \leftarrow \text{Inverse hybrid param of a 2-port n/w.}$$

$$\vec{g}_{11} = \frac{1}{\vec{Z}_{11}}$$

$$\vec{g}_{22} = \frac{1}{\vec{Z}_{22}}$$

Computing the param

$$\vec{g}_{11} = \left. \frac{\vec{I}_1}{\vec{V}_1} \right|_{\vec{I}_2=0} \Rightarrow \text{open } 2-2'$$

$$\vec{g}_{21} = \left. \frac{\vec{V}_2}{\vec{V}_1} \right|_{\vec{I}_2=0} \Rightarrow ''$$

$$\vec{g}_{12} = \left. \frac{\vec{I}_1}{\vec{I}_2} \right|_{\vec{V}_1=0} \Rightarrow \text{Short } 1-1'$$

$$\vec{g}_{22} = \left. \frac{\vec{V}_2}{\vec{I}_2} \right|_{\vec{V}_1=0} \Rightarrow \text{Short } 1-1'$$

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix} = \begin{bmatrix} \vec{a}_1 & \vec{a}_2 \end{bmatrix}$$

$$\det(\vec{a}_1, \vec{a}_2) = \det(a\vec{e}_1 + c\vec{e}_2, \vec{a}_2)$$

$$= a \det(\vec{e}_1, \vec{a}_2) + c \det(\vec{e}_2, \vec{a}_2)$$

$$= a \det(\vec{e}_1, b\vec{e}_1 + d\vec{e}_2) + c \det(\vec{e}_2, b\vec{e}_1 + d\vec{e}_2)$$

$$= ab \det(\vec{e}_1, \vec{e}_1) + ad \det(\vec{e}_1, \vec{e}_2) + bc \det(\vec{e}_2, \vec{e}_1) + cd \det(\vec{e}_2, \vec{e}_2)$$

$$= 0 + ad - bc + 0$$