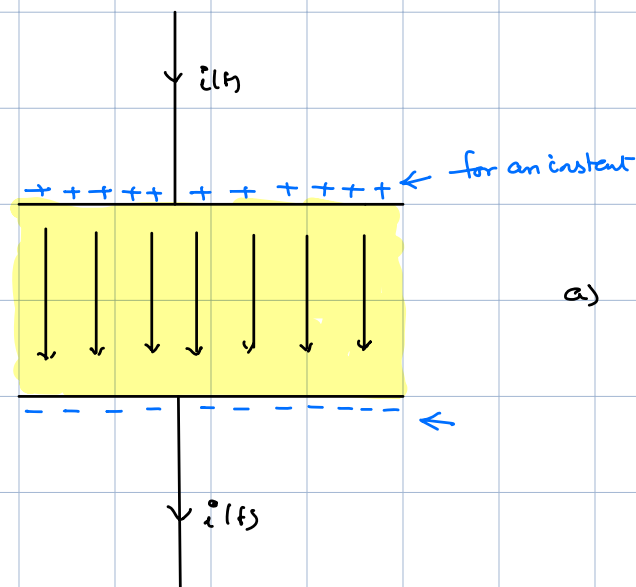


Capacitors (from a ckt point of view)

from a ckt point of view : 2 terminal elem

$$i(t) = \frac{dQ}{dt} = C \frac{dv}{dt} \quad \text{where } Q = CV$$

Capacitance [F] \rightarrow determined by geometry
and Prop of dielectric medium.



a) when current changes w.r.t time



$Q(t)$ changes w.r.t time.



$\vec{E} \ \& \ \vec{D}$ within a Cap changes w.r.t. time



$$i_d \propto \frac{d\vec{D}}{dt} = i(t)$$

displacement current

Let $i_c(t)$ be known \Rightarrow

$$\frac{dV_c}{dt} = \frac{1}{C} i_c(t) \Rightarrow dV_c = \frac{1}{C} i_c(t) dt$$

$$\int_{V_c(t_0)}^{V_c(t)} dV_c = \frac{1}{C} \int_{t_0}^t i_c(t) dt$$

$$V_c(t) = V_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(t) dt$$


Example 1:-

$i(t) = I$ (DC signal) ; $V_c(0) = 0$.

$$i_c(t) = I u(t)$$

$$V_c(t) = \underbrace{V_c(0)}_0 + \frac{1}{C} \int_0^t I u(t) dt$$
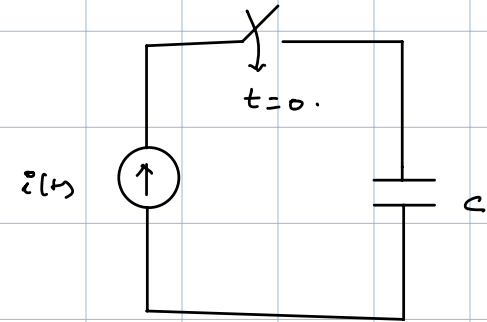
$$V_c(t) = \frac{I}{C} t \quad \text{for } t > 0.$$



Example:

$i(t) = I_m \cos(\omega t + \phi_c)$; $\phi_c = 0$ (Evaluate it using indefinite integral)

$$i_c(t) = i(t) u(t) = I_m \cos(\omega t + \phi_c) u(t)$$

$$V_c(t) = \frac{1}{C} \int I_m \cos(\omega t) u(t) dt = \frac{I_m}{\omega C} \sin \omega t + C =$$

C : some const $\rightarrow ??$

Voltage across a capacitor cannot change instantly.

$$i_c = C \frac{dV}{dt}$$

if $V_c(t)$ changes instantly \rightarrow impulse current

(or)

to make $V_c(t)$ change instantly \rightarrow impulse current

Not possible
in a
real world
scenario.

\Downarrow

Voltage across a Cap cannot
change instantly ($\phi(t)$ as well)

Example:

$$i(t) = I_m \cos(\omega t + \phi_i) ; \quad \phi_i = 0 \quad (\text{evaluate it using indefinite integral})$$

$$i_c(t) = i(t) u(t) = I_m \cos(\omega t + \phi_i) u(t)$$

$$V_c(t) = \frac{1}{C} \int I_m \cos(\omega t) u(t) dt = \frac{I_m}{\omega C} \sin \omega t + C =$$

$$C : \text{Voltage continuity} \Rightarrow V_c(0) = 0 \Rightarrow C = 0$$

$$V_c(t) = \frac{I_m}{\omega C} \sin \omega t$$

Sinusoidal steady-state behavior of a capacitor:-

$$i_c(t) = I_m \cos(\omega t + \phi_i) \Rightarrow \vec{I}_c = \frac{I_m}{\sqrt{2}} \angle \phi_i$$

$$\text{in sinusoidal steady state: } v_c(t) = \frac{1}{C} \int i_c(t) dt = \frac{I_m}{\omega C} \sin(\omega t + \phi_i) \Rightarrow \vec{V}_c = \frac{I_m}{\sqrt{2} \omega C} \angle \phi_i - \pi/2 \\ = \underline{\underline{V \angle \phi_v}}$$

$$V = \frac{I_m}{\sqrt{2} \omega C} = \frac{I}{\omega C}$$

$$\phi_v = \phi_i - \pi/2$$

In steady state, the current phasor leads the voltage phasor by $\pi/2$

$$\theta = \phi_v - \phi_i = -\pi/2.$$

$$\text{Impedance of a Cap } \vec{Z} = \frac{\vec{V}}{\vec{I}} = \underbrace{\frac{V}{I}}_{\omega C} \angle \phi_v = \frac{1}{\omega C} \angle \phi_v = \frac{1}{\omega C} \angle \phi_i - \pi/2 \\ \vec{Z} = \frac{1}{j\omega C}.$$

mag of imp Z of a Cap $\propto \frac{1}{\omega} \Rightarrow$ impedance is large at lower freq
low at high freq.

Phase of imp of a Cap : $\angle \vec{Z} = -\pi/2$

Power associated with a Capacitor: $\vec{I} = I \angle \phi_c$
(Sinusoidal steady-state)

$$\vec{V} = V \angle \phi_v = \frac{I}{\omega C} \angle \phi_c - \pi/2$$

$$\begin{aligned} \text{Complex power } \vec{S} &= \vec{V} \vec{I}^* = \frac{I}{\omega C} \angle \phi_c - \pi/2 \cdot \underbrace{I \angle -\phi_c}_{\vec{I}^*} \\ &= -j \frac{I^2}{\omega C} = P + jQ \end{aligned}$$

$$\text{Active power} = 0$$

$$\text{Reactive power } (Q) < 0 \Rightarrow |Q| = \frac{I^2}{\omega C} ; Q = -\frac{I^2}{\omega C}$$

$$\text{Power factor} = \cos 0 = 1 \text{ (lead)}$$

$$\text{Power factor angle } \theta = -\pi/2$$

$$\text{Instantaneous Power } s(t) = Q \sin 2\omega t \quad (\because P=0) \Rightarrow -\frac{I^2}{\omega C} \sin 2\omega t$$


energy associated with a Cap:

$$E(t) = \int_0^t s(t) dt = \int_0^t \underbrace{\frac{I^2}{\omega C}}_{\text{shifting the time ref.}} \sin 2\omega t dt$$

$$= \frac{I^2}{\omega C} \left. \frac{\cos 2\omega t}{2\omega} \right|_0^t = \frac{I^2}{2\omega^2 C} (1 - \cos 2\omega t) = \frac{I^2}{2\omega^2 C} (2 \sin^2 \omega t)$$

$$= \frac{I^2}{\omega^2 C} \sin^2 \omega t$$

$$= C V^2 \sin^2 \omega t$$

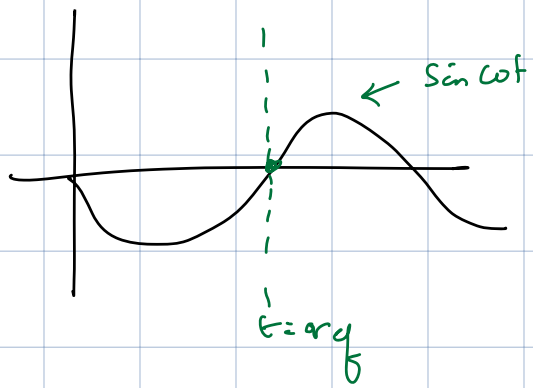

$$E(t) = -CV^2 \sin^2 \omega t \Rightarrow \frac{1}{2} C \underbrace{V_m^2 \sin^2 \omega t}_{|V(t)|^2}$$

$$E(t) = \underline{\underline{\frac{1}{2} C |V|^2}} .$$