
EE1101: Circuits and Network Analysis

Lecture 18: Power in AC Circuits

September 9, 2025


Topics :

1. Instantaneous Power, Active and Reactive Power
 2. Complex Power and Power Factor
-

Phasor Diagram - Lag and Lead

time-domain $\begin{cases} v(t) = V_m \cos(\omega t + \phi_v) \Rightarrow \vec{V} = \frac{V_m}{\sqrt{2}} \angle \phi_v \\ i(t) = I_m \cos(\omega t + \phi_i) \Rightarrow \vec{I} = \frac{I_m}{\sqrt{2}} \angle \phi_i \end{cases}$ $\left\{ \begin{array}{l} \text{rep of signal in phasor domain} \\ \text{(or) freq. domain} \end{array} \right.$

Phasor diagram (Scenario 1)

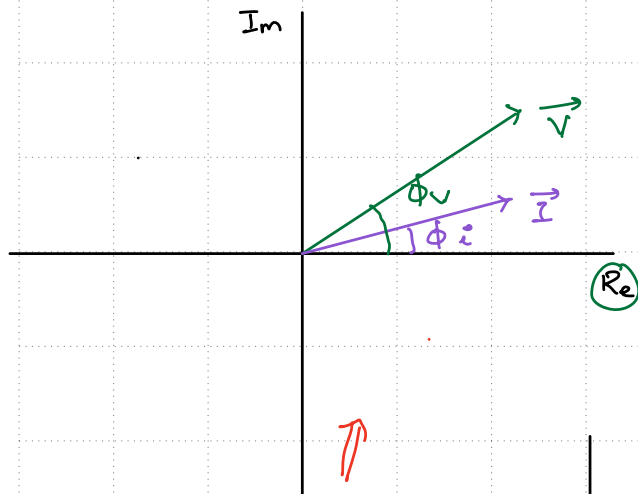

$\because \phi_v, \phi_i > 0 \Rightarrow$ time to nearest peak \downarrow $t_{p_v}, t_{p_i} < 0$

$\phi_v > \phi_i \Rightarrow t_{p_v} < t_{p_i} \Rightarrow |t_{p_v}| > |t_{p_i}|$

(or) peak of $i(t)$ is closer to $t=0$ than peak of $v(t)$ (not efficient)

Instead def lagging phasor & leading phasor.

Phase (for this course) is always def in the range

\downarrow using this cond $-\pi$ to π .


Multiple statements

- \vec{V} leads \vec{I} by $\phi_v - \phi_i$ (or)
- \vec{I} lags \vec{V} by $\phi_v - \phi_i$ (or)
- \vec{V} and \vec{I} have a phase difference of $\phi_v - \phi_i$

\vec{A} is leading \vec{B} if $\phi_a > \phi_b$ where ϕ_a, ϕ_b Phase angles of $\vec{A} \in \vec{B}$ [Phase ang. diff = $\phi_a - \phi_b$]

\vec{A} is lagging \vec{B} if $\phi_a < \phi_b$ where ϕ_a, ϕ_b Phase angles of $\vec{A} \in \vec{B}$ [\vec{A} lags \vec{B} by $\phi_b - \phi_a$]
(or) phase ang. diff b/w $\vec{A} \in \vec{B}$ is $\vec{A} - \vec{B}$

Instantaneous Power in AC Circuits

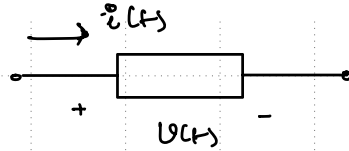


$$v(t) = V_m \cos(\omega t + \phi_v)$$


$$i(t) = I_m \cos(\omega t + \phi_i)$$

Phasor exp: $\vec{V} = \frac{V_m}{\sqrt{2}} \angle \phi_v$ and $\vec{I} = \frac{I_m}{\sqrt{2}} \angle \phi_i$ def θ as phase ang diff b/w \vec{V} & \vec{I}

Phasor diagram:

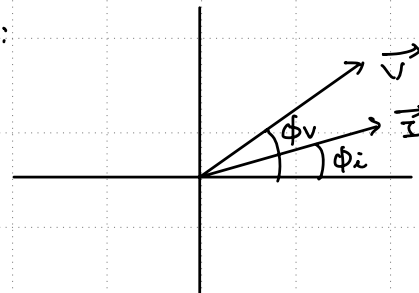

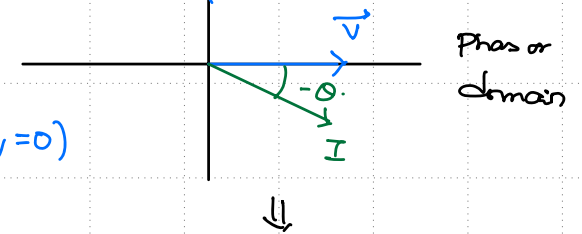\Rightarrow with a shifted time ref ($t + \phi_v = 0$)



$$v(t) = V_m \cos(\omega t) \quad \text{time domain}$$

$$i(t) = I_m \cos(\omega t - \theta)$$

def $s(t)$: instantaneous power = $v(t) i(t)$


$$= V_m \cos(\omega t) I_m \cos(\omega t - \theta)$$

$$= \frac{V_m I_m}{2} \left[\underbrace{\cos(2\omega t - \theta)}_{\text{double freq comp}} + \underbrace{\cos \theta}_{\text{DC Component}} \right]$$

$s(t)$ is periodic with period $T/2$, $f_{\text{freq}} = 2\omega$ & Avg value = $\frac{V_m I_m}{2} \cos \theta$.

Active and Reactive Power

$$\begin{aligned}
 S(t) &= \frac{V_m I_m}{2} [\cos(2\omega t - \theta) + \cos \theta] \\
 (VA) &= \frac{V_m I_m}{2} [\cos 2\omega t \cos \theta + \sin 2\omega t \sin \theta + \cos \theta] \\
 &= \underbrace{\frac{V_m I_m}{2} \cos \theta (1 + \cos 2\omega t)}_{\text{def as instantaneous active power } P(t) \text{ [W]}} + \underbrace{\frac{V_m I_m}{2} \sin \theta \sin 2\omega t}_{\text{Instantaneous Reactive power } (VAR) \text{ } \phi(t)}
 \end{aligned}$$

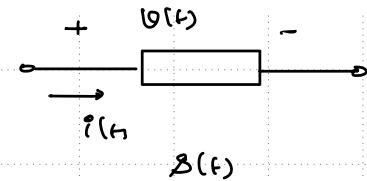


$$\begin{aligned}
 \text{Avg value of } P(t) &= \frac{V_m I_m}{2} \cos \theta \\
 &\text{def (Active Power } P)
 \end{aligned}$$

$$\begin{aligned}
 \text{def of Active power} &= \text{Avg of } P(t) \text{ or } S(t) \\
 &= \underbrace{VI \cos \theta}_{\text{RMS values}}
 \end{aligned}$$

$$\text{maximum value of } P(t) = \frac{V_m I_m}{2} \cos \theta \quad (2P)$$

$$\text{minimum value of } P(t) = 0$$

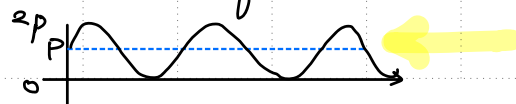


Instantaneous Reactive power (VAR)
 $\phi(t)$

$$\text{Avg value of } \phi(t) = 0$$

$$\text{maximum value} = \frac{V_m I_m}{2} \sin \theta$$
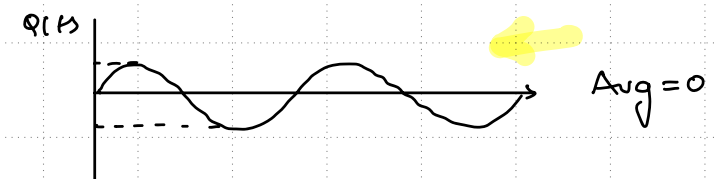
$$\text{minimum value} = -\frac{V_m I_m}{2} \sin \theta$$



$$\begin{aligned}
 \text{def: Reactive power } (\phi) &= \frac{V_m I_m}{2} \sin \theta \\
 &= VI \sin \theta
 \end{aligned}$$

$$S(t) = \underbrace{P(1 + \cos 2\omega t)}_{P(t)} + \underbrace{\phi \sin(2\omega t)}_{\phi(t)}$$

Complex Power

define Complex power $\vec{S} = VI \cos \theta + j VI \sin \theta = \underbrace{VI}_{\vec{V}} e^{j(\theta)} = VI e^{j(\phi_V - \phi_i)}$

$$\vec{S} = \vec{V} \vec{I}^* \quad [\text{VA}]$$

$$= \underbrace{V e^{j\phi_V}}_{\vec{V}} \underbrace{I e^{-j\phi_i}}_{(\vec{I})^*}$$

$$= P + jQ$$

def Apparent power $S = |\vec{S}| = \sqrt{P^2 + Q^2} = VI$

def Power factor angle $\theta = \phi_V - \phi_i = \tan^{-1}(Q/P) = \cos^{-1}(P/S) = \sin^{-1}(Q/S)$

def Power factor $= \cos \theta = P/S$

Power Factor

