

.

EE1101: Circuits and Network Analysis

Lecture 28: Second-Order Circuits

October 10, 2025

Topics :


1. Forced Response of Second-Order Circuits
-

Example (contd.)

$$Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \rightarrow (1)$$

Step ① \rightarrow diff ① w.r.t $t \Rightarrow \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i(t) = 0 \rightarrow (2)$

Step ②: $\left\{ \begin{array}{l} \text{Initial Cond: } i_L(0) = 10 \text{ A} \\ \left. \frac{di_L}{dt} \right|_{t=0} = \frac{V_L(t=0)}{L} = \frac{-V_R(t=0) - V_C(0)}{L} \\ = -\frac{10R}{L} \end{array} \right.$

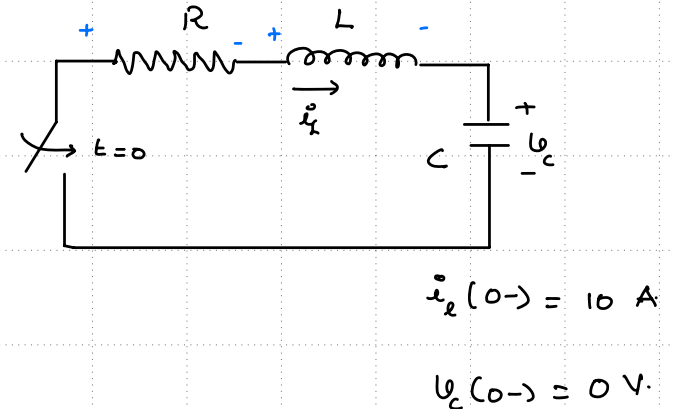

Step ③: Nature of the Complementary Sol: Compare with standard 2nd order ODE

$$\omega_n^2 = 1/LC \Rightarrow \omega_n = \sqrt{1/LC}$$

$$2\xi\omega_n = R/L \Rightarrow \xi = \frac{R}{2} \sqrt{\frac{C}{L}}$$

if $\xi > 1$: $x(t) = c_1 e^{s_1 t} + c_2 e^{s_2 t}$ where s_1, s_2 are roots of $s^2 + 2\xi\omega_n s + \omega_n^2 = 0$

$\xi = 1$: $x(t) = c_1 e^{s_1 t} + c_2 t e^{s_1 t}$ where s_1 is the repeated root of $s^2 + 2\xi\omega_n s + \omega_n^2 = 0$.

$0 \leq \xi < 1$: $x(t) = 2\eta e^{-\xi\omega_n t} \cos(\omega_d t + \theta)$ $s = -\xi\omega_n \pm j\omega_d$

$\xi = 0$: $x(t) = 2\eta \cos(\omega_n t + \theta)$

Example (contd.)

Case A: $R = 30\Omega$, $L = 10\text{H}$, $C = 0.1\text{F}$


$$\omega_n = 1\text{rad/s} \quad \xi = \frac{30}{20} = 1.5 > 1$$

characteristic eqn: $s^2 + 3s + 1 = 0$.

$$\text{roots are } s_1 = \frac{-3 + \sqrt{5}}{2}, \quad s_2 = \frac{-3 - \sqrt{5}}{2}$$

$$\approx -0.4, \quad \approx -2.6$$

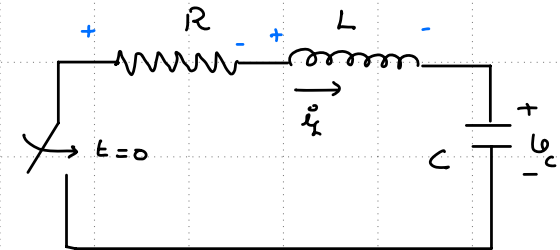gen sol $i(t) = C_1 e^{-0.4t} + C_2 e^{-2.6t}$



$$i_L(0^-) = 10\text{ A}$$

$$V_c(0^-) = 0\text{ V}$$

Step ④: apply I.C. to get final sol $i(0) = 10\text{A} = C_1 + C_2$.

$$\left. \frac{di}{dt} \right|_{t=0} = -0.4C_1 - 2.6C_2 = -10(R/L) = -30$$

$$C_2 = 130/11 \text{ and } C_1 = -20/11$$

$$i(t) = -20/11 e^{-0.4t} + 130/11 e^{-2.6t}$$

Example (contd.)

Case B: $R = 10 \Omega$, $L = 10 \text{ H}$, $C = 0.1 \text{ F}$


$$\omega_n = 1 \text{ rad/s} \quad \xi = 10/20 = 0.5 (< 1)$$

characteristic eqn: $s^2 + s + 1 = 0$.

$$\text{roots are } = -\xi\omega_n \pm j\omega_d$$

$$= -\frac{1}{2} \pm j\frac{\sqrt{3}}{2} = \underline{\underline{-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}}}$$
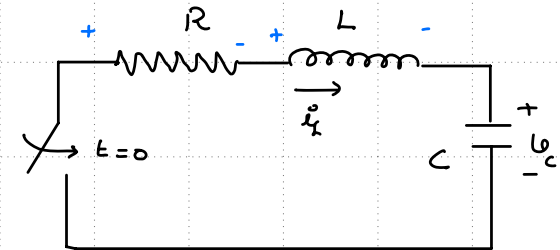
$$\text{gen sol } i(t) = 2\pi e^{-0.5t} \cos\left(\frac{\sqrt{3}}{2}t + \theta\right)$$



$$i_L(0^-) = 10 \text{ A}$$

$$v_C(0^-) = 0 \text{ V}$$

Step ④: apply i.c. to get final sol

$$i(0) = 10 \text{ A} = 2\pi \cos \theta \rightarrow \textcircled{\text{I}}$$

$$\left. \frac{di}{dt} \right|_{t=0} = -\pi \cos \theta - \sqrt{3}\pi \sin \theta = -10R/L = -10 \rightarrow \textcircled{\text{II}}$$

Solve $\textcircled{\text{I}}$ & $\textcircled{\text{II}}$ to get π and θ . & then the final sol.

Solution of Second-Order Differential Equations

Solve $\frac{d^2 x}{dt^2} + 2\xi\omega_n \frac{dx}{dt} + \omega_n^2 x = f(t) \rightarrow (1)$
 $\hookrightarrow A \cos(\omega t + \phi) \text{ or } A \sin(\omega t + \phi)$

\hat{x} : $\frac{d^2 \hat{x}}{dt^2} + 2\xi\omega_n \frac{d\hat{x}}{dt} + \omega_n^2 \hat{x} = A e^{j(\omega t + \phi)} \rightarrow (2)$

sol of (1) $x(t) = \operatorname{Re}\{\hat{x}(t)\}$ if $f(t)$ is \cos .
 $= \operatorname{Im}\{\hat{x}(t)\}$ if $f(t)$ is \sin

Complementary sol $\hat{x} = \hat{x}_c(t) + \hat{x}_p(t)$ ← Particular sol
 \hookrightarrow sol to $\frac{d^2 \hat{x}}{dt^2} + 2\xi\omega_n \frac{d\hat{x}}{dt} + \omega_n^2 \hat{x} = 0 \rightarrow$ can be computed by solving CE & adopting the process discussed

as $t \rightarrow \infty$, $x_c(t) \rightarrow 0$ unless $\xi = 0$.

$\hat{x}_p(t) \rightarrow$ 2 ways $\begin{cases} \text{guess the function from (v) for this course} \\ \text{Systematic approach (in course on D.E. and Transform Techniques)} \end{cases}$

Method of Undetermined Coefficients \rightarrow guess $\hat{x}_p(t)$

$$\hat{x}_p(t) = \mathcal{M} e^{j(\omega t + \phi - \theta)}$$

\mathcal{M} and θ are not known

(for complex exponential fits) $f(t) = A e^{j(\omega t + \phi)}$