

.

---

# EE1101: Circuits and Network Analysis

## Lecture 06: DC Circuit Analysis

August 7, 2025

---

### Topics :

1. Node Analysis
-

## Node Analysis - Overview of the approach

goal for any circuit analysis: To solve for unknown voltages / currents in a N/c

in Node Analysis: solve for unknown node voltages.

↓  
Potential of a  
Particular node  
w.r.t ref node.


Claim: if all node voltages are known / can be computed,  
then any other quantity ( $I, P$ ) can be determined.

① given a circuit where the reference node is specified, the goal of node analysis is to  
compute voltages at other nodes.

basic idea: Application of KCL at every node (where the potential is not known)  
 ↳ Standard form: in terms of currents but the unknowns are node voltages.  
 ↳ where is branch currents can be written in terms of unknown node voltages.  
 (not always)

Need to ensure that 'n' linearly independent equations are generated for finding 'n' unknowns
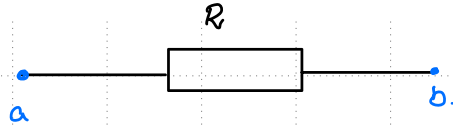
## Node Analysis - Overview of the approach




if  $V_a$  &  $V_b$  are known,

$$I_{ab} = \frac{V_a - V_b}{R} \quad \text{and} \quad I_{ba} = \frac{V_b - V_a}{R}$$


Current through the branch leaving node A. =  $I_{ab} = \frac{V_a - V_b}{R}$

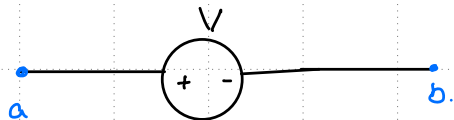Current through the branch leaving node B. =  $I_{ba} = \frac{V_b - V_a}{R}$



either a or b is ref nodes.


↓  
other node voltage is known

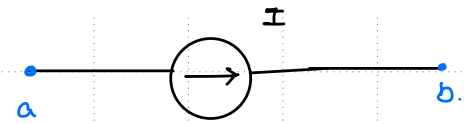

either a & b can be a ref node.

Current through the branch leaving node A. =  $I$

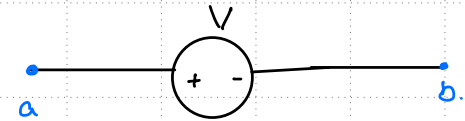Current through the branch leaving node B. =  $-I$



neither a nor b is a ref node.

↓  
writing an expression  
for  $I$  is not straightforward.

Start : a) ckt's that do not contain Voltage Sources.


b) " " contain Voltage Sources b/w node & ref node.

c) " " " " " b/w non-ref nodes.

## Node analysis with current sources and resistors

Apply KCL to one node in such a n/w.

(a)

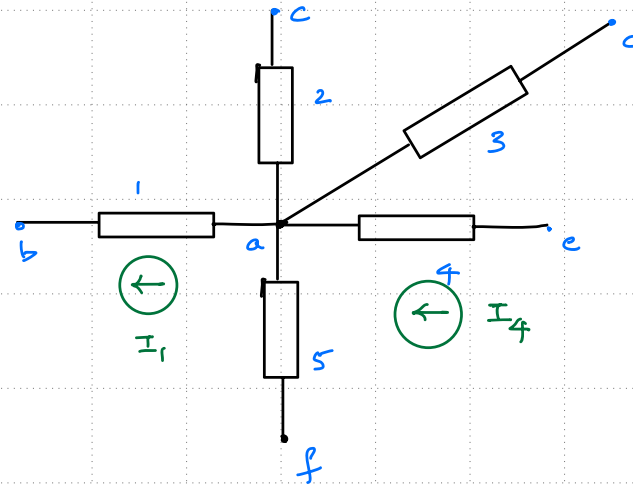

Basic idea:

KCL

used in this form

$\sum I_{\text{leaving the node}} = 0$   
through the connected branches

branches

Scenario 1:-

1 & 4 Constant Sources

( $I_1$  &  $I_4$ )

2, 3 & 5 are Resistors.

( $R_2, R_3, R_5$ )


$$I_1 + \frac{V_a - V_c}{R_2} + \frac{V_a - V_d}{R_3} - I_4 + \frac{V_a - V_f}{R_5} = 0$$

$$\underbrace{\left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right)}_{G_{aa}} V_a - \underbrace{\frac{1}{R_2}}_{G_{ac}} V_c - \underbrace{\frac{1}{R_3}}_{G_{ad}} V_d - \underbrace{\frac{1}{R_5}}_{G_{af}} V_f = I_4 - I_1$$

## Node analysis with current sources and resistors

Apply KCL to one node in such a n/c.

(a)

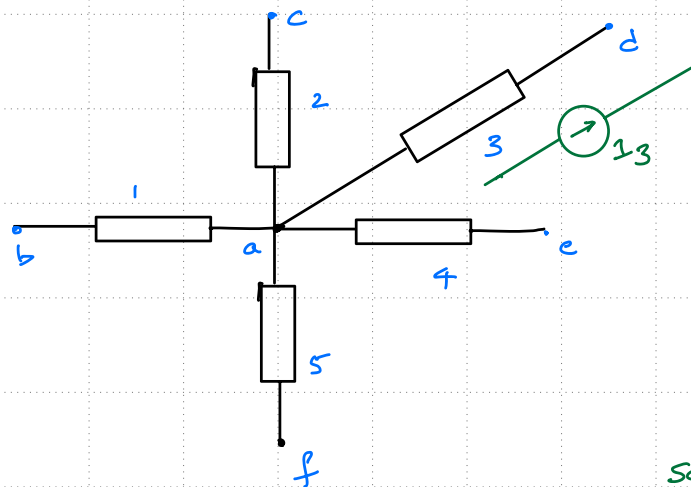

Basic idea:


KCL  
↓  
used in this form  
↓  
 $\sum I_{\text{leaving the node}} = 0$   
through the connected branches

Scenario 2: branch 3:  $I_3$

branches 1, 2, 4 & 5:  $R_1, R_2, R_4$  &  $R_5$  resp

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5}\right)V_a - \frac{1}{R_1}V_b - \frac{1}{R_2}V_c - \frac{1}{R_4}V_e - \frac{1}{R_5}V_f = -I_3$$
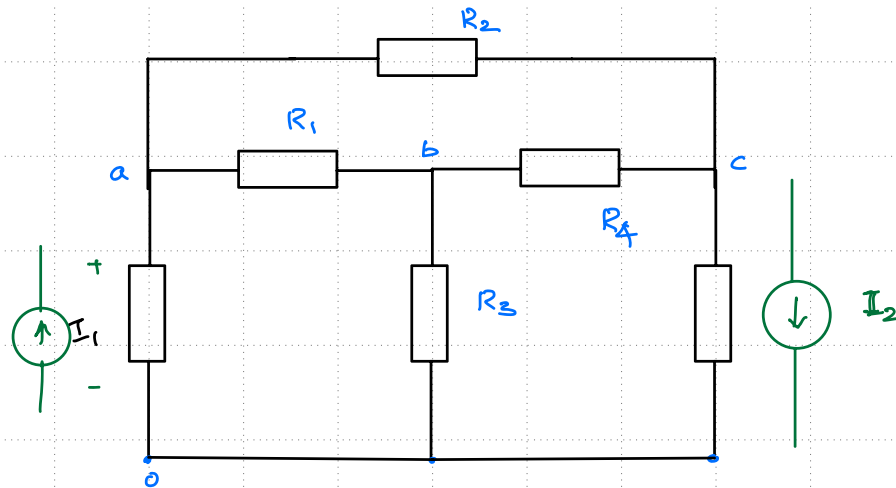
## Example - Use of Matrices in Node Analysis



3 nodes of unknown potential

$$\text{at } a: \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_a - \frac{1}{R_1} V_b - \frac{1}{R_2} V_c = I_1$$

$$\text{at } b: -\frac{1}{R_1} V_a + \left( \frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3} \right) V_b - \frac{1}{R_4} V_c = 0$$

$$\text{at } c: -\frac{1}{R_2} V_a - \frac{1}{R_4} V_b + \left( \frac{1}{R_4} + \frac{1}{R_2} \right) V_c = -I_2.$$

use matrices  $[G][V] = [I]$

Conductance matrix  $[G]$  (vector of unknown voltages)

vector of unknown voltages  $[V]$  (vector of node voltages)

$$[V] = [V_a, V_b, V_c]^T$$