

---

# EE1101: Circuits and Network Analysis

## Lecture 03: Circuit Domain Essentials

August 1, 2025

---

### Topics :

1. Power and Energy
  2. Two Teriminal Elements in DC Circuits
-

## Energy and Power in Circuits

from potential  $\Rightarrow$  external energy req to move a unit positive charge can be  
 $W_{ext}$  Computed

What is  $W_{ext}$  in moving a unit positive charge from  $b$  to  $a$ ?  $W_{ext} = V_a - V_b = V_{ab}$ .  
 $(V_b) (V_a)$

$W_{ext}$  in moving a charge  $q$  from  $b$  to  $a$ ?  $W_{ext} = q(V_{ab})$   
 $(V_b) (V_a)$

Scenario I:-  $V_a > V_b$  :

$$W_{ext} = q V_{ab} > 0.$$

(from  $b$  to  $a$ )

$$W_{sys} = -W_{ext} < 0$$

(energy in the elec  
form)

charge moving from lower  
Potential to higher potential  $\Rightarrow$  system gaining  
some energy.

Scenario II  $V_a < V_b$  :

$$W_{ext} = q V_{ab} < 0.$$

(from  $b$  to  $a$ )

$$W_{sys} = -W_{ext} > 0 \rightarrow \text{System is dissipating energy.}$$


(energy in the elec  
form)

charge moving from higher  
Potential to lower potential  $\Rightarrow$  sys dissipates  
energy.

## Energy and Power in Circuits

$$\begin{aligned}
 \text{Power} &= \text{rate of change of } W \quad \text{or} \quad \frac{dW}{dt} \\
 &= \frac{dW}{dQ} \times \frac{dQ}{dt} \\
 &= VI
 \end{aligned}$$


for DC CKts  $P = VI$

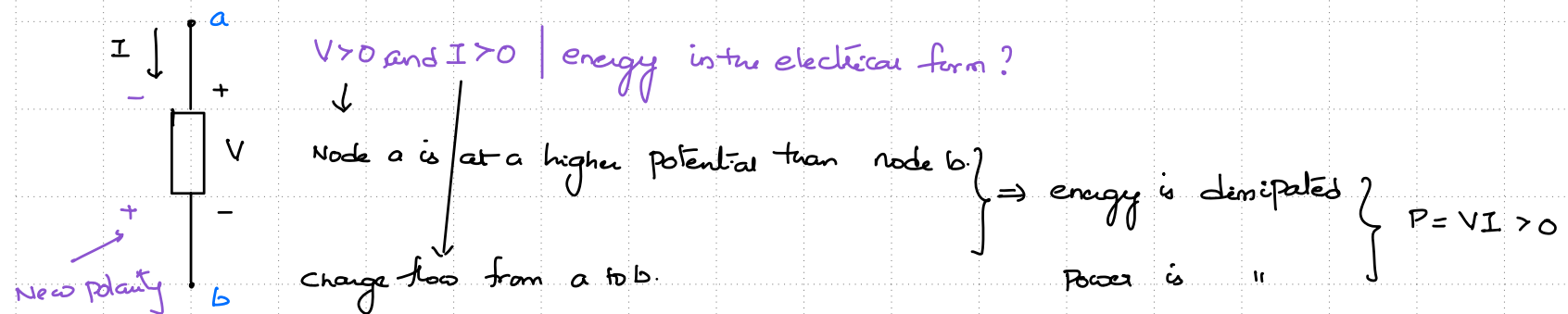

Same scenario with a different polarity

Under new polarity  $V < 0$ ,  $I > 0$ , energy | power is dissipated,  $P < 0$

Example 3:-

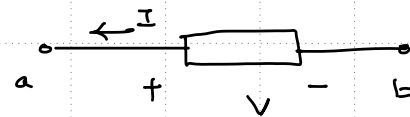

observation:  $V > 0$  and  $I > 0$

$V_a > V_b$

charge flows from b to a.


energy is generated  $\Rightarrow P > 0$ .

## Active and Passive Sign Convention

A systematic way to assign Polarity & reference

Should keep us in inferring whether energy | Power is gen | dissipated from the sign of  $P$ .

Active Sign Convention

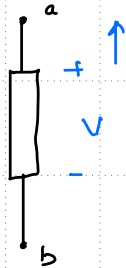

typically used for Sources


→ for a Chosen polarity for Voltage, Current ref is  
Chosen to be out of the +ve Terminal

→ for active Convention

$P > 0 \Rightarrow$  elem is gen energy | power  
↓  
elem is a Source.

$P < 0 \Rightarrow$  elem is dissipating power | energy  
↓  
elem is a Sink | load.

Passive Sign Convention

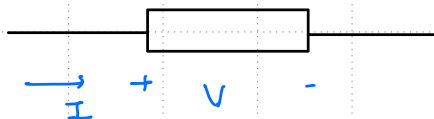


typically used for Sink

ref for current is into the +ve terminal

$P > 0 \Rightarrow$  Sink and  $P < 0 \Rightarrow$  Source.
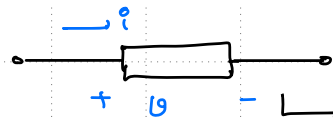
## Circuit Elements from the Point of View of Terminal Characteristics




elements are defined based on voltage across it  
and the current through it



} for circuits

in EM  $\rightarrow$  interested in internal behavior as well.

$v-i$  characteristic

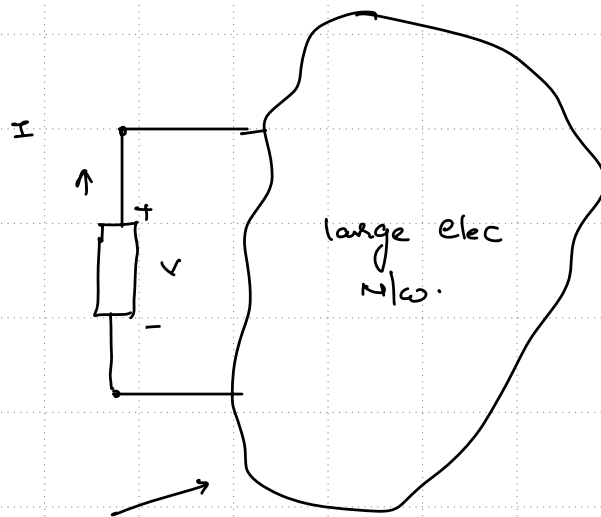


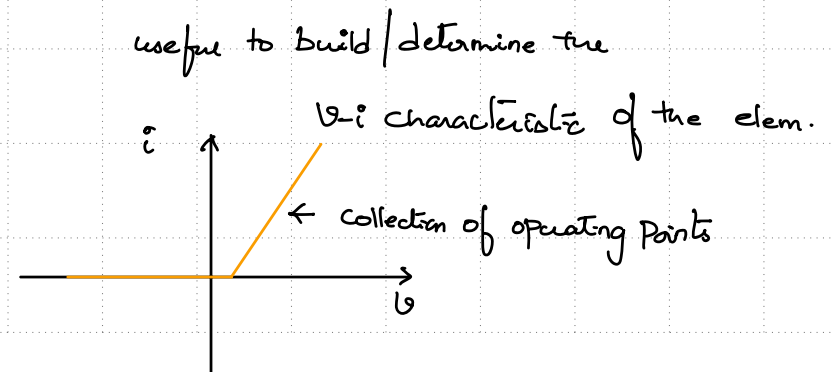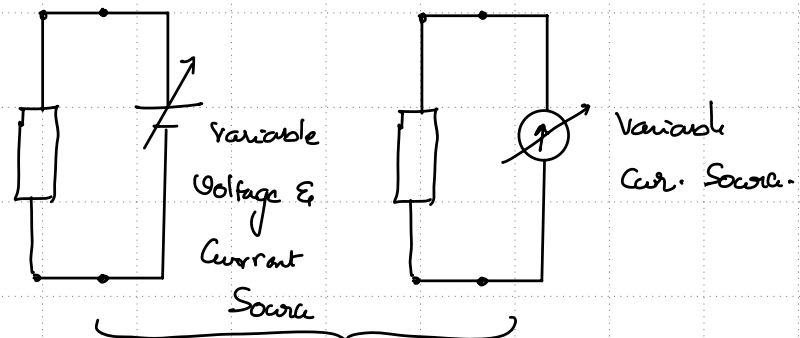$(v, i)$  is one point on the  
 $v-i$  characteristic




## Ideal Voltage Source (DC)


Circuit symbol/representation

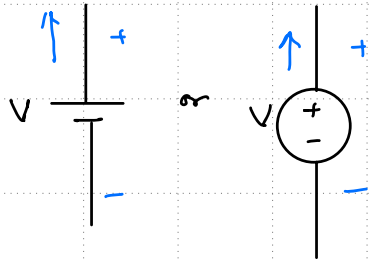

Characterizing Ckt

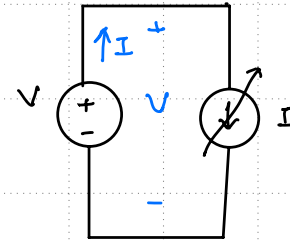

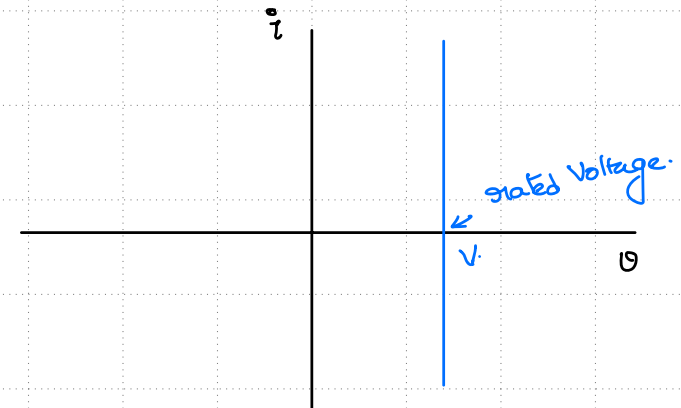→ Voltage across the terminals is independent of the current through/out of the element



operating points lie in Quad I and IV.

$P > 0$

↓

Source

$P < 0$


↓

Sink


(charging mode)

## Ideal Current Source (DC)


Circuit symbol/representation

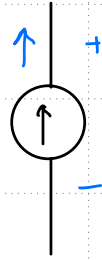

Characterizing Ckt

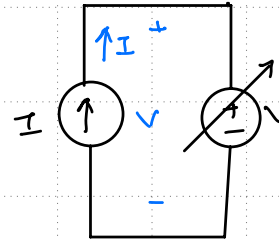

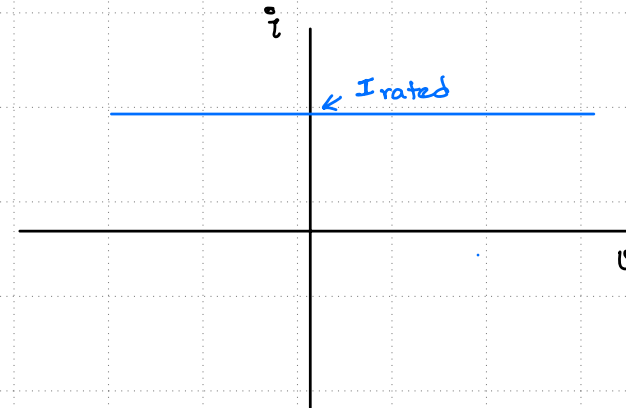→ Current is independent of Vol across the element



operating points lie in Quad I and II

$P > 0$

↓

Source

$P < 0$

↓

Sink