
EE1101: Circuits and Network Analysis

Lecture 23: First-Order Circuits

September 19, 2025

Topics :

1. Solving First-order Differential Equations
2. Examples of First-order Circuits

① for the ckt's covered in this
course both
KCL & KVL are
Valid.

Solving First-order Differential Equations - Integrating Factor Method

given $\frac{dx}{dt} + P(t)x(t) = \phi(t)$

goal: compute $x(t) \rightarrow$ parametric form (constants)

determined by using either
current cont. (inductors)
voltage cont. (capacitors)

When $P(t) \equiv 0$ ($=0 \forall t$): $\frac{dx}{dt} = \phi(t)$

$$\Rightarrow x(t) = \int \phi(t) dt$$

When $P(t) \neq 0$: $\frac{dx}{dt} + P(t)x(t) = \phi(t) \rightarrow \textcircled{1}$

Integrating factor: mul $\textcircled{1}$ on both sides with $u(t)$ s.t. it can be reduced into a form where integrating on both sides can be employed.

$$\textcircled{1} \times u(t): \text{ both } \frac{dx}{dt} + u(t)P(t)x(t) = u(t)\phi(t) \rightarrow \textcircled{2}$$

LHS of $\textcircled{2}$ can be taken to the form $\frac{d}{dt}(u(t)x(t))$ if

$$\frac{du}{dt} = u(t)P(t) \Rightarrow u(t): \frac{du}{u} = P(t) dt$$

$$\Rightarrow \ln(u) = \int P(t) dt \Rightarrow u = e^{\int P(t) dt}$$

Solving First-order Differential Equations - Integrating Factor Method (Contd.)

reg DE when mul $u(t) \Rightarrow \frac{d}{dt} (u(t)x(t)) = u(t)q(t)$

Integrate on both sides

$$u(t)x(t) = \int u(t)q(t) dt + C$$

$$\Rightarrow x(t) = \frac{1}{u(t)} \left[\int u(t)q(t) dt + C \right]$$

Steps involved in solving $\frac{dx}{dt} + P(t)x(t) = q(t) :-$

- ① Determine the integrating factor : $e^{\int P(t) dt}$
- ② Multiply on both sides of DE with IF & simplify $\Rightarrow \frac{d}{dt} (u(t)x(t)) = u(t)q(t)$
- ③ Integrate on both sides to get $x(t)$
- ④ Determine the Constant based on the appropriate Principle.

Examples of First-order Circuits

Set 1:

$$\text{for } t > 0 : -V_S + v_R(t) + v_L(t) = 0$$

$$\Rightarrow L \frac{di}{dt} + Ri = V_S$$

$$\text{for } t < 0 : i_L(t) = 0.$$

Alt:

$$L \frac{di}{dt} + Ri = V_S u(t) \quad \text{and} \quad i(0) = 0.$$

$$\text{In std form: } \frac{di}{dt} + \underbrace{\frac{R}{L}}_{P(t)} i(t) = \underbrace{\frac{V_S}{L}}_{Q(t)} u(t)$$


$$\textcircled{1} \text{ Integrating factor} = e^{\int P(t) dt} = e^{\int R/L dt} = e^{R/L t}$$

$$\begin{aligned} \textcircled{2} \text{ mul on b.s. by IF} &\Rightarrow \frac{d}{dt} (e^{R/L t} i(t)) = e^{R/L t} \frac{V_S}{L} u(t) \\ &\Rightarrow e^{R/L t} i(t) = \frac{V_S}{L} \int e^{R/L t} u(t) dt \\ &= \frac{V_S}{L} e^{R/L t} \cdot \frac{L}{R} + C. \end{aligned}$$

$$e^{R/L t} i(t) = \frac{V_S}{R} e^{R/L t} + C$$

$$\Rightarrow i(t) = \frac{V_S}{R} + C e^{-R/L t}$$
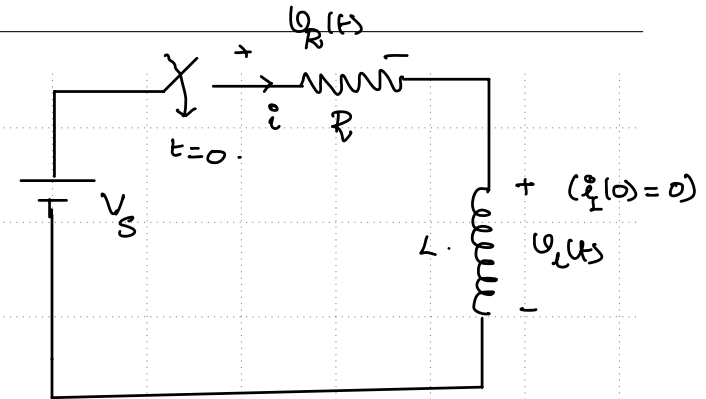
$$C: i(0) = 0 \Rightarrow C = -V_S/R \quad \& \quad i(t) = \frac{V_S}{R} (1 - e^{-R/L t}) \quad (t \geq 0)$$




Examples of First-order Circuits (Contd.)

Response:


$$i(t) = \frac{V_S}{R} (1 - e^{-R/L t}) \quad (t \geq 0)$$

and $i(t) = 0 \quad \forall t < 0$.

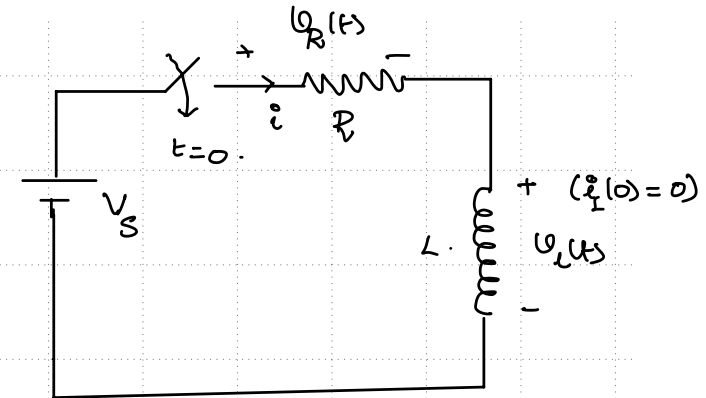

① Check if resp of circuit is finite as $t \rightarrow \infty$.
 if true \rightarrow Steady-state exists.

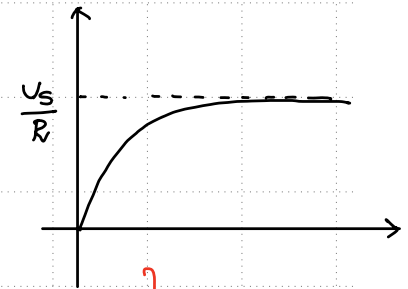When $t \rightarrow \infty$: $i(t) = \frac{V_S}{R}$ (Steady state Current)



resp of the ckt till it reaches steady state \leftarrow Transient Part
 \downarrow To characterize

time-constant \leftarrow In addition

\downarrow
 $(\tau = L/R)$

- a) rise time
- b) settling time
- c) Peak overshoot.

more on this
in next lecture