

---

# EE1101: Circuits and Network Analysis

## Lecture 36: Examples of Two-Port Networks

~~October 28, 2025~~

October 31, 2025

---

### Topics :

1. Examples of Two-Port Networks
-

# Example 1: Pi Network (Y-Parameters)

$$\begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} \vec{y}_{11} & \vec{y}_{12} \\ \vec{y}_{21} & \vec{y}_{22} \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}$$

$$\vec{y}_{11} = \left. \frac{\vec{I}_1}{\vec{V}_1} \right|_{\vec{V}_2=0}$$

$$\vec{y}_{21} = \left. \frac{\vec{I}_2}{\vec{V}_1} \right|_{\vec{V}_2=0}$$

$$\vec{y}_{22} = \left. \frac{\vec{I}_2}{\vec{V}_2} \right|_{\vec{V}_1=0}$$



$$\vec{y}_{12} = \left. \frac{\vec{I}_1}{\vec{V}_2} \right|_{\vec{V}_1=0}$$

Solving a circuit  
column 2-2'

Shorted

Solving a circuit  
column 1-1'

Shorted

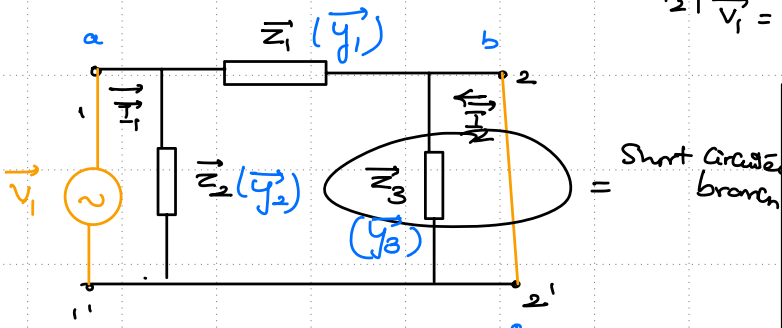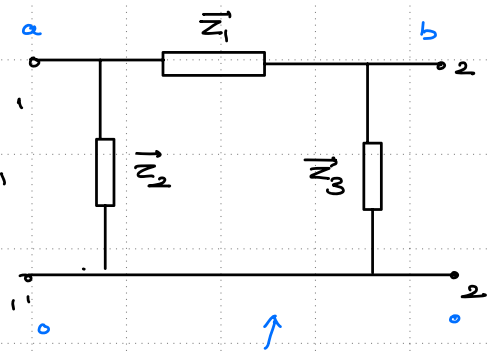


$$\vec{I}_1 = \frac{\vec{V}_1}{(\vec{Z}_1 \parallel \vec{Z}_2)} = \frac{\vec{V}_1}{\vec{Z}_1 \vec{Z}_2} (\vec{Z}_1 + \vec{Z}_2)$$

$$= \vec{V}_1 (\vec{y}_1 + \vec{y}_2)$$

$$\vec{I}_2 = -ve \text{ of } \vec{I} \text{ through } \vec{Z}_1$$
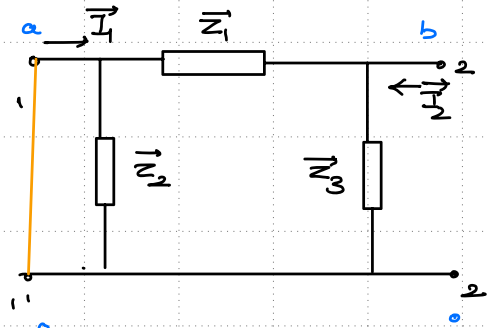
$$= - \frac{\vec{V}_1}{\vec{Z}_1} = -\vec{y}_1 \vec{V}_1$$




$$\vec{I}_1 = -\vec{y}_1 \vec{V}_2 \text{ (or)} - \frac{\vec{V}_2}{\vec{Z}_1}$$

$$\vec{I}_2 = \frac{\vec{V}_2}{\vec{Z}_3 \parallel \vec{Z}_1} \text{ (or)} \vec{V}_2 (\vec{y}_3 + \vec{y}_1)$$


$$\begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} \vec{y}_1 + \vec{y}_2 & -\vec{y}_1 \\ -\vec{y}_1 & \vec{y}_1 + \vec{y}_3 \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}$$

## Example 1: Pi Network (z-Parameters)

$$\begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} \vec{Z}_{11} & \vec{Z}_{12} \\ \vec{Z}_{21} & \vec{Z}_{22} \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} \quad \left. \begin{array}{l} \vec{Z}_{11} = \left. \vec{V}_1 \right|_{\vec{I}_2=0} \\ \vec{Z}_{21} = \left. \vec{V}_2 \right|_{\vec{I}_2=0} \end{array} \right\} \begin{array}{l} \text{Solving a CKT} \\ \text{with } 2-2' \text{ open} \end{array}$$

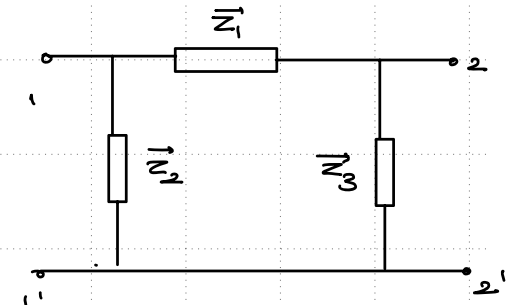

$$\left. \begin{array}{l} \vec{Z}_{12} = \left. \vec{V}_1 \right|_{\vec{I}_1=0} \\ \vec{Z}_{22} = \left. \vec{V}_2 \right|_{\vec{I}_1=0} \end{array} \right\} \begin{array}{l} \text{Solving a CKT} \\ \text{with } 1-1' \text{ open.} \end{array}$$

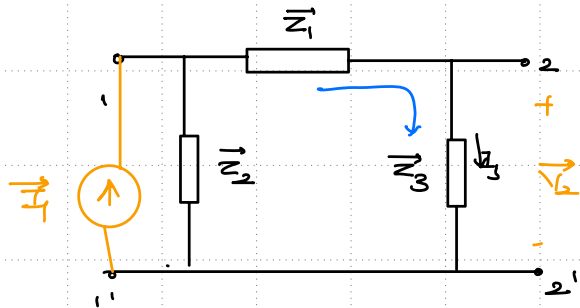


$$\vec{V}_1 = \left[ (\vec{Z}_1 + \vec{Z}_3) \parallel \vec{Z}_2 \right] \vec{I}_1$$

$$\Rightarrow \vec{Z}_{11} = \vec{Z}_2 \parallel (\vec{Z}_1 + \vec{Z}_3)$$

$$\vec{V}_2 = \vec{Z}_3 (\vec{I}_3) = \vec{Z}_3 \left( \frac{\vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2 + \vec{Z}_3} \right) \vec{I}_1$$
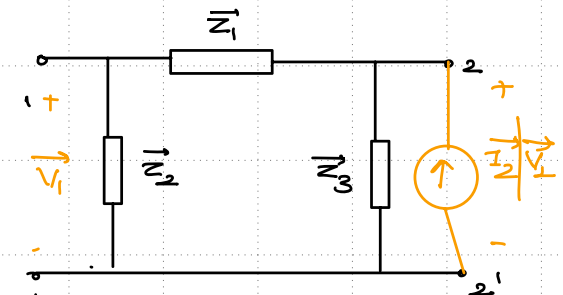
$$\Rightarrow \vec{Z}_{21} = \frac{\vec{Z}_2 \vec{Z}_3}{\vec{Z}_1 + \vec{Z}_2 + \vec{Z}_3}$$



$$\vec{V}_2 = \left[ \vec{Z}_3 \parallel (\vec{Z}_1 + \vec{Z}_2) \right] \vec{I}_2$$

$$\Rightarrow \vec{Z}_{22} = \vec{Z}_3 \parallel (\vec{Z}_1 + \vec{Z}_2)$$


$$\vec{V}_1 = \frac{\vec{Z}_3 \vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2 + \vec{Z}_3} \vec{I}_2$$

$$\vec{Z}_{12} = \frac{\vec{Z}_3 \vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2 + \vec{Z}_3}$$

## Example 2: T Network (z-parameters)


$$\begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} \vec{Z}_{11} & \vec{Z}_{12} \\ \vec{Z}_{21} & \vec{Z}_{22} \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} \quad \left. \begin{array}{l} \vec{Z}_{11} = \left. \frac{\vec{V}_1}{\vec{I}_1} \right|_{\vec{I}_2=0} \\ \vec{Z}_{21} = \left. \frac{\vec{V}_2}{\vec{I}_1} \right|_{\vec{I}_2=0} \end{array} \right\}$$

Solving a CKT  
withn 2-2' open

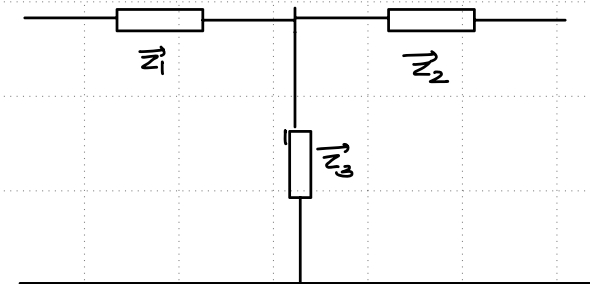


$$\left. \begin{array}{l} \vec{Z}_{12} = \left. \frac{\vec{V}_1}{\vec{I}_2} \right|_{\vec{I}_1=0} \\ \vec{Z}_{22} = \left. \frac{\vec{V}_2}{\vec{I}_2} \right|_{\vec{I}_1=0} \end{array} \right\}$$

Solving a CKT  
withn 1-1' open.

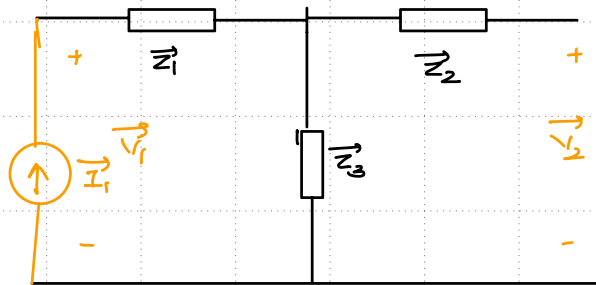

$$\vec{V}_1 = (\vec{Z}_1 + \vec{Z}_3) \vec{I}_1 \Rightarrow \vec{Z}_{11} = \vec{Z}_1 + \vec{Z}_3$$

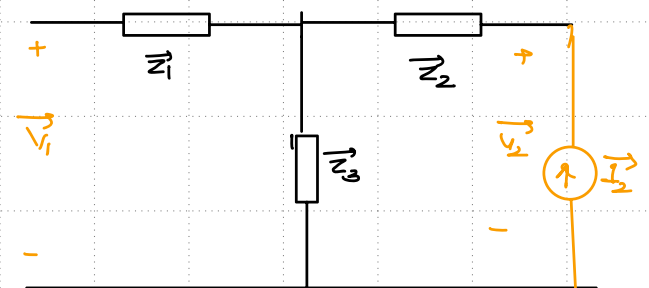
$$\vec{V}_2 = \vec{Z}_3 \vec{I}_1 \Rightarrow \vec{Z}_{21} = \vec{Z}_3$$



$$\vec{V}_1 = \vec{Z}_3 \vec{I}_2 \Rightarrow \vec{Z}_{12} = \vec{Z}_3$$


$$\vec{V}_2 = (\vec{Z}_2 + \vec{Z}_3) \vec{I}_2 \Rightarrow \vec{Z}_{22} = \vec{Z}_2 + \vec{Z}_3$$

$$\begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} \vec{Z}_1 + \vec{Z}_3 & \vec{Z}_3 \\ \vec{Z}_3 & \vec{Z}_2 + \vec{Z}_3 \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix}$$

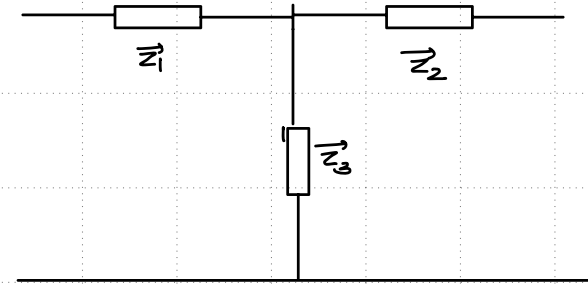**Example 2: T Network** ( *$\gamma$ -parameters*)
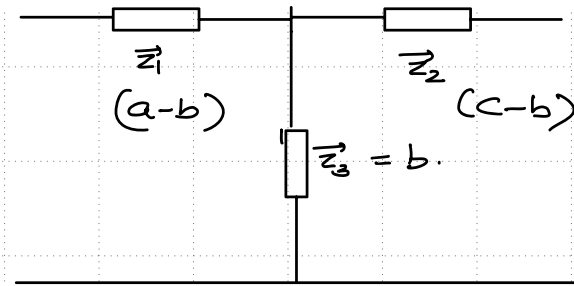
### Example 3: Equivalent Circuit for a Given Z-Parameter Matrix

given  $\vec{Z} = \begin{bmatrix} a & b \\ b & c \end{bmatrix} \Rightarrow$



$$\vec{Z}_3 = b$$

$$\vec{Z}_1 + \vec{Z}_3 = a$$

$$\vec{Z}_1 = a - b$$

given  $\vec{h} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \Rightarrow \begin{bmatrix} \vec{V}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} \vec{h}_{11} & \vec{h}_{12} \\ \vec{h}_{21} & \vec{h}_{22} \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{V}_2 \end{bmatrix}$

