
EE1101: Circuits and Network Analysis


Lecture 05: DC Circuit Analysis

August 5, 2025

Topics :

1. Voltage and Current Divider Circuits
 2. Port and its characteristics
-

Voltage and Current Divider Circuits

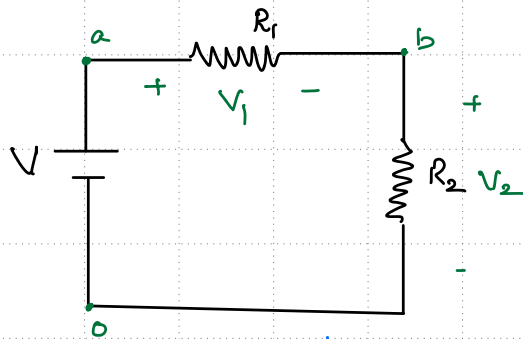



Voltage divider → what happens when $R_2 \rightarrow \infty$ (open circuit)

$$V_1 = \frac{R_1}{R_1 + R_2} V.$$

$$\text{and } V_2 = \frac{R_2}{R_1 + R_2} V.$$

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}.$$

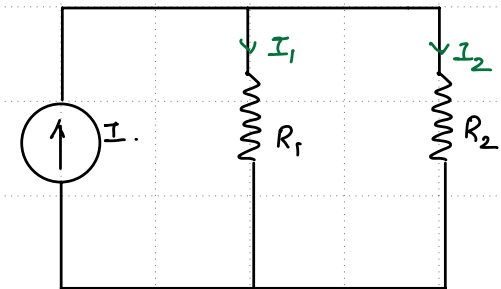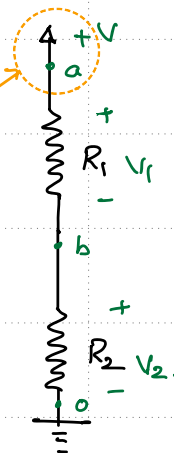alternate rep:
alternate way
of rep the
DC Source.



Current divider

$$I_1 = \frac{R_2}{R_1 + R_2} I \quad I_2 = \frac{R_1}{R_1 + R_2} I.$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

In a Current divider circuit

what happens if $R_2 \rightarrow 0$ (short circuit)

$$I_2 \rightarrow I \text{ and } I_1 \rightarrow 0.$$

$$V \rightarrow 0.$$

what happens when $R_2 \rightarrow \infty$ (open circuit)


$$I_1 \rightarrow I, \quad I_2 \rightarrow 0$$

$$V \rightarrow IR_1$$

Port and its Characteristics ($v-i$ characteristic)

Any pair of terminals in a n/w. : rep (node 1 - node 2) or $1-1'$ or $2-2'$
 ↓
 one of these two scenarios


Aim: to derive its characteristics such that when you interface the port to an external n/w, one can easily study the behavior of the sub ckt behind the port.

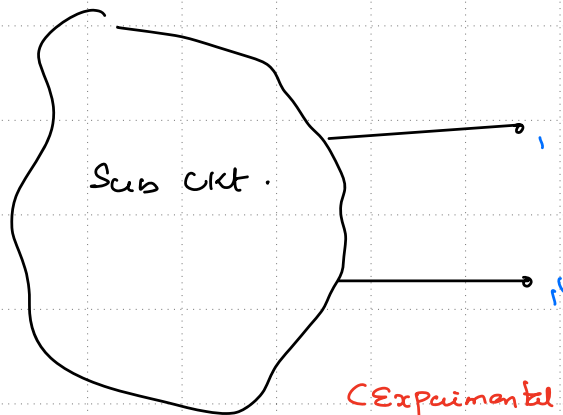

Scenario 1. (Experimental means when sub ckt is not known)


goal:- To derive the $v-i$ characteristic of a sub ckt (refer to as characteristic of a port)

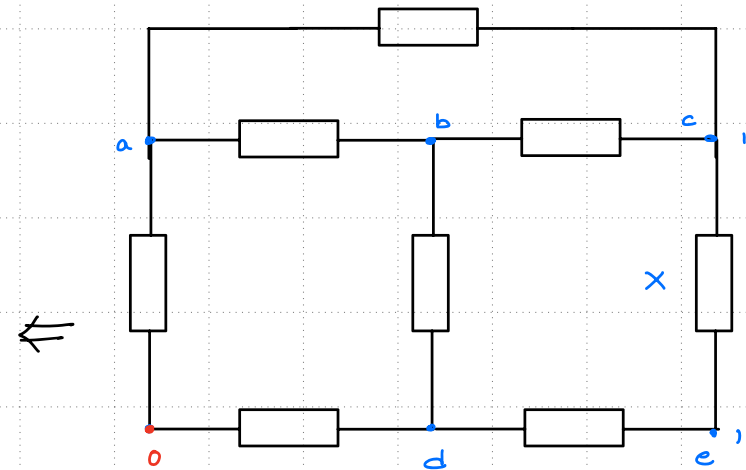claim:- using the $v-i$ characteristic of a port and the " " of the elem connected across the port } → one can find the operating point.



if an elem is connected b/w the terminals of a port → remove it and consider the rest of the ckt as a sub ckt

Port and its Characteristics (V - i characteristics)

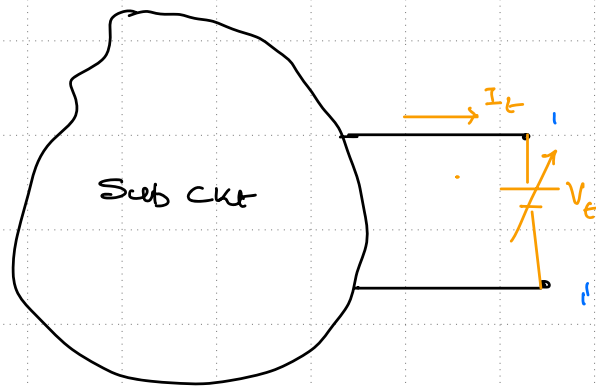



Scenario 1

(when the components/models
of the sub circuit is not known)



Terminal characteristics of port can
be obtained experimentally

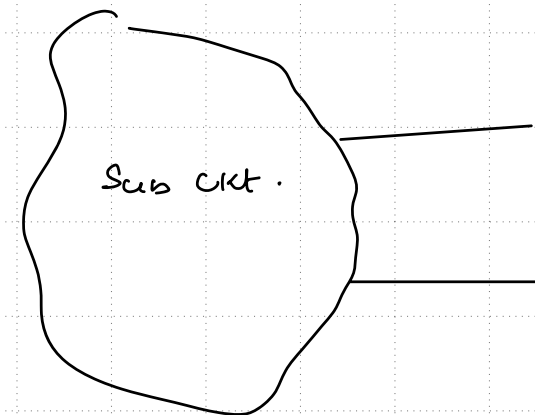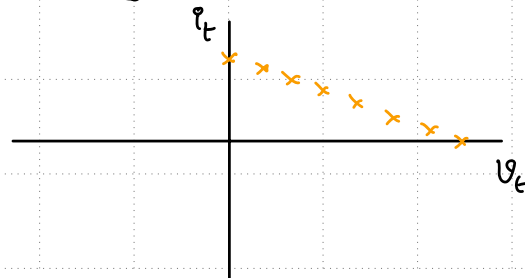For example, Connect a Variable Voltage Source
and plot the (V_t, i_t) for various values of V_t



if the sub ckt is known

We use analysis techniques to
Plot the terminal characteristics

for linear sub circuits

- a) open circuit voltage (V_{oc})
- b) short circuit current (I_{sc})
- c) Equivalent Resistance (R_{eq})

can give the
 V - i characteristics
of a port.


(i) Null the other sources in the ckt

(ii) Connect a V/I source at port

(iii) Measure I/V

(iv) $R_{eq} = V/I$

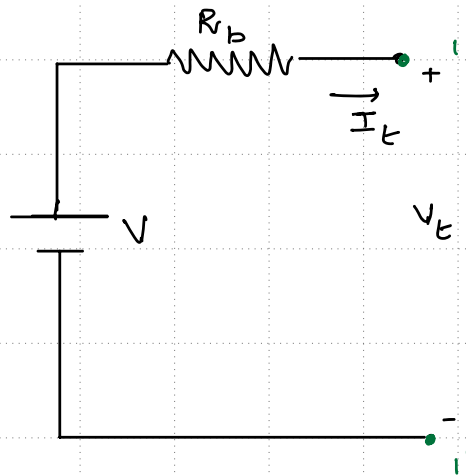Example 01 - Terminal characteristics of a practical voltage source



Open ckt voltage : $V_t = V$ and $I_t = 0$


Short ckt current : $I_t = V/R_b$ and $V_t = 0$

Eq. resistance

Short the V source } Nulling the
open the I source } other
source.

$$R_{eq} = \frac{V_t}{I_t} = -R_b.$$

↑
bec of sign convention.

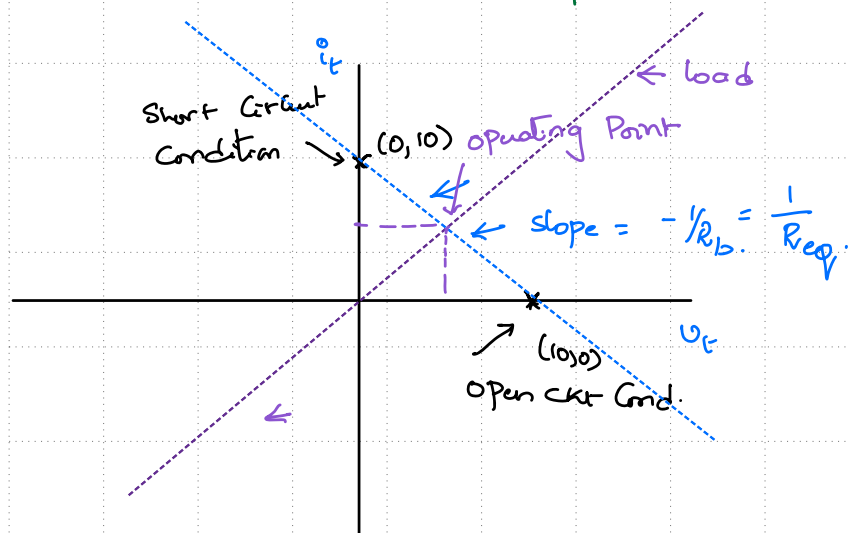

Example: $V = 10V$ $R_b = 1\Omega$. line through $(0, 10)$ and $(10, 0)$

when we connect a load of 1Ω (R_L) $V_t = 5V$.

Example 02

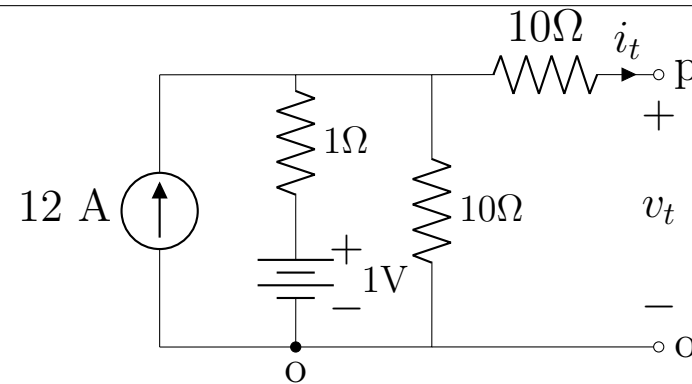


Fig. 1: Circuit for Example 02

Open ckt vol: $130/11$ V. ✓

sc Current: $13/12$ A

Eq. Resistance: $120/11$ Ω.