

---

# EE1101: Circuits and Network Analysis

## Lecture 29: Second-Order Circuits

October 13, 2025

---

### Topics :

1. Method of Undetermined Coefficients
  2. Sinusoidal Forcing Functions
-

## Method of Undetermined Coefficients - Second-Order Circuits

$$DE: \frac{d^2 x}{dt^2} + 2\xi\omega_n \frac{dx}{dt} + \omega_n^2 x = f(t) \rightarrow A \cos(\omega t + \phi)$$

Instead solve  $\frac{d^2 \hat{x}}{dt^2} + 2\xi\omega_n \frac{d\hat{x}}{dt} + \omega_n^2 \hat{x} = A e^{j(\omega t + \phi)} \rightarrow (2)$

and  $x = \text{Re}\{\hat{x}\}$

general sol:  $\hat{x}(t) = \underbrace{\hat{x}_c(t)}_{\text{Complementary or homogeneous sol}} + \hat{x}_p(t) \rightarrow \text{guess.}$

guess for  $\hat{x}_p(t)$ :  $\hat{x}_p(t) = \underbrace{x_p e^{j(\omega t + \phi - \phi_p)}}_{\text{that need to be computed}}$

How to compute  $x_p$  and  $\phi_p$ :

$$\left. \begin{aligned} \frac{d\hat{x}_p}{dt} &= j\omega \hat{x}_p(t) \\ \frac{d^2 \hat{x}_p}{dt^2} &= -\omega^2 \hat{x}_p(t) \end{aligned} \right\} \text{ Plug in } \hat{x}_p, \frac{d\hat{x}_p}{dt}, \frac{d^2 \hat{x}_p}{dt^2} \text{ into (2)}$$

$$(-\omega^2 + j2\xi\omega_n\omega + \omega_n^2) \hat{x}_p = A e^{j(\omega t + \phi)}$$

$$[(\omega_n^2 - \omega^2) + j(2\xi\omega_n\omega)] \hat{x}_p = A e^{j(\omega t + \phi)}$$

$$B e^{j\phi_B}$$

$$B = \sqrt{(\omega_n^2 - \omega^2)^2 + 4\xi^2\omega_n^2\omega^2} \quad \phi_B = \tan^{-1}\left(\frac{2\xi\omega_n\omega}{\omega_n^2 - \omega^2}\right)$$

$$DE: \frac{d^2 x}{dt^2} + 2\xi\omega_n \frac{dx}{dt} + \omega_n^2 x = K \downarrow f(t)$$

gen:  $x = x_c(t) + x_p(t)$

guess for  $x_p$ :  $x_p = C$   
 need to be computed

## Sinusoidal Forcing Functions

How to compute  $\mathcal{X}_p$  and  $\phi_p$ :

$$\left. \begin{aligned} \frac{d\hat{x}_p}{dt} &= j\omega \hat{x}_p(t) \\ \frac{d^2\hat{x}_p}{dt^2} &= -\omega^2 \hat{x}_p(t) \end{aligned} \right\} \text{ Plug in } \hat{x}_p, \frac{d\hat{x}_p}{dt}, \frac{d^2\hat{x}_p}{dt^2} \text{ into (2)}$$

$$(-\omega^2 + j2\xi\omega_n\omega + \omega_n^2) \hat{x}_p = A e^{j(\omega t + \phi)}$$

$$\left[ (\omega_n^2 - \omega^2) + j(2\xi\omega_n\omega) \right] \hat{x}_p = A e^{j(\omega t + \phi)}$$

$$B e^{j\phi_B}$$

$$B = \sqrt{(\omega_n^2 - \omega^2)^2 + 4\xi^2\omega_n^2\omega^2} \quad \phi_B = \tan^{-1}\left(\frac{2\xi\omega_n\omega}{\omega_n^2 - \omega^2}\right)$$

$$\hat{x}_p = \frac{A}{B} e^{j(\omega t + \phi - \phi_B)} \rightarrow \textcircled{I}$$

When  $\textcircled{I}$  &  $\hat{x}_p = \mathcal{X} e^{j(\omega t + \phi - \theta)}$  are compared

$$\mathcal{X} = \frac{A}{B} = \frac{A}{\sqrt{(\omega_n^2 - \omega^2)^2 + 4\xi^2\omega_n^2\omega^2}}$$

$$\theta = \phi_B = \tan^{-1}\left(\frac{2\xi\omega_n\omega}{\omega_n^2 - \omega^2}\right)$$

Complete sol for sinusoidal  $f(t)$  : ① Compute  $\hat{x}_c(t)$  (don't use init cond).

② Compute  $\hat{x}_p(t)$

③ real part of sol  $\hat{x}(t) = \hat{x}_c(t) + \hat{x}_p(t)$


## Example

$$R = 30\Omega, \quad L = 10\text{H}, \quad C = 0.1\text{F}$$

$$\omega = 100\pi$$

$$\phi = \pi/4$$

$$V = 10$$

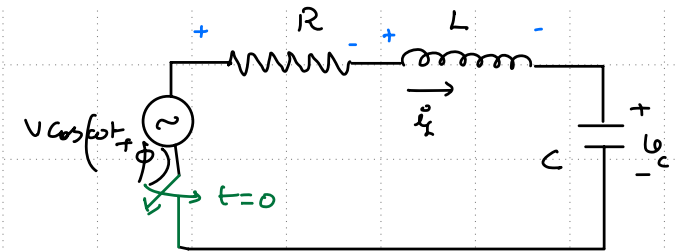

$$i_L(0) = 10\text{A}$$

$$v_C(0) = 0\text{V}$$

Step 1: Setup the DE and Init cond

$$R\dot{i}_L + L\frac{d\dot{i}_L}{dt} + v_C = v_s \rightarrow \textcircled{1}$$

diff ① w.r.t  $t$ ,  $\frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L = \frac{1}{L} \frac{dv_s}{dt}$

$$\dot{i}_L(0) = 10$$

at  $t=0$ ,  $v_s(0) = R\dot{i}_L(0) + L\left.\frac{d\dot{i}_L}{dt}\right|_{t=0} + \underbrace{v_C(0)}_0 = R\dot{i}_L(0) + L\left.\frac{d\dot{i}_L}{dt}\right|_{t=0} + 0$

$$\left.\frac{d\dot{i}_L}{dt}\right|_{t=0} = \frac{v_s(0) - R\dot{i}_L(0)}{L}$$

$$= -\underline{\underline{29.293}}$$

Step 2: Compute complementary sol

$$i_L(t) = c_1 e^{-0.4t} + c_2 e^{-2.6t}$$

## Example

$$\begin{aligned}
 \frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L &= \frac{1}{L} \frac{dV_S}{dt} = \frac{1}{L} \frac{d}{dt} (V \cos(\omega t + \phi)) \\
 &= -\frac{V\omega}{L} \sin(\omega t + \phi) \\
 &= \frac{V\omega}{L} \cos(\omega t + \underbrace{\phi + \frac{\pi}{2}}_{\phi'})
 \end{aligned}$$

Step 3: Compute  $\hat{x}_p(t)$ : response to  $Ae^{j(\omega t + \phi')}$

$$= \eta e^{j(\omega t + \phi' - \theta)}$$

$$\eta = \frac{A}{B}, \quad \theta = \phi_B$$

$$\text{where } B = \sqrt{(\omega_0^2 - \omega^2)^2 + (2\xi\omega_0\omega)^2}, \quad \phi_B = \tan^{-1} \left( \frac{2\xi\omega_0\omega}{\omega_0^2 - \omega^2} \right)$$

Step 4: Real part of sol:  $x(t) = \text{Re} \{ \hat{x}_c(t) + \hat{x}_p(t) \}$

Step 5: Determine the constants/parameters in the solution using initial conditions

## Method of Undetermined Coefficients - <sup>Sinusoidal</sup> ~~Constant~~ Forcing Function

$$\begin{aligned}
 x &= \operatorname{Re} \{ \hat{x}_c(t) + \hat{x}_p(t) \} \\
 &= \underbrace{\operatorname{Re} \{ \hat{x}_c(t) \}}_{\substack{\rightarrow 0 \\ \text{as } t \rightarrow \infty}} + \operatorname{Re} \{ \hat{x}_p(t) \}
 \end{aligned}$$

$\hat{x}_c(t) \rightarrow 0$  except when  $\varepsilon = 0$

$$\begin{aligned}
 \text{as } t \rightarrow \infty; \quad x(t) &= \operatorname{Re} \{ \hat{x}_p(t) \} = \operatorname{Re} \{ \sigma_p e^{j(\omega t + \phi - \theta_p)} \} \\
 &= \sigma_p \cos(\omega t + \phi - \theta_p)
 \end{aligned}$$

In steady state

$$\begin{aligned}
 v_s(t) &= V \cos(\omega t + \phi) \rightarrow \frac{V}{\sqrt{2}} \angle \phi \\
 i_L(t) &= \sigma_p \cos(\omega t + \phi - \theta_p) \rightarrow \frac{\sigma_p}{\sqrt{2}} \angle \phi - \theta_p
 \end{aligned}
 \left. \vphantom{\begin{aligned} v_s(t) \\ i_L(t) \end{aligned}} \right\} \begin{array}{l} \text{by constructing the} \\ \text{phasor domain Eq} \\ \text{of the ckt.} \end{array}$$