

.

EE1101: Circuits and Network Analysis

Lecture 08: DC Circuit Analysis

August 12, 2025

Topics :

1. Mesh Analysis
2. Concept of Supermesh

Mesh Analysis - Overview of the approach

goal of any ckt analysis tool:- To Compute/solve the Voltages & Currents associated with various elem in the circuit.

In Mesh Analysis: \rightarrow Compute the currents associated with the loops in the ckt.

loop \rightarrow closed path.

\downarrow
Not always the current through an element.

Basic idea: Apply KVL in loops/mesh associated with the ckt.

\rightarrow standard form: Typically in terms of Voltage / Potential Difference.

\downarrow
Try to express in terms of currents, wherever possible.

Claim:- if all loop currents are known

\rightarrow enough to compute (V, I, P) associated with every ckt element.

Steps:- ① identify the no. of loops & indicate the unknown loop currents (m)

② Set up m LI eqns by using KVL.

Mesh Analysis - Overview of the approach

Can an element be a part of

a) single loop : Yes

for choice ①, 3 such elements.

for choice ② NO

b) two loops : Yes


for choice ① : 3 such elements.

for choice ② : 4 such elements

c) more than two loops : Yes

for choice ③ : NO.

d) not a part of any loop:

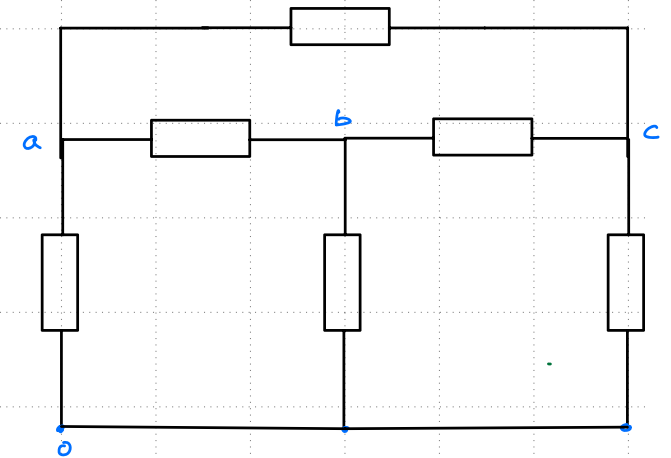

Choice 1. {

- loop 1: $o-a-b-o$: i_1
- loop 2: $a-c-b-a$: i_2
- loop 3: $o-b-c-o$: i_3



Choice 2: {

- loop 1: $o-a-b-o$: i_1
- loop 2: $o-a-c-o$: i_2
- loop 3: $o-b-a-c-o$: i_3

Choice 3: {


- loop 1: $o-a-b-o$:
- loop 2: $o-a-b-c-o$:
- loop 3: $o-a-c-o$:

Mesh Analysis - Overview of the approach

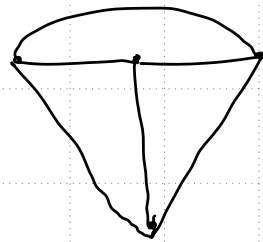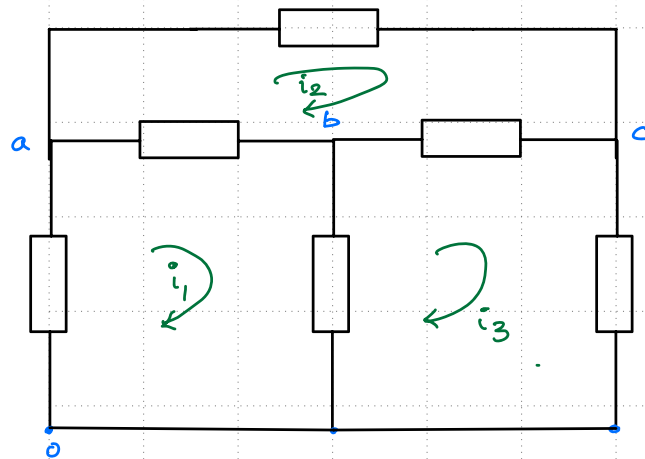

Choice 1. $\begin{cases} \text{loop 1: } 0-a-b-0 : i_1 \\ \text{loop 2: } a-b-c-a : i_2 \\ \text{loop 3: } 0-b-c-0 : i_3 \end{cases}$


$$\left. \begin{aligned} i_{0a} &= i_1 \\ i_{ab} &= i_1 - i_2 \\ i_{bc} &= i_3 - i_2 \\ i_{ac} &= i_2 \\ i_{bo} &= i_1 - i_3 \\ i_{co} &= i_3 \end{aligned} \right\} \begin{array}{l} \text{Currents through} \\ \text{branches that are a part} \\ \text{of at least one loop.} \end{array}$$

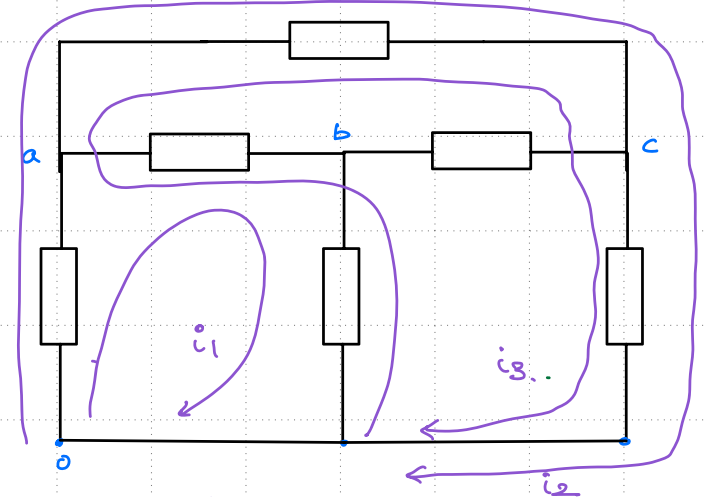

Choice 2: $\begin{cases} \text{loop 1: } 0-a-b-0 : i_1 \\ \text{loop 2: } 0-a-c-0 : i_2 \\ \text{loop 3: } 0-b-a-c-0 : i_3 \end{cases}$

$$\left. \begin{aligned} i_{0a} &= i_1 + i_2 \\ i_{ab} &= i_1 - i_3 \\ i_{bc} &= \text{Not a part of any loop.} \\ i_{ac} &= i_2 + i_3 \\ i_{bo} &= i_1 - i_3 \\ i_{co} &= i_2 + i_3 \end{aligned} \right\} \begin{array}{l} \text{can be computed by applying} \\ \text{KCL at node } c \end{array}$$

Mesh Analysis - Overview of the approach

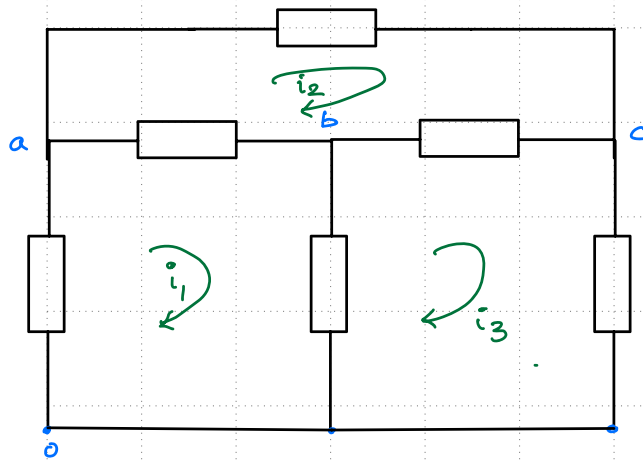

Choice 1. $\left\{ \begin{array}{l} \text{loop 1: } o-a-b-o : i_1 \\ \text{loop 2: } a-b-c-a : i_2 \\ \text{loop 3: } o-b-c-o : i_3 \end{array} \right.$

$$i_{oa} = i_1$$

$$i_{ab} = i_1 - i_2$$

$$i_{bc} = i_3 - i_2$$

$$i_{ac} = i_2$$

$$i_{bo} = i_1 - i_3$$


$$i_{co} = i_3$$

Currents through
branches that are a part
of at least one loop.

Step 1: Mark loops

Step 2: write KVL.

2a)

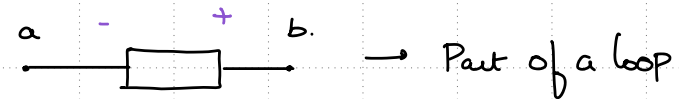

$$\underbrace{\sum V}_{?} \underbrace{-a-b-}_{\sum V = 0}$$

a) if its a Resistor $V_{ab} = R(i_{ab})$

b) if its a voltage source $V_{ab} = \pm V_s$

c) if its a Current source: $V_{ab} = ?$

$$I_{ab} = \sum i_k \quad \left. \vphantom{\sum i_k} \right\} \text{Super mesh.}$$


2b) formal application of KVL:

$$\text{loop 1: } V_{oa} + V_{ab} + V_{bo} = 0$$

$$\text{loop 2: } V_{ac} + V_{cb} + V_{ba} = 0$$

$$\text{loop 3: } V_{ob} + V_{bc} + V_{co} = 0$$

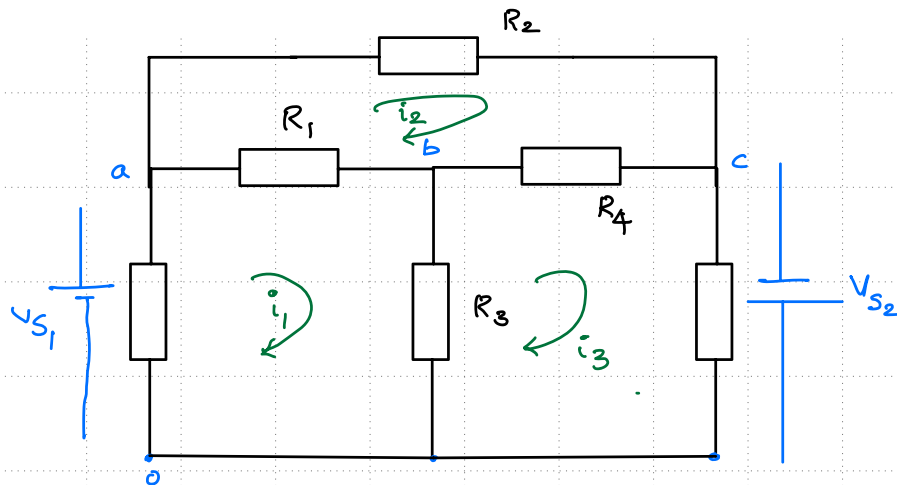Mesh analysis with ^{Voltage}current sources and resistors



$$\text{loop 1:- } -V_{S1} + R_1(i_1 - i_2) + R_3(i_1 - i_3) = 0$$

$$(R_1 + R_3)i_1 - R_1 i_2 - R_3 i_3 = V_{S1}$$

$$\text{loop 2:- } R_2 i_2 + R_4(i_2 - i_3) + R_1(i_2 - i_1) = 0$$

$$(R_2 + R_1 + R_4)i_2 - R_4 i_3 - R_1 i_1 = 0$$

$$\text{loop 3:- } R_3(i_3 - i_1) + R_4(i_3 - i_2) - V_{S2} = 0$$

$$(R_3 + R_4)i_3 - R_3 i_1 - R_4 i_2 = V_{S2}$$

$$\underbrace{\begin{bmatrix} R_1 + R_3 & -R_1 & -R_3 \\ -R_1 & R_2 + R_1 + R_4 & -R_4 \\ -R_3 & -R_4 & R_3 + R_4 \end{bmatrix}}_{[Z]} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} V_{S1} \\ 0 \\ V_{S2} \end{bmatrix}$$

$$[Z][I] = [V]$$