

.

EE1101: Circuits and Network Analysis

Lecture 07: Node Analysis

August 11, 2025

Topics :

1. Node Analysis - Circuits with Voltage Sources
-

Example - Use of Matrices in Node Analysis


Recall:- by applying KCL at nodes of unknown potential

$$\sum I_{\text{leaving}} = 0$$

$$\sum_{j \in i} I_{ij} = 0$$

Current from node 'i' to node 'j'

all nodes connected to node 'i'

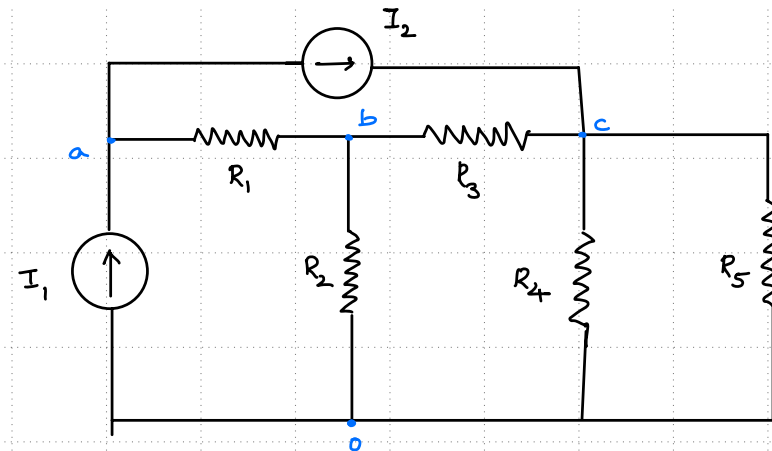

for the Example :-

$$\text{Node a: } \frac{1}{R_1} V_a - \frac{1}{R_1} V_b = I_1 - I_2 \rightarrow \textcircled{1}$$

$$\text{Node b: } -\frac{1}{R_1} V_a + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_b - \frac{1}{R_3} V_c = 0 \rightarrow \textcircled{2}$$

$$\text{Node c: } -\frac{1}{R_3} V_b + \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) V_c = I_2 \rightarrow \textcircled{3}$$


Example - Use of Matrices in Node Analysis

Develop an Equation of the form

$$[G][V] = [I] \rightarrow I_{eq} \text{ (injected at each node)}$$

Vector of unknown node voltages.

Conductance matrix

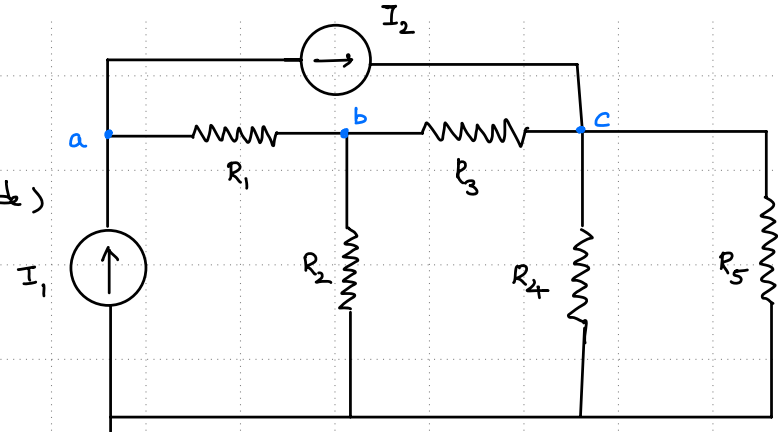

for the system of Eqn's to be consistent, we first


need to define $[V] = [V_a, V_b, V_c]^T$

for Example:

$$\begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} & 0 \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ 0 & -\frac{1}{R_3} & \sum_{i=3}^5 \frac{1}{R_i} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ 0 \\ I_2 \end{bmatrix}$$

Circuits with Voltage Sources - Between Node and Reference Node

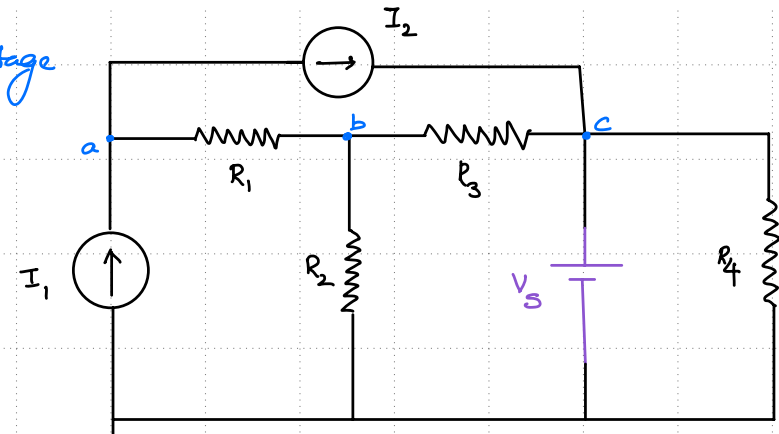that particular node voltage
is known
↓
apply KCL at nodes of
unknown potential.



for example: $V_c = V_s$

Node a :- $\frac{1}{R_1} V_a - \frac{1}{R_1} V_b = I_1 - I_2.$

Node b: $-\frac{1}{R_1} V_a + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) V_b = \frac{V_s}{R_3}$ Σφ. Current.

In matrix form

$$[V] = [V_a, V_b]$$


$$\begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ \frac{V_s}{R_3} \end{bmatrix}$$

Circuits with Voltage Sources - Between two non-reference Nodes

Approach 1:-

Introduce a new variable (i.e., Current through the Voltage Source)

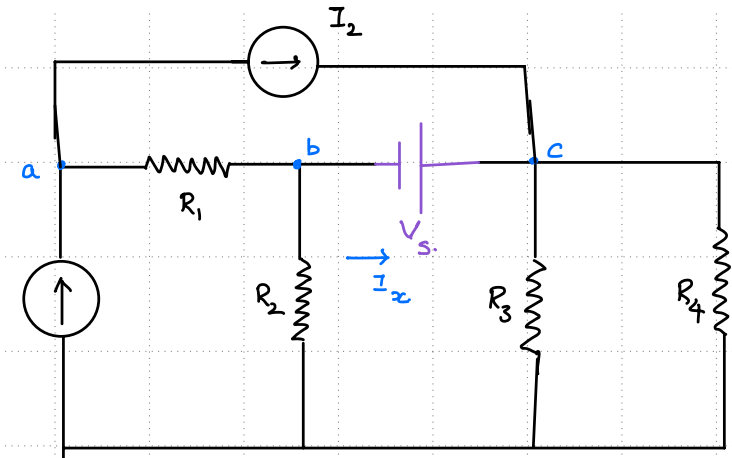↓
introduces new set of unknowns
↓
as many no. of equations from the P.D from the two nodes



3 unknown node voltages (V_a, V_b, V_c) & unknown Current I_x .

3 Eqn's by applying KCL

$$V_c - V_b = V_s$$

at Node a: $\frac{1}{R_1} V_a - \frac{1}{R_1} V_b = I_1 - I_2 \rightarrow \textcircled{1}$

at Node b: $-\frac{1}{R_1} V_a + \left(\frac{1}{R_2} + \frac{1}{R_1}\right) V_b + I_x = 0 \rightarrow \textcircled{2}$

at Node c: $\left(\frac{1}{R_3} + \frac{1}{R_4}\right) V_c - I_x = I_2 \rightarrow \textcircled{3}$

$$V_c - V_b = V_s \rightarrow \textcircled{4}$$

Solve $\textcircled{1} - \textcircled{4}$

to find V_a, V_b, V_c, I_2

(or)

Solve $\textcircled{1}, \textcircled{5} \& \textcircled{4}$


to find V_a, V_b, V_c .

from $\textcircled{2} \& \textcircled{3} \Rightarrow -\frac{1}{R_1} V_a + \left(\frac{1}{R_2} + \frac{1}{R_1}\right) V_b + \left(\frac{1}{R_3} + \frac{1}{R_4}\right) V_c = I_2 \rightarrow \textcircled{5}$

Circuits with Voltage Sources - Between two non-reference Nodes

focus on $\Sigma \phi$ (5)

$$\underbrace{-\frac{1}{R_1} V_a + \left(\frac{1}{R_2} + \frac{1}{R_1}\right) V_b}_{\text{KCL at Node b}} + \underbrace{\left(\frac{1}{R_3} + \frac{1}{R_4}\right) V_c}_{\text{KCL at Node c}} = \underline{I_2} \rightarrow (5)$$

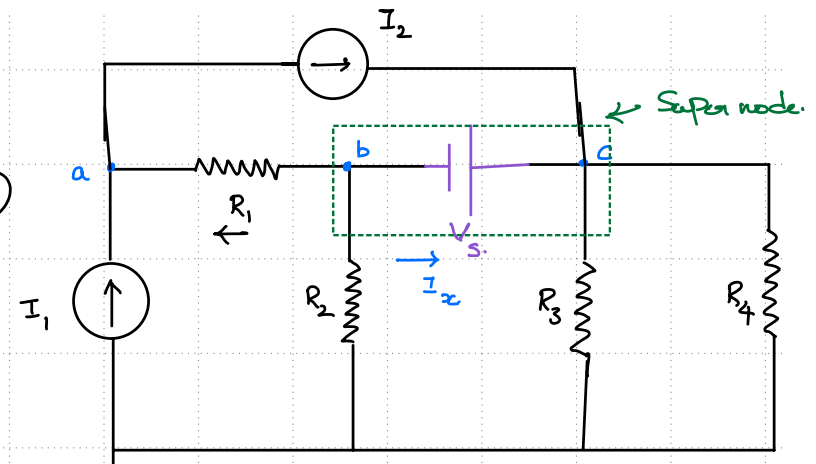Approach 2:- def Super node

Apply KCL at Super node + PD Eqn

2 set of Eqn's for the 2 unknown node potentials.

for the example:

at Supernode bc :-

$$\frac{V_b - V_a}{R_1} + \frac{V_b}{R_2} + \frac{V_c}{R_3} + \frac{V_c}{R_4} = I_2.$$