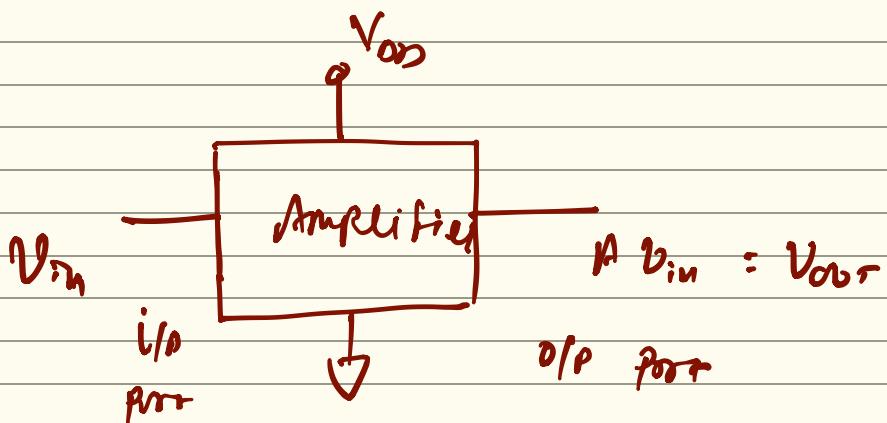


DATE: 19 Jan

## Analog Elec


=>



=> Non linear Active devices ->


Transistors.

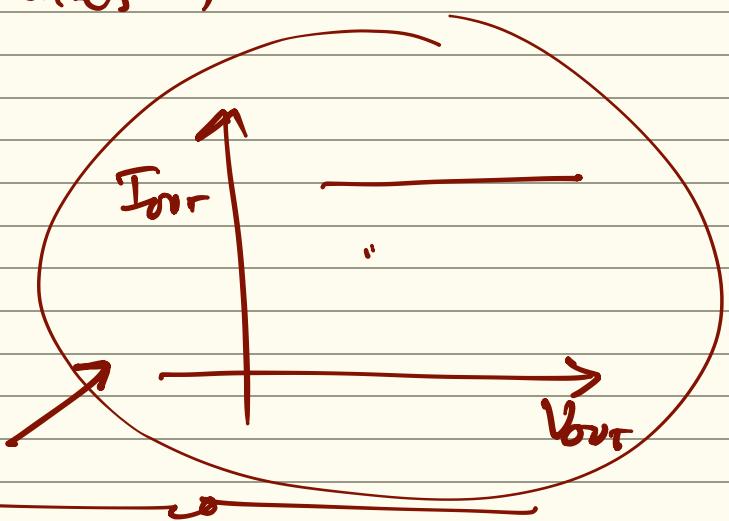BJT - Active  
MOS - Sat<sup>n</sup>. { -



=> i/p  $\rightarrow$  Amp (i/p)


→ Biasing → operating points.

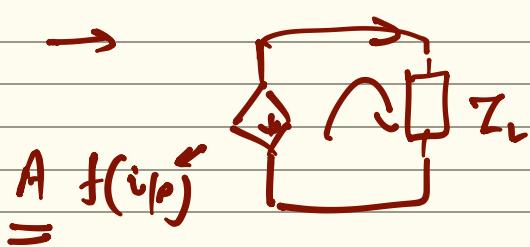


; ; ; ; Amplification →

transistor

=>


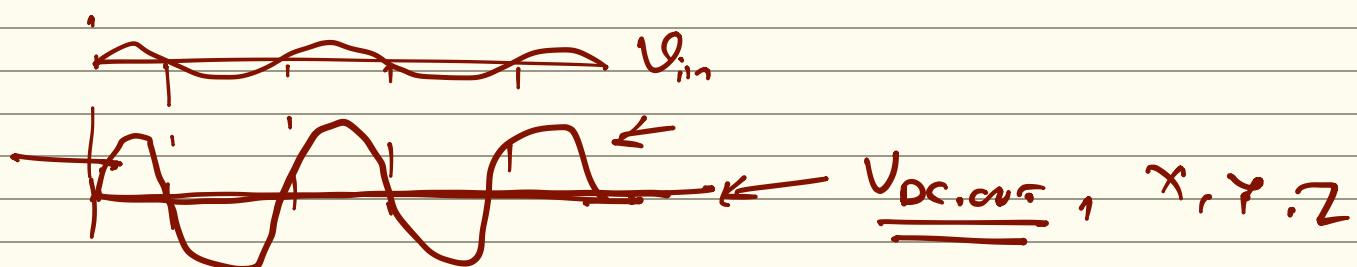


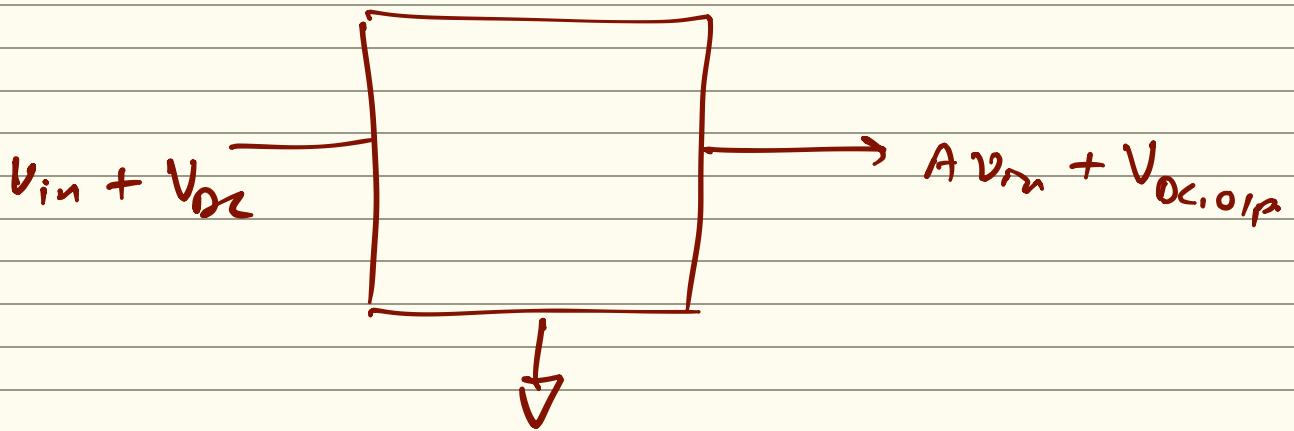


→ Operating Re. must be fixed

↳ independent to the ip (small signal)

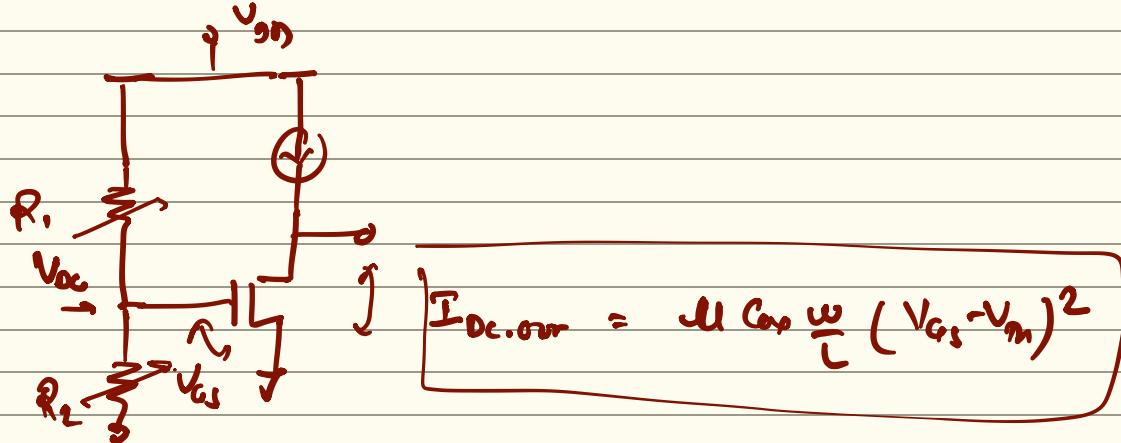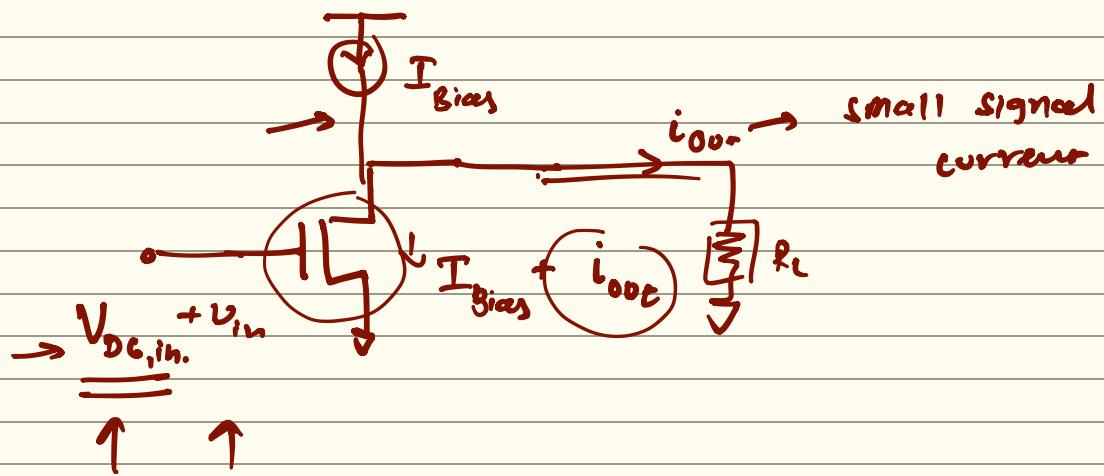
→ Amplification factor must be indep. of D.C. values


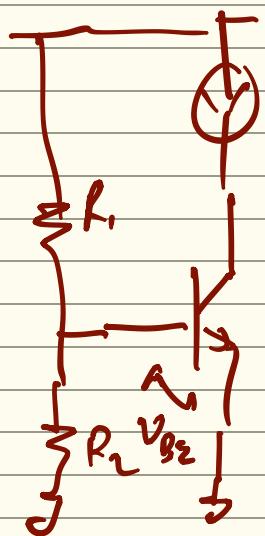
$$V_{Dc,in.} = \frac{V_{DD} \cdot R_L}{R_s + R_L}$$


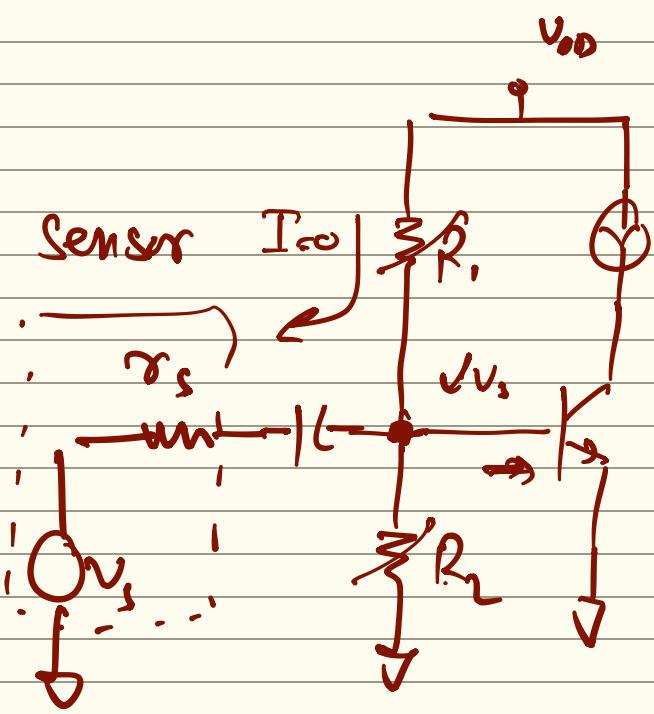
$$I_{out DC} = I_B (e^{\frac{V_{B2}}{nV_T}} - 1)$$



$$V_{out} =$$

if you want  
 $V_s$  to appear  
at i/p

$$\Rightarrow \boxed{V_{i/p} = \frac{V_s \cdot R_2 || R_1}{R_2 || R_1 + R_s}}$$






|

$-K_s$



$+K_s$

for amplification  $\rightarrow$

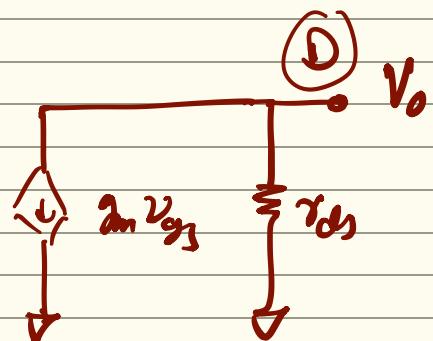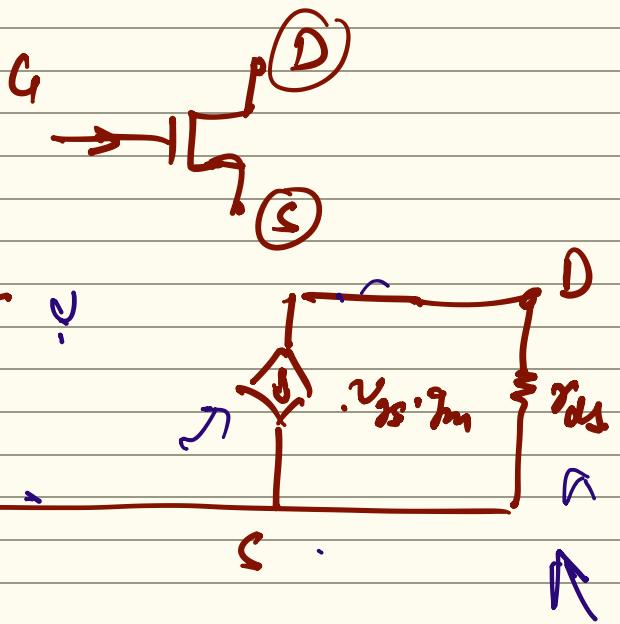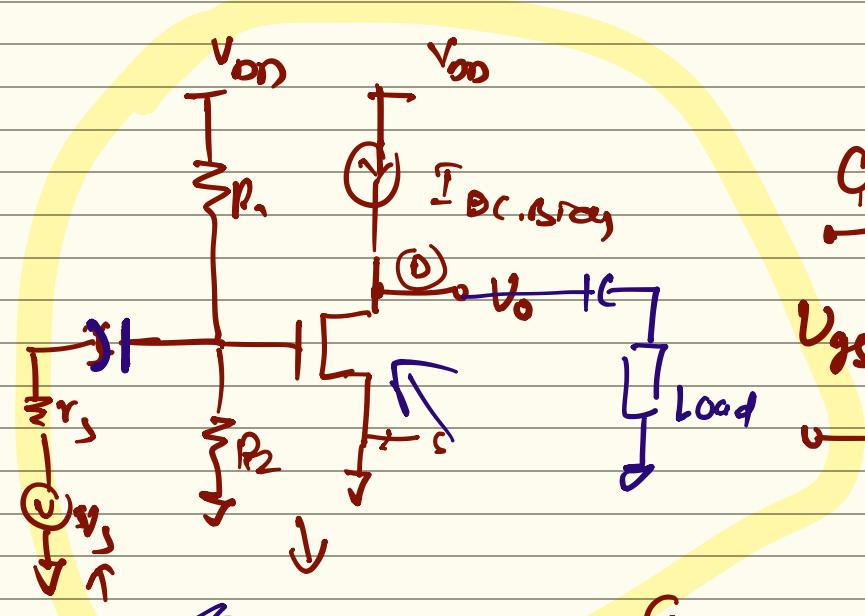


$$\frac{v_o}{v_s} = \text{small signal voltage gain}$$

$B$   $I_C$   $\epsilon$

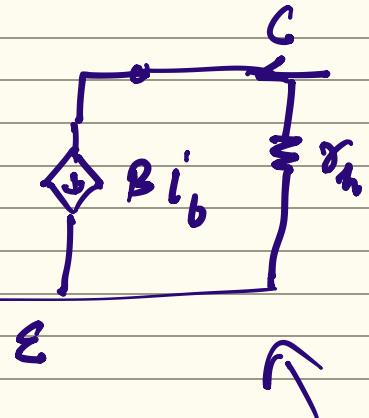
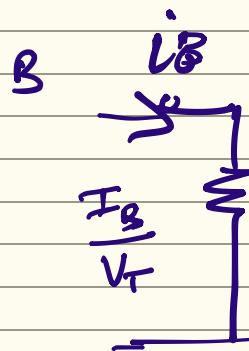


$\Rightarrow$

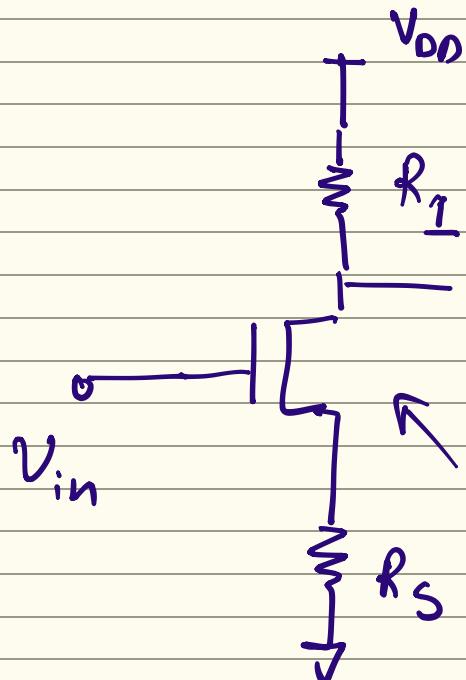

gain ?

$=$

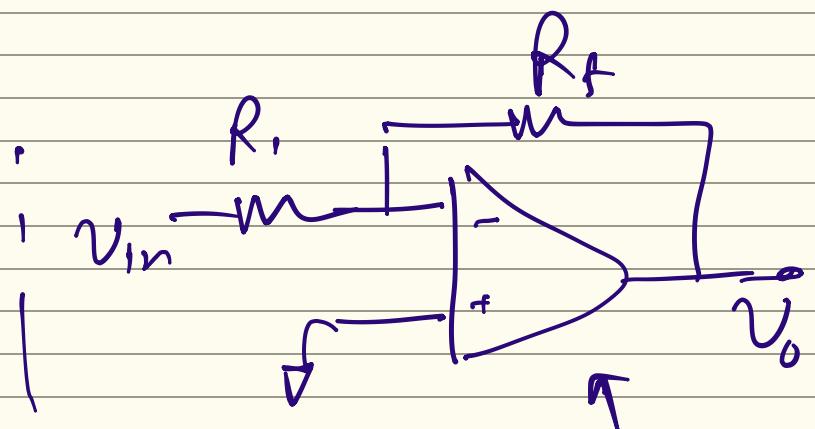
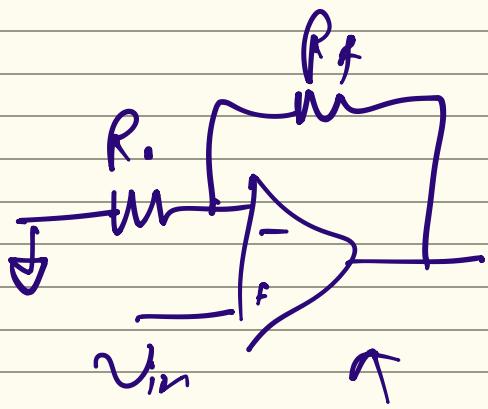


$$\frac{V_0}{V_{in}} = 1 + \frac{R_f}{R_i}$$


non inverting conf. :

$$\frac{V_0}{V_{in}} = - \frac{R_f}{R_i}$$

inverting configuration

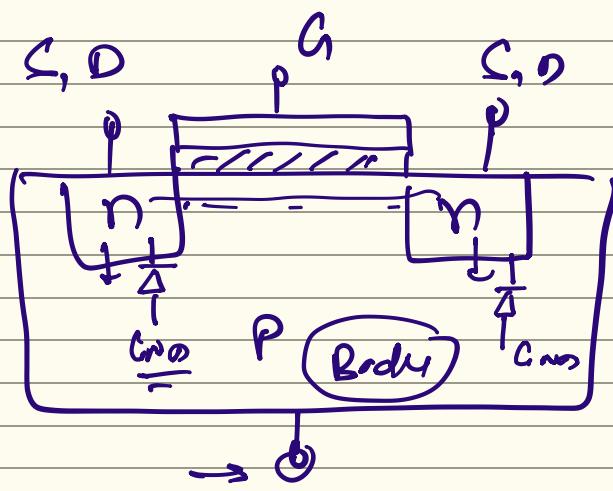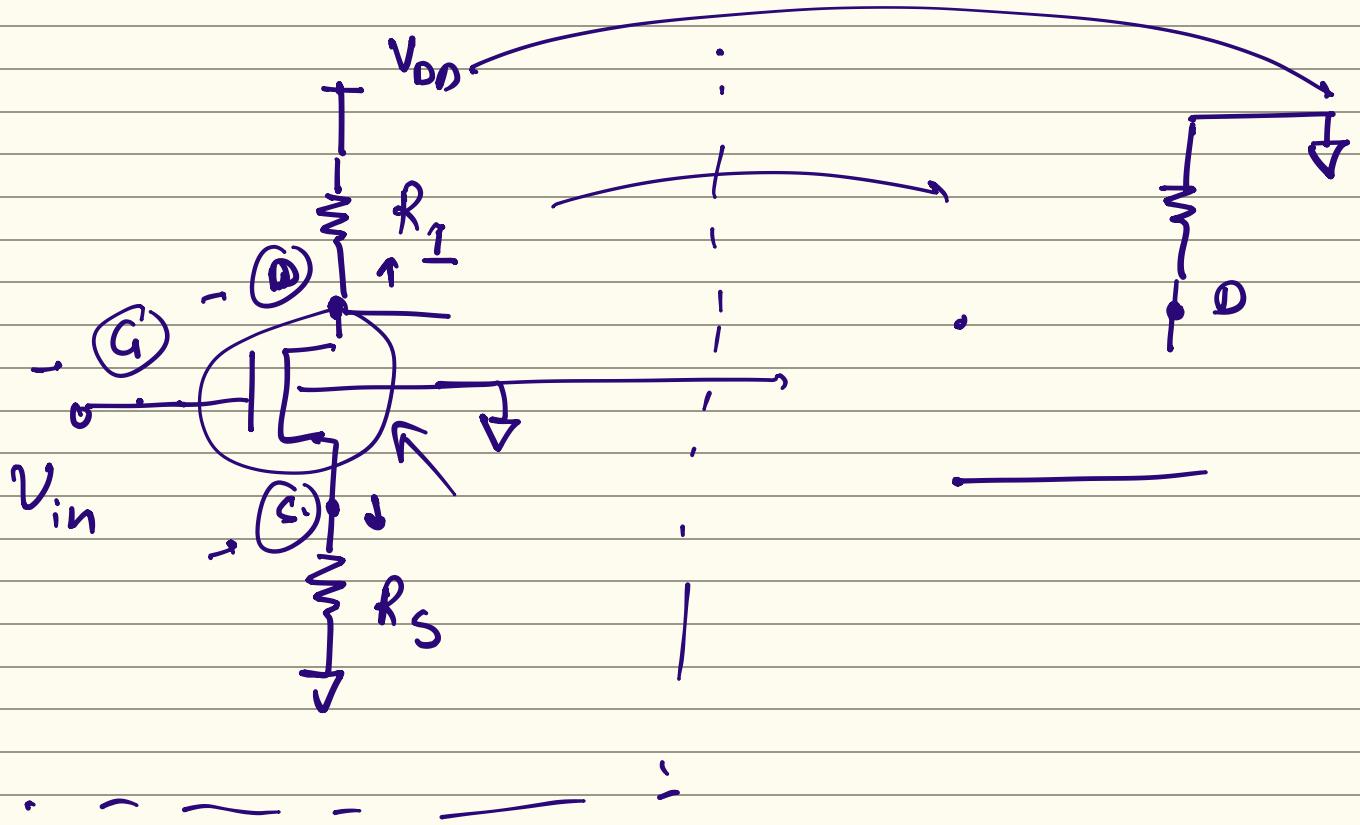

Small signal modeling

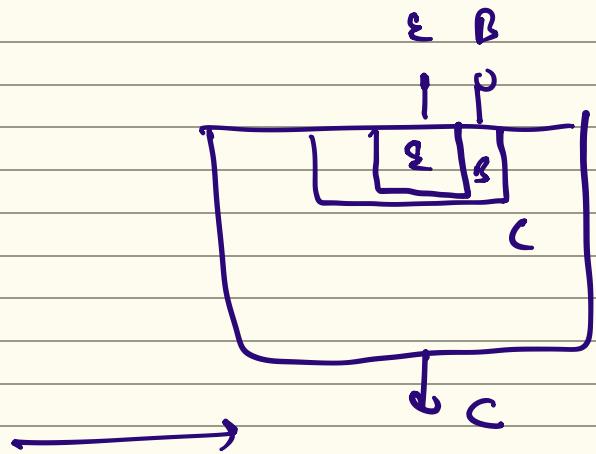



N-Mosfer

$$\rightarrow V_H = \underline{\underline{\text{Drain}}} \\ V_L = \underline{\underline{\text{Source}}}$$

PMos
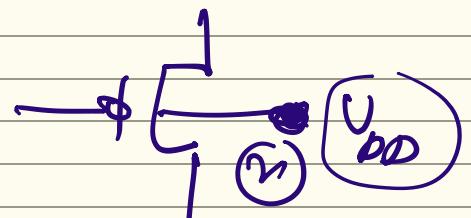
$$V_H = \underline{\underline{\text{Source}}} \\ V_L = \underline{\underline{\text{Drain}}}$$



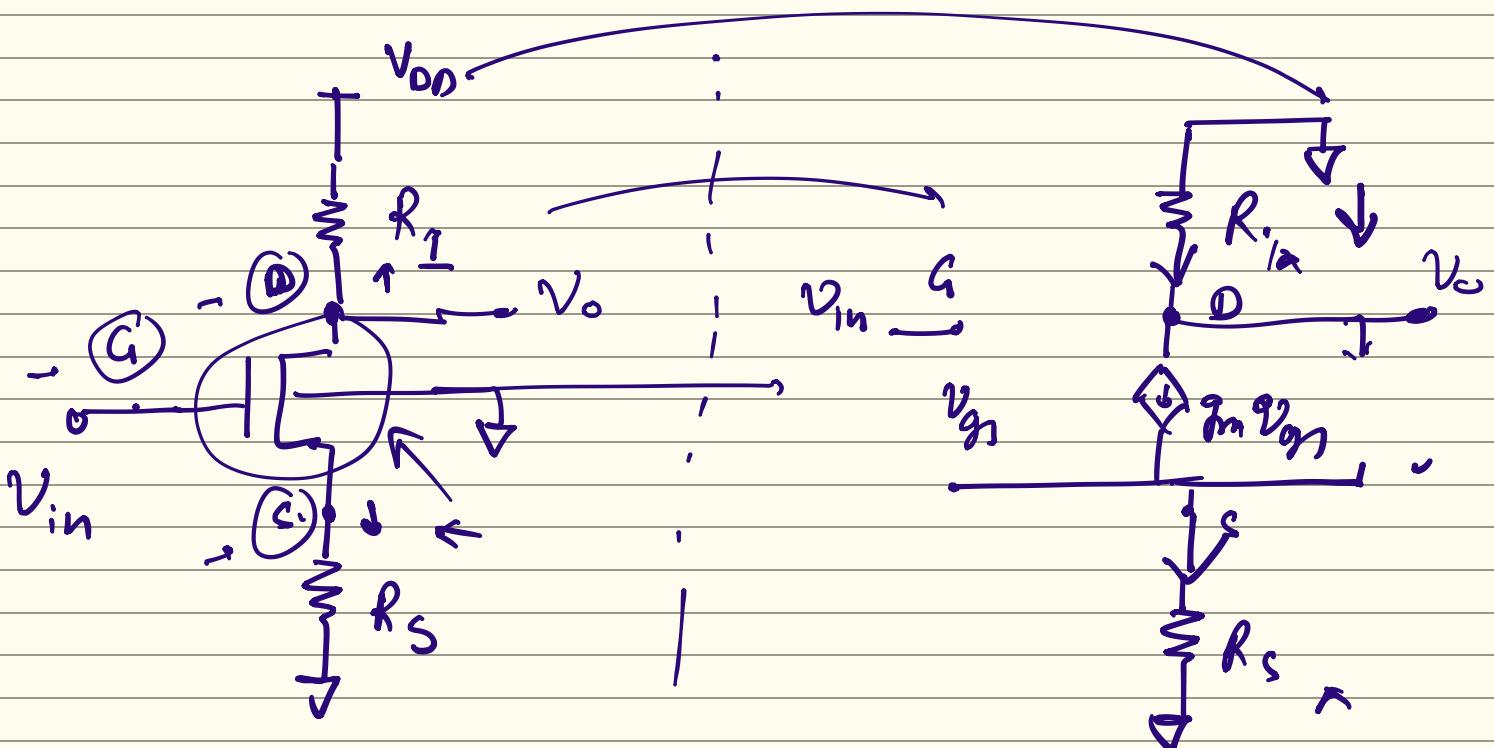

$$V_{gs} = V_{in} - V_s$$

$$\frac{-V_o}{R_1} = g_m (V_{in} - V_s)$$

$$\frac{-V_o}{R_1} = g_m \left( V_{in} + \frac{V_o R_1}{R_1} \right) \Leftrightarrow$$



$$\frac{-V_o}{R_1} = \frac{V_s}{R_s}$$

$$\frac{-V_o}{R_1} = g_m \left( \frac{R_1 V_{in} + V_o R_s}{R_1} \right);$$



$$\frac{-V_o \cdot R_s}{R_1} = V_s$$


$$-V_o - g_m R_s V_o = g_m R_1 V_{in}$$
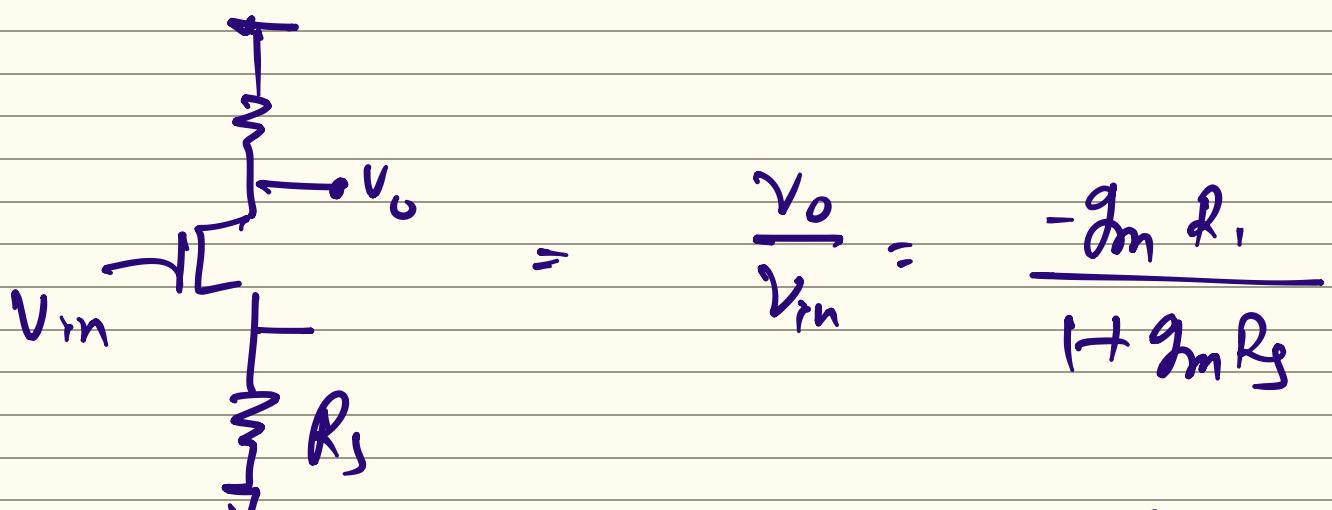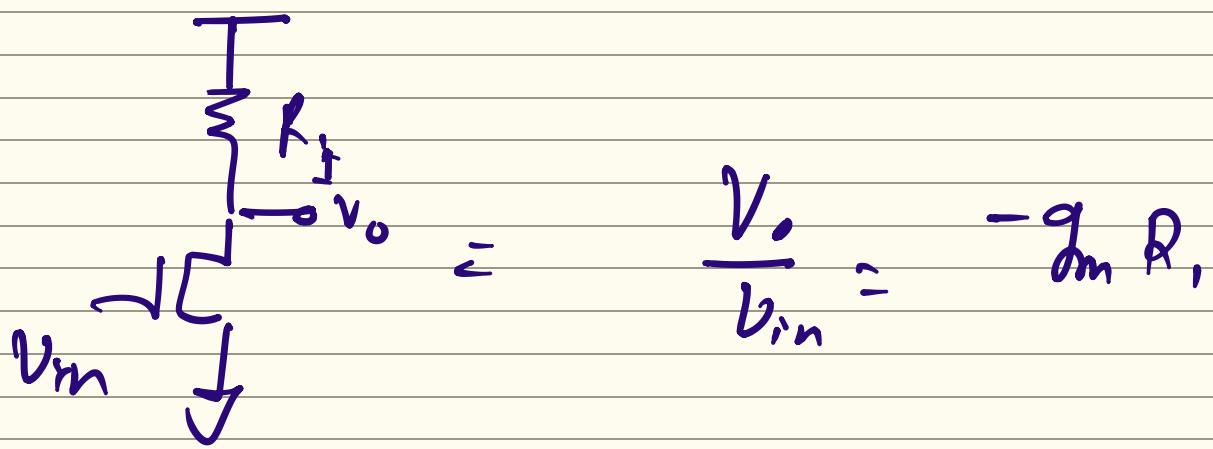
$$\left[ \frac{V_o}{V_{in}} = \frac{-g_m R_1}{1 + g_m R_s} \right] \Leftrightarrow$$



$$G = -\frac{R_s}{R_s}$$

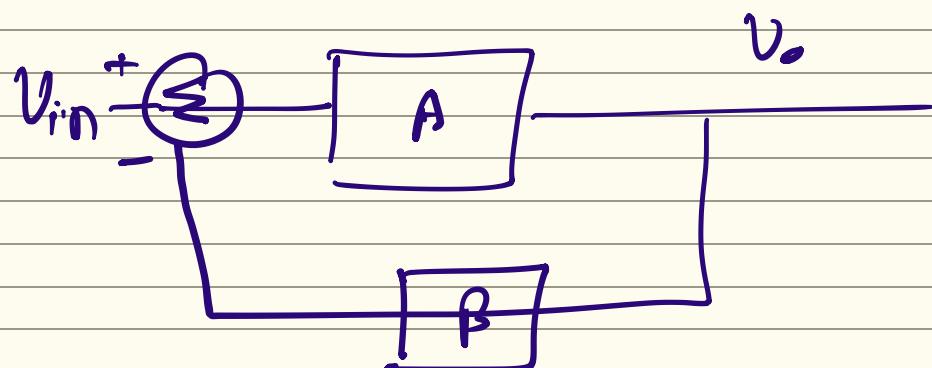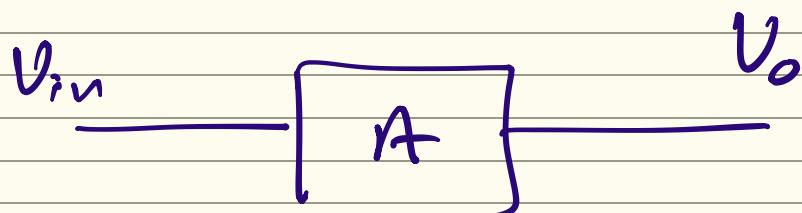

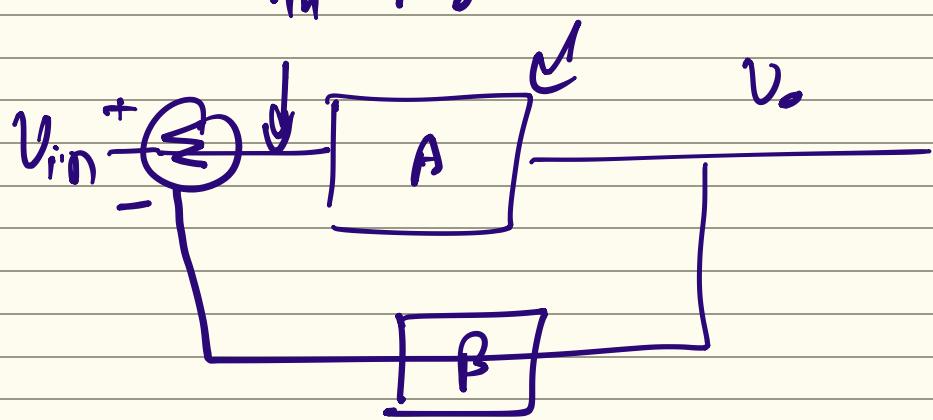



$$V_o = A(V_{in} - \beta V_o)$$


$$V_o(1 + A\beta) = A V_{in}$$

$A$  = open loop


Gain
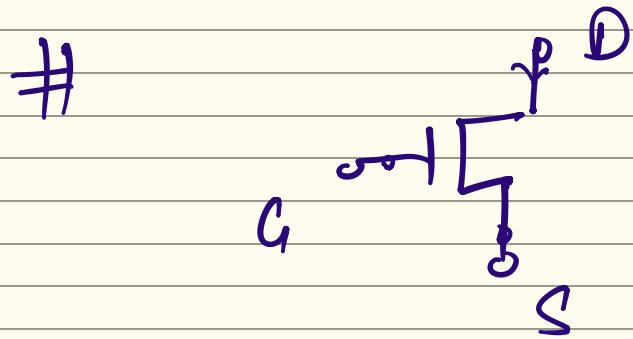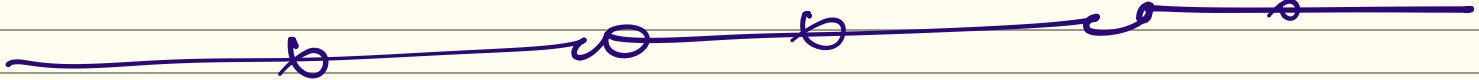
$$\frac{V_o}{V_{in}} = \frac{A}{1 + A\beta}$$



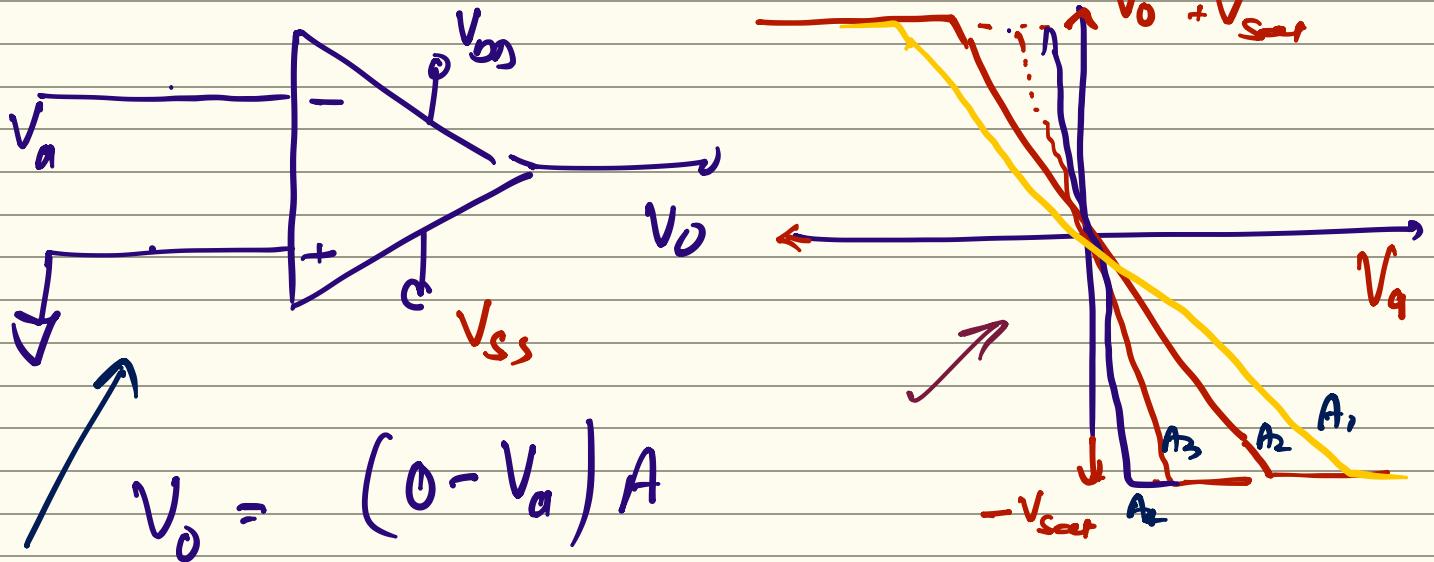


$$A_1 < A_2 < A_3 < A_4$$


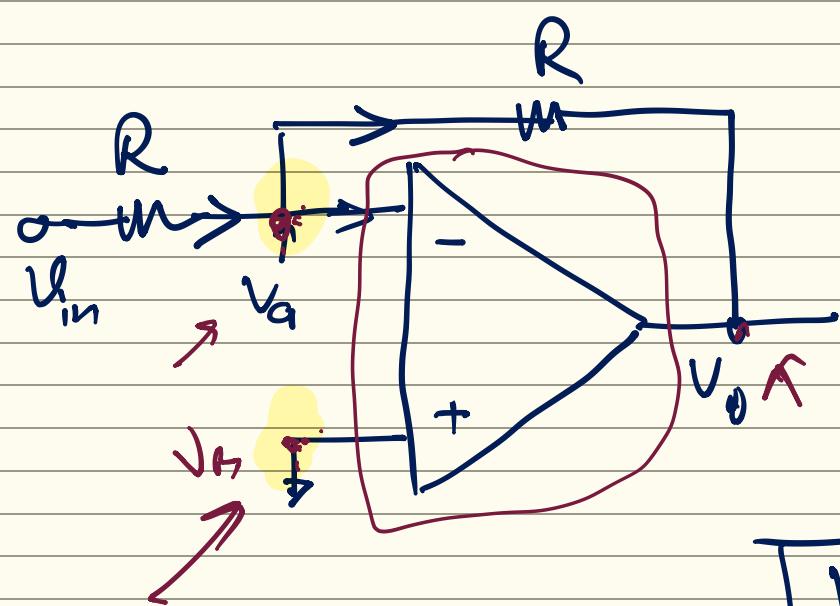




$$\frac{V_{in} - V_a}{R} = \frac{V_a - V_o}{R}$$

$$2V_a = V_o + V_{in}$$

$$V_o = 2V_a - V_{in}$$

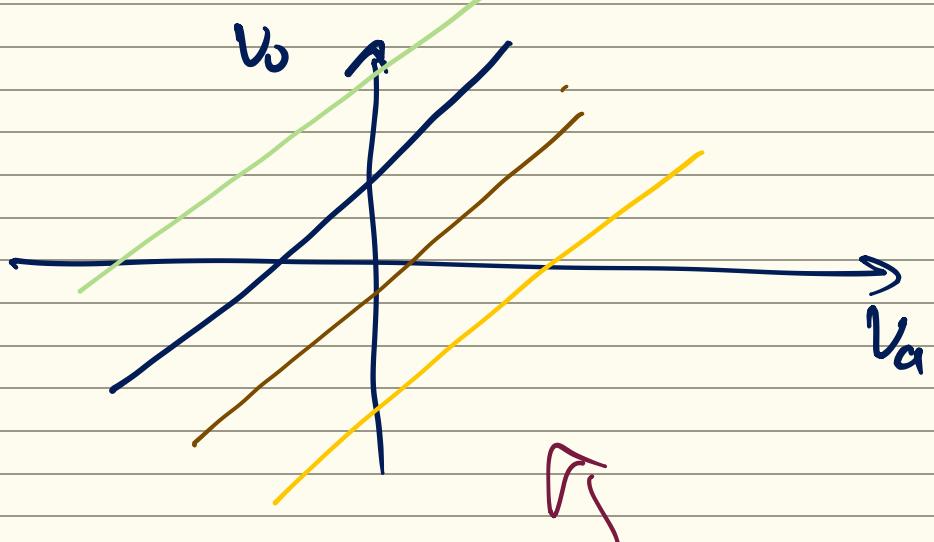

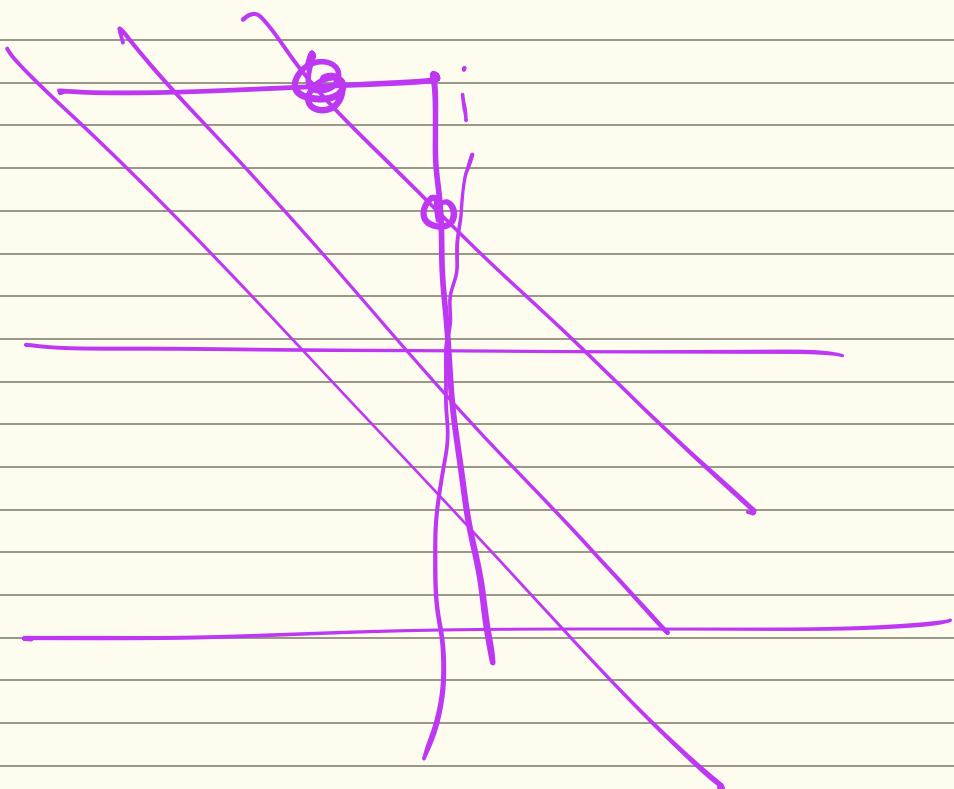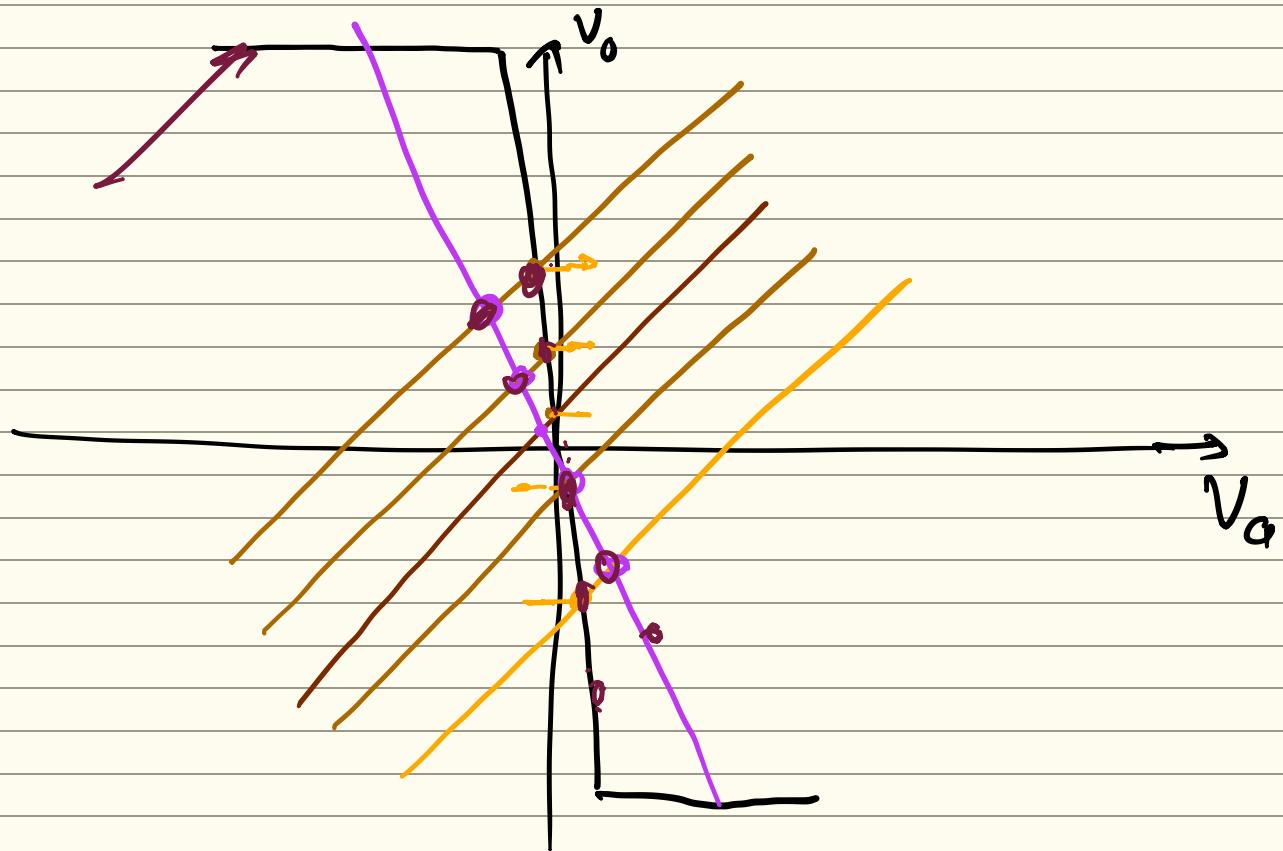

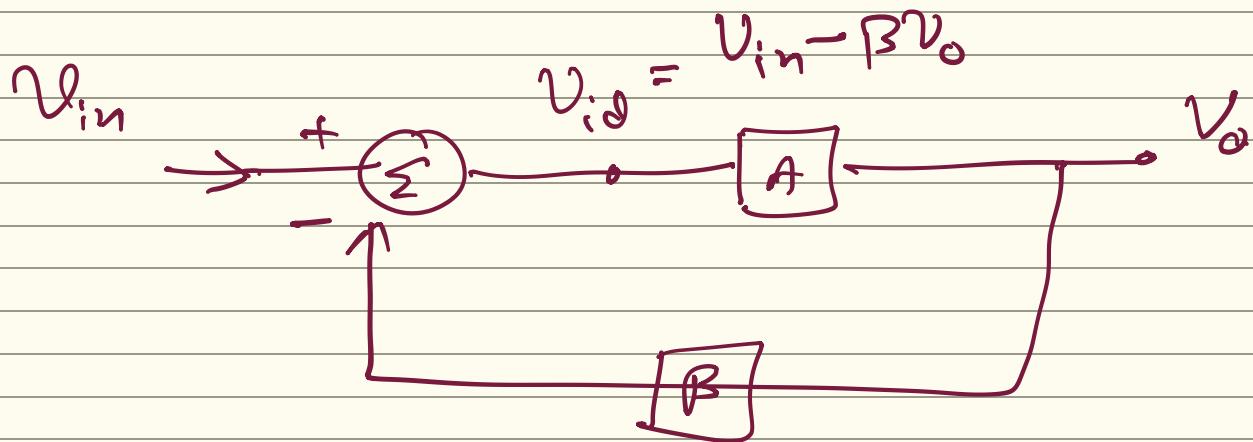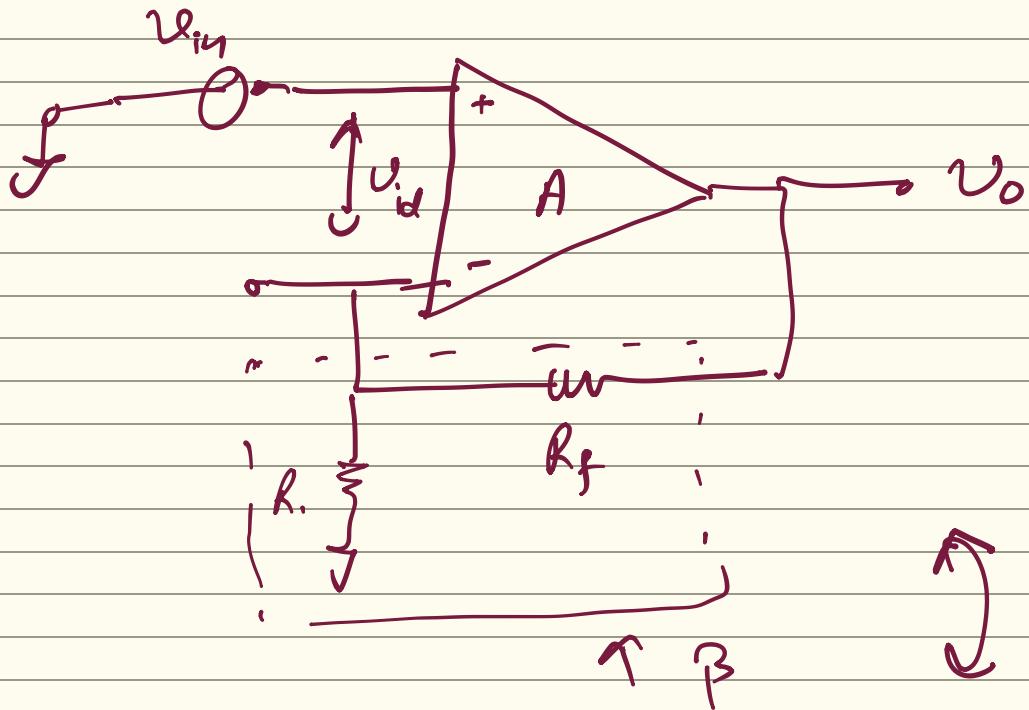

$$\Rightarrow V_o = \frac{V_{in} A}{1 + AB}$$

if we are assuming perfect system  
meaning  $A = \infty \Rightarrow V_o \leq \infty$

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_{in}$$

$\Rightarrow$

# OPAMP

IDEAL

$$\Rightarrow B.W = \infty$$


$\Rightarrow$

practical


$$k\text{Hz}, M\text{Hz}, G\text{Hz},$$




ON

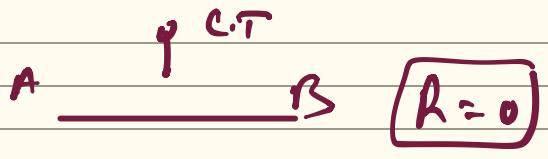

off

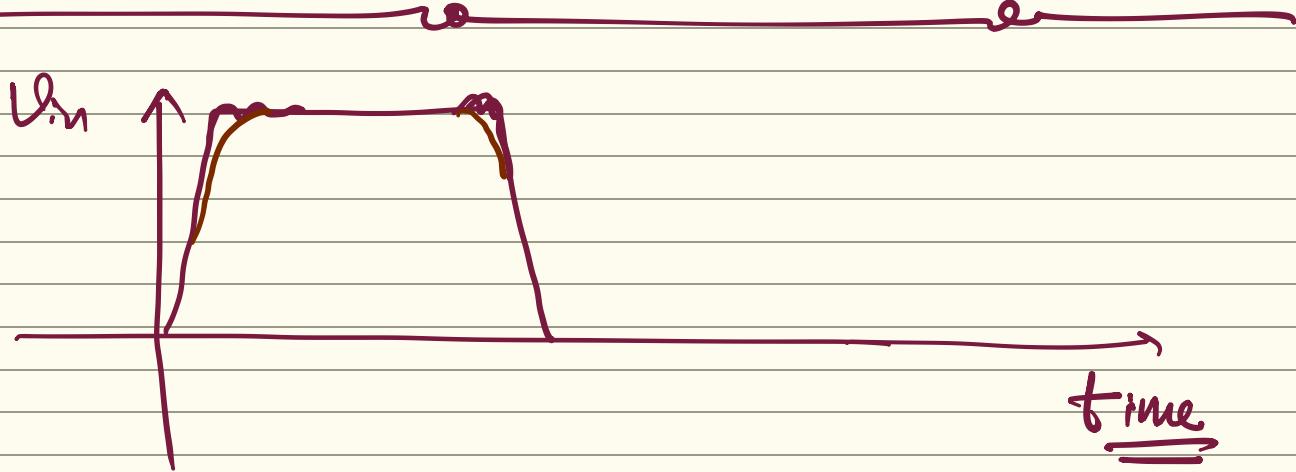

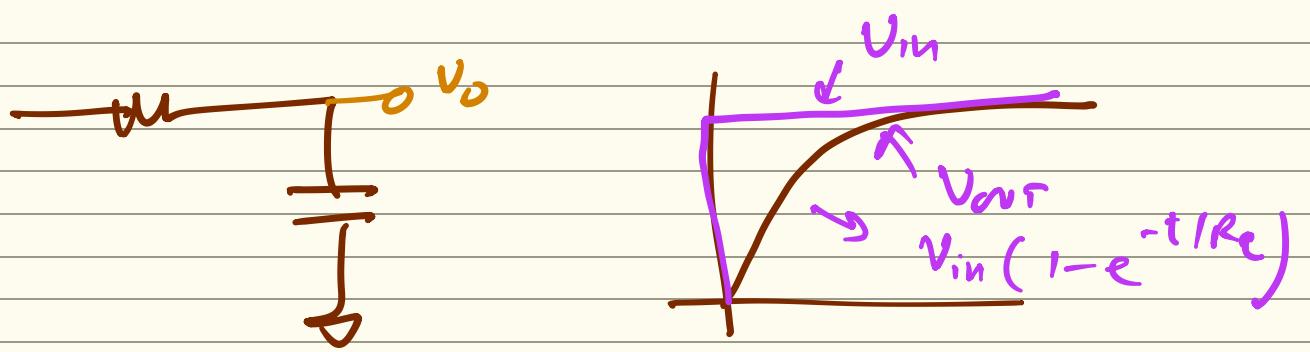



$$\underline{R_C = ?}$$



$$t = R_C$$

$$v_o(t = R_C)$$

$$= \frac{v_{in}}{\sqrt{2}}$$

$$= 0.69 \cdot v_{in}$$

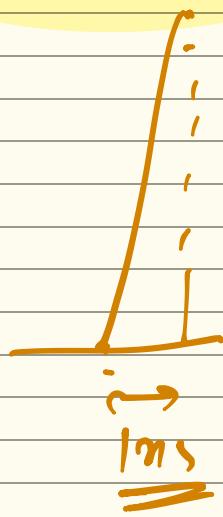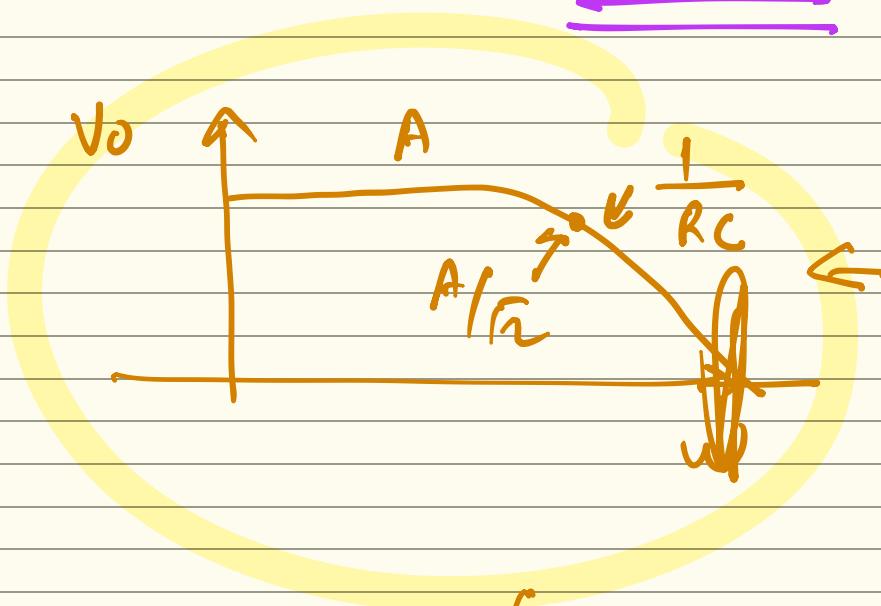

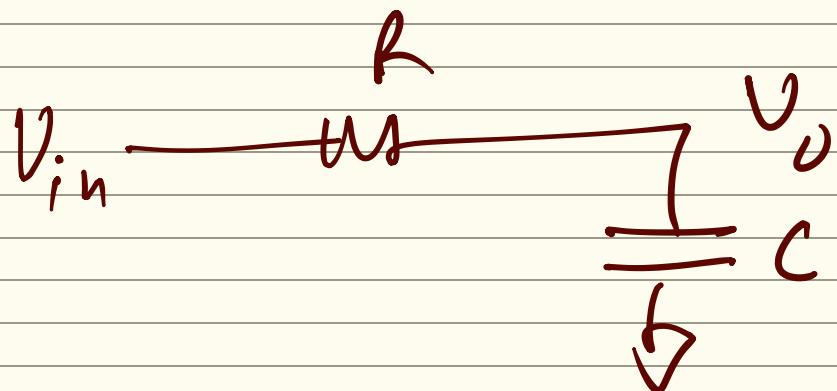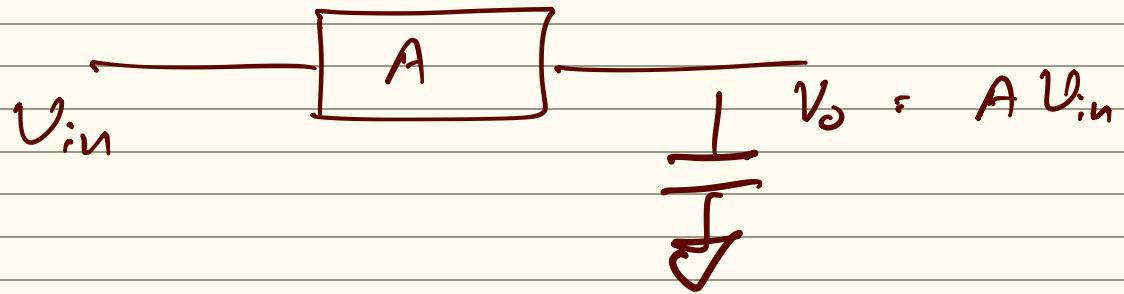



$$V_o = V_{in} \cdot 1/s_C$$

$$\underbrace{R + \frac{1}{s_C}}_{= R_{eq} + j} \quad V_{in}$$

$$\Rightarrow \frac{V_{in}}{\frac{s}{a} + j}$$


$$a = \frac{1}{R_e}$$

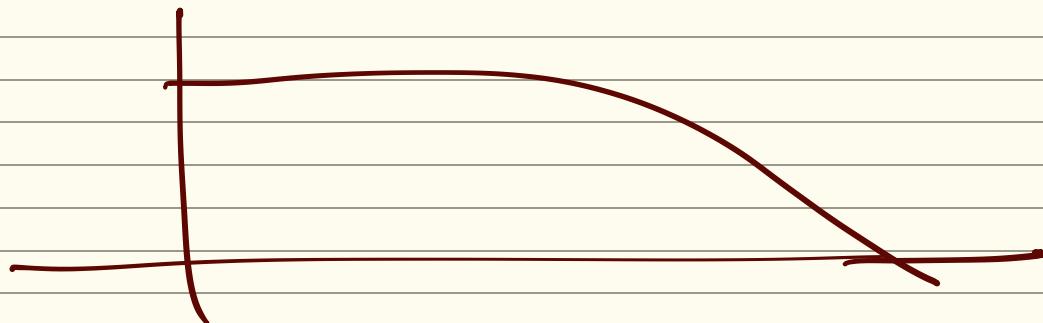


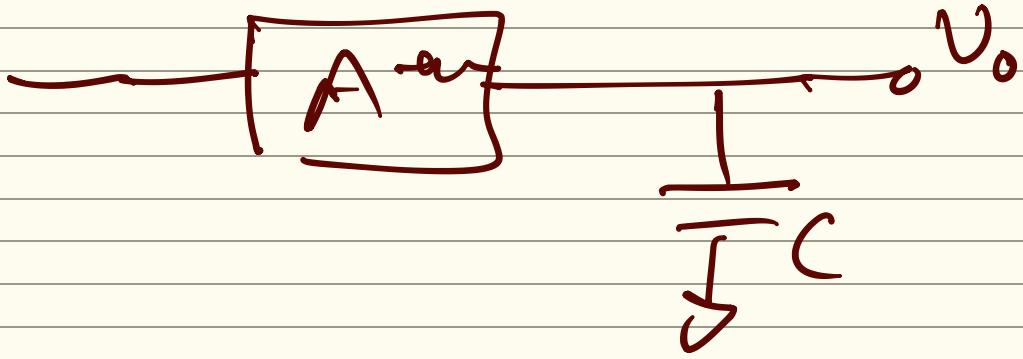

$$U_o = A \cdot U_{in}$$
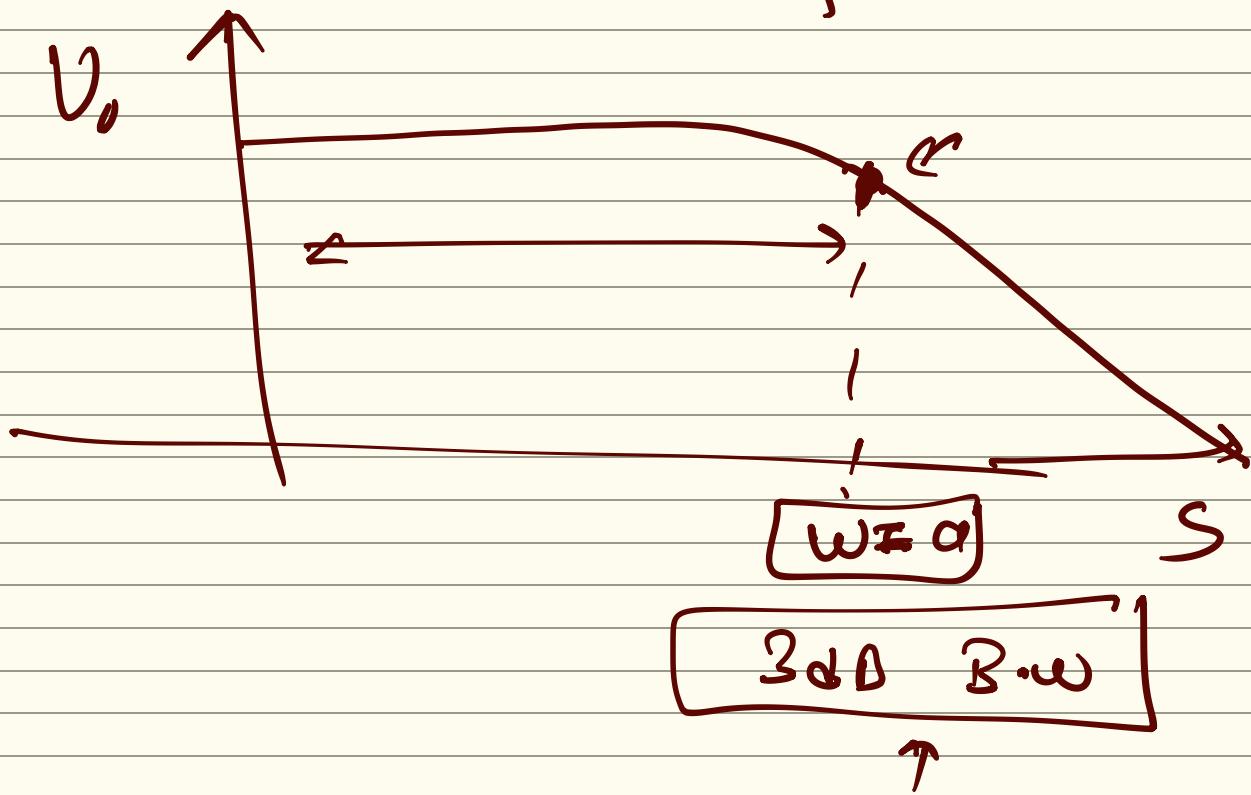
$$U_o = \frac{A}{1 + \sum \frac{1}{a}} \cdot U_{in}$$



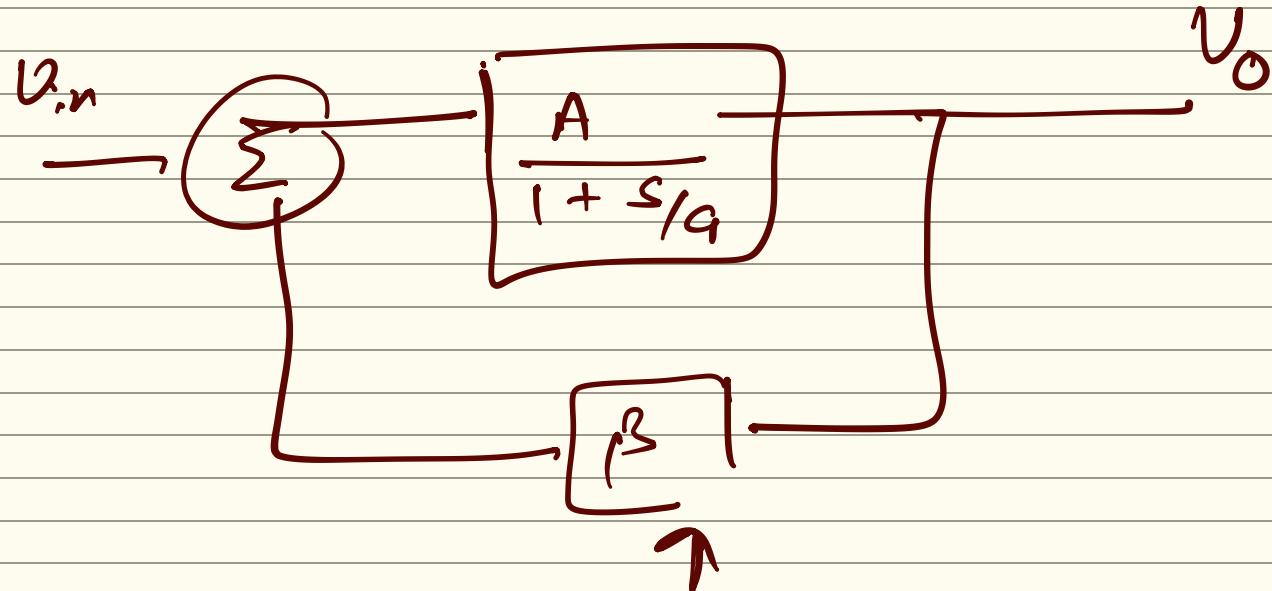

$$V_O = \frac{A}{1 + A\beta} \quad \left| \begin{array}{l} A \rightarrow \frac{A}{1 + \frac{S}{\omega_a}} \\ \beta \cdot \omega_a = \alpha \end{array} \right.$$

?

$$\frac{A}{1 + \frac{S}{\omega_a}}$$


$$1 + \frac{A}{1 + \frac{S}{\omega_a}} \cdot \beta$$

$$\frac{A}{(1 + \frac{S}{\omega_a})}$$

$$1 + \frac{\omega_a}{\omega} + A \cdot \beta$$

$$(1 + \frac{S}{\omega})$$
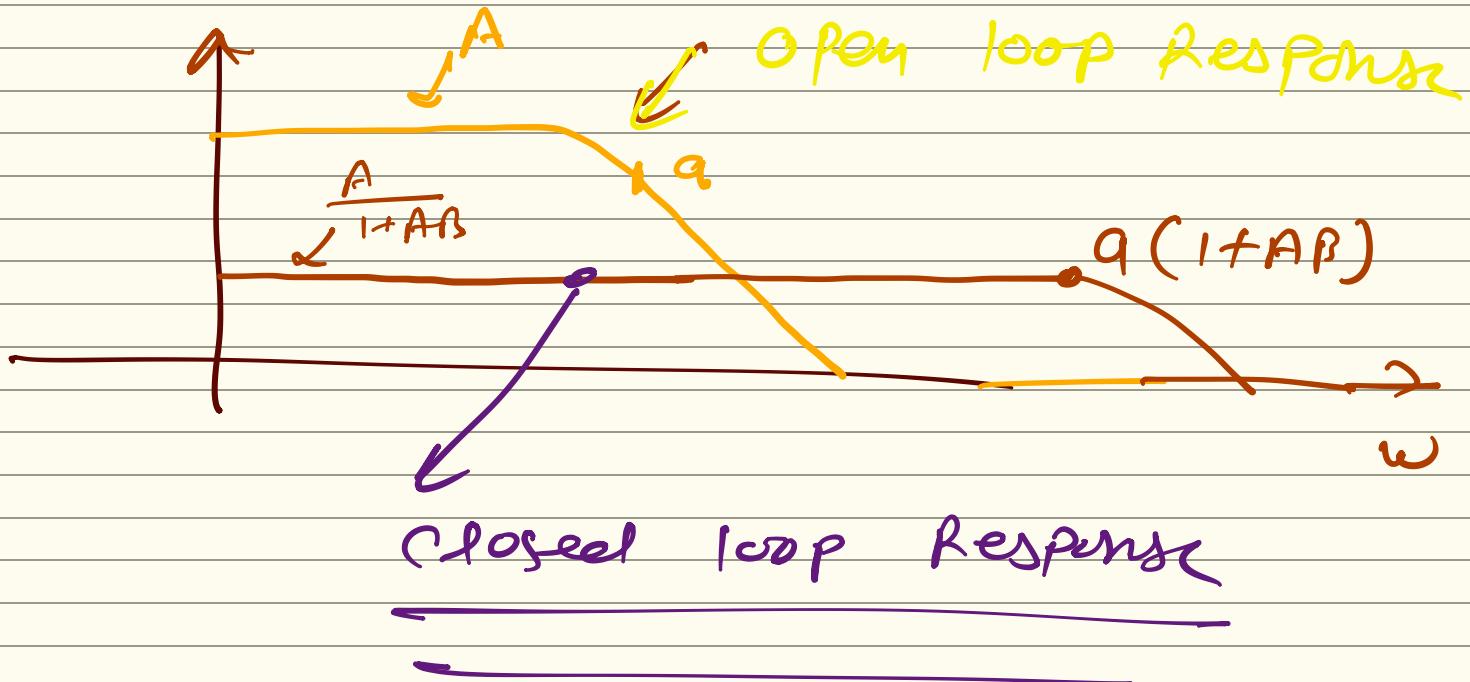
$$\Rightarrow \frac{A}{1 + A\beta} \left\{ 1 + \frac{S}{\omega(1 + A\beta)} \right\} = \frac{V_O}{U_{in}}$$



When single pole system is to be considered  $\rightarrow$

$$B \cdot \omega \times \text{GAIN} = \underline{\underline{\text{const.}}}$$

$$A \cdot q = \frac{A}{1+AB} \cdot A(1+AB)$$

$$= A \cdot q$$

Open loop ; Closed loop

                          $\omega$