

.

EE1101: Circuits and Network Analysis


Lecture 14: Operational Amplifier

August 29, 2025

Topics :

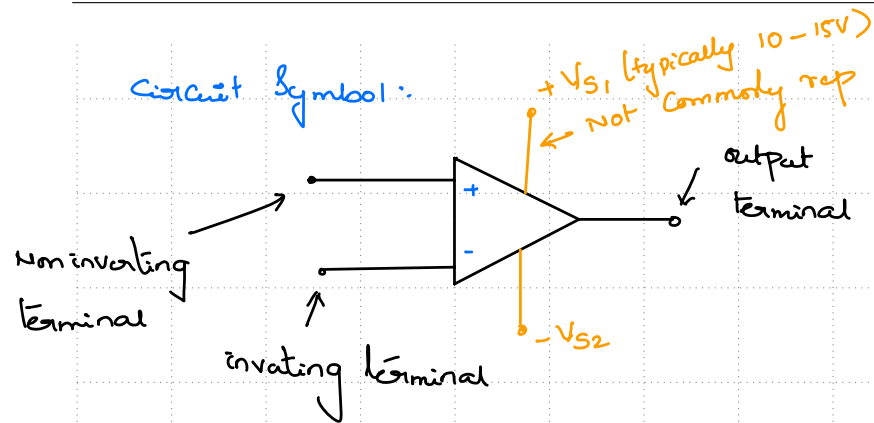1. Operational Amplifier (Op-Amp)
 2. Virtual Short Principle
-

Operational Amplifier from a Circuit Perspective



only operates as an amplifier
& not as a switch.

Characteristic Eqn


$$V_{out} = A(V_+ - V_-)$$

gain V/V is typically very large.


when $V_- = 0 \Rightarrow V_{out} = AV_+$

when $V_+ = 0 \Rightarrow V_{out} = -AV_-$

In Practice

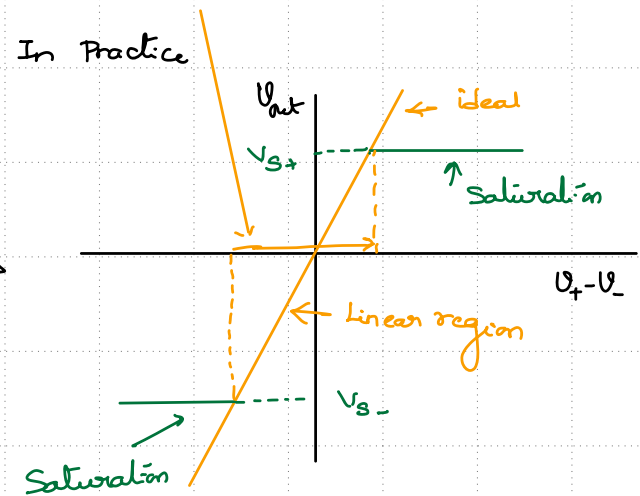

Equivalent Circuit (Non-ideal)

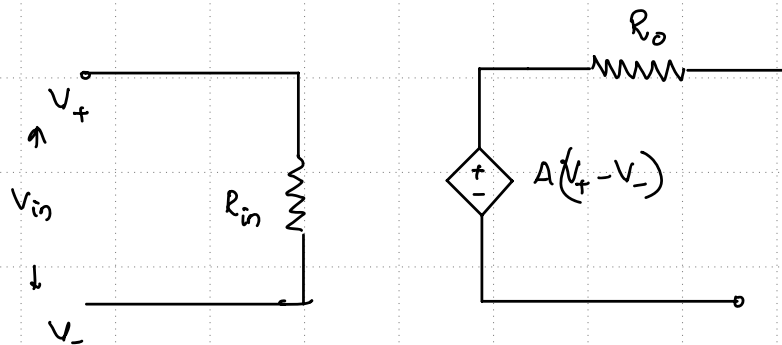


$R_{in} \rightarrow$ typically very large

$A \rightarrow$ very high

$R_o \rightarrow$ typically low

Example

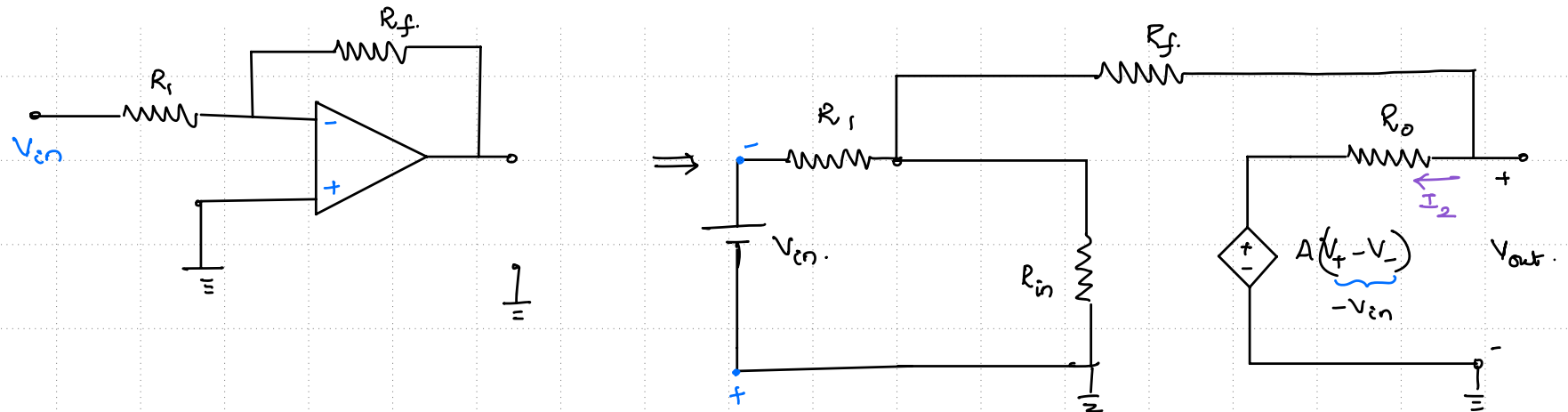

$$V_{out} = -A V_{in} + I_2 R_o$$

↑
Compute I_2 ?

Complete by choosing Numerical values


$R_{in} \rightarrow \text{large}$

$R_o \rightarrow \text{small}$


$$\frac{R_f}{R_i} \approx 10$$

Virtual Short Concept

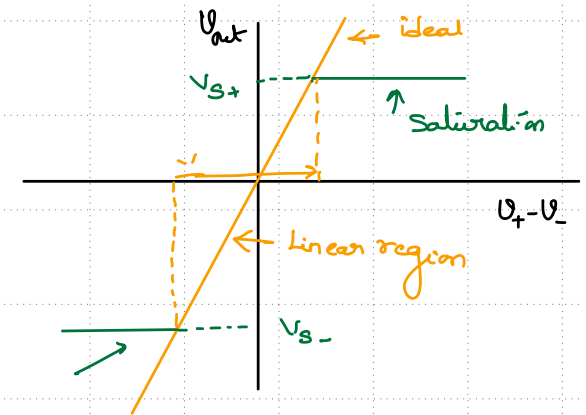- ① given that $V_S = 10-15$ (range) }
 and gain is high
 range of linear operation is very small
 (typically mV)
 \downarrow
 $V_+ - V_- \approx 0 \Rightarrow$ Virtual short
 i.e. $V_+ \approx V_-$




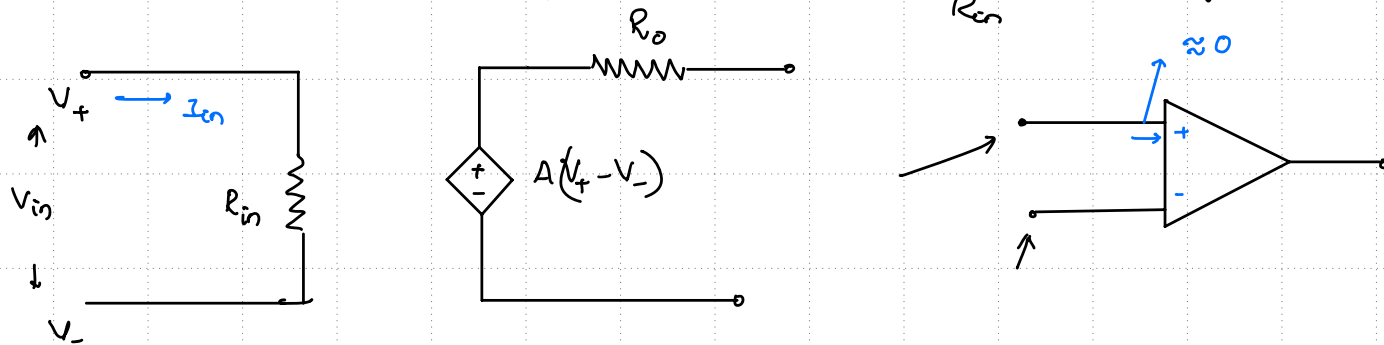- ② Since $R_{in} \rightarrow$ large & $V_+ - V_-$ is very small, $I_{in} = \frac{V_+ - V_-}{R_{in}} \rightarrow$ neg. small



- ③ **Caution:** Not all CKTs can be analyzed using virtual short
 Majority of the CKTs can be analyzed using Virtual Short.

Example (using Virtual short)

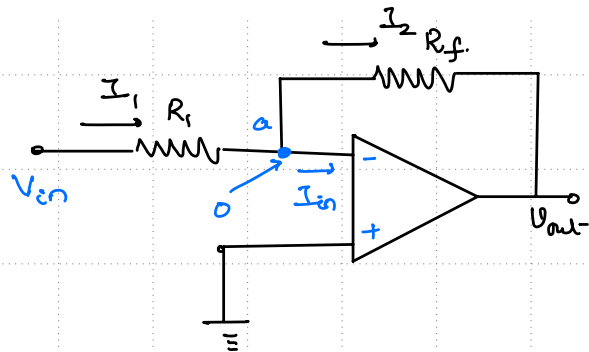

Step 1:- by virtual short $V_a = 0$

Step 2:- Since $V_a = 0 \Rightarrow I_1 = \frac{V_{in}}{R_i}$

Step 3:- by virtual short, $I_{in} = 0$
 $\Rightarrow I_2 = I_1$

Step 4:- $V_{out} = V_a - I_2 R_f$
 $= 0 - \frac{V_{in}}{R_i} R_f = -\frac{R_f}{R_i} V_{in}$

$G \leftarrow$ adjusted
by choosing
 $R_f \& R_i$


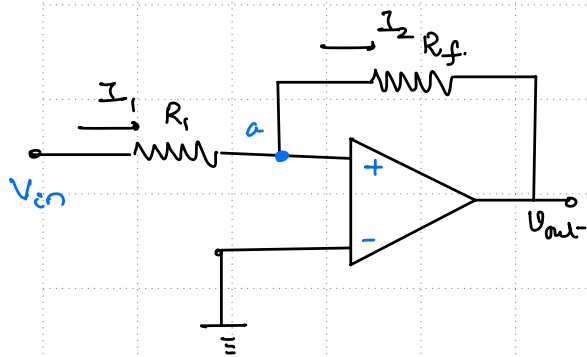


figure out if virtual short
concept can be
applied to this
circuit.

Examples

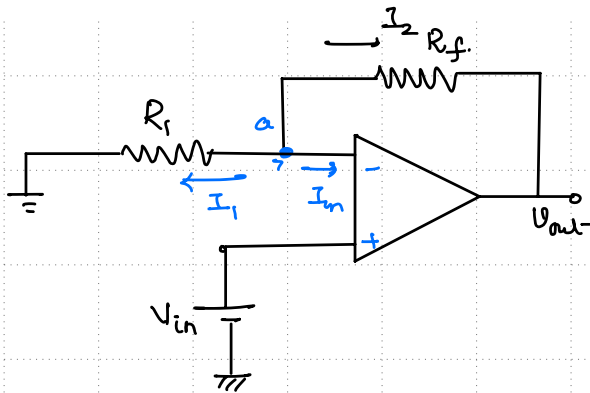

Step 1:- by VS: $V_a = V_{in}$

Step 2:- $I_1 = \frac{V_{in}}{R_i}$

Step 3:- by VS: $I_{in} = 0 \Rightarrow I_2 = -I_1 = -\frac{V_{in}}{R_i}$

Step 4:- $V_{out} = V_a - I_2 R_f$

$$= V_{in} + V_{in} \frac{R_f}{R_i}$$

$$= \left(1 + \frac{R_f}{R_i}\right) V_{in}$$