

.

EE1101: Circuits and Network Analysis

Lecture 39: Series and Parallel Resonance

November 7, 2025

Topics :

1. Series and Parallel Resonance
 2. Quality Factor and Bandwidth
-

Series Resonance

Question: Condition on freq for which $|\vec{I}|$ is maximum?

Sol: $\omega : x_{eq} = 0$.

Example 1

(Series RL Ckt)

for $\omega = 0$, $x_{eq} = 0$

↓
True for any ckt that

comprises of $R \& L$

(along with sources)

(Series RC Ckt)

for $\omega = \infty$, $x_{eq} = 0$

↓
True for any ckt that

comprises of $R \& C$

(along with sources)

Example 2

Series RLC Ckt

for $\omega = \frac{1}{\sqrt{LC}}$, $x_{eq} = 0$. $[\omega_0]$

Prop 1: at resonance \vec{V} and \vec{I} are in
Phase

Prop 2: Net power drawn from the source

is active power $P = |\vec{I}|^2 R$


$$P = \frac{|\vec{V}_s|^2}{R}$$

Prop 3: $e_L(t) = \frac{1}{2} L i_m^2$ & $e_C(t) = \frac{1}{2} C v_C^2$

$$e_L(t) + e_C(t) = \frac{1}{2} L i_m^2 \quad (\text{constant})$$

Prop 4: $e_d \propto t$; $E_d (\text{per cycle}) = \frac{|\vec{I}|^2 R T}{2} = \frac{1}{2} i_m^2 R T$

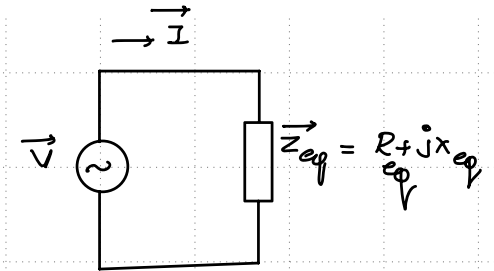Prop 5: energy from source = $e_d(t)$. [in steady state]



Series Resonance

def: for a ckt that comprises of L & C (in addition to other linear ckt elem)
 → if it exists
 the cond at which $x_{eq} = 0$ is called Resonance.
 and the freq at which Resonance occurs → Resonant freq (ω_0)

Resonant freq for Series RLC ckt $\omega_0 = \frac{1}{\sqrt{LC}}$

At frequencies other than ω_0 :-



$$\textcircled{1} \quad \vec{Z}_{eq} = R + j\left(\omega L - \frac{1}{\omega C}\right) \quad |\vec{Z}_{eq}| =$$

at lower freq → capacitive in nature

at high freq → inductive in nature

$$\textcircled{2} \quad P, \phi \text{ from source} \quad P = |\vec{I}|^2 R_{eq}$$

$$\phi = (\vec{I})^2 x_{eq}$$

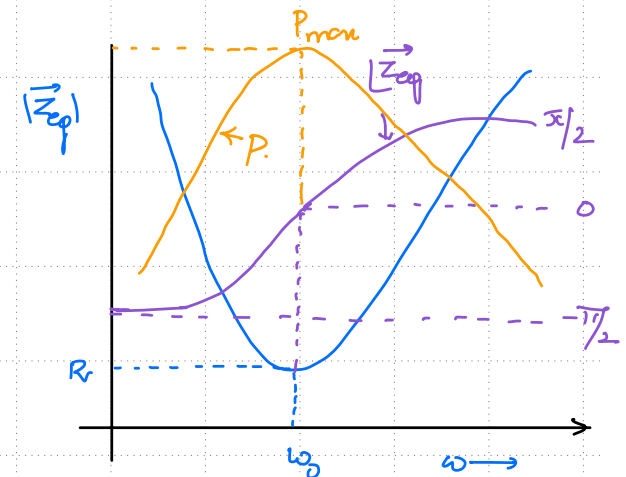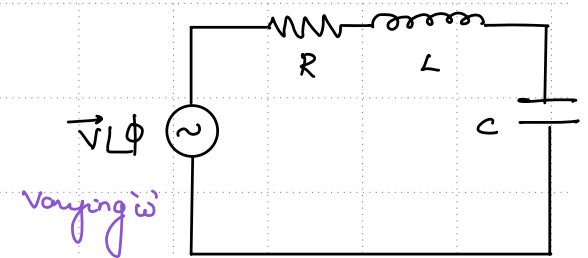

Quality Factor and Bandwidth

$$Q = (2\pi) \frac{\text{energy stored in ckt at resonance}}{E_d(t) \rightarrow \text{E/dt per cycle.}}$$

$$= 2\pi \frac{E_s(t)}{E_d(t)} = 2\pi \frac{\frac{1}{2} L I_m^2}{|I|^2 R T.}$$

$$= \frac{2\pi}{T} \frac{L}{R}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\sqrt{LC}} \frac{L}{R} = \sqrt{\frac{L}{C}} \cdot \frac{1}{R}$$

↳ characteristic imp.


$$Q = \frac{1}{\cos \phi} \quad \text{when energy stored is computed in terms of } V_0 \text{ across the cap.}$$

Bandwidth: range of freq for which $P \geq \frac{1}{2} P_{\max}$.

$$P = |I|^2 R = \frac{|V|^2}{|Z_{eq}|^2} R = \frac{V^2}{R^2 + (\omega L - \frac{1}{\omega C})^2} R$$

$$\frac{1}{2} P_{\max} = \frac{1}{2} \frac{|V|^2}{R}$$
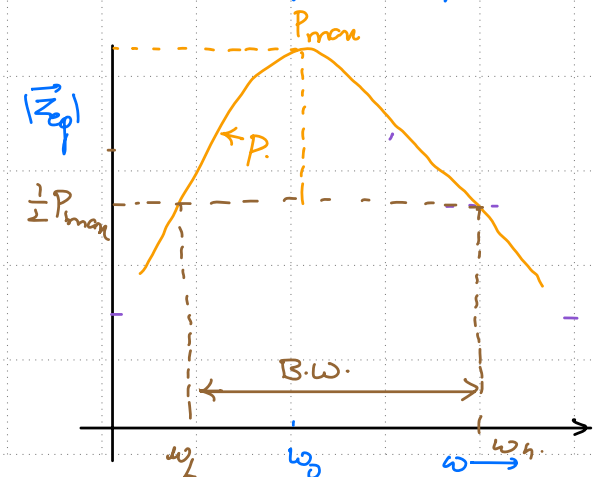
$$\omega_L \text{ \& } \omega_H \text{ are freq for which } \omega L - \frac{1}{\omega C} = \pm R$$



Quality Factor and Bandwidth

Compute ω : $\omega L - \frac{1}{\omega C} = \pm R$: if ω_a is sol to $\omega L - \frac{1}{\omega C} = \pm R$
 then $-\omega_a$ is also a sol to $\omega L - \frac{1}{\omega C} = \pm R$

$$\frac{\omega L}{R} - \frac{1}{\omega RC} = -1$$

$$\frac{\omega Q}{\omega_0} - \frac{Q\omega_0}{\omega} = -1$$

$$Q = \frac{\omega L}{R} = \frac{1}{\omega_0 RC}$$

$$\Rightarrow Q\omega^2 + \omega_0\omega - Q\omega_0^2 = 0.$$

$$\omega = \frac{-\omega_0 \pm \sqrt{\omega_0^2 + 4Q^2\omega_0^2}}{2Q} = \frac{\omega_0}{2Q} (-1 \pm \sqrt{1+4Q^2})$$

$$\sqrt{1+4Q^2} > 1 : \text{ roots } = \frac{\omega_0}{2Q} (-1 + \sqrt{1+4Q^2}) > 0 \rightarrow \omega_2, \omega_3$$

$$\frac{\omega_0}{2Q} (-1 - \sqrt{1+4Q^2}) < 0$$

$$\text{other positive root } (1 + \sqrt{1+4Q^2}) \frac{\omega_0}{2Q} \rightarrow \omega_h$$

$$B.W = \omega_h - \omega_2 = \frac{\omega_0}{Q}$$