

.

EE1101: Circuits and Network Analysis

Lecture 31: Network Theorems

October 15, 2025

Topics :

1. Linearity and Superposition
 2. Thevenin's Theorem
-

Linearity and Superposition

A typical time domain description of a ckt:
(encountered so far)

n^{th} order ordinary DE with
Constant Coefficients

$$a_n \frac{d^n x}{dt^n} + a_{n-1} \frac{d^{n-1} x}{dt^{n-1}} + \dots + a_1 x = f(t) \rightarrow \textcircled{1}$$

$a_n \dots a_1 \rightarrow \text{Constants}$

from the context of DEs: $\textcircled{1}$ as a linear non-homogeneous ODE if $f(t) \neq 0$

$\textcircled{2}$

homogeneous ODE if $f(t) \equiv 0$

if $x(t)$ is a sol to DE
then $\alpha x(t)$ must also be
a solution $\forall \alpha$.

if x_1 is a sol of ODE to $f_1(t)$

and x_2 is a sol of DE to $f_2(t)$

then $\alpha x_1 + \beta x_2$ is also a sol to $\alpha f_1(t) + \beta f_2(t)$

$\alpha, \beta \in \mathbb{C}$

for this course: Any circuit whose describing equation is a linear ODE is
considered as a linear circuit.

Linearity and Superposition

for a linear circ, $\Rightarrow a_n \frac{d^n x}{dt^n} + a_{n-1} \frac{d^{n-1} x}{dt^{n-1}} + \dots + a_1 x = f(t)$

\downarrow given linearity

$f(t)$ as a sum of many simple functions
 \downarrow (if complex)

\downarrow Compute the response of DE to the simple functions


\downarrow Sum of all the responses

① $f(t) = \sum f_i(t)$

② Solve the DE with $f_i(t)$ on the RHS

$$x_i(t) : a_n \frac{d^n x_i}{dt^n} + a_{n-1} \frac{d^{n-1} x_i}{dt^{n-1}} + \dots + a_1 x_i = f_i(t)$$

③ $x = \sum x_i(t)$

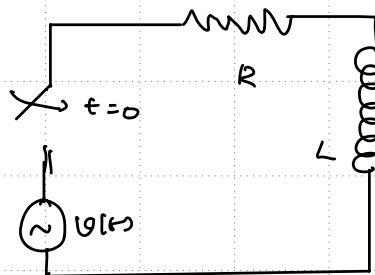

if $v(t) = V$, $i(t) = \frac{V}{R} (1 - e^{-t/\tau})$

if $v(t) = V_m \cos \omega t$ $i(t) = \frac{V}{\sqrt{\omega^2 L^2 + R^2}} \cos(\omega t - \theta) + \underbrace{\hspace{2cm}}_{\text{Transient Part.}}$

if $v(t)$ is as shown below

$\Rightarrow \sum_n \sin(n\omega t + \phi_n) A_n \longrightarrow x_n$
 \downarrow
 $\sum x_n$

Linearity and Superposition (Steady State Analysis)

for a given CK+ (R, L, C , sources) \rightarrow Convert into Phasor domain
 \downarrow apply Node analysis

$$[Y][V] = [I]$$

assumption: is full rank

$$[V] = [Y]^{-1}[I]$$


if $[I] = [I_1] + [I_2]$, then

$$[V] = [V_1] + [V_2] \text{ where } [V_1] = [Y]^{-1}[I_1] \text{ and}$$

$$[V_2] = [Y]^{-1}[I_2]$$

if $[I] = \sum I_i [e_i]$, then $[V] = \sum [V_i]$ where

$$[V_i] = I_i [Y]^{-1} [e_i]$$

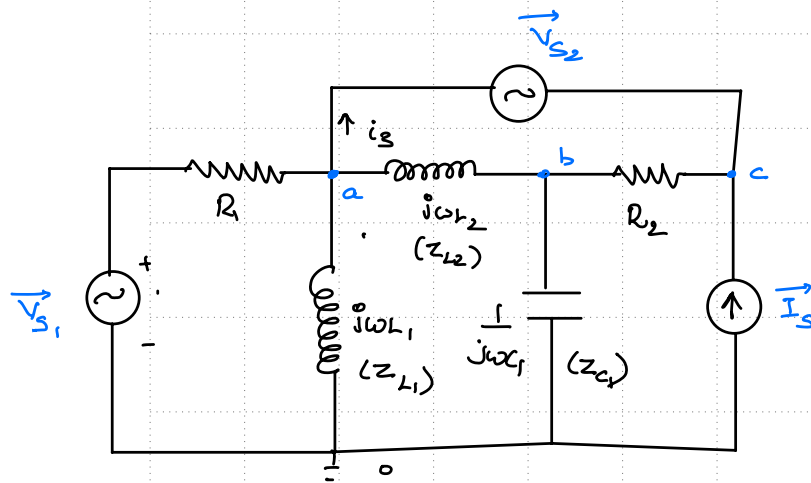

$$\begin{bmatrix} -\frac{1}{Z_{L2}} & \frac{1}{Z_{L2}} + \frac{1}{Z_{C1}} + \frac{1}{R_2} & -\frac{1}{R_2} \\ \left(\frac{1}{R_1} + \frac{1}{Z_{L1}} + \frac{1}{Z_{L2}}\right) & -\frac{1}{Z_{L2}} - \frac{1}{R_2} & \frac{1}{R_2} \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 0 \\ \frac{V_{S1}}{R_1} + I_s \\ V_{S2} \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ I_s \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{V_{S1}}{R_1} \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ V_{S2} \end{bmatrix}$$

$$Y V_1 = I_1 \quad Y V_2 = I_2 \quad Y V_3 = I_3$$

$$V = V_1 + V_2 + V_3$$

Linearity and Superposition

the overall response of any circuit is the sum of responses of subcircuits
 independent
 where one source is present
 at a time
 (or)

Typical Practice:-

Consider subcircuits when only one source is present

(Null all other sources)

independent

subcircuits might contain

combination of sources


present at a time.

response of orig ckt = resp of all sub ckt's
 ↓
 make sure that all sources are spanned

if I source $\rightarrow \infty$
 V " $\rightarrow \text{sc.}$

Substitution Theorem

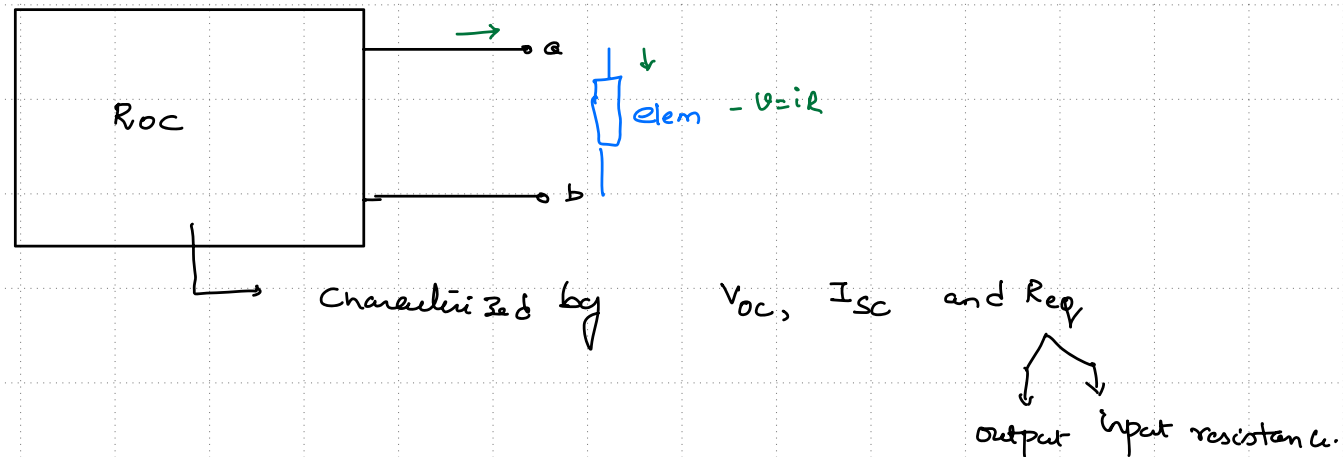aim: to explore if it's possible to replace a ckt elem with an other elem such that response does not change.




one way to find the sol at nodes a & b : graphical route (load line analysis)

formal statement: if \vec{V}_x and \vec{I}_x denote the Voltage & Current associated with a ckt elem,

replacing it with a Voltage

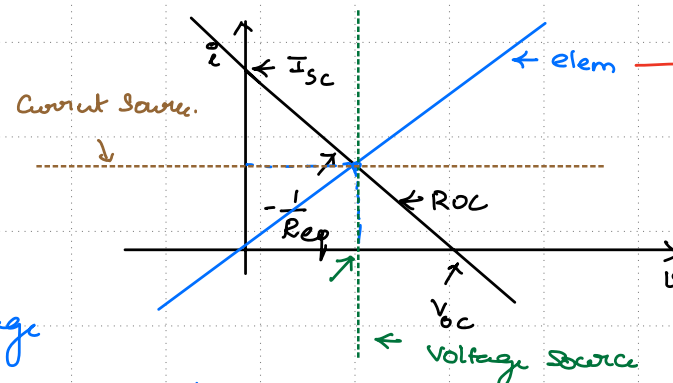source of \vec{V}_x or a Current source of \vec{I}_x does not effect the ckt response.



change the characteristic in any manner as long as the point of intersection does not change
 \downarrow linearity
 entire ckt response does not change