

.

EE1101: Circuits and Network Analysis

Lecture 11: Dependent Sources


August 22, 2025

Topics :

1. Dependent Sources
2. Three Terminal Circuit Elements

Dependent Sources


So far: Voltage | Current Source
(Independent Sources)

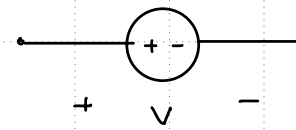

Voltage across is not
dependent on external ckt

Dependent Sources: → Value is determined based on Voltage | Current in an external ckt element.

① Voltage Controlled Voltage Source

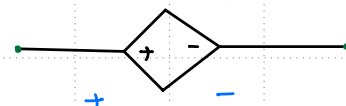


$$V_S = A_V V_{xc}$$

$A_V V_{xc}$ ← Voltage across an ext. ckt elem
(or)
gain (V/V) controlling parameter: Voltage.

used to model an

operational Amplifier
(OPAMP)

② Current Controlled Voltage Source

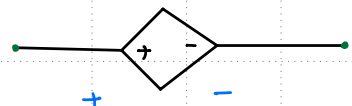


$$V_S = R i_{xc}$$

$R i_{xc}$ ← Current through an ext. ckt elem
(or)
gain (Ω) controlling parameter: Current

can be constructed using
an opAmp


Dependent Sources

③ Voltage Controlled Current Source

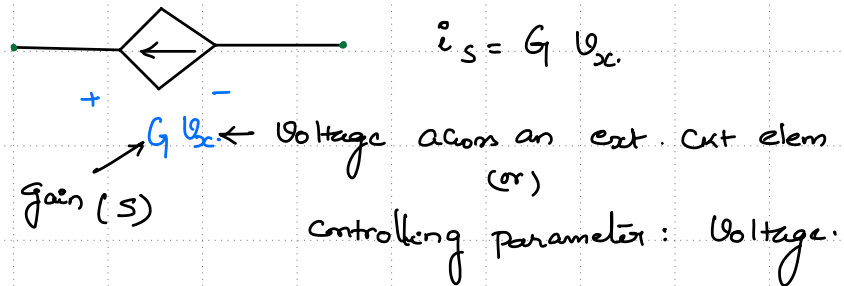


model MOSFET

④ Current Controlled Current Source

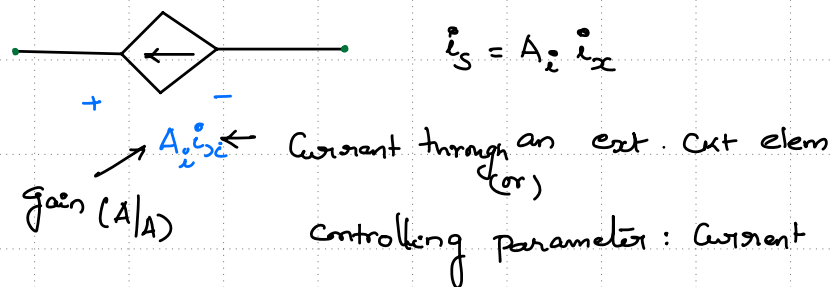

model a BJT

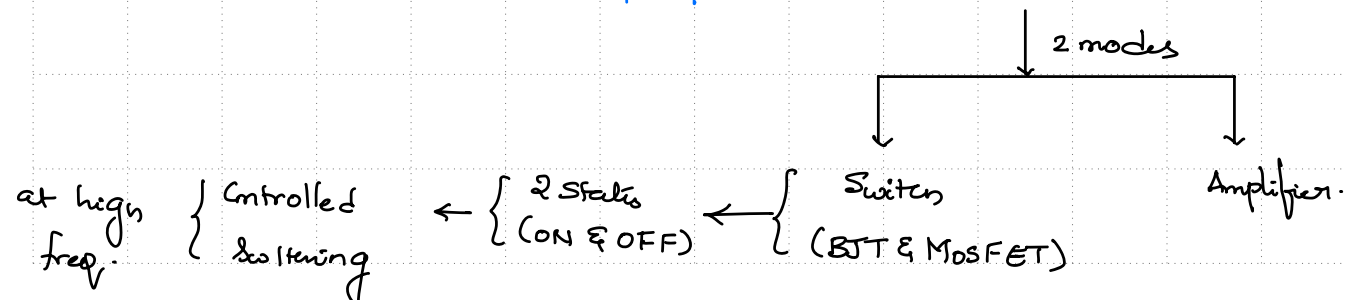BJT, MOSFET & opAmp \rightarrow 3-Terminal devices.



Three Terminal Circuit Elements (as a switch)

Example: A 3 terminal ckt elem operating as a switch.

Control port is

b/w A & C.


$V_{AC} > 0$: ON state

B & C \rightarrow Short
($R \rightarrow 0$)


$V_{AC} < 0$:

B & C \rightarrow open

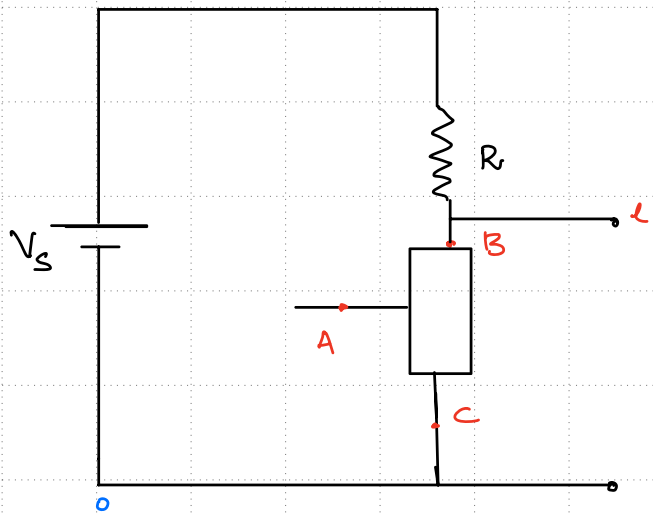($R \rightarrow \infty$) for any 3-terminal element


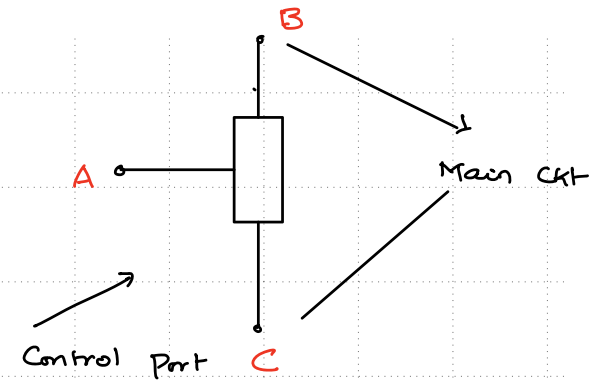
$$V_L = \begin{cases} 0 \text{ (assuming ideal)} & \text{when } V_{AC} > 0 \\ V_s \text{ (DC)} & \text{when } V_{AC} < 0 \end{cases}$$



determines the current/voltage
across the other two
terminals.

- def Control Port & main ckt
(A-C) (B-C)
- Conditions on Control port
(& main ckt)

- Switch (ON & OFF)
- Amplifier \downarrow short \downarrow open

Three Terminal Circuit Elements (as a switch)

Example: A 3 Terminal CKT elem operating as a switch.

Control port is


b/w A & C.

if $V_{AC} > 0$: ON state

B & C \rightarrow Short
($R \rightarrow 0$)

if $V_{AC} < 0$:

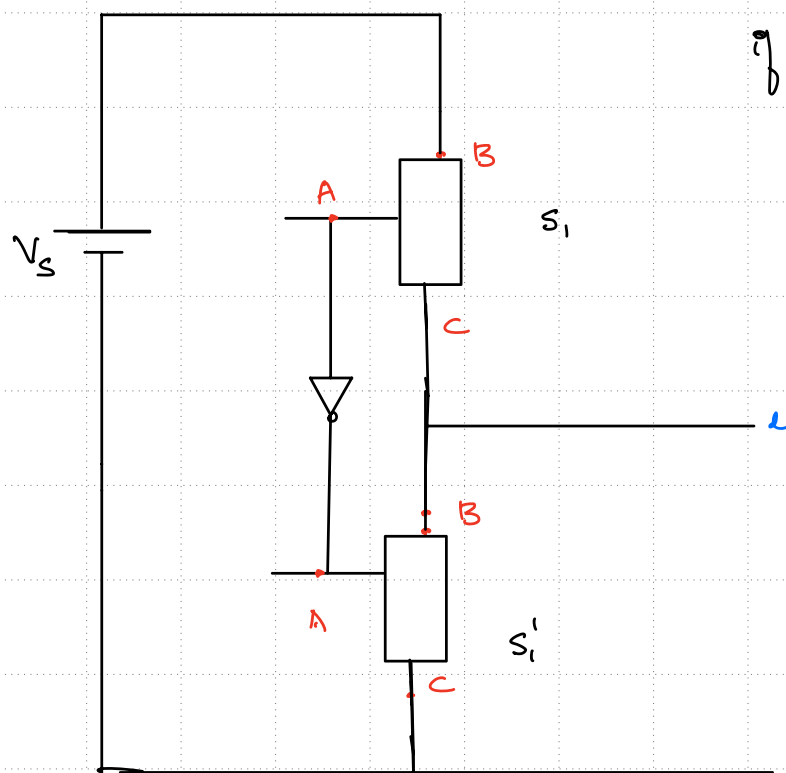B & C \rightarrow Open
($R \rightarrow \infty$)



when $V_{AC} > 0 (S_1) \Rightarrow V_{AC} < 0 (S'_1)$

$$V_L = V_S$$

when $V_{AC} < 0 (S_1) \Rightarrow V_{AC} > 0 (S'_1)$

$$V_L = 0$$

