

EE1101: Circuits and Network Analysis - Quiz 4

Name: _____

Roll No: _____

Instructions

1. The exam duration is 45 minutes, starting at 15:40. Ensure that you return the paper by 16:15. Please be aware that **late submissions** may incur **penalties**.
2. Go through all the questions carefully. Any misinterpretations will **not** be considered. Write your solutions in the designated space provided for each question. Answers written outside these areas will not be accepted.
3. Adopting unfair practices will lead to an F grade and will be reported to the disciplinary committee.

I hereby declare that I have read all the instructions carefully and will adhere to them.

Signature: _____

1. (2 points) Compute the maximum value of inductor current for the circuit shown in Fig. 1. Assume that t_0 is large enough for the circuit to operate in steady state before t_0 . Assume $i_l(0) = 0$ and $v_c(0) = 0$. Enter your answer here

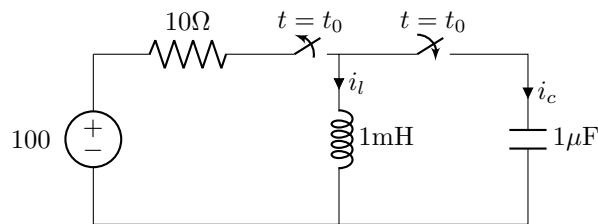


Fig. 1: Circuit for question 1

_____.

2. (8 points) Consider the circuit shown in Fig. 2.

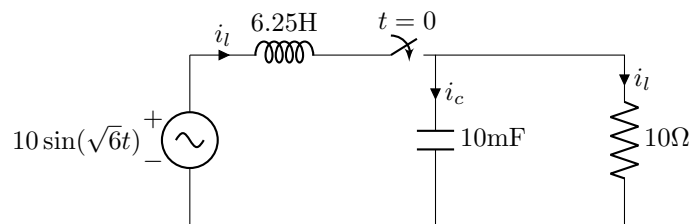


Fig. 2: Circuit for question 2

- (a) (2 points) Compute the complete response (including the transient part) of the voltage across the resistor. Enter the expression in the space below. (Make sure that it is clearly legible.)

- (b) (2 points) Compute the steady state voltage across the resistor in phasor form. Enter your answer here:
_____.
- (c) (2 points) It is desired to steady state voltage express the voltage across the capacitor in the form $v_c(t) = V_m \sin(\sqrt{6}t + \phi)$. Compute the value of V_m and ϕ . Enter the value of V_m here _____ and ϕ here:
_____.
- (d) (2 points) Let $\mathbf{S}_s$ and $\mathbf{S}_r$ denote the complex power associated with source and resistor respectively. Compute $\mathbf{S}_s + \mathbf{S}_r$. Enter the value here: _____.

EE1101: Circuits and Network Analysis - Quiz 4

Name: _____

Roll No: _____

Instructions

1. The exam duration is 45 minutes, starting at 15:40. Ensure that you return the paper by 16:15. Please be aware that **late submissions** may incur **penalties**.
2. Go through all the questions carefully. Any misinterpretations will **not** be considered. Write your solutions in the designated space provided for each question. Answers written outside these areas will not be accepted.
3. Adopting unfair practices will lead to an F grade and will be reported to the disciplinary committee.

I hereby declare that I have read all the instructions carefully and will adhere to them.

Signature: _____

1. (2 points) Compute the maximum value of inductor current for the circuit shown in Fig. 1. Assume that t_0 is large enough for the circuit to operate in steady state before t_0 . Assume $i_l(0) = 0$ and $v_c(0) = 0$. Enter your answer here

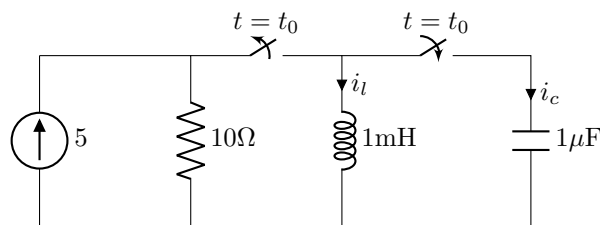


Fig. 1: Circuit for question 1

_____.

2. (8 points) Consider the circuit shown in Fig. 2.

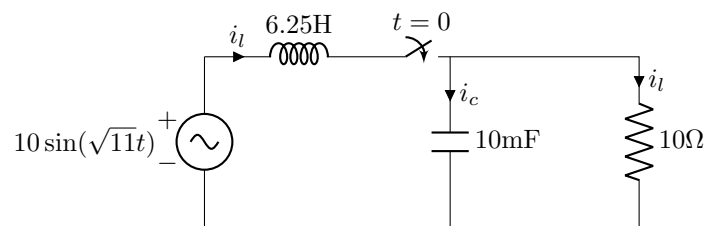


Fig. 2: Circuit for question 2

- (a) (2 points) Compute the complete response (including the transient part) of the voltage across the resistor. Enter the expression in the space below. (Make sure that it is clearly legible.)

- (b) (2 points) Compute the steady state voltage across the resistor in phasor form. Enter your answer here:
_____.
- (c) (2 points) It is desired to steady state voltage express the voltage across the capacitor in the form $v_c(t) = V_m \sin(\sqrt{11}t + \phi)$. Compute the value of V_m and ϕ . Enter the value of V_m here _____ and ϕ here:
_____.
- (d) (2 points) Let $\mathbf{S}_s$ and $\mathbf{S}_r$ denote the complex power associated with source and resistor respectively. Compute $\mathbf{S}_s + \mathbf{S}_r$. Enter the value here: _____.

EE1101: Circuits and Network Analysis - Quiz 4

Name: _____

Roll No: _____

Instructions

1. The exam duration is 45 minutes, starting at 15:40. Ensure that you return the paper by 16:15. Please be aware that **late submissions** may incur **penalties**.
2. Go through all the questions carefully. Any misinterpretations will **not** be considered. Write your solutions in the designated space provided for each question. Answers written outside these areas will not be accepted.
3. Adopting unfair practices will lead to an F grade and will be reported to the disciplinary committee.

I hereby declare that I have read all the instructions carefully and will adhere to them.

Signature: _____

1. (2 points) Compute the maximum value of capacitor voltage for the circuit shown in Fig. 1. Assume that t_0 is large enough for the circuit to operate in steady state before t_0 . Assume $i_l(0) = 0$ and $v_c(0) = 0$. Enter your answer here

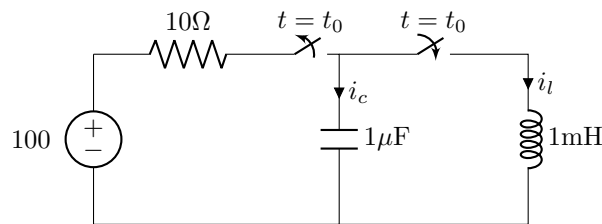


Fig. 1: Circuit for question 1

_____.

2. (8 points) Consider the circuit shown in Fig. 2.

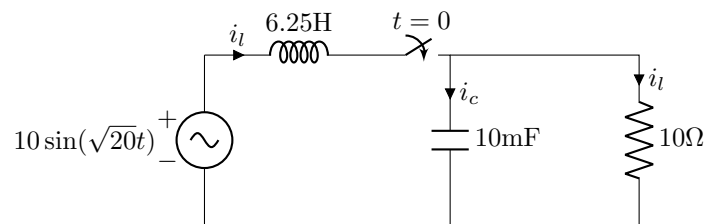


Fig. 2: Circuit for question 2

- (a) (2 points) Compute the complete response (including the transient part) of the voltage across the resistor. Enter the expression in the space below. (Make sure that it is clearly legible.)

- (b) (2 points) Compute the steady state voltage across the resistor in phasor form. Enter your answer here:
_____.
- (c) (2 points) It is desired to steady state voltage express the voltage across the capacitor in the form $v_c(t) = V_m \sin(\sqrt{20}t + \phi)$. Compute the value of V_m and ϕ . Enter the value of V_m here _____ and ϕ here:
_____.
- (d) (2 points) Let $\mathbf{S}_s$ and $\mathbf{S}_r$ denote the complex power associated with source and resistor respectively. Compute $\mathbf{S}_s + \mathbf{S}_r$. Enter the value here: _____.

EE1101: Circuits and Network Analysis - Quiz 4

Name: _____

Roll No: _____

Instructions

1. The exam duration is 45 minutes, starting at 15:40. Ensure that you return the paper by 16:15. Please be aware that **late submissions** may incur **penalties**.
2. Go through all the questions carefully. Any misinterpretations will **not** be considered. Write your solutions in the designated space provided for each question. Answers written outside these areas will not be accepted.
3. Adopting unfair practices will lead to an F grade and will be reported to the disciplinary committee.

I hereby declare that I have read all the instructions carefully and will adhere to them.

Signature: _____

1. (2 points) Compute the maximum value of capacitor voltage for the circuit shown in Fig. 1. Assume that t_0 is large enough for the circuit to operate in steady state before t_0 . Assume $i_l(0) = 0$ and $v_c(0) = 0$. Enter your answer here

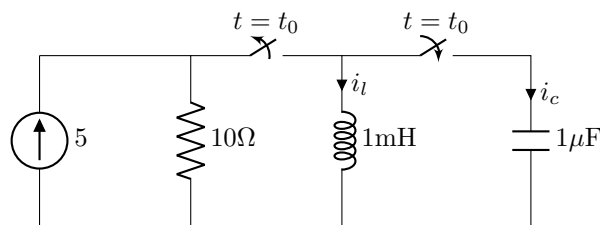


Fig. 1: Circuit for question 1

_____.

2. (8 points) Consider the circuit shown in Fig. 2.

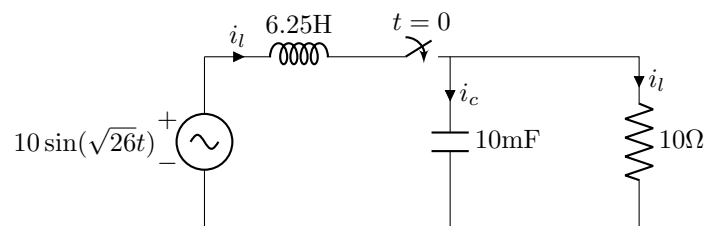


Fig. 2: Circuit for question 2

- (a) (2 points) Compute the complete response (including the transient part) of the voltage across the resistor. Enter the expression in the space below. (Make sure that it is clearly legible.)

- (b) (2 points) Compute the steady state voltage across the resistor in phasor form. Enter your answer here:
_____.
- (c) (2 points) It is desired to steady state voltage express the voltage across the capacitor in the form $v_c(t) = V_m \sin(\sqrt{26}t + \phi)$. Compute the value of V_m and ϕ . Enter the value of V_m here _____ and ϕ here:
_____.
- (d) (2 points) Let $\mathbf{S}_s$ and $\mathbf{S}_r$ denote the complex power associated with source and resistor respectively. Compute $\mathbf{S}_s + \mathbf{S}_r$. Enter the value here: _____.