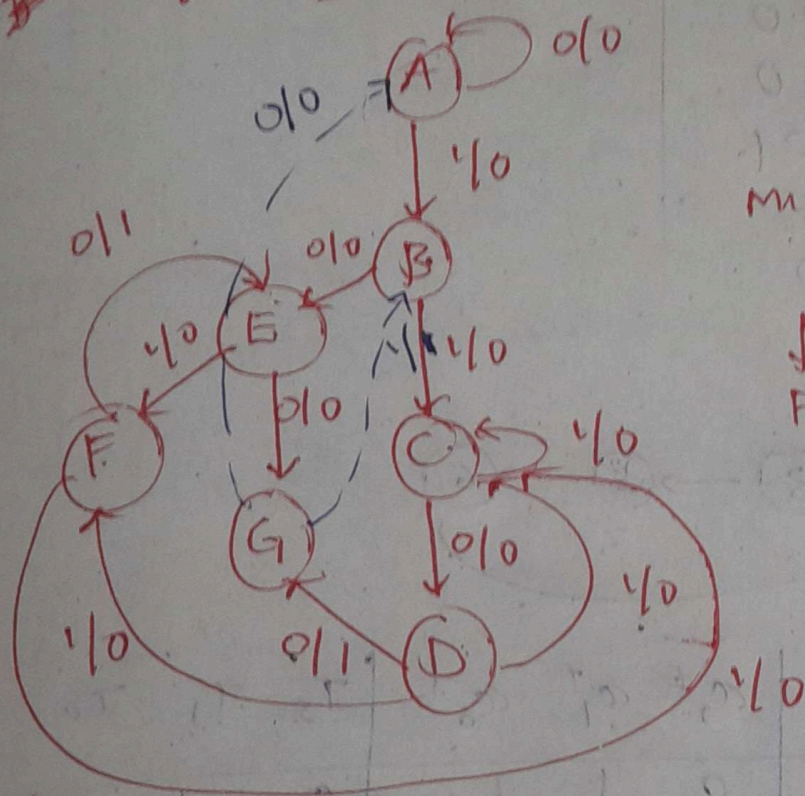


#2)
 mealy (~~non~~ overlap) ✓




min. state.

$$= 7$$

↓

$$F.F.S = 3$$

~~mealy~~ Non-overlap

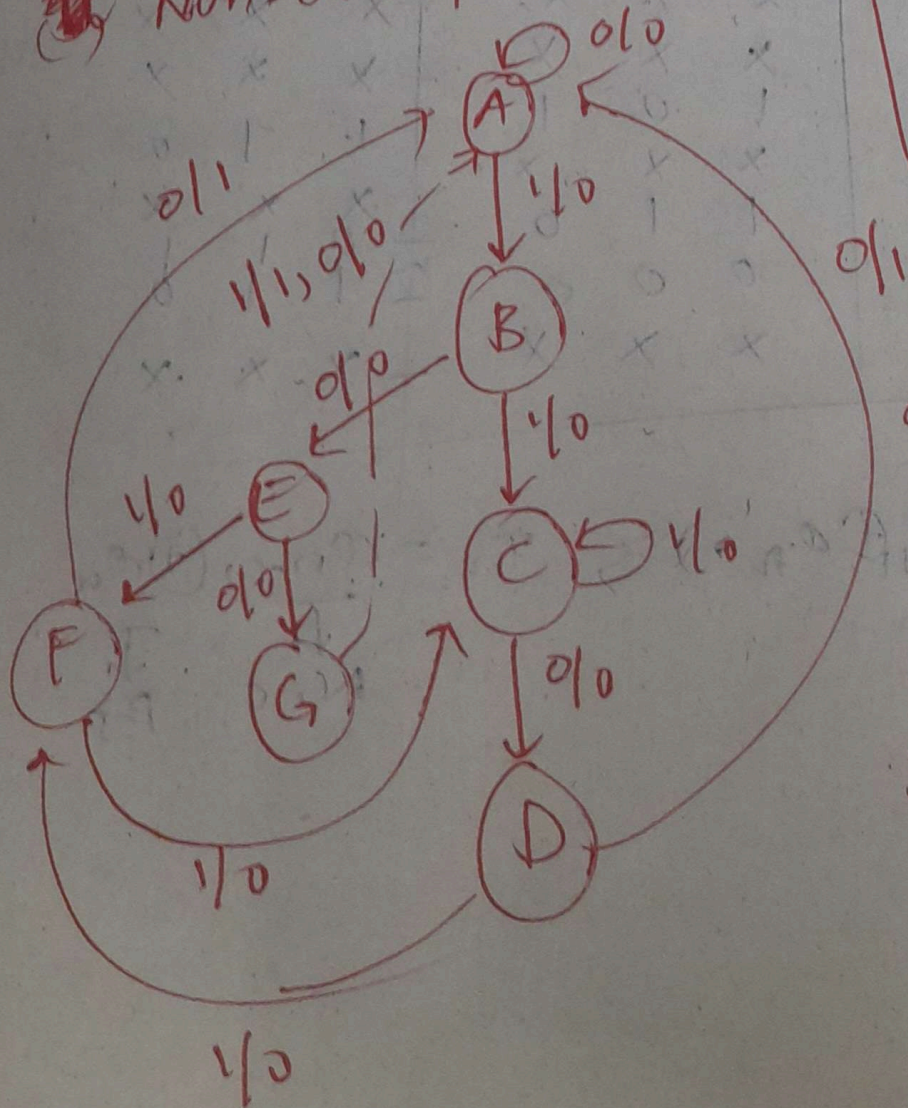


$$\begin{array}{l} a \rightarrow 8 + 2 \\ b \rightarrow 8 + 2 \end{array}$$

Que
 $a \rightarrow 8$
 $b \rightarrow 8$

F.F.S $\rightarrow$ 1
 States $\rightarrow$ 1

#

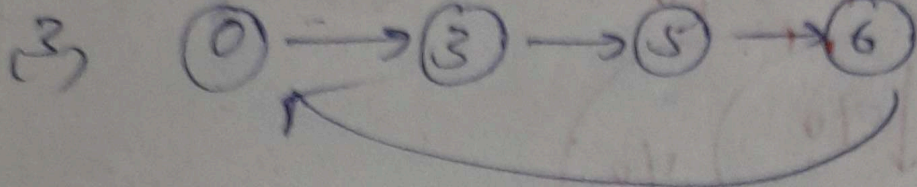

a_2	a_1	a_0	a_2^t	a_1^t	a_0^t	T_2	T_1	T_0
0	0	0	0	1	1	0	1	1
0	0	1	x	x	x	x	x	x
0	1	0	x	x	x	x	x	x
0	1	1	1	0	1	1	1	0
1	0	0	x	x	x	x	x	x
1	0	1	1	1	0	x	x	x
1	1	0	0	0	0	0	1	0
1	1	1	x	x	x	x	x	x

$$T_n = a_{n+1}^t \oplus a_n = T_{n+1} \oplus T_n$$

$\downarrow$
 N_{n+1}

$\downarrow$
 P_n


$$T_2 \quad \bar{a}_1, \bar{a}_0 \quad \bar{a}_1 a_0 \quad a_1 a_0 \quad a_1, a_0$$

$\bar{a}_2$	0	x	1	x
a_2	1	0	x	1

$$= a_1$$

$$11^h, T_1 = 1 \Rightarrow T_0 = \bar{a}_1$$

Design of Lockout:

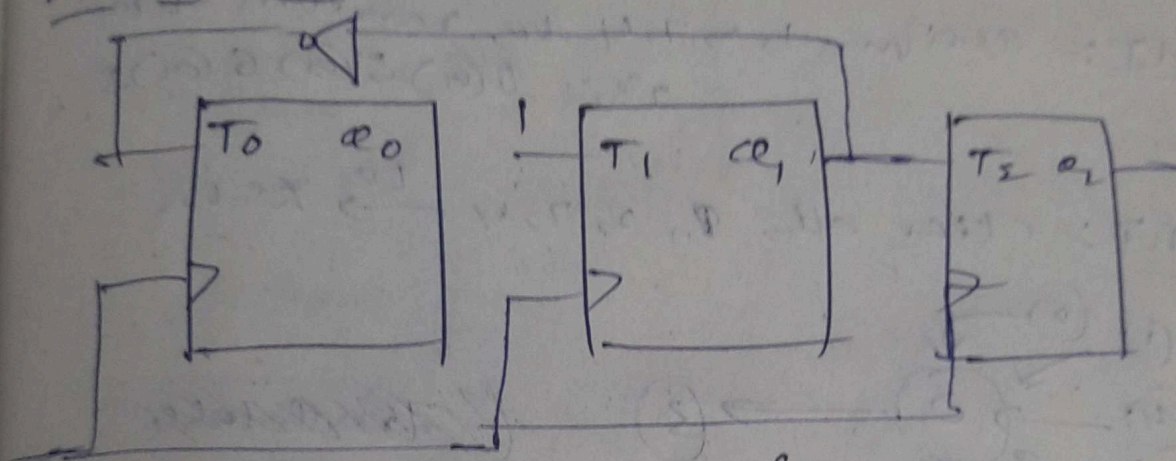

clk

$$T_n = a_{n+1} \oplus a_n$$

$$\Rightarrow a_{n+1} = T_n \oplus a_n$$

Now, states 1, 2, 4, 7

$a_2 \ a_1 \ a_0$	$a_2^+ \ a_1^+ \ a_0^+$
0 0 1	0 1 0
0 1 0	1 0 0
1 0 0	1 1 1
1 1 1	0 0 1

T_n is known

$$T_2 = a_1$$

$$T_1 = 1$$


$$T_0 = \bar{a}_1$$

$$a_2^+ = a_1 \oplus a_2$$


$$a_1^+ = 1 \oplus a_1 = \bar{a}_1$$

$$a_0^+ = \bar{a}_1 \oplus a_0 = a_1 \odot a_0$$

11

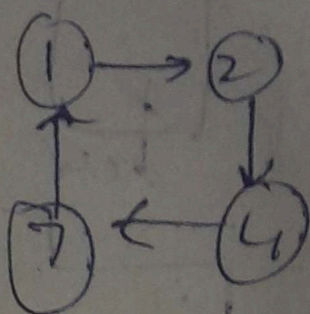

to

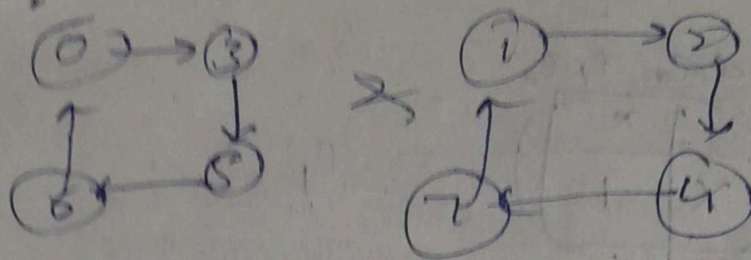



lockout!! Yes

→ Avoiding techniques

MIT: assign 1, 2, 7, 4 to random states


20, 0(0) 3(0) 6(0) 5

MIT: clear all 0, 2, 7, 4 → zero

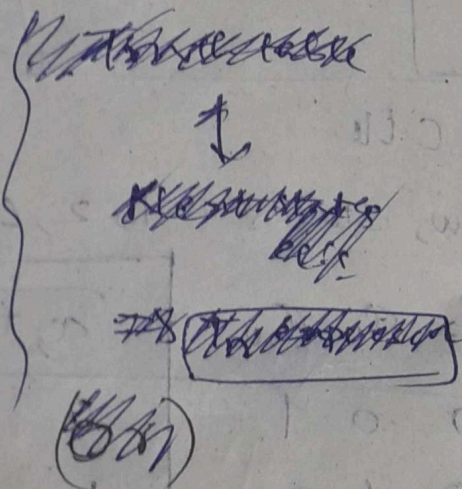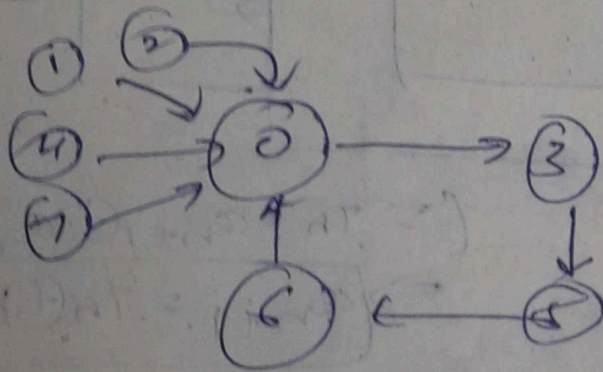

Ans:
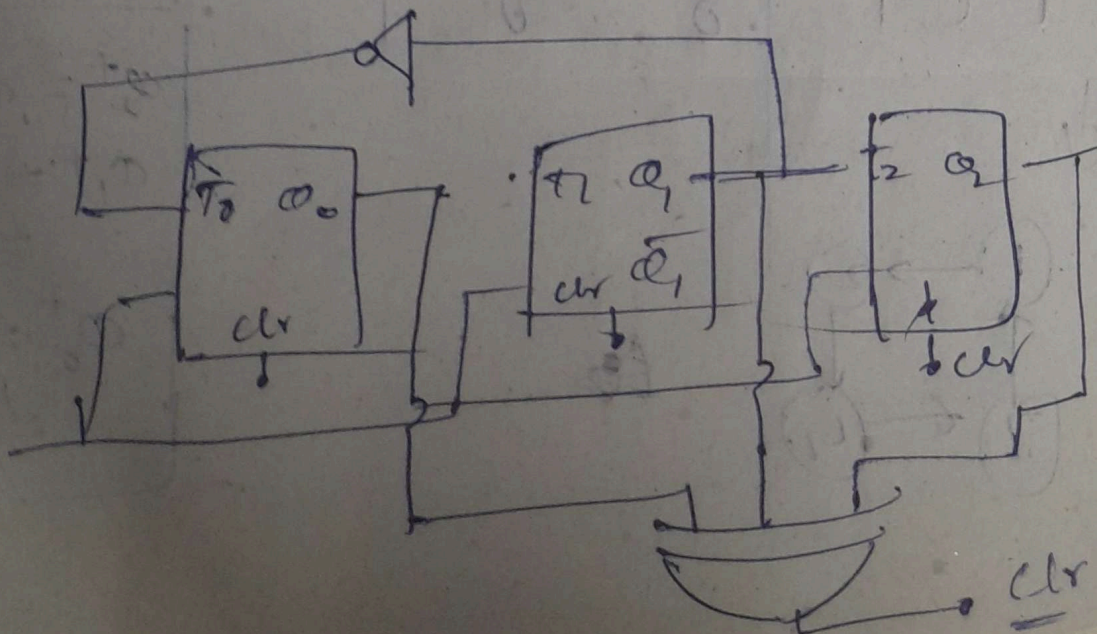
$$Ckr \in \Sigma m(1, 2, 4, 7) = q_2 \oplus q_1 \oplus q_0$$



(5)

from I_n to (b_2)

$$\begin{aligned} T_{clk} &\geq T_{clk1} + T_{dy1} + (T_{su2}) - T_{skew1} \\ &\& T_{h2} \leq T_{clk1} + T_{dy1} - T_{skew1} \end{aligned}$$

✓ from I_{nD_2} to D_3 .

$$\begin{aligned} T_{clk} &\geq (T_{clk2} + T_{skew1}) + T_{dy2} + T_{su3} \\ &\quad - (T_{skew1} + T_{skew2}) \end{aligned}$$

$$\geq T_{clk2} + T_{dy2} + T_{su3} - T_{skew2}$$

$$\& T_{h3} \leq T_{clk2} + T_{dy2} - T_{skew2}$$

$$f_{max} = \frac{1}{T_{min}}$$

$$\therefore T_{min} = \max(\min(T_{clk}), \min(T_{h2}))$$

Then $Q=1$ goes to G_4 & G_6

$$G_{out} = (\overline{Q})(R')(Y) \quad ; \quad G_6 = 0 \text{ (clk=0)}$$

$$= (1)(1)(1) = 1$$

$$\rightarrow G_8 = \boxed{Q = \overline{Q}}$$

region (F)

when $Y=0$ $Q=1$ $(1)(1)(1)(1) = 1$

$$\Rightarrow G_7 = G_6 = 0 \text{ immediately} \Rightarrow \boxed{Q = 1 = \overline{Q}}$$

this $\overline{Q}$ goes to G_3 & G_2

$$G_3 = (\overline{Q})(J')(X) = (1)(1)(1) = 1$$

$$G_2 = (X)(\text{clk})(\overline{Q}) = (1)(0)(1) = 0$$

$$\rightarrow G_4 = 1+0 = \boxed{Q = \overline{Q}}$$

After $Y=1$

still $\text{clk}=0$ $J=1$ $K=1$

$$G_3 = (\overline{Q})(J')(X) = 1$$

$$G_2 = (\overline{Q})(\text{clk})(X) = 0$$

$$\Rightarrow G_4 = 0 = G_6 \text{ (due to } Q)$$

$$\rightarrow \boxed{\overline{Q} = 1}$$

$Y = \text{clock}$

As $X=0$, $Q=1$

for $Y=0$; $Q=0$

(1c) The circuit is a negative triggered flipflop as output state (Q) changes only at negative edge of clock.

	Q_A	Q_B	Q_C	Q'_A	Q'_B	Q'_C	X'	X''	X'''	Z
1	0	0	0	1	0	0	0	0	0	0
2	0	1	0	1	1	0	1	0	0	1
3	0	0	1	1	1	1	1	1	0	1
4	1	0	0	0	1	1	1	1	1	1
5	0	1	0	0	0	1	0	1	1	1
6	0	0	1	0	0	0	0	0	1	1
7	1	0	0	1	0	0	0	0	0	0

$\therefore 6$ clock pulses $\Rightarrow \boxed{Z=0}$

after 4d', $K=0$

$$G_0 = 0$$

$$G_{60} = (clk) \cdot (y) \cdot (Q)$$

$$= (1) \cdot (1) \cdot (1)$$

$$\therefore G_{60} = \boxed{Q = 1 \rightarrow 0} \text{ still } \& \text{ this } Q \text{ goes to}$$

$$G_3 \& G_2 = 0 \cdot (1) \cdot (1) \quad \boxed{Q = 0 = 1}$$

at region ③ ie when clock goes -ve

$K'=1$ but with delay. so

$$G_7 = (K'_{\text{delay}}) \cdot Q \cdot Y = 0$$

$$G_6 = clk = 0 \therefore = 0$$

$$\Rightarrow G_8 = \frac{G_7 + G_6}{2} = \boxed{0 = 1 = 0}$$

this goes to $G_3 \& G_2$

$$G_3 = (\bar{Q} \cdot J' \cdot X) \quad \text{as } clk=0 \quad (J'=1 \text{ still})$$

$$= (1) \cdot (1) \cdot (1) = 1 \quad \therefore \text{Not atleast one '1'}$$

$$\Rightarrow \boxed{G_{40} = 0 = Q}$$

So this continues till region 4 as no change

$$\text{in } i/p \cdot (1) \cdot (1) \cdot (1) \cdot (1)$$

$$\& \text{ value stays at } \boxed{0 = 1}$$

at region 5

$clk=1$ but no change in $G_7 = G_6 = 0 = \boxed{Q=1}$

$$J' = (clk) \cdot (B) \cdot \bar{Q} \cdot Y$$

$$= (1) \cdot (0) \cdot (1) \cdot (1) = 0$$

$\therefore clk$ alone has no effect on J'

now once $B=1$ 'B=1'

$$J' = (1) \cdot (1) \cdot (1) \cdot (1) = 1 = 0 \quad (\text{But with delay})$$

after delay,

$$G_3 = (\bar{Q} \cdot J' \cdot X) = (1) \cdot (0) \cdot (1) = 0$$

$$G_2 = (\bar{Q} \cdot clk) \cdot (X) = 1 \cdot (1) \cdot (1) = 1 \quad G_{40} = \boxed{0 = Q}$$

this goes to $G_3 \& G_6$ making $\boxed{Q=1}$

after this $A=0$

$\Rightarrow K'=1$ previously $K=1 \therefore$ no change in K'

Now in region 6: when $clk=0$

$K'=1$ so no change
but $J'=1$ but with delay.

$$G_{3out} = (J'_{\text{delay}}) \cdot (\bar{Q}) \cdot (X) = 0$$

$$= 0$$

$$G_{22} = 0 \quad (\because clk=0)$$

$$\Rightarrow \boxed{G_{4out} = 1 = Q}$$

Assume 0/ps after delay as $J^1 + K^1$ then

In ① region as $T/4 \gg t_d$ so,

for G_1

$$x=0 \Rightarrow K^1=1$$

$$\text{for } G_5 \text{ clk}=0$$

$$\text{for } G_3, G_2 \text{ as } x=0 \rightarrow G_{3out} = G_{2out} = 0$$

$$\text{for } G_7 = Q \cdot K^1 \cdot Y = 0 \cdot (1) \cdot (1) = 0$$

$$G_{out} = 0 \text{ (}\because \text{clk}=0\text{)}$$

$$\rightarrow G_{80} = \frac{0}{1+0} = 0 \Rightarrow Q$$

In region ②

When $A=1$

$$\text{Still } x=0 \therefore K^1=1; \text{ Still } J^1=1$$

$$\text{Still } x=0 \rightarrow G_3 = G_2 = 0 \Rightarrow Q=1$$

$$G_7 = Q \cdot K^1 \cdot Y = (1) \cdot (1) \cdot (1) = 1$$

$$G_{6out} = \text{clk} \cdot Y \cdot Q = 1$$

$$Q_{out} = \frac{1}{1+1} = \frac{1}{2} \Rightarrow Q=0$$

now when $x=1$

$$K^1 = 1 \cdot (Q) \cdot (x) \cdot (A) \cdot (\text{clk})$$

$$= (1) \cdot (1) \cdot (1) \cdot (1) = 1$$

