

Tutorial 3:-

#1) All reset => 2 up counter

MSB LSB

Q_2 Q_1 Q_0

→ 0 0 0 ✓ =



↳ 1 0 0 ✓ = 1

↳ 0 1 0 ✓ = 0

↳ 1 1 0 ✓ = 1

↳ 0 0 1 ✓

→ 1 0 1


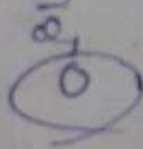
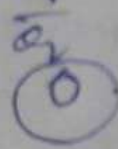



0 1 → 1

1 1 → 1

0 1 → 1


1 0 → 1

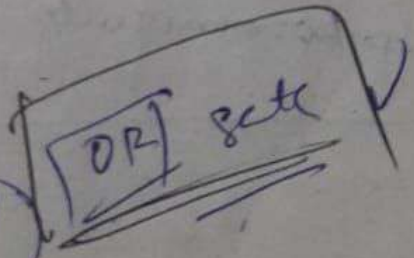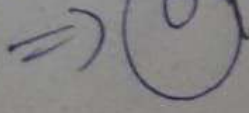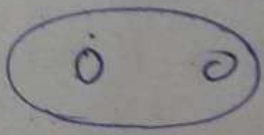

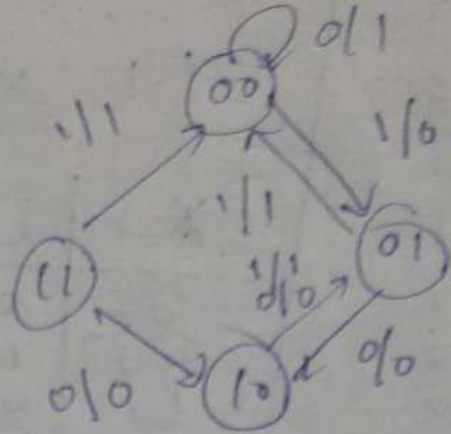

#5) $a \rightarrow 00$
 $b \rightarrow 01$
 $c \rightarrow 10$

a, a_0	y	a_1, a_0	a_1, a_0	a_1, a_0
$a \rightarrow 0$	0	0	0	0
$a \rightarrow 1$	0	1	0	1
$b \rightarrow 0$	1	0	0	0
$b \rightarrow 1$	1	1	0	0
$c \rightarrow 0$	0	0	1	0
$c \rightarrow 1$	0	1	0	0
$\{ \}$	1	0	x	x
$\{ \}$	1	1	x	x

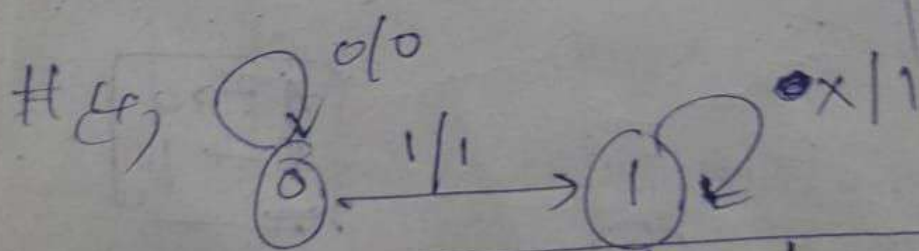

	a, a_0	a_1, a_0	a_1, a_0
a	0, a	1, b	0, 1
b	0, b	0, b	1

$$[A_1 \geq A_2]$$

$$Y \geq 1 \Rightarrow Y \geq 0$$

$$A_1 \subset A_2 \Rightarrow \boxed{X=0; Y=1}$$

Boiler

#2, initially $\rightarrow (111)_2$

(c)

$A_3 \quad A_2 \quad A_1 \quad A_0$

$\begin{array}{ccc|c} 1 & 1 & 1 & 15 \\ 1 & 1 & 0 & 0 \\ 1 & 1 & 0 & 1 \\ 1 & 1 & 0 & 0 \\ 1 & 0 & 1 & 1 \\ 1 & 0 & 1 & 0 \\ 1 & 0 & 0 & 1 \end{array}$

$$Y = I_7, I_8, 0, 0, I_5, I_3, 0, 0, \dots$$

[illegible]

Qnt)

	$\bar{T}\bar{Q}$	$T\bar{Q}$	$\bar{T}Q$	TQ
$\bar{S}\bar{R}$	0	1	0	1
$\bar{S}R$	0	0	0	1
$S\bar{R}$	0	1	0	1
SR	1	1	0	1


$$T\bar{Q} + \bar{S}\bar{R}\bar{Q} + \bar{S}T\bar{Q} + \bar{R}\bar{T}Q$$

$$\bar{T}Q$$

$$T\bar{Q} + \bar{T}(S\bar{R} + S\bar{Q} + \bar{Q}R)$$

$$= \bar{T}Q + \bar{T}(\bar{Q}(S + R) + S\bar{R})$$
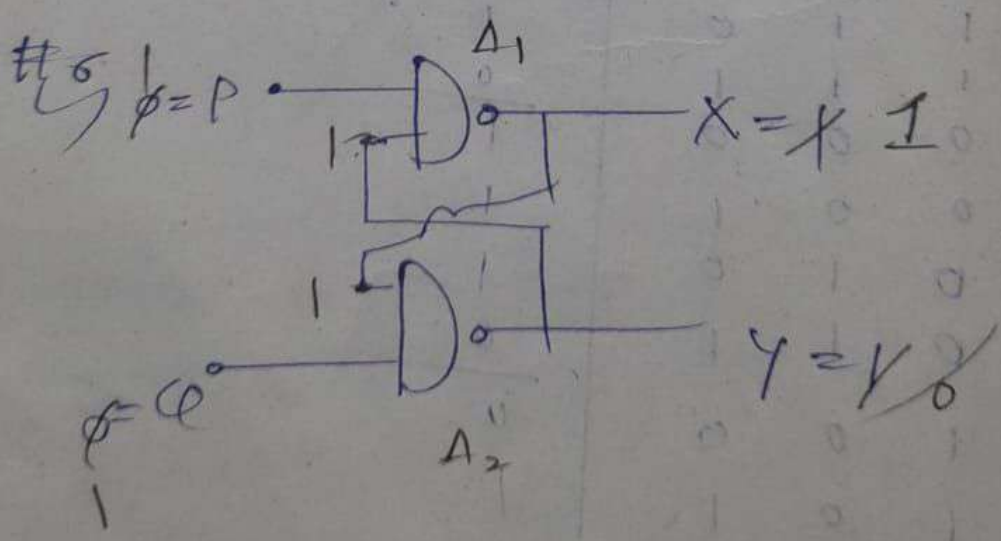
$$\boxed{T\bar{Q} + \bar{T}[\bar{Q}(S + R) + S\bar{R}]}$$



#3

	x_7	x_6	x_5	x_4	x_3	x_2	x_1	x_0
0	1	1	0	1	1	1	0	
✓ 0	0	0	1	1	0	1	1	
✓ 1	0	0	1	1	0	1	1	
✓ 0	1	0	0	1	1	0	1	*

#3

$a_1 a_2 a_3 a_4$
1 0 1 0

	a_1	a_2	a_3	a_4
✓ 1	1	0	1	0
✓ 1	1	1	0	1
✓ 0	1	1	0	1
✓ 1	0	1	1	1
✓ 0	1	0	1	0
✓ 0	0	0	1	0
✓ 1	0	0	1	0
✓ 1	0	0	1	0
✓ 1	0	0	1	0

8 *

	a_1	a_2	a_3	a_4
✓ 1	1	0	1	0
✓ 1	1	1	0	1
✓ 0	1	1	0	1
✓ 1	0	1	1	1
✓ 0	1	0	1	0
✓ 0	0	0	1	0
✓ 1	0	0	1	0
✓ 1	0	0	1	0
✓ 1	0	0	1	0

4
#4

	S	G	A	B	C _{in}
	0	0	0	0	0
↪	0	1	1	1	0

↪

1	1	1	1	0
---	---	---	---	---

C_{in} = 1
A = 1
B = 1

S = 1, G = 1

#5

S	R	T	Φ	Q _{n+1}
X	X	1		
1	0	0	1	0

X

	S	R	T	Q _n	Q _{n+1}
000	0	0	0	0	0
	0	0	0	1	1
T=1	0	0	1	0	1
	0	0	1	1	0
010	0	1	0	0	0
	0	1	0	1	0
T=1	0	1	1	0	1
	0	1	1	1	0
100	1	0	0	0	1
	1	0	0	1	1
T=1	1	0	1	0	1
	1	0	1	1	0
110	1	1	0	0	0
	1	1	0	1	1
T=1	1	1	1	0	1
	1	1	1	1	0

	a_3	a_2	a_1	a_0
→	0	0	0	0
	1	0	0	0
	1	1	0	0
	0	1	1	0
	1	1	1	1
	0	1	1	1
	0	0	1	1
	0	0	0	1
	0	0	0	0

4-bit



(8)

$\left(\frac{f_c}{8}\right) \times$

$\left(\frac{f_c}{64}\right)$

$= \left(\frac{3.6 \text{ KHz}}{64}\right)$

$= 56.25 \text{ (Hz)}$

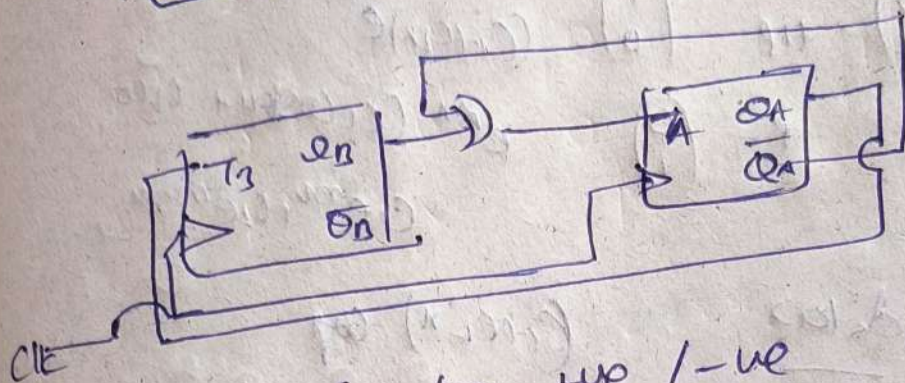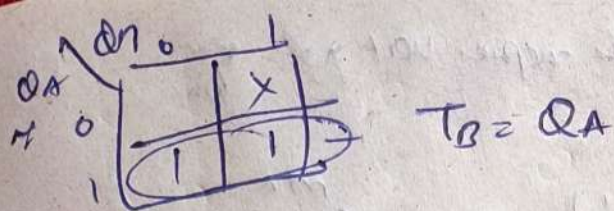


CLK can be +ve / -ve



⑭

Q_A	Q_B	Q_C	next	T_A	T_B	T_C
0	0	1	0 1 0	0	1	1
0	1	0	0 1 1	0	0	1
0	1	1	1 0 1	1	1	0
1	0	1	1 1 1	0	1	0
1	1	1	0 0 1	1	1	0
0	0	0	0 0 1	0	0	1
1	0	0	0 0 1	1	0	1
1	1	0	0 0 1	1	1	1

same for

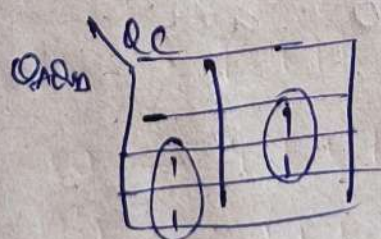

(12) $f_{sig}(b)$

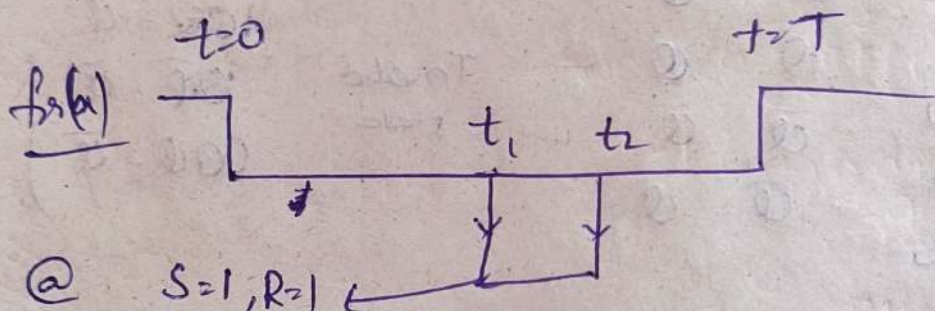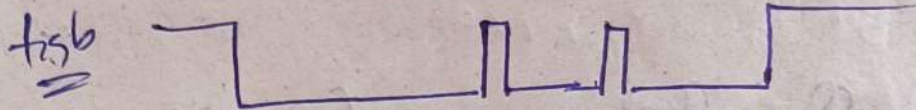

@ $S=1, R=1$
 $t_1, t_2 \Rightarrow$ Hold

remaining time $S=1$
 $R=0$ } in first given ckt

O/p of R becomes 0
 overall dp = 0


(13) $\overline{Q_2 \cdot Q_0} = 0 \Rightarrow Q_2 Q_1 Q_0$

total 5 States
 MOD 5

(14a)

Pres	Next
00	10
10	11
11	00
01	X X
$Q_A Q_B$	$Q_A^+ Q_B^+$


T_A	T_B
1	0
0	1
1	1
X	X

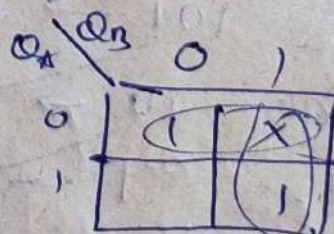

$$T_A = \overline{Q_A} + Q_B$$

9a)

X	Y	Q	Q _{n+1}
0	0	X	0
0	1	Q	Q
1	0	Q	$\bar{Q}$
1	1	X	1

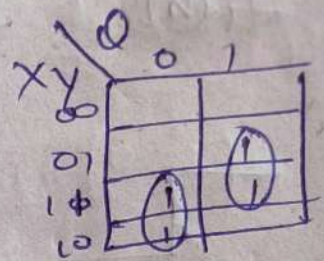

$$Q_{n+1} = X\bar{Q} + YQ$$

9b)

X	Y	Q	Q _{n+1}
0	0	Q	$\bar{Q}$
0	1	Q	Q
1	0	$\bar{Q}$	$\bar{Q}$
1	1	$\bar{Q}$	Q

Invalid state

$$(\because 00\bar{Q} = Q)$$

$$10Q = Q$$

$$10\bar{Q} = \bar{Q}$$

$$00Q = \bar{Q})$$

0000

10) $1100 \rightarrow 0000$

12 states = MOD-12

$$(\because Q_2 \cdot Q_3 = 1 \cdot 1 = 0 = C(R_1))$$

