


Tutorial-3 Extra Questions

1. A sequence detector is designed to detect precisely 3 digital inputs, with overlapping sequences detectable. For the sequence (1, 0, 1) and input data (1, 1, 0, 1, 0, 0, 1, 1, 0, 1, 0, 1, 1, 0) . What is the output of the detector.
2. Draw the state Diagram for standard flip flops
(SR , JK , D and T)
3. a) Given then following state table of an FSM with two states A and B, one input and one output

Present state A	Present state B	Input	Next state A	Next state B	Output
0	0	0	0	0	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	1	0	0
0	0	1	0	1	0
0	1	1	0	0	1
1	0	1	0	1	1
1	1	1	0	0	1

Draw the state diagram


b)

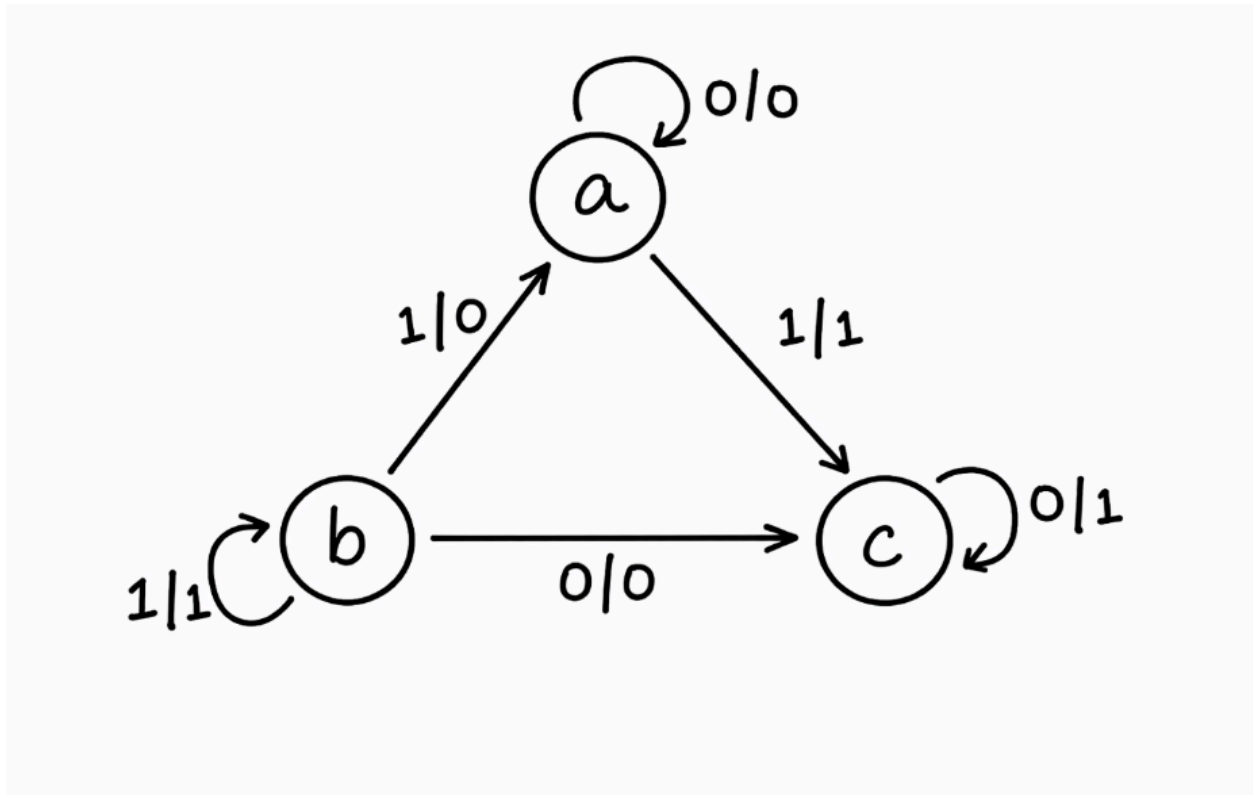

Design FSM for the given State diagram.

4.

Consider the circuit shown below

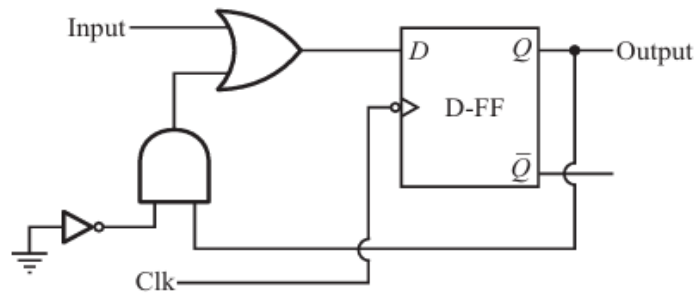

If Q is taken as the state of the circuit, then the state diagram of the above circuit can be given as

Draw state table as well

